

Isolated current-measurement circuit with $\pm 250\text{-mV}$ input and differential output




Design Goals

Current Source		Input Voltage		Output Voltage		Single Power Supply
I_{inMin}	I_{inMax}	Dif V_{INMin}	Dif V_{INMax}	Dif V_{OUTMin}	Dif V_{OUTMax}	V_{DD}
-50A	50A	-250mV	250mV	-2.05V	2.05V	3.0V to 5.5V

Design Description

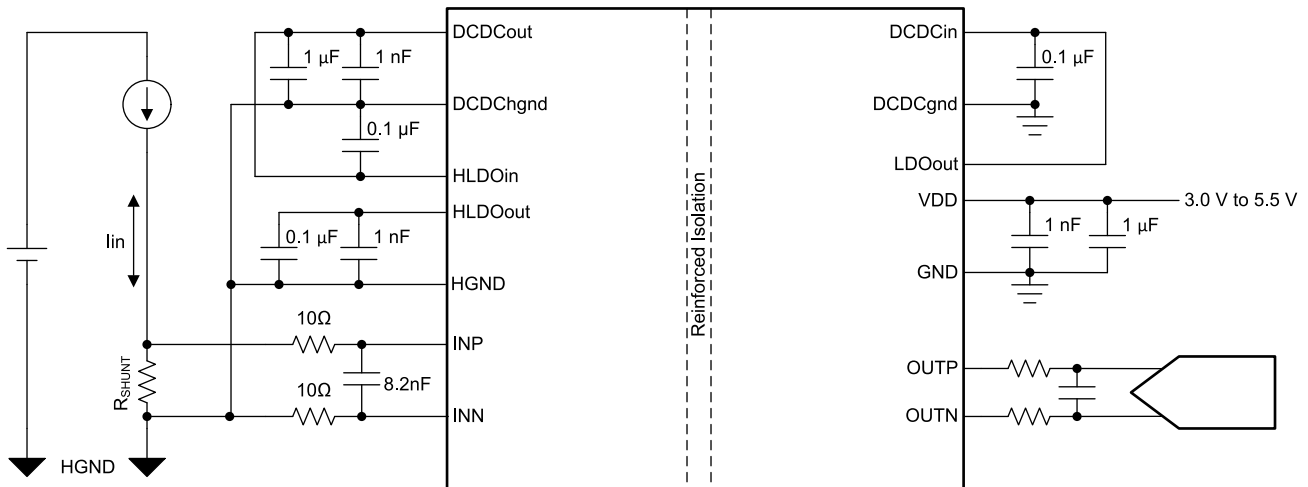This isolated single-supply bidirectional current sensing circuit can accurately measure load currents from -50A to 50A. The linear range of the input is from -250mV to 250mV with a differential output range of -2.05V to 2.05V. The gain of the circuit is fixed at 8.2V/V. The design requires 1000-V working voltage to maintain operator safety in a high-voltage application.



Design Notes

1. Select an amplifier with at least 1000-V working voltage across the isolation barrier.
2. Select input filter components to minimize voltage drop from internal bias currents and maintain a –3-dB cutoff frequency of approximately 1MHz.
3. For highest accuracy, use a precision shunt resistor with low temperature coefficient.
4. Select the current shunt for expected peak input current levels.
5. Shunt resistor power should be three to eight times larger than the expected continuous power rating of the system.

Design Steps

1. Determine the transfer equation given the input current range and the fixed gain of the isolation amplifier.

$$V_{OUT} = I_{in} \times R_{shunt} \times 8.2V$$

2. Determine the maximum shunt resistor.


$$R_{shunt} = \frac{V_{shunt}}{I_{inMax}} = \frac{250mV}{50A} = 5m\Omega$$

3. Determine the minimum shunt resistor power needed.


$$\text{Power } R_{shunt} = I_{inMax}^2 \times R_{shunt} = 2500 \times 0.005 = 12.5W$$

Design Simulations


DC Simulation Results

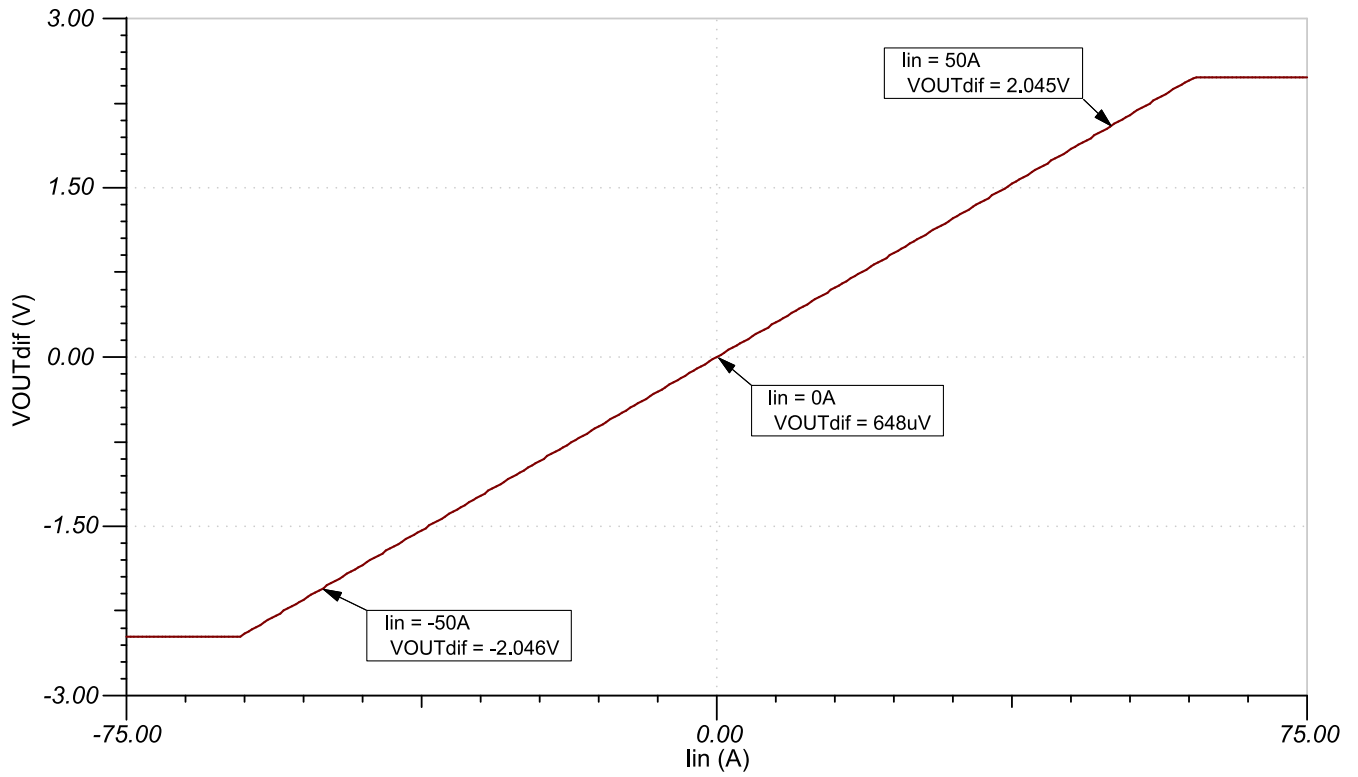

Closed Loop AC Simulation Results

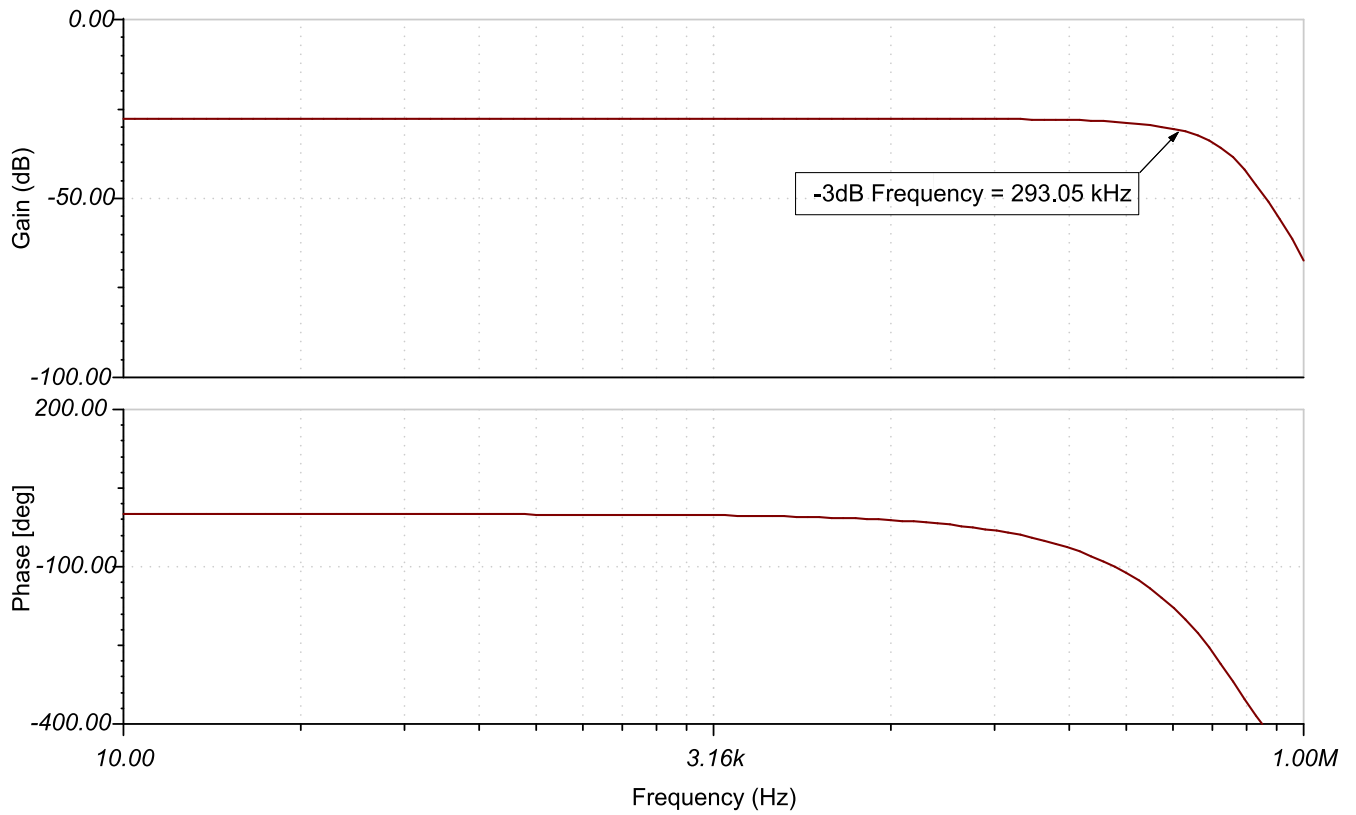

Transient Simulation Results

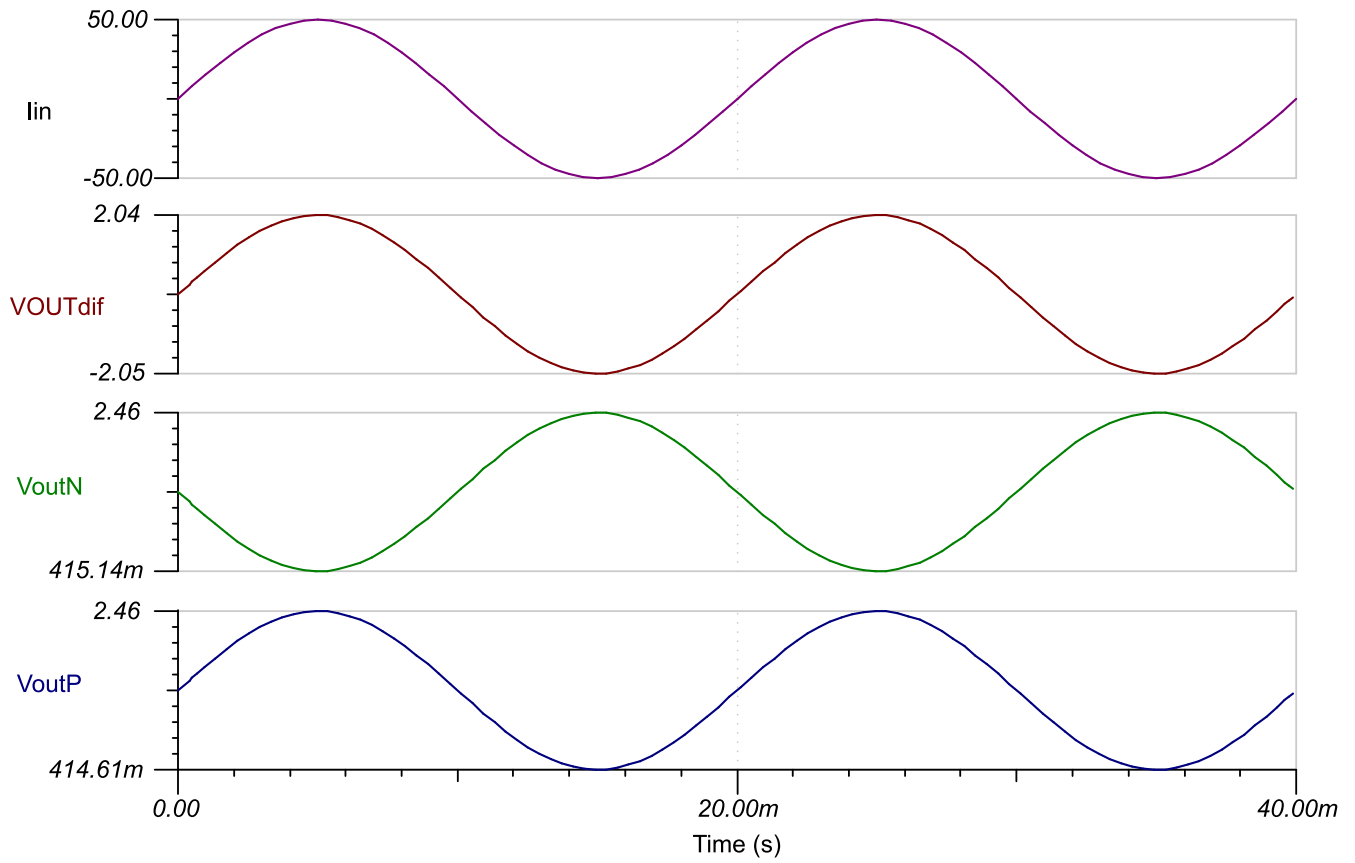

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

Link to Key Files (TINA)

Design files for this circuit – [AMC3301 TINA-TI Reference Design](#)

Design Featured Op Amp

AMC3301	
Working voltage	1000V _{RMS}
Gain	8.2V/V
Bandwidth	300kHz TYP
Linear input voltage range	±250mV
www.ti.com/product/AMC3301	

Design Alternate Op Amp

AMC3330	
Working voltage	1000V _{RMS}
Gain	2V/V
Bandwidth	310kHz TYP
Linear input voltage range	±1000mV
www.ti.com/product/AMC3330-Q1	

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated