

Noninverting circuit for high-to-low voltage level translation to drive ADC


Art Kay

Input	ADC Input	Digital Output ADS8860
-10V	0.2V	0A3D _H or 2621 _d
10V	4.8V	F5C3 _H or 62915 _d

Power Supplies		
V _{ref}	AVDD	DVDD
5V	3.0V	3.0V

Design Description

This circuit document describes how to translate a high-voltage signal (for example, $\pm 10\text{V}$) to a low voltage ADC input (for example, 0V to 5V). This circuit does not require any high-voltage supply to operate, but rather uses a voltage divider and level shift to translate the input signal. This circuit shows the [OPA320](#) op amp and [ADS8860](#) SAR ADC, but the topology could be applied to many different ADCs. This design can be used in a wide range of applications where a high-voltage input needs to be translated such as [analog input modules](#) for PLCs, [lab instrumentation](#), and [factory automation](#).

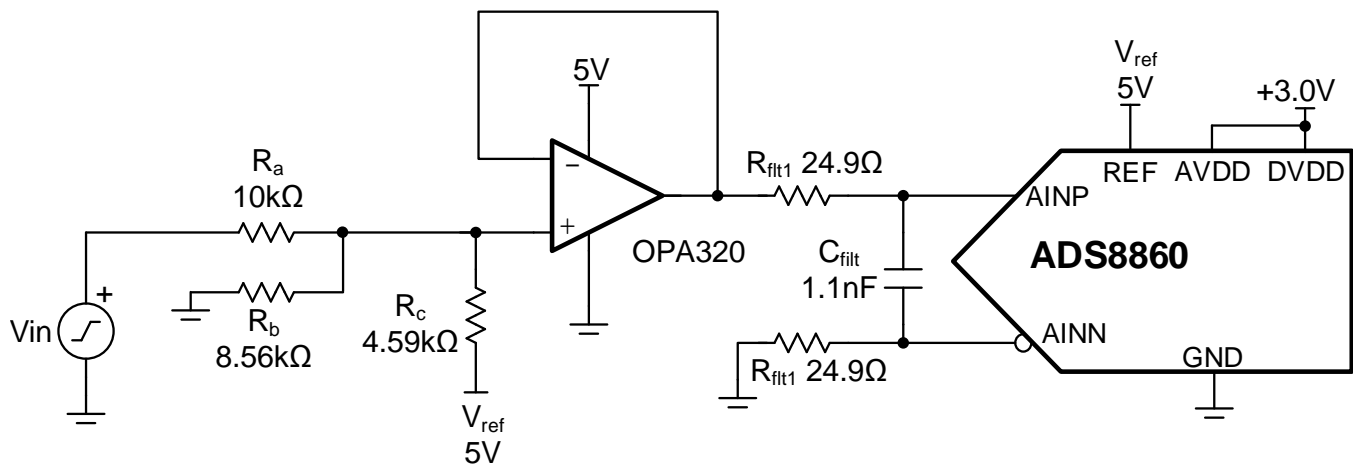

Specifications


Specification	Goal	Calculated	Simulated
Bandwidth	> 1MHz	2.9MHz	4.06MHz
Noise	< 1/2LSB = 38.1 μ V	23.56 μ V _{RMS}	21.04N μ V _{RMS}
Transient settling error	< 1/2 LSB = 38.1 μ V		35 μ V

Design Notes

1. Select a C0G type capacitor for C_{filt} to minimize distortion.
2. Use 0.1% 20ppm/°C film resistors or better to minimize gain error and drift.
3. The input impedance of this circuit is $R_{in} = R_a + R_b || R_c$. For a high-impedance input, use a high-voltage amplifier buffer (for example, V_{cc} = +15V and V_{ee} = -15V). Alternatively, increase the input impedance by multiplying R_a, R_b, and R_c by the same factor. However, increasing the resistance on all the resistors will impact the system noise.

Component Selection

- The first step is to select the amplifier input and output range. In this example, the input range is -10V to $+10\text{V}$. The amplifier output range is set according to the ADC input and the amplifier linear output range. The ADC input range in this example is set by the reference voltage and is 5V . The amplifier supply is set to 5V to match the ADC input range. The output of the amplifier cannot swing to the power supply rails because of output swing limitations (that is, linear range for OPA320 $0.1\text{V} < V_{\text{OUT}} < 4.9\text{V}$). For this example, an output swing of 0.2V to 4.8V is selected for the input signal of -10V to 10V . The output range could have been set as 0.1V to 4.9V to match the linear range, but in this example design margin is added to account for power supply variation.
- Use the [Analog Engineer's Calculator](#) in the next step to select component values. Enter the input and output voltages and reference voltage ($-10\text{V} < V_{\text{IN}} < +10\text{V}$, and $0.2\text{V} < V_{\text{OUT}} < 4.8\text{V}$). The range of acceptable reference voltages is given at the bottom of the tool (3.35V to 12V , in this example). A reference of 5V is selected as this reference voltage is available elsewhere in the circuit. The tool outputs the 0.1% resistors required to map the voltages ($R_a = 10\text{k}\Omega$, $R_b = 8.56\text{k}\Omega$, $R_c = 4.59\text{k}\Omega$).

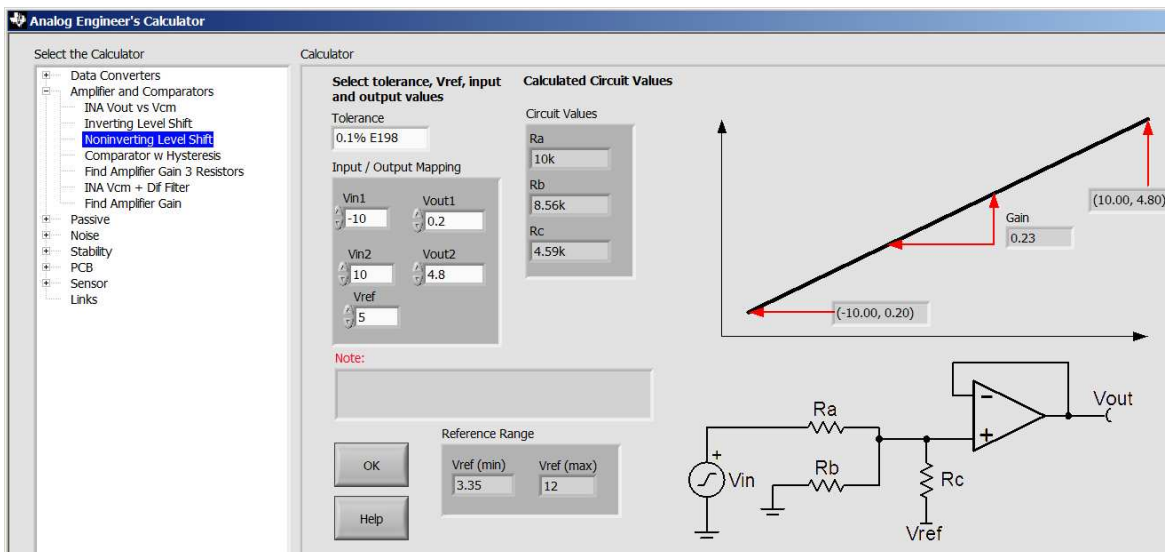

- The following equations show the transfer function for the non-inverting level-shift topology. It is possible to use these equations to solve for the different component values rather than the calculator. To do this, choose a reference value and fix the value of R_a to $10\text{k}\Omega$. Once this is done, solve for R_b and R_c for two different values of output signal. The algebra for this problem is a little complex, so the calculator is the suggested method. Use the equations to verify the transfer function as the equation following shows.

$$V_O = \frac{(R_b \parallel R_c)}{R_a + (R_b \parallel R_c)} \cdot V_{\text{IN}} + \frac{(R_a \parallel R_b)}{R_c + (R_a \parallel R_b)} \cdot V_{\text{ref}}$$

where

$$R_b \parallel R_c = \frac{R_b \cdot R_c}{R_b + R_c} \text{ and } R_a \parallel R_b = \frac{R_a \cdot R_b}{R_b + R_c}$$

Using the values from the calculator:

$$R_a = 10\text{k}\Omega, R_b = 8.56\text{k}\Omega, R_c = 4.59\text{k}\Omega$$

$$V_O = 0.23005V \cdot V_{\text{IN}} + 2.506V$$


$$V_O(-10\text{V}) = 0.2055V$$

$$V_O(+10\text{V}) = 4.8065V$$

- Find R_{filt} and C_{filt} to allow for settling at 1Mps . The [Refine the Rfilt and Cfilt Values](#) video from the *TI Precision Labs - ADCs* video series shows the algorithm for selecting R_{filt} and C_{filt} . The final value of 24.9Ω and 1.1nF proved to settle to well below $\frac{1}{2}$ of a least significant bit (LSB).

DC Transfer Characteristics


The following graph shows the linear output response for a -10-V to 10-V input. In this case, the amplifier output is approximately 0.2V for a -10-V input and 4.8V for a +10-V input. This design was scaled so that the output range avoids the nonlinear power supply rails by 0.2V. See the TI Precision Labs - ADCs [Determining a SAR ADC's Linear Range when using Operational Amplifiers](#) video for detailed theory on this subject.

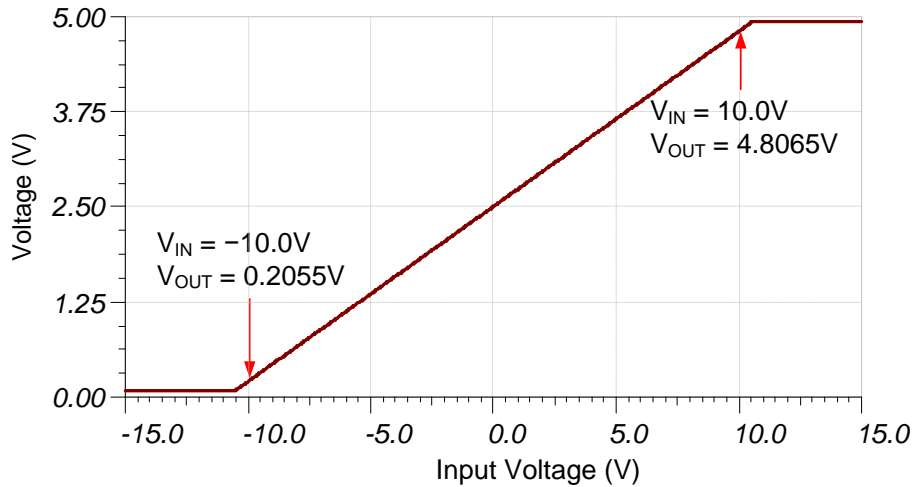

AC Transfer Characteristics


The bandwidth is limited by the RC charge bucket circuit. The calculated and simulated bandwidth compare well (calculated $f_c = 2.9\text{MHz}$, simulated $f_c = 4.06\text{MHz}$). The small discrepancy in the bandwidth is due to gain peaking on the OPA320 device. See the [Op Amps Bandwidth](#) video series for more details on this subject.
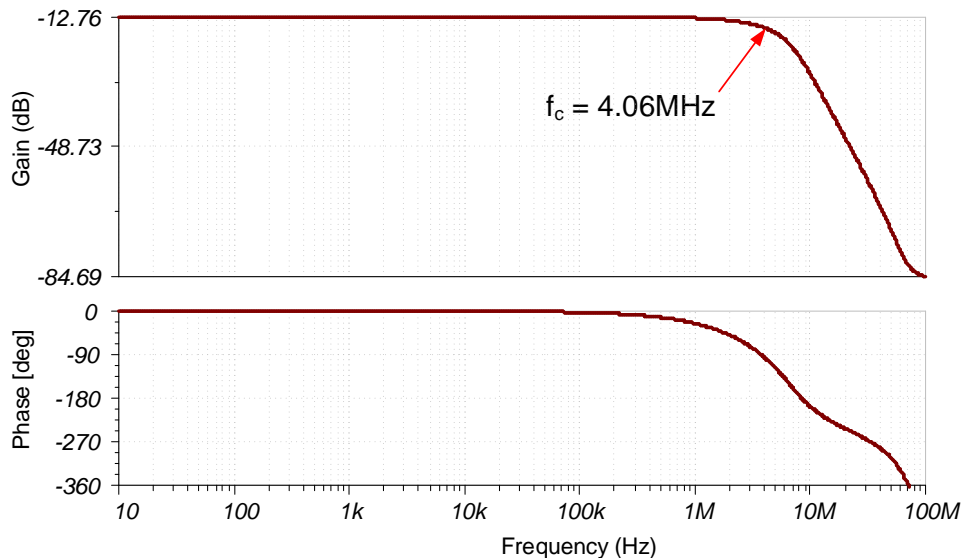
$$f_c = \frac{1}{2\pi \cdot (2 \cdot 24.9\Omega) \cdot (1.1\text{nF})} = 2.9\text{MHz}$$



Transient ADC Input Settling Simulation

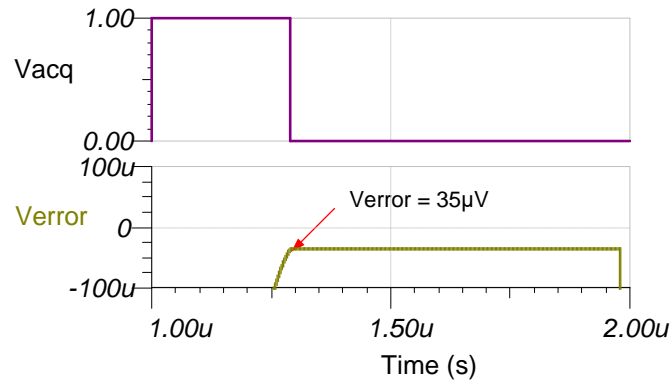The following simulation shows settling to a +10-V DC input signal. This type of simulation shows that the sample and hold kickback circuit is properly selected. See the [Final SAR ADC Drive Simulations](#) for detailed theory on this subject.



Noise Simulation

The following noise calculation takes into account the thermal noise of the resistor network, the amplifier noise, and the bandwidth limit from the RC filter. The calculated total noise is $23.5\mu\text{V}_{\text{RMS}}$ and the simulated total noise is $21.04\mu\text{V}_{\text{RMS}}$. See the [Op Amp Noise Calculation](#) video for detailed theory on amplifier noise calculations, and the [Calculating the Total Noise for ADC Systems](#) video for data converter noise.

Noise equivalent input resistor network:

$$R_{\text{eq}} = \frac{1}{\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c}} = \frac{1}{\frac{1}{10\text{k}\Omega} + \frac{1}{8.56\text{k}\Omega} + \frac{1}{4.59\text{k}\Omega}} = 2.3\text{k}\Omega$$

Resistor network noise:

$$e_{\text{nReq}} = \sqrt{4\text{kTR}} = \sqrt{4 \cdot (1.381 \cdot 10^{-23}) \cdot (273 + 25) \cdot 2.3\text{k}\Omega} = 6.164 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$


OPA320 noise density:

$$e_{\text{nOPA320}} = 7 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$

Total noise:

$$e_{\text{nTOT}} = \sqrt{e_{\text{nOPA320}}^2 + e_{\text{nReq}}^2} \cdot \sqrt{K_n \cdot f_c}$$
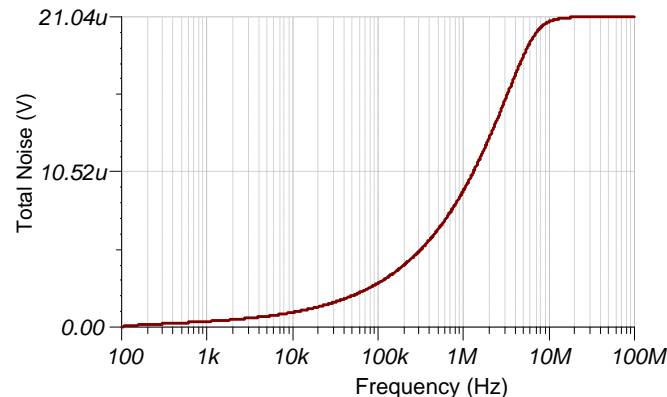
$$e_{\text{nTOT}} = \sqrt{\left(7 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2 + \left(6.164 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2} \cdot \sqrt{1.57 \cdot 4.06\text{MHz}} = 23.56\mu\text{V}_{\text{RMS}}$$



Design Featured Devices and Alternative Parts

Device	Key Features	Link	Other Possible Devices
ADS8860	16-bit resolution, SPI, 1-Msps sample rate, single-ended input, Vref input range 2.5V to 5.0V.	http://www.ti.com/product/ADS8860	http://www.ti.com/adcs
OPA320	20-MHz bandwidth, rail-to-rail with zero crossover distortion, $V_{OS(MAX)} = 150\mu V$, $V_{OS(DriftMAX)} = 5\mu V/^{\circ}C$, $e_n = 7nV/\sqrt{Hz}$	http://www.ti.com/product/OPA320	http://www.ti.com/opamps

Link to Key Files

TINA source files – <http://www.ti.com/lit/zip/SBAC250>.

Design References

See *Analog Engineer's Circuit Cookbooks* for TI's comprehensive circuit library.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated