

# DC+ Bus Power-Supply Solution Using Bootstrap Charge Pump Technique



Eason Tian

Precision ADC

## ABSTRACT

DC+ (DC bus positive side) overcurrent protection is widely used in industrial systems. Compared with the traditional discrete solution, the isolated comparator (AMC23C11) can achieve better performance. This article introduces a cost-effective approach for generating the power supply for the isolated comparator sitting on the DC+ side. This approach uses a bootstrap charge pump technique to generate a stable power supply on DC+.

## Table of Contents

<b>1 Background</b> .....	2
<b>2 Overcurrent Protection on DC+</b> .....	3
<b>3 DC+ Power Supply Solution</b> .....	4
3.1 Selection of Charge Pump Capacitor.....	5
3.2 Simulation in PSpice® for TI.....	5
3.3 Hardware Test.....	7
3.4 Low-Cost Power Supply Solution.....	7
<b>4 Power-On Short-Circuit Risk and Solution</b> .....	8
<b>5 Reference</b> .....	9

## List of Figures

Figure 2-1. DC+ Overcurrent Protection.....	3
Figure 3-1. DC+ Power Supply Solution.....	4
Figure 3-2. Simulation Model.....	5
Figure 3-3. 1 kHz, 20% Duty Cycle Power Supply.....	6
Figure 3-4. Increase Capacitor Value From 1 $\mu$ F to 30 $\mu$ F.....	6
Figure 3-5. Low-Cost Power Supply Solution.....	7
Figure 4-1. Output Behavior for Long Settling Times of the Reference Voltage (AMC23C11).....	8
Figure 4-2. Add DC- Short-Circuit Protection.....	8

## List of Tables

Table 3-1. 1-kHz Switching Frequency.....	7
Table 3-2. 20-kHz Switching Frequency.....	7

## Trademarks

PSpice® is a registered trademark of Cadence Design Systems, Inc..  
All trademarks are the property of their respective owners.


## 1 Background

Fault-detection mechanisms are a necessity in high-power industrial systems such as motor drives and solar inverters, as well as automotive systems including electric vehicle (EV) chargers, traction inverters, onboard chargers and DC/DC converters. DC bus-based overcurrent protection is widely used in electric motor drives. The traditional implementation of overcurrent (OC) fault detection is discrete with a combination of non-isolated multichannel comparators and either optocouplers or digital isolators. To meet the growing needs of fault detection, TI is introducing a new family of basic and reinforced isolated comparators to the TI isolation portfolio. The primary use case is ultra-fast overcurrent, overvoltage, over temperature detection in high-voltage industrial and automotive HEV/EV systems. Its smaller PCB area is particularly suitable for applications with miniaturization and high-power density needs. Compared with traditional solutions, it has significant advantages in CMTI, response time, threshold accuracy, hysteresis, and latching function.

The power supply on DC+ for overcurrent protection can be generating by either adding a transformer or adding an additional secondary winding to an existing transformer. However, technical challenges such as transformer size limitations or the proximity of these transformers to the actual OC implementation will practically limit such a transformer-based implementation.

## 2 Overcurrent Protection on DC+

Figure 2-1 shows how the OC protection based on the DC+ bus can protect three short-circuit situations: a shoot-through fault of IGBT (blue), DC+ ground fault (red), and phase-to-phase short fault (yellow).

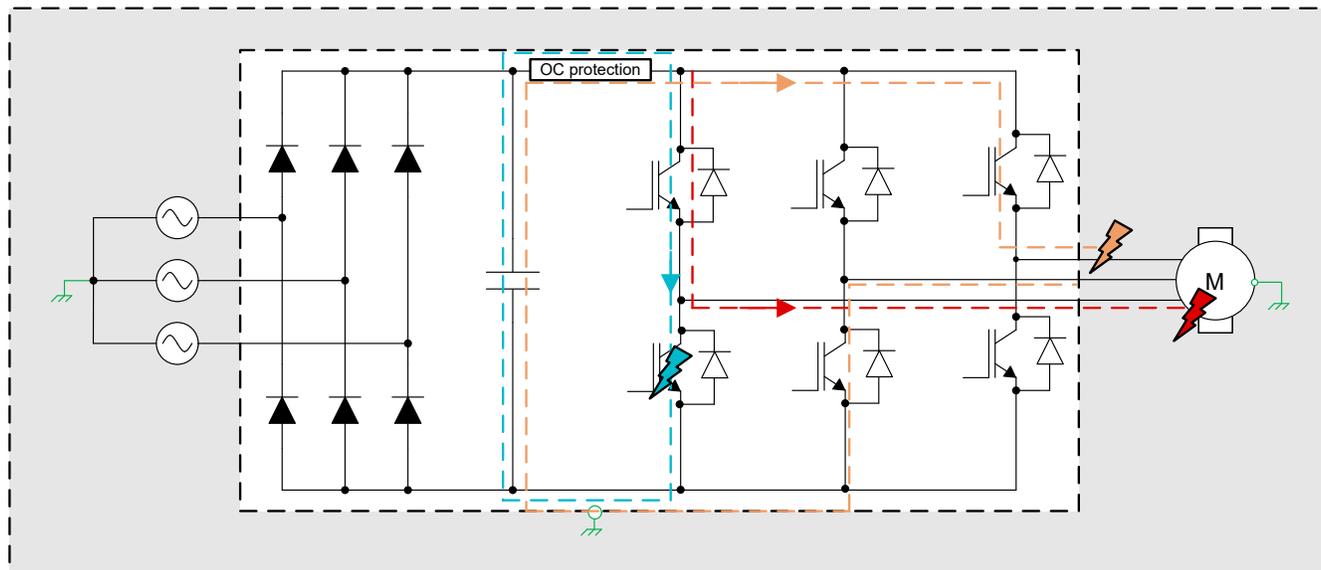

**Figure 2-1. DC+ Overcurrent Protection**

Adding an isolated comparator such as a single threshold comparator AMC23C11 for OC detection ensures appropriate detection and protection of power circuits from these three conditions. The dual-threshold version (AMC23C14) can achieve both short circuit and overload protection.

As there is no need for a power supply on DC+ other than for an isolated comparator, a simple, low-cost, and low BOM implementation is critical.



### 3.1 Selection of Charge Pump Capacitor

The selection of the two capacitors, C2 and C7, is important to minimize the ripple on the generated power supply. The following is an example to calculate the capacitor value under extreme conditions. The good news is that the integrated low-dropout (LDO) regulator on the high-side of the AMC23C11 eases the pre-regulation requirements of this power supply. As an example, this design is capable of taking a ripple voltage of 3 V, and other parameters are as follows:

- Half-bridge circuit switching frequency  $f = 1 \text{ kHz}$
- Duty cycle  $D = 20\%$
- Current required for isolated comparator  $I = 3.3 \text{ mA (max)}$
- Low-side driver supply  $U_{\text{low side}} = 15 \text{ V}$

Switching frequencies in motor drive systems are typically 1 kHz to 20 kHz. Lower switching frequencies result in larger ripple because of longer discharge times. Increasing the capacitance reduces the ripple but increases the charging time. Assume the switching frequency is 1 kHz and 20% duty cycle in the extreme case. This case means that the isolated comparator is powered only by the capacitor C2 of the charge pump for 80% of a PWM cycle, the minimum capacitance required for C2 under this condition is:

$$Q = I \times t = \Delta U \times C \tag{1}$$


$$C = \frac{I \times t}{\Delta U} = \frac{3.3 \text{ mA} \times 0.8 \text{ ms}}{3 \text{ V}} = 0.88 \text{ } \mu\text{F} \tag{2}$$

In this design, C2 takes a capacitance of 1  $\mu\text{F}$  and the bootstrap capacitor C7 is also 1  $\mu\text{F}$ . R4 and R6 limit the high currents that may occur during initial power-up. Typical values for this resistor are 5  $\Omega$  to 10  $\Omega$ . A larger resistance increases the time constant of the RC circuit and prolong the time to reach the minimum supply. When R4 is taken as 10  $\Omega$ , the maximum current at initial power-up is 1.36 A:

$$I_{\text{Rboot}} = \frac{15 \text{ V} - 0.7 \text{ V} \times 2}{10 \text{ } \Omega} = 1.36 \text{ A} \tag{3}$$

The two diodes D1 and D2 should be able to withstand the voltage of DC bus. For a motor drive system with a 380 VAC input, the diodes need to have a withstand voltage value  $\geq 1200 \text{ V}$ , and must have fast reverse recovery characteristics to minimize the recovery charge and thereby ensure the stability of the supply circuit. The circuit can theoretically generate a supply voltage of 13.6 V, which is 15 V minus the voltage drop of the two diodes (0.7 V).


### 3.2 Simulation in PSpice® for TI

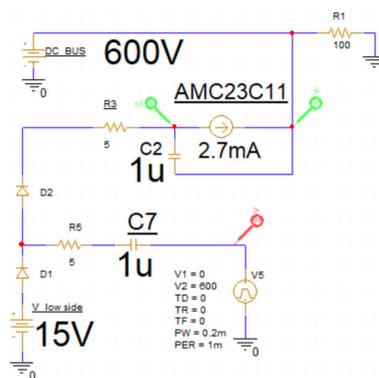

**Figure 3-2. Simulation Model**

The DC bus in the simulation model is 600 V, a 2.7-mA current source is used to simulate the isolated comparator, the square wave source V5 simulates the switch of the half bridge. The low-side supply is 15 V. Both capacitors, C2 and C7, are 1  $\mu\text{F}$  and the current-limiting resistors R3 and R5 are 5  $\Omega$ .


The supply voltage of the isolated comparator ( $V_{\text{DC+}}$ ) and the half-bridge center point voltage ( $V_{\text{half bridge}}$ ) are measured at 1-kHz switching frequency and 20% duty cycle as [Figure 3-3](#) shows.

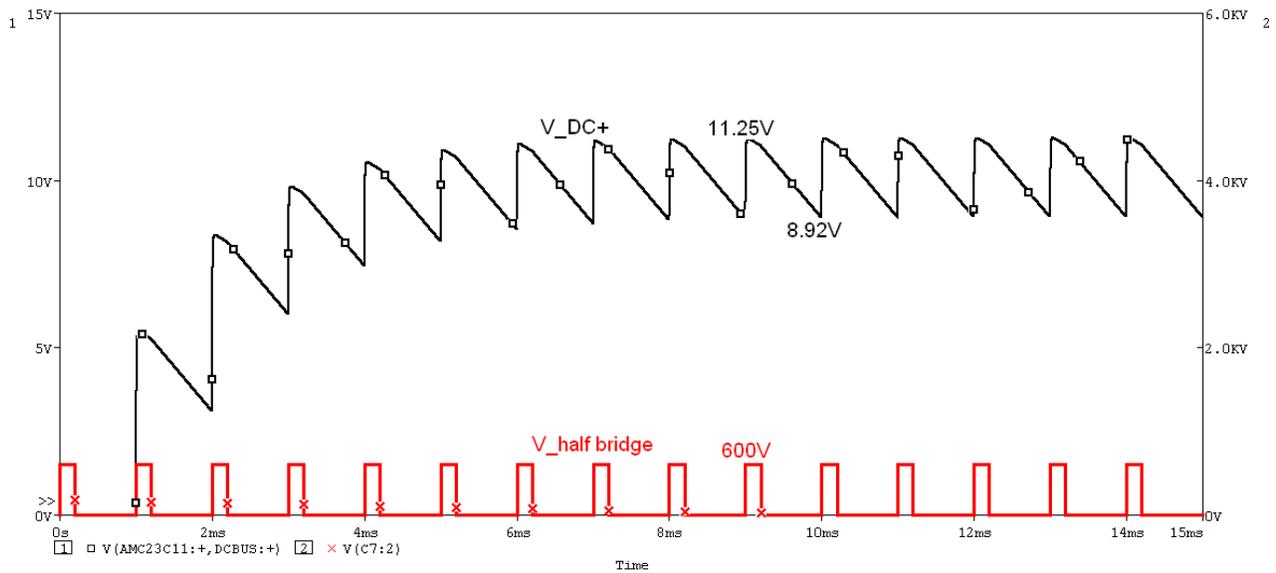

**Figure 3-3. 1 kHz, 20% Duty Cycle Power Supply**

In **Figure 3-3**, the power supply is stabilized between 11.25 V and 8.92 V after a few PWM cycles, that is, there is a ripple of 2.33 V. Since the half-bridge circuit turns on the upper IGBT first in the first cycle, the isolated comparator is not powered until one cycle later, that is, the system is not protected from power-up short-circuit in the first cycle. An optimized solution to minimize risk is provided in **Section 4**.

Keeping the same switching frequency and duty cycle, increase the C2 and C7 simultaneous capacitance value from 1  $\mu\text{F}$  to 30  $\mu\text{F}$  gradually. This method reveals that the supply voltage gradually increases and gets closer to the ideal value (13.6 V), and the power supply ripple also decreases.

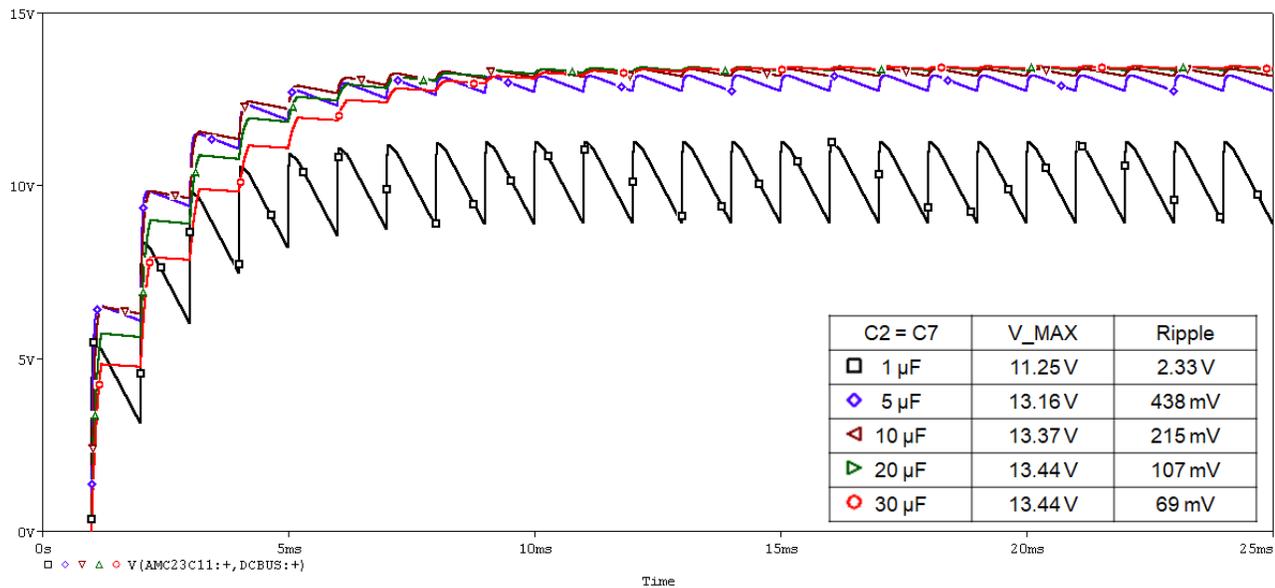

**Figure 3-4. Increase Capacitor Value From 1  $\mu\text{F}$  to 30  $\mu\text{F}$**

In **Figure 3-4**, V\_MAX is the maximum voltage value that can be achieved with a stable supply. Therefore, controlling the capacitance of the two capacitors above 5  $\mu\text{F}$  to obtain a more stable supply voltage is recommended. But a capacitance value that is too large will also increase the charging time.

### 3.3 Hardware Test

The actual circuit is built according to the circuit diagram in [Figure 3-1](#), where the capacitor  $C2 = C7 = 1 \mu\text{F}$ ,  $R4 = 10 \Omega$ ,  $R6 = 5 \Omega$ , the low-side driver supply is 15 V, and the DC bus voltage is 10 V. The supply voltage and ripple are tested at different duty cycles for 1 kHz and 20 kHz.

**Table 3-1. 1-kHz Switching Frequency**

Duty Cycle	V_MAX	Ripple
20%	11.4 V	3.44 V
50%	11.9 V	2.96 V
80%	12.2 V	2.16 V


**Table 3-2. 20-kHz Switching Frequency**

Duty Cycle	V_MAX	Ripple
20%	12.9 V	352 mV
80%	12.9 V	104 mV

[Table 3-1](#) and [Table 3-2](#) show that lower switch frequency and lower duty cycle bring lower supply voltage ( $V_{MAX}$ ) and larger ripple. A similar result is obtained for the 150-V DC bus voltage.

### 3.4 Low-Cost Power Supply Solution

The bootstrap circuit in [Section 3.1](#) is similar to the power supply of the high-side gate driver. Through reuse, this power supply can reduce the cost. As shown in [Figure 3-5](#), VCC is the power pin of the high-side gate driver and this solution removes a high-voltage diode (D1) and RC (C7, R6).

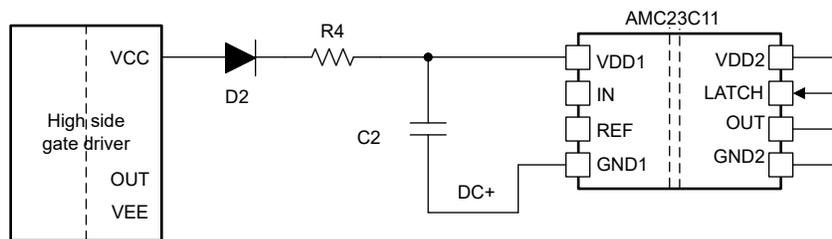

**Figure 3-5. Low-Cost Power Supply Solution**

The solution shown in [Figure 3-5](#) increases a load for the power supply of the gate driver, so it is necessary to pay attention to the impact of the gate driver. Increasing the current-limit resistance ( $R4$ ) can reduce the impact. This solution still has the limitation because the isolated comparator power supply is dependent on the half-bridge circuit operation.

## 4 Power-On Short-Circuit Risk and Solution

Since the bootstrap circuit and charge pump need to wait for one cycle of half-bridge operation before they power the isolated comparator. After VDD1 has powered up to greater than 3 V, the capacitor on the reference pin must charge to the threshold voltage before the isolated comparator is functional. Figure 4-1 shows that output of isolated comparator is valid when reference voltage is within 1% of the set value.

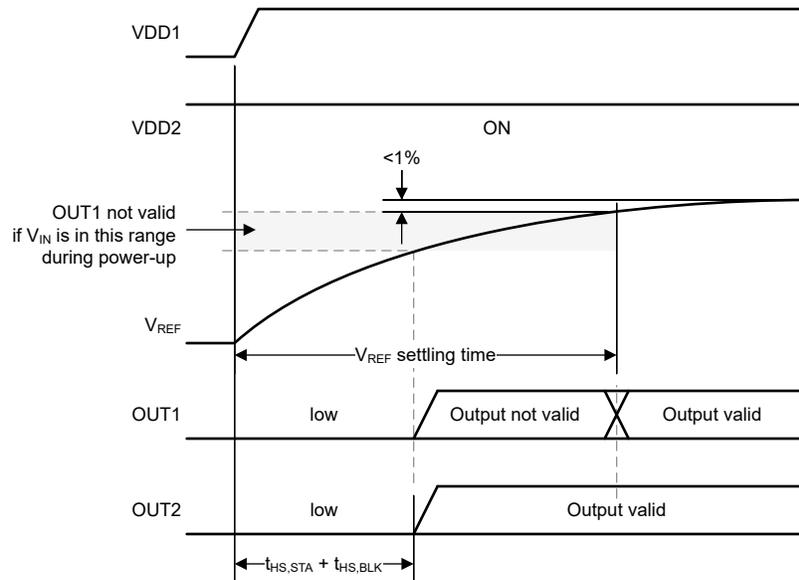


Figure 4-1. Output Behavior for Long Settling Times of the Reference Voltage (AMC23C11)

Therefore, the boot strap charge pump solution is not able to provide OC protection during the initial start-up of the motor drive. This risk can be reduced by adding DC- OC protection and pre-turn on the three low-side IGBTs.

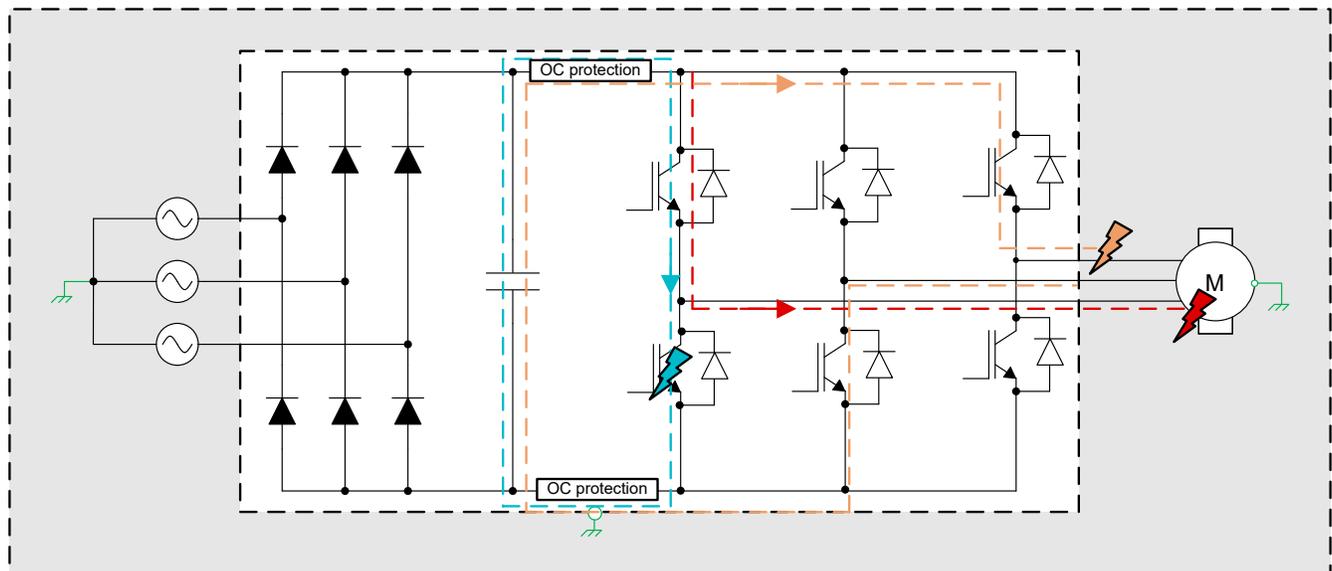


Figure 4-2. Add DC- Short-Circuit Protection

The added DC- protection can share power with the low-side driver, so there is always protection on the DC-. The DC- protection protects against both shoot-through fault (blue) and phase-to-phase short fault (yellow). However, the DC+ ground fault (red) cannot be protected directly through the DC-. Turn on the three lower IGBTs before the IGBT module starts working to detect whether there is a short to ground, and also to charge the bootstrap capacitor.

## 5 Reference

1. Texas Instruments, [TIDA-010036 One-phase shunt electricity meter reference design using standalone ADCs](#) Reference Design
2. Texas Instruments, [AMC23C11 Fast Response, Reinforced Isolated Comparator With Adjustable Threshold and Latch Function](#) Data Sheet
3. Texas Instruments, [Using Isolated Comparators for Fault Detection in Electric Motor Drives](#) Analog Design Journal

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated