

IMPROVE OPA541 CURRENT-LIMIT STABILITY

By Hubert Biagi (602) 746-7422 and R. Mark Stitt

OPA541 is the industry's highest performance monolithic power amplifier. It can operate on $\pm 40V$ power supplies and put out 5A continuously (10A peak). Internal current-limit circuitry can be user-programmed with a single external resistor to protect the amplifier and load from fault conditions.

Under some conditions, the OPA541 may oscillate during current limit. In some applications, this is acceptable. However, you can improve stability during current limit by adding external compensation as shown in Figure 1.

The compensation circuit consists of an R, C network connected to the amplifier drive output as shown. Component values for the network depend on the output current limit desired. Table I below shows recommended values.

CURRENT LIMIT (A)	R _{CL} (Ω)	R ₁ (Ω)	C ₁ (μF)
0.08 to 0.16	10 to 5	0.68 ⁽¹⁾	0.68
0.17 to 0.77	5 to 1	1.3 ⁽¹⁾	0.33
0.78 to 10.0	1 to 0	2.7	0.068

NOTE: (1) You can use two or four parallel connected 2.7Ω resistors to make 1.3Ω or 0.68Ω.

TABLE I. R₁, C₁ Network Values for OPA541—see Figure 1.

CALCULATING CURRENT LIMIT RESISTOR VALUE

OPA541M

$$R_{CL} = \frac{0.809}{I_{CL}} - 0.057$$

OPA541P

$$R_{CL} = \frac{0.813}{I_{CL}} - 0.020$$

Where:

R_{CL} = Current limit resistor (Ω)

I_{CL} = Current limit (A)

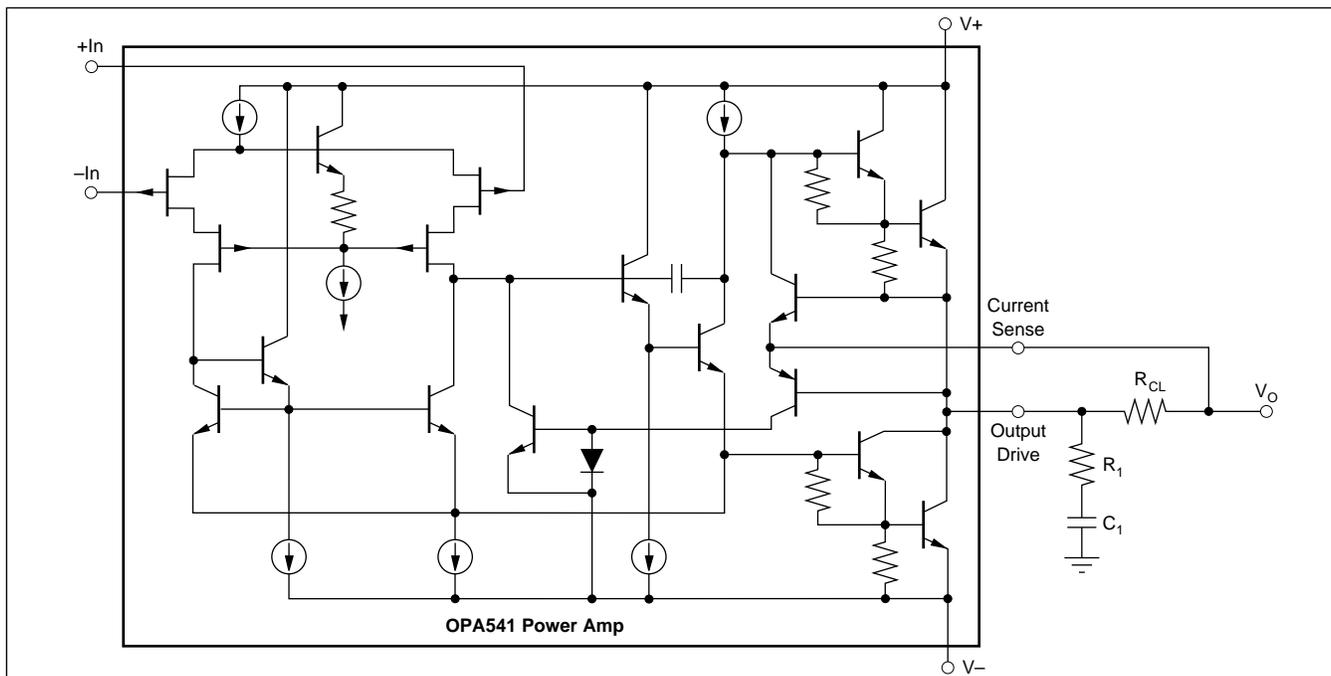


FIGURE 1. An R₁, C₁ network can be added to the OPA541 output to improve stability during current limit.

The information provided herein is believed to be reliable; however, BURR-BROWN assumes no responsibility for inaccuracies or omissions. BURR-BROWN assumes no responsibility for the use of this information, and all use of such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. BURR-BROWN does not authorize or warrant any BURR-BROWN product for use in life support devices and/or systems.

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.