

Transimpedance Considerations for High-Speed Amplifiers

Xavier Ramus
High-Speed Products

ABSTRACT

Designing high-resolution detection circuits using photodiodes presents considerable challenges because bandwidth, gain, and input-referred noise are coupled together. This application note reviews the basic issues of transimpedance design, provides a set of detailed design equations, explains those equations, and develops an approach to easily compare potential solutions.

Contents

1	Introduction	2
2	Stability Analysis	2
3	Bandwidth Considerations	5
4	Noise Considerations	6
5	Example	7
6	DC-Parameters Consideration	8
7	Conclusion	8

List of Figures

1	Transimpedance Circuit with Modeled Elements	2
2	Bode Plot Magnitude	3
3	Maximum Achievable Bandwidth for Selected Op Amps (10pF Source Capacitance)	5
4	Noise Analysis Circuit	6
5	310kΩ Transimpedance Gain with 200pF Source Capacitance Circuit.....	8
6	Maximum Achievable Bandwidth vs Transimpedance Gain for Selected Op Amps	8

1 Introduction

The purpose of a transimpedance circuit is to convert an input current from a current source (typically a photodiode) into an output voltage. The simplest method to achieve this conversion is to use a resistor connected to ground. However, the achievable gain using this method is limited by the following factors:

1. The current source input impedance;
2. The load impedance; and
3. Desired bandwidth.

A closed-loop approach, using an operational amplifier, is normally beneficial to most applications as it has the potential of eliminating those issues. A typical circuit with all necessary components for this analysis is shown in [Figure 1](#). In this circuit, the generator is a photodiode, whose role is to convert the photons into a current. This current is then amplified by the feedback resistor R_F . Working with an ideal amplifier for now, we can see that because no bias current is present, all the signal generated by the photodiode is going to be converted to the output. Note that the source impedance is not of interest here; it is isolated from the output. Note also that the output is low impedance, allowing a wide variety of load to be connected. The bandwidth is going to be a function of the source capacitance (C_S), the feedback capacitance (C_F), and the gain bandwidth product of the actual amplifier used.

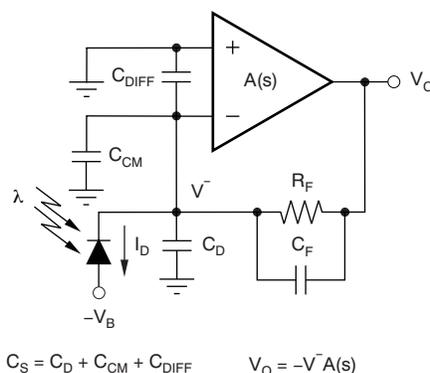


Figure 1. Transimpedance Circuit with Modeled Elements

The source capacitance (C_S) is the sum of the photodiode capacitance (C_D), the common-mode capacitance of the amplifier (C_{CM}), and the differential capacitance of the amplifier (C_{DIFF}). C_{CM} and C_{DIFF} include both the board layout and the op amp parasitic capacitance.

2 Stability Analysis

The first non-ideal op-amp characteristic we examine here is the non-infinite open-loop gain. The architecture for the operational amplifier used in the rest of this application report is a single pole op-amp model, as shown in [Equation 1](#). This model allows us to analyze the resulting transimpedance design as a second-order, closed-loop transfer function.

$$A(s) = \frac{A_{OL} \cdot \omega_A}{s + \omega_A} \quad (1)$$

Expressing the Laplace transfer function in Bode analysis form yields the following equation.

$$\frac{V_O}{I_D} = \frac{-Z_F}{1 + \left(\frac{1 + \frac{Z_F}{Z_G}}{A(s)} \right)} \quad (2)$$


where:

$$Z_F = R_F \parallel \frac{1}{s \cdot C_F} = \frac{1}{s + \frac{1}{R_F \cdot C_F}} \quad (3)$$

$$Z_G = \frac{1}{s \cdot C_S} \quad (4)$$

At dc, and if the open-loop gain of the amplifier is infinite, the amplifier gain is set by the feedback resistor. This effect can be seen by setting $s = 0$ in Equation 3 and plugging the result into Equation 2 while setting $A(s) = \infty$.

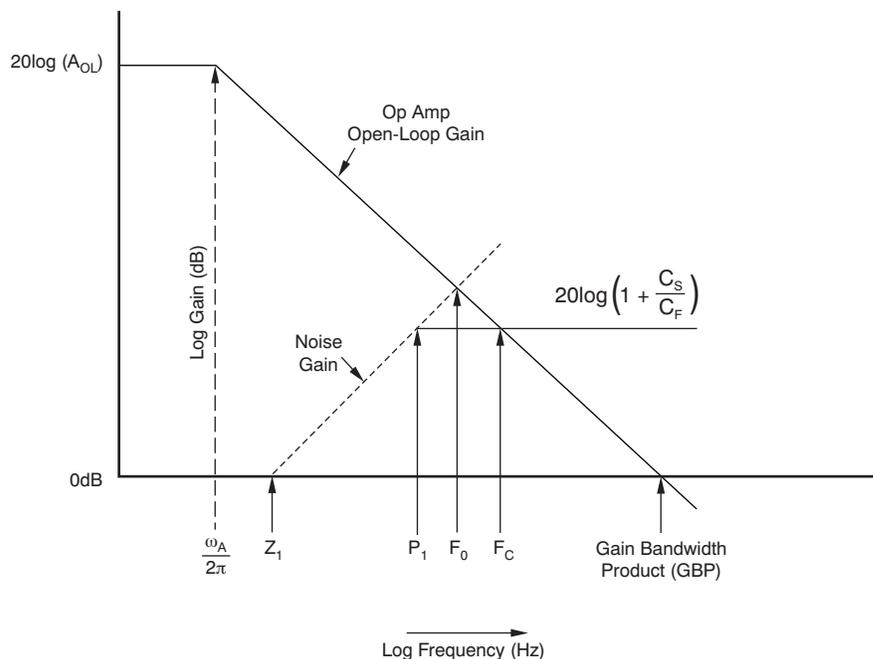$1 + \frac{Z_F}{Z_G}$ is the noise gain. The loop gain is the difference between the open-loop gain (A_{OL}) and the noise gain. The noise gain is plotted in Figure 2 alongside the single pole, open-loop gain model of the amplifier.



$$Z_1 = \frac{1}{2\pi R_F (C_S + C_F)} \text{ Hz}$$

$$P_1 = \frac{1}{2\pi R_F C_F} \text{ Hz}$$

$$F_0 = \sqrt{Z_1 \cdot \text{GBP}}$$

$$F_C = \frac{\text{GBP}}{\left(1 + \frac{C_S}{C_F}\right)}$$

Figure 2. Bode Plot Magnitude

At dc, the gain is indeed the expected transimpedance gain R_F , while at high frequency, it is $1 + \frac{C_S}{C_F}$. Note that only the feedback capacitor (C_F) and the source capacitance (C_S) are used for stability; consequently, it can be noted that a unity-gain stable amplifier is not necessary for transimpedance applications. In fact, it is recommended to use a decompensated amplifier instead, because these decompensated amplifiers offer better voltage noise specifications and larger gain bandwidth products than any compensated version. This fact is easily illustrated by two families of devices: the [OPA842/3/6/7](#) and the [OPA656/7](#). The OPA842 is unity-gain stable and has 2.7nV/ $\sqrt{\text{Hz}}$ input voltage noise. The OPA843 is stable for gains greater than 3V/V and has a voltage noise of 2nV/ $\sqrt{\text{Hz}}$. The OPA846 is stable for gains greater than 7V/V and has a 1.2nV/ $\sqrt{\text{Hz}}$ voltage noise. Finally, the OPA847 has a voltage noise of 0.85nV/ $\sqrt{\text{Hz}}$ and is stable for gains greater than 12V/V. For FET devices such as the OPA656 and OPA657, the OPA656 provides unity-gain stability with a 7nV/ $\sqrt{\text{Hz}}$ input voltage noise; the OPA657 has a 4.8nV/ $\sqrt{\text{Hz}}$ voltage noise, but is stable for gains greater than 7V/V.

Coming back to the analysis and expressing the full transfer function as a function of ω_0 and Q.—given in Equation 5 with Equation 6 and Equation 7 expressing ω_0 and Q with physical elements of the circuit—yields the following results:

$$\frac{V_O}{I_D} = R_F \cdot \frac{A_{OL}}{A_{OL} + 1} \cdot \frac{\omega_o^2}{s^2 + s \cdot \frac{\omega_o}{Q} + \omega_o^2} \quad (5)$$

$$\omega_o = 2\pi \cdot F_0 = \sqrt{\frac{(A_{OL} + 1) \cdot \omega_A}{R_F \cdot (C_S + C_F)}} \quad (6)$$

$$Q = \frac{\sqrt{\frac{(A_{OL} + 1) \cdot \omega_A}{R_F \cdot (C_S + C_F)}}}{\omega_A \cdot \left(1 + A_{OL} \cdot \frac{C_F}{C_S + C_F}\right) + \frac{1}{R_F \cdot (C_S + C_F)}} \quad (7)$$

Setting $Z_1 = \frac{1}{R_F \cdot (C_S + C_F)}$, and recognizing that the gain bandwidth product (GBP) is equal to $GBP = \frac{A_{OL} \cdot \omega_A}{2\pi}$ and using the following algebraic simplifications:

- $C_S \gg C_F$ to simplify Z_1
- $(A_{OL} + 1) \cdot \omega_A \cong A_{OL} \cdot \omega_A = 2\pi \cdot GBP$
- $\left(1 + A_{OL} \cdot \frac{C_F}{C_S + C_F}\right) \cong A_{OL} \cdot \frac{C_F}{C_S + C_F}$

Leads to the following:

$$F_0 = \sqrt{Z_1 \cdot GBP} \quad (8)$$

$$Q = \frac{F_0}{Z_1 + F_C} \quad (9)$$

Further simplification on Q leads to these easier-to-use equations:

$$F_0 = \sqrt{Z_1 \cdot GBP}$$

$$Q = \frac{P_1}{F_0} \quad (10)$$

with:

$$P_1 = \frac{1}{2\pi \cdot R_F C_F} \quad (11)$$

3 Bandwidth Considerations

Maximum bandwidth will be achieved for a Butterworth response with $Q = 0.707$. This result is an interesting point because this is also equivalent to saying that the -3dB bandwidth is equal to F_0 , and allows us to derive a design equation that proves very useful for amplifier selection.

$$\text{GBP} = 2\pi \cdot F_{-3\text{dB}}^2 \cdot R_F C_S \tag{12}$$

Note that the -3dB bandwidth and the transimpedance gain are desired parameters and the source capacitance is known. Thus, Equation 12 allows you to do the following:

- Knowing the bandwidth required by the application, the photodiode capacitance, and the transimpedance gain specification, calculate the minimum GBP requirement for the amplifier
- Knowing the amplifier, the transimpedance gain, and the photodiode capacitance, calculate the maximum achievable bandwidth

We can use this last point to calculate the maximum achievable bandwidth for a few selected amplifiers. The OPA847 is a 3.9GHz GBP amplifier with $0.85\text{nV}/\sqrt{\text{Hz}}$ input voltage noise. The OPA846 has a 1.75GHz GBP with a $1.2\text{nV}/\sqrt{\text{Hz}}$ input voltage noise. The OPA843 is a 800MHz GBP device with a $2\text{nV}/\sqrt{\text{Hz}}$ input voltage noise. All three amplifiers—OPA847, OPA846 and OPA843—are bipolar amplifiers. Finally, the OPA657 is a 1.65GHz GBP device with a $4.8\text{nV}/\sqrt{\text{Hz}}$ input voltage noise. Unlike the other three devices, the OPA657 is a FET input amplifier.

Figure 3 shows an example of achievable bandwidth versus transimpedance gain for a 10pF source capacitance for various amplifiers.

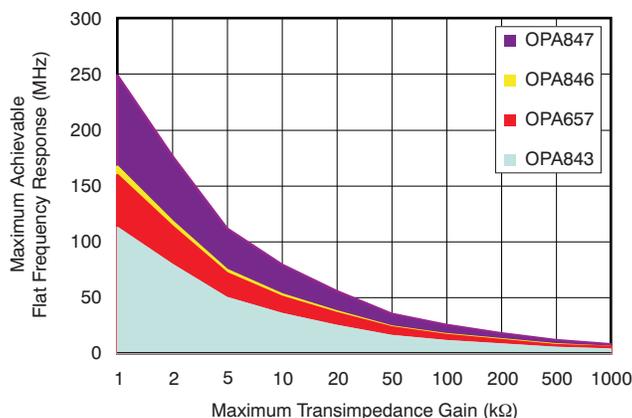


Figure 3. Maximum Achievable Bandwidth for Selected Op Amps (10pF Source Capacitance)

The relative performance for each amplifier is maintained as the source capacitance varies. Note that the source capacitance in this example considers the amplifier parasitic, both common-mode and differential capacitance. When multiple amplifiers can be selected to meet the desired performance—for example, for $R_F = 20\text{k}\Omega$, $f_{-3\text{dB}} = 10\text{MHz}$ —other considerations such as noise or power dissipation must be considered before making the amplifier selection.

At first glance, using a FET input amplifier does not present any advantages and has one major inconvenience: its high input voltage noise. The noise analysis will be developed next and then the relative performance of bipolar technology will be compared with FET technology.

4 Noise Considerations

The equivalent input current noise for a transimpedance amplifier makes the following assumptions:

- This evaluation is an integrated noise analysis that uses spot noise over frequency, and is not intended to be used as a spot noise equation for narrowband applications.
- The application is dc-coupled, pulse-oriented where the integrated noise is of interest.
- The final signal bandwidth for both the transimpedance design and any post-filtering is greater than 10 times the 1/f noise corner frequency of any of the amplifier noise terms. This consideration allows those effects to be neglected.
- The transimpedance bandwidth is set greater than the post-filtering.
- The current noise term on the noninverting is either negligible or made negligible by providing adequate bypassing.

With these assumptions at hand, the noise terms of interest are shown in [Figure 4](#).

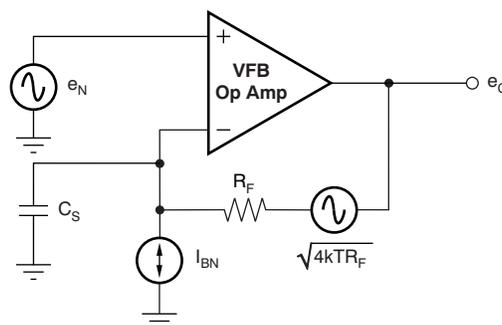


Figure 4. Noise Analysis Circuit

The equivalent input-referred noise current for wideband transimpedance design is provided in [Equation 13](#).

$$i_{EQ} = \sqrt{i_B^2 + \frac{4kT}{R_F} + \left(\frac{e_N}{R_F}\right)^2 + \frac{(e_N 2\pi F C_S)^2}{3}} \quad (13)$$

where:

- i_B = inverting input spot current noise
- $4kT = 16 \times 10^{-21} \text{J}$ at 290 degrees Kelvin
- R_F = feedback resistor
- e_N = noninverting input spot voltage noise
- C_S = inverting input total capacitance
- F = noise integration frequency limit

All these parameters except the noise integration frequency limit can be found in the respective operational amplifier product data sheet. The noise integration frequency limit (F) represents the equivalent *brick-wall* filter of a post-amplifier passive filter.

Using [Equation 13](#) and comparing two amplifiers with very similar GBP—the OPA846 and the OPA657—we can then determine an appropriate transimpedance gain threshold. Below this threshold, it is preferable to use bipolar technology to achieve lower noise, while above the threshold it is better to use FET technology. For this comparison, we will consider that the noise integration frequency limit is the same for both amplifiers. This problem is expressed in [Equation 14](#).

$$\sqrt{i_{B(BIP)}^2 + \frac{4kT}{R_F} + \left(\frac{e_{N(BIP)}}{R_F}\right)^2 + \frac{(e_{N(BIP)} \cdot 2\pi \cdot F \cdot C_{S(BIP)})^2}{3}} = \sqrt{i_{B(FET)}^2 + \frac{4kT}{R_F} + \left(\frac{e_{N(FET)}}{R_F}\right)^2 + \frac{(e_{N(FET)} \cdot 2\pi \cdot F \cdot C_{S(FET)})^2}{3}} \quad (14)$$

The solution for R_F is shown in Equation 15.

$$R_F = \sqrt{\frac{e_{N(FET)}^2 - e_{N(BIP)}^2}{i_{B(BIP)}^2 - i_{B(FET)}^2 + \frac{2\pi \cdot F}{3} \cdot (C_{S(BIP)} \cdot e_{N(BIP)}^2 - C_{S(FET)} \cdot e_{N(FET)}^2)}} \quad (15)$$

For example, with a band-limit filter bandwidth set at 10MHz and a 10pF diode capacitance, all other parameters are set according to Table 1 (taken from the OPA657 and OPA846 product data sheets).

Table 1. Device Performance Comparison

Device	Element Specifications
OPA657	$e_{N(FET)} = 4.8nV/\sqrt{Hz}$
	$I_{B(FET)} = 1.3fA/\sqrt{Hz}$
	$C_{S(FET)} = 10pF + 5.2pF = 15.2pF$
OPA846	$e_{N(BIP)} = 1.2nV/\sqrt{Hz}$
	$I_{B(BIP)} = 2.8pA/\sqrt{Hz}$
	$C_{S(BIP)} = 10pF + 3.8pF = 13.8pF$

The result is that for a resistor lower than 2kΩ, the bipolar amplifier offers a noise advantage; we can therefore conclude that even though the voltage noise of the OPA657 is high, the total input-referred noise generated by the OPA657 FET amplifier will be lower than that of the OPA846 bipolar amplifier for any transimpedance gain greater than 2kΩ. If a larger post-amplifier filter bandwidth is necessary, the bipolar amplifier (such as the OPA846) will have the lowest noise contribution independent of the resistor.

In general (and from a noise perspective), FET input amplifiers such as the OPA657 are best for large or very large transimpedance gain with low-to-medium bandwidth because of the post-amplifier filter limitations, whereas bipolar amplifiers such as the OPA846 are best for medium-to-large transimpedance gain applications with high bandwidth as limited by the post-amplifier filter.

5 Example

From Figure 3, the maximum achievable bandwidth versus transimpedance gain, it is difficult to separate the OPA846 from the OPA657 simply by achievable bandwidth. In order to help assess the behavioral differences between these two amplifiers, first consider the following application circuit (Figure 5).


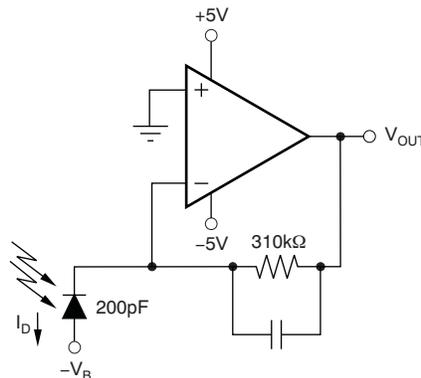


Figure 5. 310kΩ Transimpedance Gain with 200pF Source Capacitance Circuit

In this circuit, using Equation 12, the OPA846 achieves 2.1MHz while the OPA657 achieves 2MHz, making them equivalent on that specification. Looking at the noise, the OPA657 yields a $5\text{pA}/\sqrt{\text{Hz}}$ equivalent input noise current if we assume the noise power bandwidth limit is set at 1.4MHz. This noise is dominated by the third term of the total noise equation, which is the effect of the rising portion of the noise gain curve times the relatively high $4.8\text{nV}/\sqrt{\text{Hz}}$ input voltage noise for the OPA657. The OPA846, which has a much lower voltage noise but much higher current noise, actually yielded a lower equivalent input noise current of $3\text{pA}/\sqrt{\text{Hz}}$. So why is the OPA846 not used in this application?

6 DC-Parameters Consideration

The input bias current of the OPA846, $19\mu\text{A}$, generates an output offset voltage with the feedback resistor of $310\text{k}\Omega$ of 5.89V . Because the OPA846 is operating on a $\pm 5\text{V}$ power supply, this offset voltage sends the output into saturation. Adding a $310\text{k}\Omega$ resistor on the noninverting input allows bias current cancellation but now puts 5.89V common-mode voltage on the input, exceeding the common-mode input range of the OPA846. Figure 6 shows the maximum achievable bandwidth as a function of the transimpedance gain for a few operational amplifiers when taking into consideration dc parameters. The difference between bipolar technology and FET-input technology is now easy to establish. FET-input operational amplifiers, such as the OPA657, are capable of higher transimpedance, where decompensated bipolar operational amplifiers are capable of much higher bandwidth but are limited in gain range.

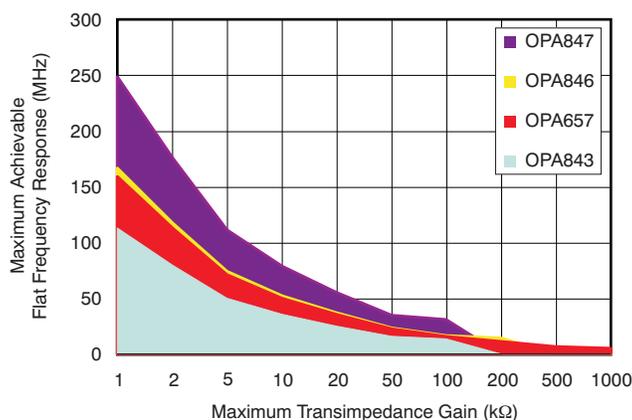

This measurement takes into consideration a dc parameter for a 10pF source capacitance.

Figure 6. Maximum Achievable Bandwidth vs Transimpedance Gain for Selected Op Amps

7 Conclusion

Although all operational amplifiers can be used in transimpedance applications, the limit in performance is always limited by the transimpedance gain, the bandwidth, and the noise. Many potential problems have been discussed along with suggestions and solutions. This application report developed an emphasis on the methodology to approach transimpedance designs as well as component selection.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated