

High-Side Motor Current Monitoring for Over-Current Protection

Scott Hill, Current Sensing Products



High power, precision motor systems commonly require detailed feedback such as speed, torque and position to be sent back to the motor control circuitry in order to precisely and efficiently control the motor's operation. Other motor control applications, such as fixed motion tasks, do not require the same level of system complexity in order to carry out their jobs. Ensuring that the motor has not stalled or encountered an unintended object in the motor's path or that a short in the motor's winding exists can frequently be all of the information provided back to the motor control circuitry. More complex motor control systems implementing dynamic control and active monitoring can also benefit from adding simple out-of-range detection function because of the faster indication of out-of-range events.

By placing a current sense amplifier in series with the DC power supply driving the high side of the motor drive circuitry as shown in Figure 1, the overall current to the motor can be measured easily detecting out-of-range conditions. To detect small leakages the low-side return current can also be measured. A difference between the high-side and low-side current levels indicates a leakage path exists within the motor or motor control circuitry.

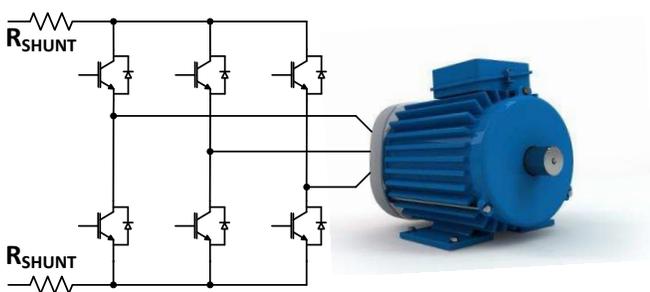


Figure 1. Low & High-Side Current Sensing

The DC voltage level varies depending on the voltage rating of the motor leading to multiple current measurement solutions to accommodate the corresponding voltage levels. For low voltage motors (~5V) the selection of a circuitry to monitor this current is much simpler with multiple amplifier types (current sense, operational, difference, instrumentation) are able to perform the current measurement function to support this common-mode input voltage range.

For larger voltage motors (24V and 48V for example), the available options decrease down to dedicated current sense and differential amplifiers. As the voltage requirements continue to increase, measurement errors begin to impact the ability to effectively identify out-of-range conditions. One specification that describes an amplifier's effectiveness at operating at high input voltage levels is the common-mode rejection (CMR) term. This specification directly describes how well an amplifier's input circuitry can reject the influence of large input voltages.

Ideally, an amplifier is able to completely reject and cancel out any voltage common to both input pins and amplify only the differential voltage seen between them. However, as the common-mode voltage is increased, leakage currents in the amplifier's input stage result in additional input offset voltage. Larger input range levels being monitored will create proportionally larger measurement errors.

For example, an amplifier (difference amplifier or current sense amplifier) that has a CMR (Common-Mode Rejection) specification of 80dB will have a significant offset voltage introduced in the measurement based on the input voltage level. An 80dB CMR specification corresponds to an additional 100 μ V of offset voltage induced into the measurement for every volt applied to the input.

Many devices are specified under defined conditions ($V_{CM} = 12V$ and $V_S = 5V$ for example) which establishes the base-line for the default specifications (CMR and PSRR specifically). In this example operating at 60V common-mode voltage creates a change in V_{CM} of 48V (60V-12V). A 48V change with a 80db CMR results in an additional 4.8mV of offset voltage in addition to the specified input offset voltage found in the device's datasheet.

Applications employing calibration schemes are less concerned by this additional induced offset voltage. However, for applications where system calibration cannot account for this shift in offset, selection of an amplifier with better common-mode voltage rejection is required.

The **INA240** is a dedicated current sense amplifier with a common-mode input voltage range of -4V to +80V and a worst case CMR (Common-Mode Rejection) specification of 120dB over the entire input and temperature range of the device. 120dB of CMR corresponds to an additional 1µV of input offset voltage induced for every 1V change in common-mode voltage. The temperature influence on the amplifier's ability to rejection common-mode voltages is not well documented in many product datasheets so it should be evaluated in addition to the room temperature specification. The INA240 maintains a guaranteed 120dB CMR specification over the entire -40°C to +125°C temperature range. The typical CMR performance for the INA240 over the entire temperature range is 135dB (less than 0.2µV for every 1V change) as shown in [Figure 2](#).

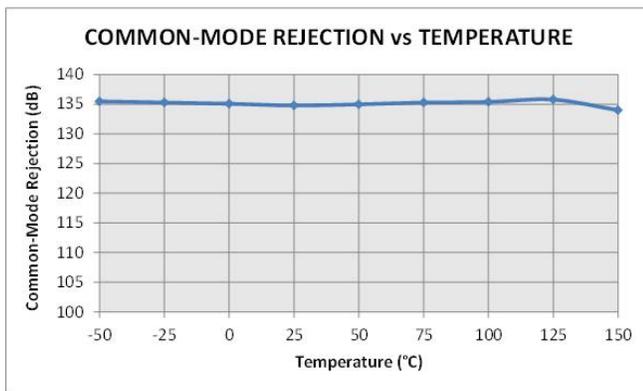


Figure 2. Common-Mode Rejection vs. Temperature

A system controller has the ability to utilize the current sense amplifier's measurement to evaluate the operation of the system. Comparing the current information to pre-defined operating threshold allows for detection of out-of-range events. A comparator following the high-side current sense amplifier can easily detect and provide alerts quickly to the system allowing for corrective actions to be taken.

[Figure 3](#) illustrates the signal chain path for monitoring and detecting out-of-range excursions when measuring currents on a high voltage rail driving the motor drive circuitry. The output signal proportional to the measured input current is directed to the ADC in addition to be sent to the comparator to detect overcurrent events. The comparator alert will assert if the input current level exceeds the predefined threshold connected as the comparators reference voltage.

A key requirement for over-current detection circuitry is the ability to detect and respond quickly to out-of-range conditions. A signal bandwidth 100kHz and 2V/µs allows for the INA240 to accurately measure and amplify the input current signal, send the output to the high-speed comparator for an alert to be issued based on a shorted condition in the span of a few microseconds. This fast response ensures other critical system components are not damaged by the unintended excess current flowing in the system.

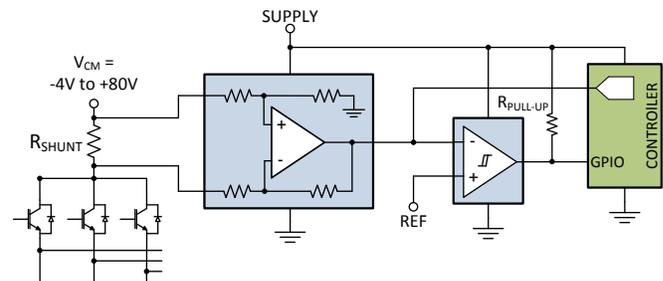


Figure 3. High-Side Over-Current Detection

Alternate Device Recommendations

For applications measuring high voltage capability needing a faster signal bandwidth or smaller package, use the LMP8640. For applications requiring higher voltage capability, the INA149 is a high performance difference amplifier capable of interfacing with common-mode voltages up to +/-275V off of a +/-15V supply and has a guaranteed CMR of 90dB (or 31.6µV for every 1V input change). The INA301 is a precision current sense amplifier with an on-board comparator that is ideal for detecting over-current events on common-mode voltages up to 36V.

Table 1. Alternate Device Recommendations

| Device | Optimized Parameter | Performance Trade-Off |
|-----------|---|-----------------------------|
| LMP8640HV | Package: SOT23-6, Signal Bandwidth | Accuracy |
| INA149 | V _{CM} Range: +/-275V | CMR, Gain |
| INA301 | On-Board Comparator; 35µV V _{OS} | V _{CM} : 0V to 36V |

Table 2. Related TI TechNotes

| | |
|---------|--|
| SBOA160 | High Precision, Low-Drift In-Line Motor Current Measurements |
| SBOA161 | Low-Drift, Low-Side Current Measurements for Three-Phase Systems |
| SBOA162 | Measuring Current To Detect Out-of-Range Conditions |
| SBOA165 | Precision Current Measurement On High Voltage Power Rail |

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated