

Single-supply, 2nd-order, multiple feedback band-pass filter circuit




Amplifiers

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45V	+2.45V	0.05V	4.95V	5V	0V

Gain	Low Cut-off Frequency (f_l)	High Cut-off Frequency (f_h)	V_{ref}
1V/V	1kHz	10kHz	1.25V and 2.5V

Design Description

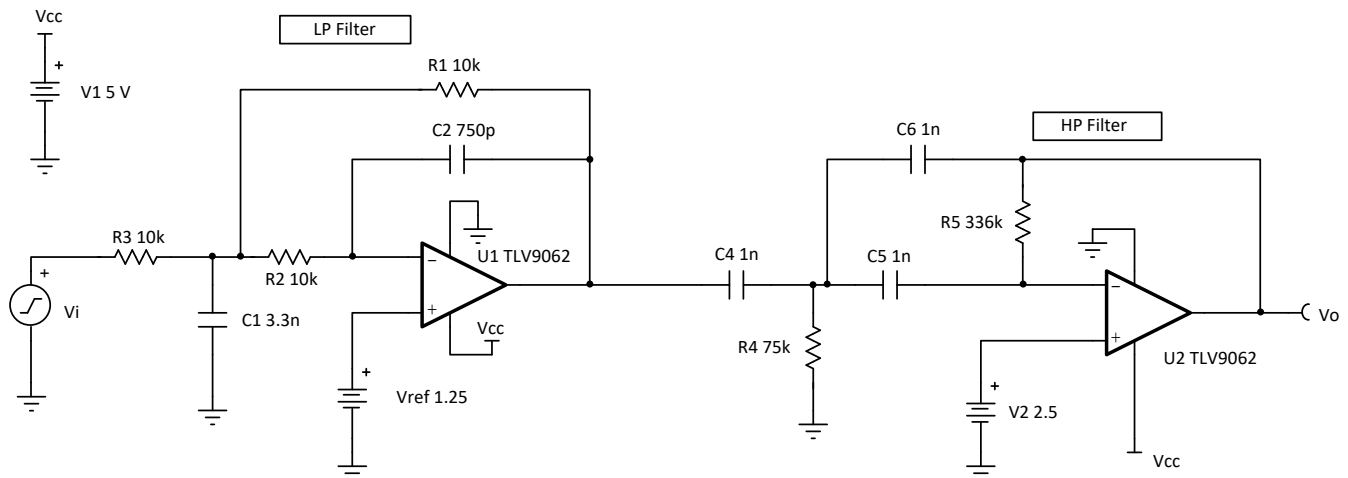This circuit is a 2nd-order multiple feedback (MFB) band-pass (BP) filter. This BP filter is created by cascading a low-pass and a high-pass filter. V_{ref} provides a DC offset to accommodate for single-supply applications.



Design Notes

1. Select an op amp with sufficient input common-mode range and output voltage swing.
2. Add V_{ref} to bias the input signal to meet the input common-mode range and output voltage swing.
3. Select the capacitor values first since standard capacitor values are more coarsely subdivided than the resistor values. Use high-precision, low-drift capacitor values to avoid errors in f_l and f_h .
4. To minimize the amount of slew-induced distortion, select an op amp with sufficient slew rate (SR).
5. For HP filters the maximum frequency is set by the gain bandwidth (GBW) of the op amp. Therefore, be sure to select an op amp with sufficient GBW.

Design Steps

This BP filter design involves two cascaded filters, a low-pass (LP) filter and a high-pass (HP) filter. The lower cutoff frequency (f_l) of the BP filter is 1kHz and the higher cutoff frequency (f_h) is 10kHz. The design steps show an LP filter design with f_h of 10kHz and a HP filter design with f_l of 1kHz. See [MFB low-pass filter design](#) and [MFB high-pass filter design](#) in the circuit cookbook for details on transfer function equations and calculations.

LP Filter Design

1. Use [MFB low-pass filter design](#) to determine R_1 , R_2 , and R_3 .

$$R_1 = 10\text{k}\Omega,$$

$$R_2 = 10\text{k}\Omega,$$

$$R_3 = 10\text{k}\Omega$$

2. Use [MFB low-pass filter design](#) to determine C_1 and C_2 .

$$C_1 = 3.3\text{nF (Standard Value)}, C_2 = 750\text{pF (Standard Value)}$$

HP Filter Design

1. Use [MFB high-pass filter design](#) to determine C_4 , C_5 , and C_6 .

$$C_4 = 1\text{nF},$$

$$C_5 = 1\text{nF},$$

$$C_6 = 1\text{nF}$$


2. Use [MFB high-pass filter design](#) to determine R_4 and R_5 .

$$R_4 = 75\text{k}\Omega,$$


$$R_5 = 336\text{k}\Omega$$

Design Simulations


AC Simulation Results

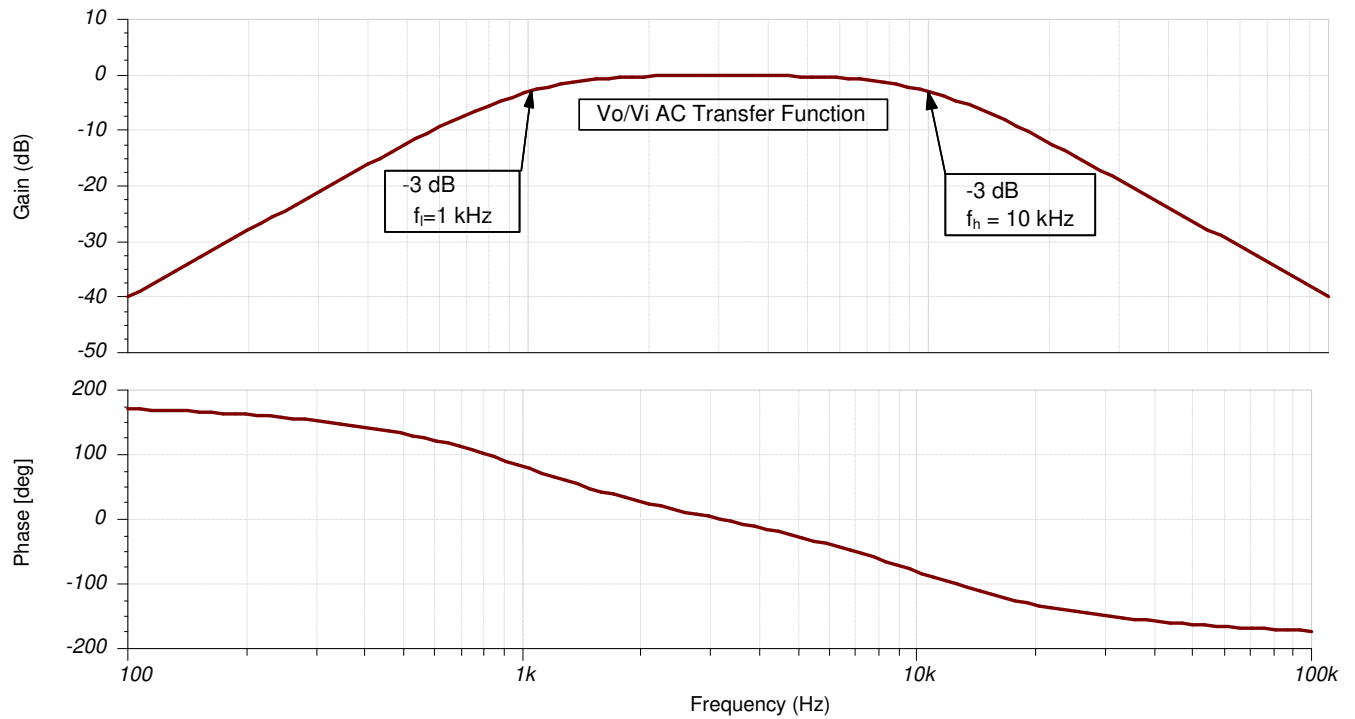


Transient Simulation Results

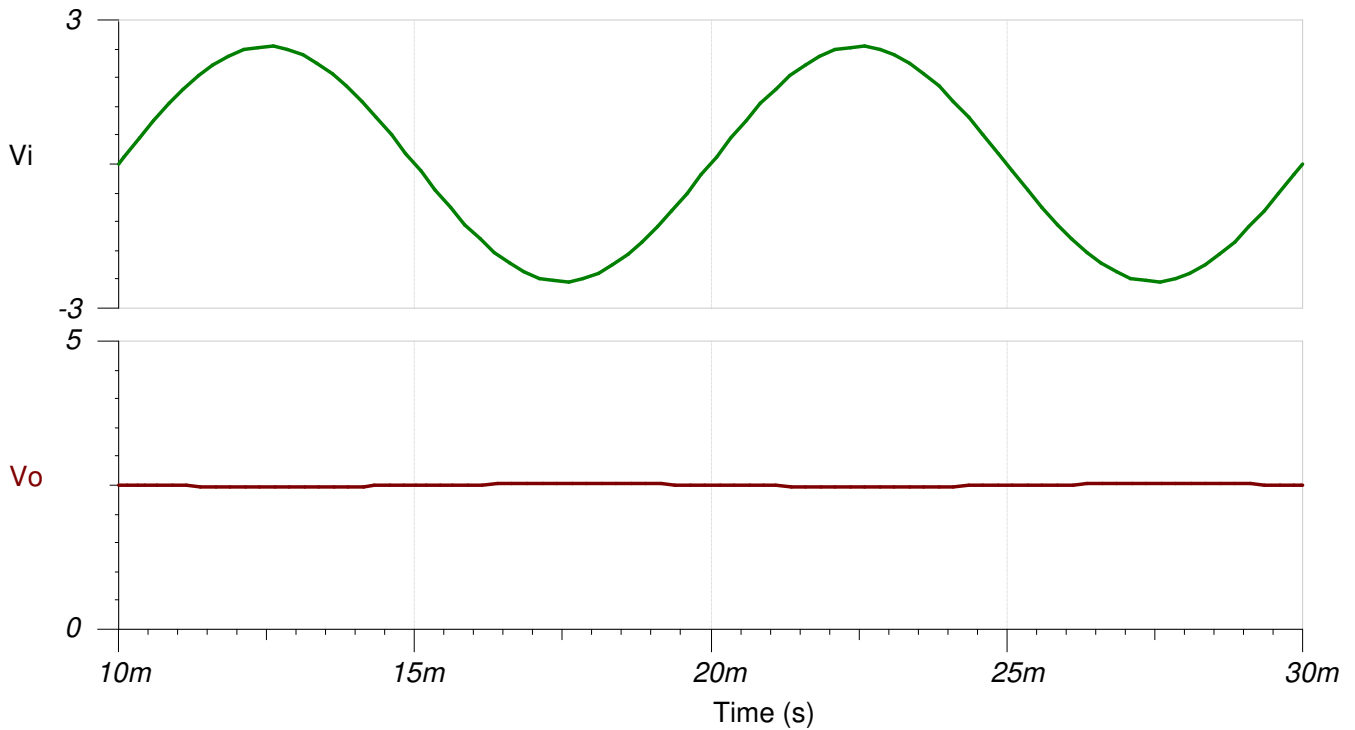

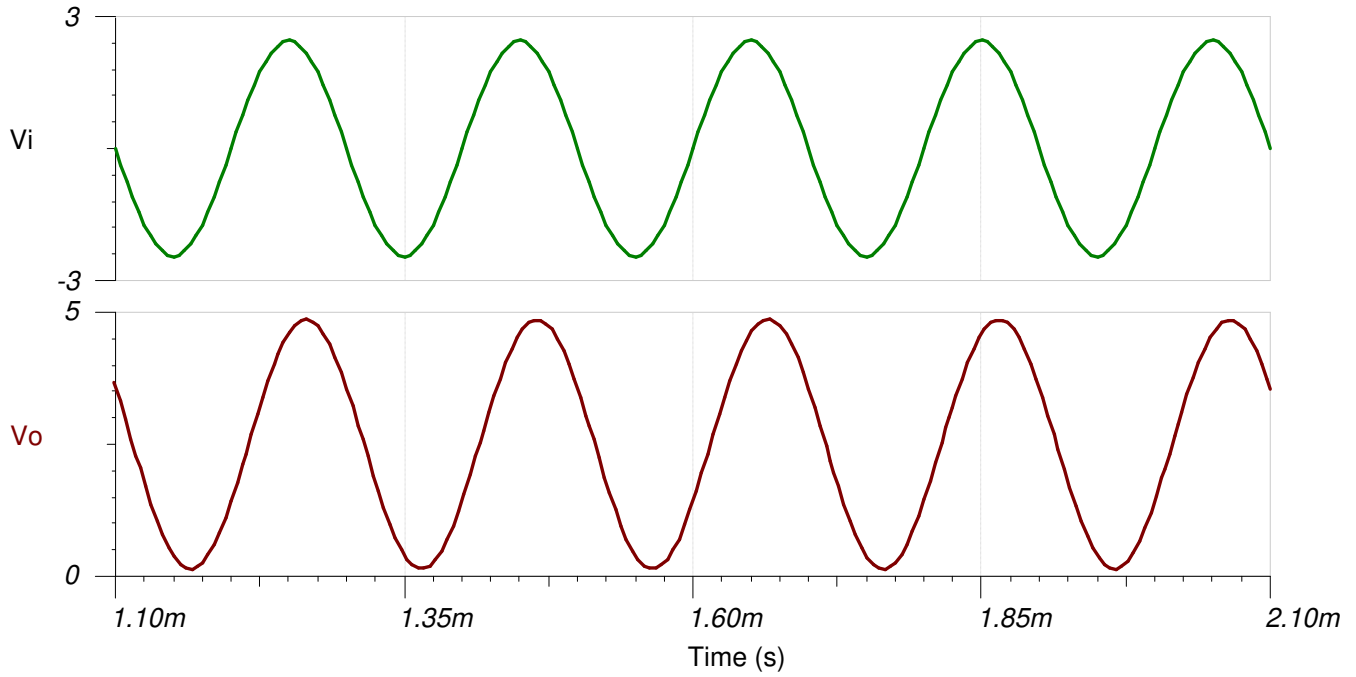Filter Output in Response to a 5-Vpp, 100-Hz Input Signal (Gain = 0.01V/V)



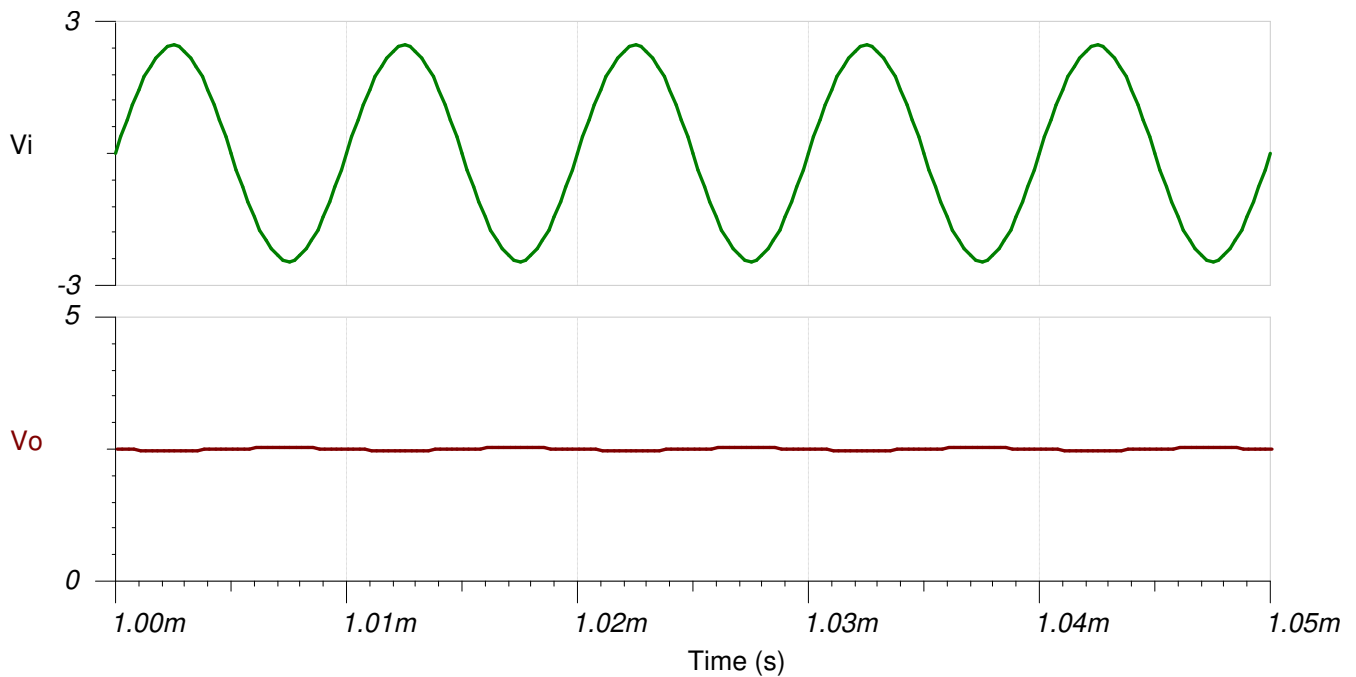Filter Output in Response to a 5-Vpp, 5-kHz Input Signal (Gain = 1V/V)



Filter Output in Response to a 5-Vpp, 100-kHz Input Signal (Gain = 0.01V/V)

Design References

1. See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.
2. SPICE Simulation File: [SBOC596](#).
3. [TI Precision Labs](#).

Design Featured Op Amp

TLV9062	
Vss	1.8V to 5.5V
VinCM	Rail-to-Rail
Vout	Rail-to-Rail
Vos	0.3mV
Iq	538 μ A
Ib	0.5pA
UGBW	10MHz
SR	6.5V/ μ s
#Channels	1, 2, 4
www.ti.com/product/TLV9062	

Design Alternate Op Amp

	TLV316	OPA325
Vss	1.8V to 5.5V	2.2V to 5.5V
VinCM	Rail-to-Rail	Rail-to-Rail
Vout	Rail-to-Rail	Rail-to-Rail
Vos	0.75mV	0.150mV
Iq	400 μ A	650 μ A
Ib	10pA	0.2pA
UGBW	10MHz	10MHz
SR	6V/ μ s	5V/ μ s
#Channels	1, 2, 4	1, 2, 4
	www.ti.com/product/TLV316	www.ti.com/product/OPA325

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated