


Inverting op amp with inverting positive reference voltage circuit

Design Goals

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-5V	-1V	0.05V	3.3V	5V	0V	5V

Design Description

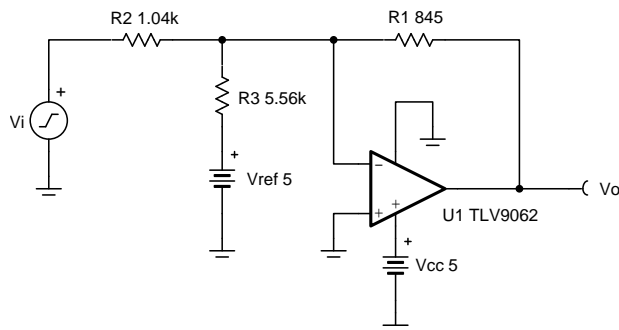This design uses an inverting amplifier with an inverting positive reference to translate an input signal of -5V to -1V to an output voltage of 3.3V to 0.05V. This circuit can be used to translate a negative sensor output voltage to a usable ADC input voltage range.



Design Notes

1. Use op amp linear output operating range. Usually specified under A_{OL} test conditions.
2. Common mode range must extend down to or below ground.
3. V_{ref} output must be low impedance.
4. Input impedance of the circuit is equal to R_2 .
5. Choose low-value resistors to use in the feedback. It is recommended to use resistor values less than 100k Ω . Using high-value resistors can degrade the phase margin of the amplifier and introduce additional noise in the circuit.
6. The cutoff frequency of the circuit is dependent on the gain bandwidth product (GBP) of the amplifier. Additional filtering can be accomplished by adding a capacitor in parallel to R_1 . Adding a capacitor in parallel with R_1 will also improve stability of the circuit if high-value resistors are used.

Design Steps

$$V_o = -V_i \times \left(\frac{R_1}{R_2}\right) - V_{ref} \times \left(\frac{R_1}{R_3}\right)$$

1. Calculate the gain of the input signal.

$$G_{input} = \frac{V_{o,max} - V_{o,min}}{V_{i,max} - V_{i,min}} = \frac{3.3V - 0.05V}{-1V - (-5V)} = 0.8125 \frac{V}{V}$$

2. Calculate R_1 and R_2 .

Choose $R_1 = 845\Omega$

$$R_2 = \frac{R_1}{G_{input}} = \frac{R_1}{0.8125 \frac{V}{V}} = 1.04 \text{ k}\Omega$$

3. Calculate the gain of the reference voltage required to offset the output.

$$G_{ref} = \frac{R_1}{R_3} \quad () \quad ()$$

$$-V_{i,min} \times \frac{R_1}{R_2} - V_{ref} \times \frac{R_1}{R_3} = V_{o,min}$$


$$\frac{R_1}{R_3} = \frac{V_{o,min} + V_{i,min} \times \frac{R_1}{R_2}}{-V_{ref}} = \frac{0.05V + (-1V) \times \frac{845\Omega}{1.04k\Omega}}{-5} = 0.1525 \frac{V}{V}$$

4. Calculate R_3 .


$$R_3 = \frac{R_1}{G_{ref}} = \frac{845\Omega}{0.1525 \frac{V}{V}} = 5.54 \text{ k}\Omega \approx 5.56 \text{ k}\Omega$$

Design Simulations

DC Simulation Results

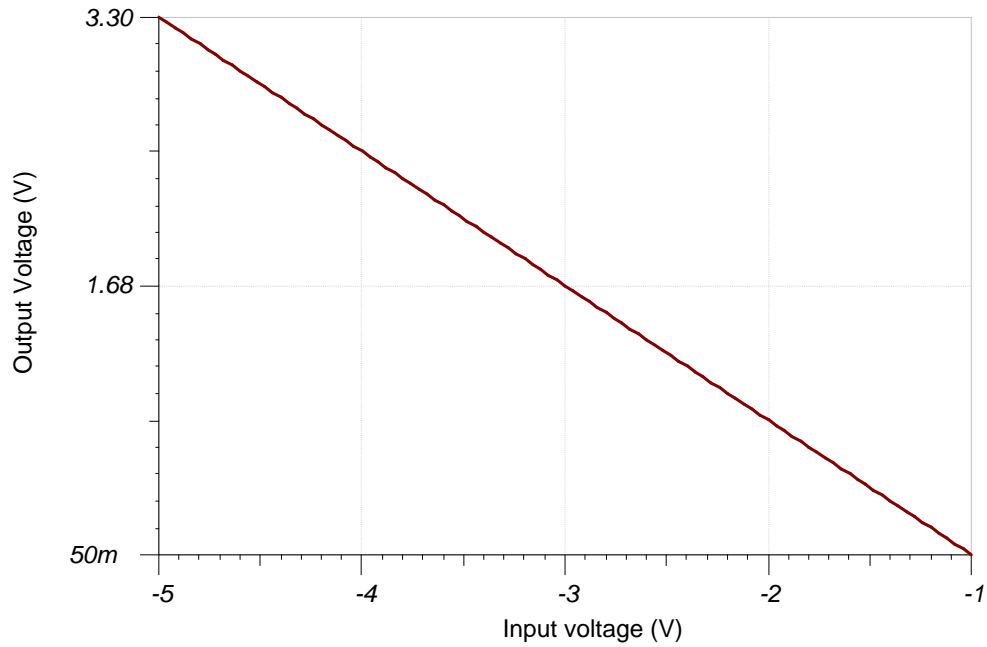

AC Simulation Results

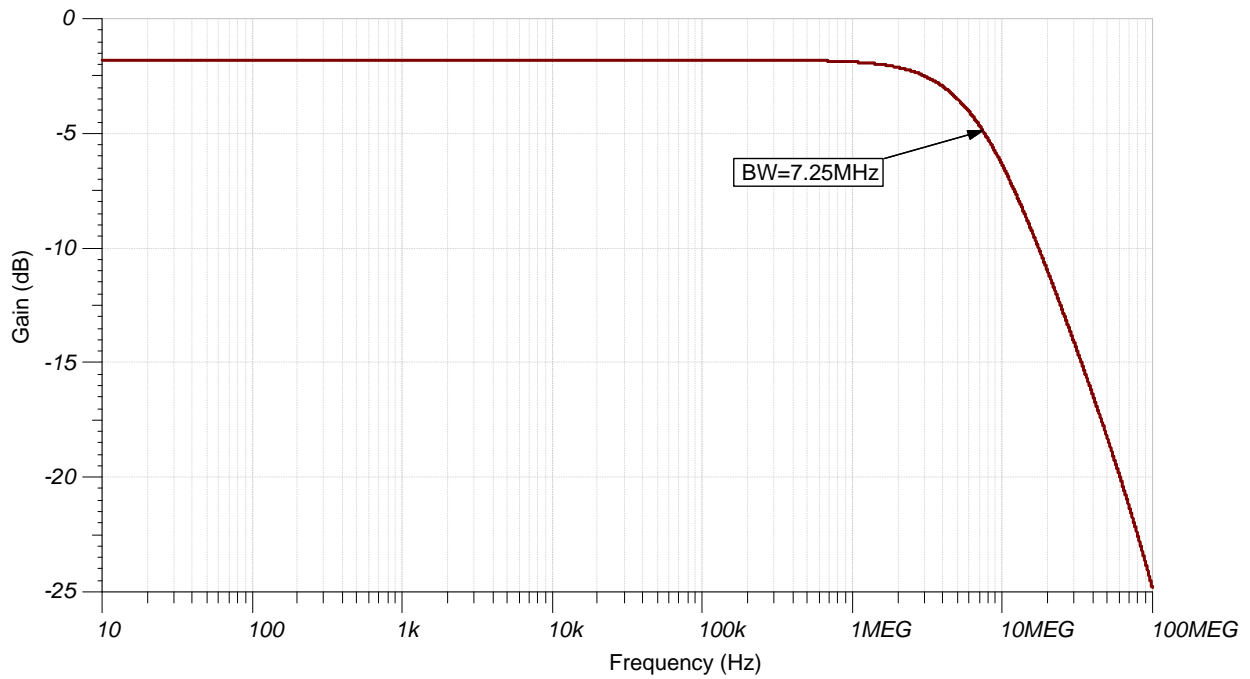

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See the circuit SPICE simulation file [SBOC511](#).

See [Designing Gain and Offset in Thirty Seconds](#).

Design Featured Op Amp

TLV9062	
V_{SS}	1.8V to 5.5V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{os}	0.3mV
I_q	538 μ A
I_b	0.5pA
UGBW	10MHz
SR	6.5V/ μ s
#Channels	1, 2, 4
www.ti.com/product/tlv9062	

Design Alternate Op Amp

OPA197	
V_{SS}	4.5V to 36V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{os}	25 μ V
I_q	1mA
I_b	5pA
UGBW	10MHz
SR	20V/ μ s
#Channels	1, 2, 4
www.ti.com/product/opa197	

Revision History

Revision	Date	Change
A	February 2019	Downscale the title and changed title role to 'Amplifiers'. Added links to circuit cookbook landing page and SPICE simulation file.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated