


## ***Non-inverting op amp with non-inverting positive reference voltage circuit***

### Design Goals

Input		Output		Supply		
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$V_{ref}$
-1V	3V	0.05V	4.95V	5V	0V	2.5V
 
### Design Description

This design uses a non-inverting amplifier with a non-inverting positive reference to translate an input signal of -1V to 3V to an output voltage of 0.05V to 4.95V. This circuit can be used to translate a sensor output voltage with a positive slope and negative offset to a usable ADC input voltage range.



Copyright © 2018, Texas Instruments Incorporated

### Design Notes

1. Use op amp linear output operating range. Usually specified under  $A_{OL}$  test conditions.
2. Check op amp input common mode voltage range.
3.  $V_{ref}$  output must be low impedance.
4. Input impedance of the circuit is equal to the sum of  $R_3$  and  $R_4$ .
5. Choose low-value resistors to use in the feedback. It is recommended to use resistor values less than 100k $\Omega$ . Using high-value resistors can degrade the phase margin of the amplifier and introduce additional noise in the circuit.
6. The cutoff frequency of the circuit is dependent on the gain bandwidth product (GBP) of the amplifier.
7. Adding a capacitor in parallel with  $R_1$  will improve stability of the circuit if high-value resistors are used.

## Design Steps

$$V_o = V_i \times \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_2} \right) + V_{ref} \times \left( \frac{R_3}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_2} \right)$$

1. Calculate the gain of the input voltage to produce the desired output swing.

$$G_{input} = \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_2} \right)$$

$$V_{o,max} - V_{o,min} = V_{i,max} - V_{i,min} \times \frac{R_4}{R_3 + R_4} \times \frac{R_1 + R_2}{R_2}$$

$$\frac{V_{o,max} - V_{o,min}}{V_{i,max} - V_{i,min}} = \frac{R_4}{R_3 + R_4} \times \frac{R_1 + R_2}{R_2}$$

$$\frac{4.95V - 0.05V}{3V - (-1V)} = \frac{R_4}{R_3 + R_4} \times \frac{R_1 + R_2}{R_2}$$

$$1.225V = \frac{R_4}{R_3 + R_4} \times \frac{R_1 + R_2}{R_2}$$

2. Select a value for  $R_1$  and  $R_4$  and insert the values into the previous equation. The other two resistor values must be solved using a system of equations. The proper output swing and offset voltage cannot be calculated if more than two variables are selected.

$$R_1 = R_4 = 1 \text{ k}\Omega$$

$$1.225V = \frac{1 \text{ k}\Omega}{R_3 + 1 \text{ k}\Omega} \times \frac{1 \text{ k}\Omega + R_2}{R_2}$$

3. Solve the previous equation for  $R_3$  in terms of  $R_2$ .

$$R_3 = \frac{1 \text{ M}\Omega + (1 \text{ k}\Omega \times R_2)}{1.225 \times R_2} - 1 \text{ k}\Omega$$

4. Select any point along the transfer function within the linear output range of the amplifier to set the proper offset voltage at the output (for example, the minimum input and output voltage).

$$V_{o,min} = V_{i,min} \times \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_2} \right) + V_{ref} \times \left( \frac{R_3}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_2} \right)$$

$$0.05V = -1 \text{ V} \times \frac{1 \text{ k}\Omega}{R_3 + 1 \text{ k}\Omega} \times \frac{1 \text{ k}\Omega + R_2}{R_2} + 2.5V \times \frac{R_3}{R_3 + 1 \text{ k}\Omega} \times \frac{1 \text{ k}\Omega + R_2}{R_2}$$

5. Insert  $R_3$  into the equation from step 1 and solve for  $R_2$ .

$$0.05V = -1 \text{ V} \times \left( \frac{1 \text{ k}\Omega}{\frac{1 \text{ M}\Omega + 1 \text{ k}\Omega \times R_2}{1.225 \times R_2} - 1 \text{ k}\Omega + 1 \text{ k}\Omega} \right) \left( \frac{1 \text{ k}\Omega + R_2}{R_2} \right) + 2.5V \times \left( \frac{\frac{1 \text{ M}\Omega + 1 \text{ k}\Omega \times R_2}{1.225 \times R_2} - 1 \text{ k}\Omega}{\frac{1 \text{ M}\Omega + 1 \text{ k}\Omega \times R_2}{1.225 \times R_2} - 1 \text{ k}\Omega + 1 \text{ k}\Omega} \right) \left( \frac{1 \text{ k}\Omega + R_2}{R_2} \right)$$

$$R_2 = 1360.5\Omega \approx 1370\Omega$$


6. Insert  $R_2$  into the equation from step 1 to solve for  $R_3$ .

$$R_3 = \frac{1 \text{ M}\Omega + 1 \text{ k}\Omega \times (1370\Omega)}{1.225 \times (1370\Omega)} - 1 \text{ k}\Omega$$


$$R_3 = 412.18\Omega \approx 412\Omega$$

**Design Simulations**

**DC Simulation Results**

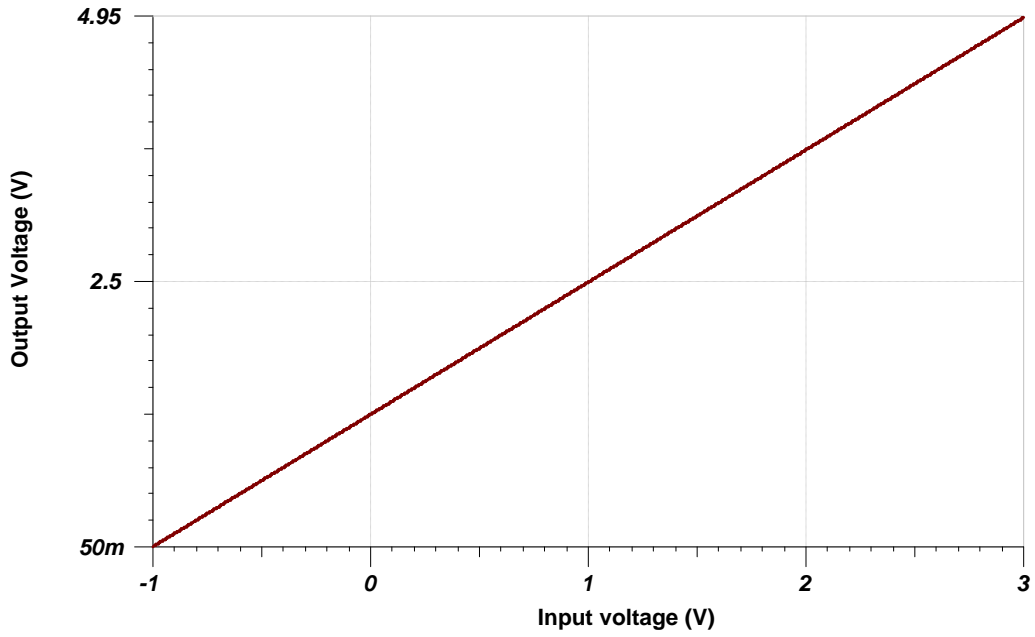

**AC Simulation Results**

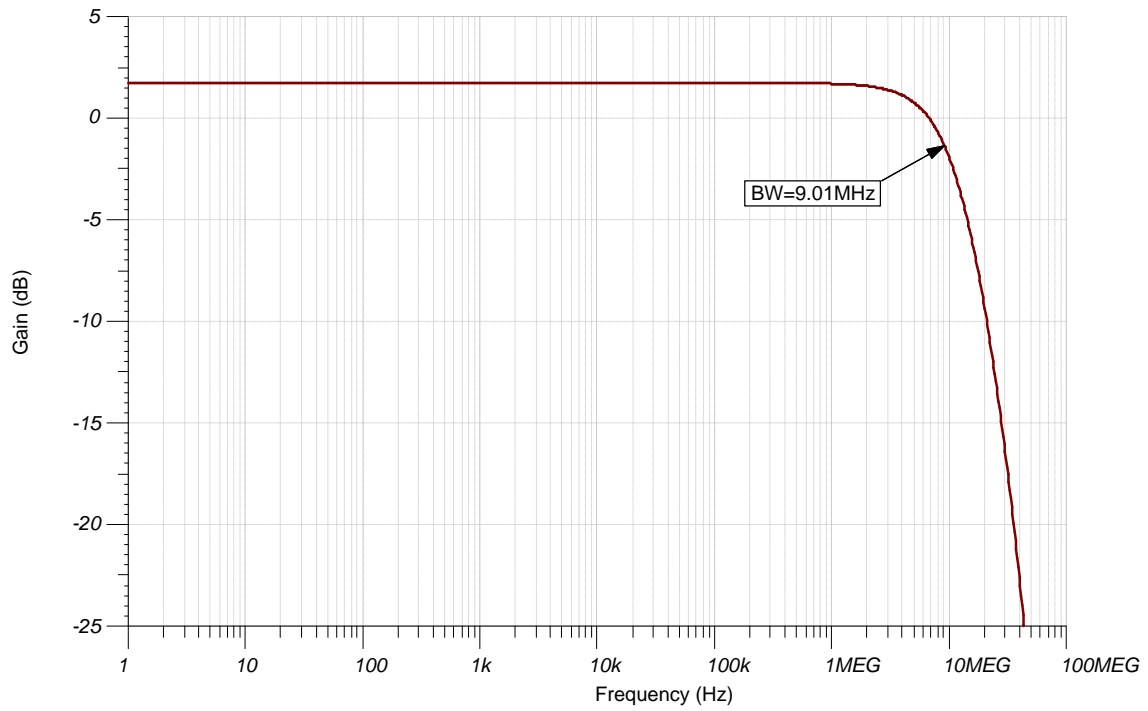

## Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See the circuit SPICE simulation file [SBOC513](#).

See [Designing Gain and Offset in Thirty Seconds](#).

## Design Featured Op Amp

MCP6292	
$V_{SS}$	2.4V to 5.5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	0.3mV
$I_q$	600 $\mu$ A
$I_b$	1pA
UGBW	10MHz
SR	6.5V/ $\mu$ s
#Channels	1, 2, 4
<a href="http://www.ti.com/product/MCP6292">www.ti.com/product/MCP6292</a>	

## Design Alternate Op Amp

OPA388	
$V_{SS}$	2.5V to 5.5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	0.25 $\mu$ V
$I_q$	1.9mA
$I_b$	30pA
UGBW	10MHz
SR	5V/ $\mu$ s
#Channels	1, 2, 4
<a href="http://www.ti.com/product/opa388">www.ti.com/product/opa388</a>	

## Revision History

Revision	Date	Change
A	February 2019	Downscale the title and changed title role to 'Amplifiers'. Added links to circuit cookbook landing page and SPICE simulation file.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2019, Texas Instruments Incorporated