

On-Chip Thin Film Resistors Enable High-Performance Audio Circuitry

Tyler Noyes, John Caldwell, Alexander Davis



Introduction

High-performance circuit design requires careful selection of both active and passive components in the signal path. It is common for designers to assume that using a high-performance integrated circuit ensures a high-performance system. However, selecting passive components solely for lowest cost can significantly degrade the performance of the system. In audio products requiring small size, low distortion, or excellent matching, on-chip thin-film resistors (TFRs) can provide superior performance compared to discrete resistors.

Modern Amplifier Architecture

TFRs are formed by first depositing a thin layer of a resistive material, typically a metal alloy, onto a substrate such as a silicon wafer. Lithography is then used to pattern the resistive layer into regions of known resistance, often called links. In order to match two resistors closely, each may be broken into many links connected in parallel. The resistive links comprising each resistor are placed in an interdigitated fashion on the wafer, effectively allowing both resistors to occupy the same location of the wafer. This ensures that any variation in thin-film resistive material on the wafer affects both resistors equally. Figure 1 shows an example of the process.

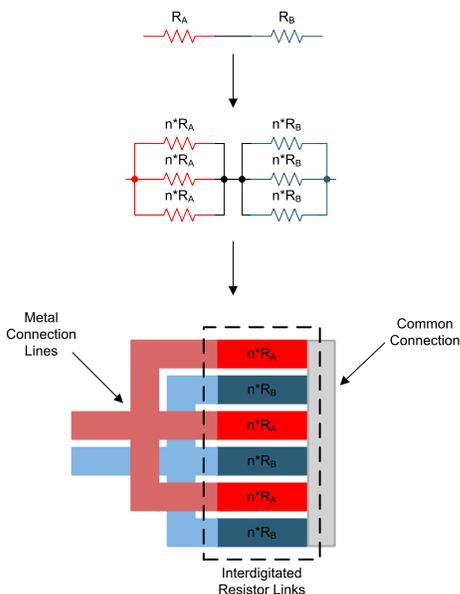


Figure 1. TFR Network to Achieve Matched Values

Modern semiconductor layout techniques, combined with simulations of extracted parasitics on the chip allow this process to produce resistor arrays with exceptional matching without laser trimming. For example, the INA1620 integrates a dual operational amplifier (op amp) with four arrays of thin-film resistors. Each array consists of two 1-kΩ resistors connected as a voltage divider. These resistors typically are matched to better than 0.005% error.

Improving CMRR in a Difference Amplifier Circuit With Integrated Thin Film Resistors

The exceptional matching offered by TFRs is useful in many audio circuits. Line receivers, microphone preamplifiers, and audio digital-to-analog converter (DAC) output circuits all benefit from closely matched resistors. Improved common mode rejection ratio (CMRR) is one benefit of an integrated TFR pair. The CMRR of a typical audio DAC output circuit as seen in Figure 2 depends on how well the resistors are matched in the DAC output circuit.

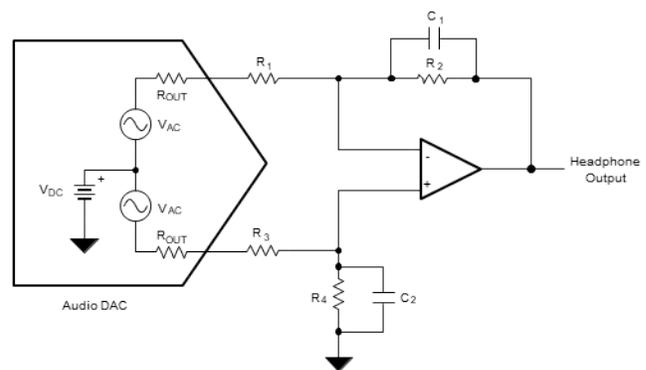


Figure 2. Audio DAC Output Circuit

CMRR was measured on this configuration using the INA1620 and OPA1622. The results can be seen in Figure 3.

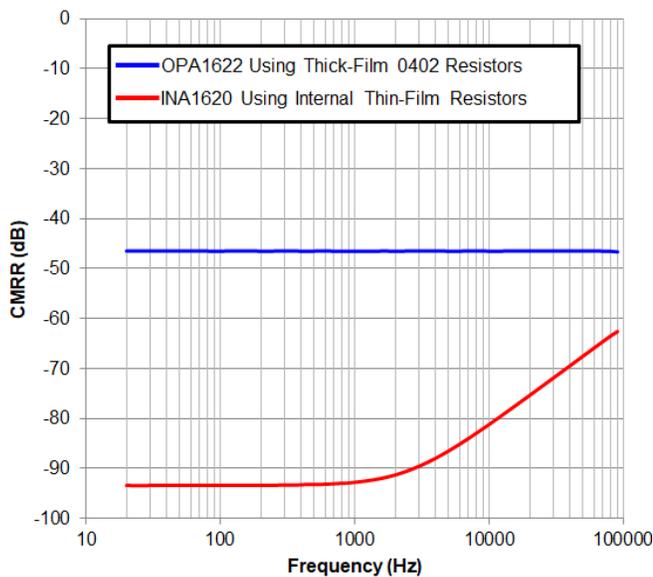


Figure 3. CMRR vs Frequency

The higher absolute value of the CMRR the better the amplifier rejects common-mode signals. Since the thin film process yields very high tolerance resistors, the CMRR can be significantly improved from standard resistor tolerance values. See [Table 1](#) for how resistor tolerance affects CMRR. The INA1620 used in this test shows close to 93dB of CMRR which corresponds to 0.001% resistor matching. The worst case resistor matching for the INA1620 is 0.02% which corresponds to 74dB of CMRR. For more information on how CMRR affects a Difference Amplifier please see .

Table 1. Worst Case CMRR based on Resistor Tolerance

RESISTOR TOLERANCE	WORST CASE CMRR (dB)
10.000%	14
5.000%	20
1.000%	34
0.010%	74
0.001%	94

Improved Distortion Using Integrated TFRs

Harmonic distortion is the addition of unwanted frequencies that degrade the audio quality. It is easy to ignore the negative impact on distortion that is created by discrete components; most of an engineer's focus is typically on the amplifier. The discrete components surrounding an audio circuit are very important to consider when designing for good distortion characteristics.

Due to the difference in manufacturing process between thin film resistors and thick film resistors, they have very different properties. Thin film resistors are built using a vacuum deposition process that allows for much lower temperature coefficients and lower noise. Using the same devices and configuration from [Figure 2](#), the THD+N was measured for the two devices. The results from the test can be seen in [Figure 4](#). The thick film resistors show a 6-dB worse distortion than the thin film resistors. This shows that the resistors can make a significant impact on the THD+N in a circuit.

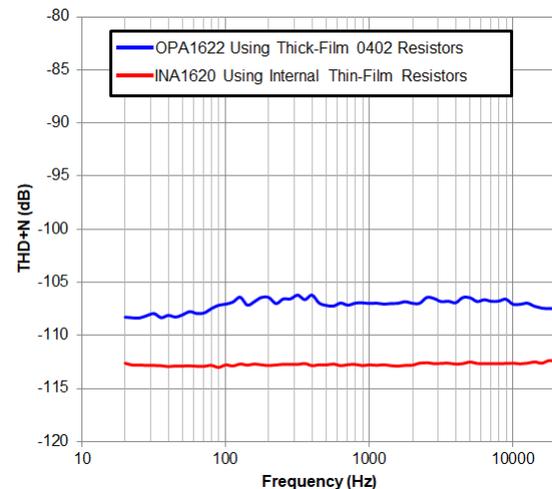


Figure 4. THD+N vs Frequency

Additional Resources

Table 2. TI Audio Amplifiers with Integrated Thin Film Resistors

DEVICE	Description
INA1620	Headphone Amplifier: Bipolar input 2.8 nV/√Hz, -119 dB THD+N, 32 MHz GBW, Integrated resistor matching of 0.004%
INA1650	Differential Line Receiver: -104.7dBu Noise Floor, -120dB THD+N, 91dB CMRR, 1 MΩ Differential Input Impedance

Table 3. Related Documentation

Literature Number	Name of Article
SBOT041	EMI-Hardened Operational Amplifiers Reduce Inaccuracies
SBOA274	Difference Amplifier (Subtractor) Circuit

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated