

Low Voltage, High Slew Rate Op-amps for Motor Drive Circuits

Paul Goedeke, General Purpose Amps Apps



The requirements for operational amplifiers and other ICs used in motor control systems have increased because of the need to extract higher performance from a motor while maintaining low system cost. Measuring motor current is an easy and inexpensive way to understand the torque and direction of the motor, so current sensing forms the backbone of many common motor control schemes for the three common DC motor types: stepper, brushed DC and brushless DC (BLDC).

Motor current relates proportionally to torque, allowing a motor controller to monitor the motor load through current sensing. It can also protect the motor from over-torque or overload conditions in the event of a jam or some other system failure. Typically, motors are controlled with a pulse width modulation (PWM) scheme generated by a controller driving different MOSFET half-bridge driver configurations. An H-bridge is used for brushed DC motors as shown in Figure 1, dual H-bridge for stepper motors, or triple half-bridge for BLDC motors. When the MOSFETs are switched on and off with a PWM input, the inductance of the motor acts like a low pass filter and produces an RMS current that depends on the duty cycle of the PWM signal.

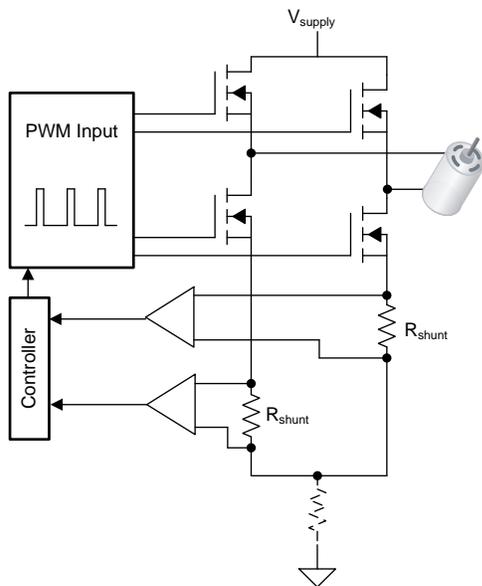


Figure 1. H-Bridge Motor Driver with Low-Side Current Sensing

The simplest and lowest cost motor control schemes use a single low-side shunt resistor (shown as a dotted resistor to ground in Figure 1) and sum the leg currents to get an average value used for torque control and simple fault detection like over-torque or overload. In many cases, the demands on the current sense amplifier are lower because over-torque conditions can be monitored over multiple switching cycles with lower accuracy requirements. These schemes generally do not push the boundaries of frequency or duty cycles either.

However, the single summing shunt method may not provide the level of information required to use control schemes such as field oriented control (FOC) in BLDC motors. Accurately measuring the current through each leg of the driving circuit is used to maximize torque, efficiency or optimize other system goals. This can be seen in Figure 1 where each leg has its own shunt resistor (labeled Rshunt). FOC control schemes have more demanding requirements for the low-side current sense amplifiers because measurement accuracy is critical to the control algorithm, PWM frequencies and duty cycles are likely to be more extreme, and measurements are made in each PWM cycle. DC measurement accuracy is important for FOC control schemes, requiring consideration of the offset voltage, rail to rail behavior and input common mode range of the op-amp.

Let's look at how a typical low-side current sense amplifier responds to a sudden large current in the shunt resistor. When a PWM pulse is applied, the low side transistor turns on and the current steps up from nearly 0 A through Rshunt to the value of the motor winding current. This current creates a voltage jump and therefore a large signal input into the non-inverting pin of the op-amp. Any large signal step into an op-amp's inputs causes the amplifier to go into slew limit, where the rise time is determined by how fast the amplifier can charge the Miller capacitance between the input and output stages of the amplifier. Once the signal is within a few hundred millivolts of the final value, the small signal response of the op-amp starts to take over and the signal settling time is determined by the AC response of the op amp circuit. The key is that the overall settling time is dictated by the slew rate and the small signal settling time of the op-amp, as seen in Figure 2. The amplifier must settle before the

PWM cycle ends so that the controller can make an accurate measurement. For a given low-side current sense amplifier circuit, the settling time is constant, meaning that there is an upper limit for the PWM frequency and a lower limit for the duty cycle.

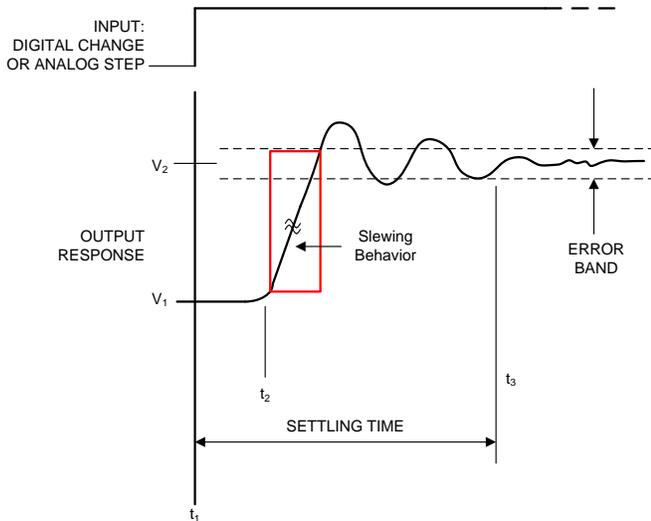


Figure 2. Large Signal Response of an Op-Amp

So what can be done to get a shorter acquisition time? One option is to choose an op-amp with a higher slew for the current sense circuit. [Figure 3](#) shows a simple comparison of two op-amps with different slew rates driving the same load. One has a slew rate of 13 V/μs and the other has a slew rate of 2 V/μs. It is easy to see that the higher slew rate amplifier has a much shorter overall settling time because less time is spent in the op-amp's slew rate limit. The larger the input step, the more time the op-amp will spend in slew limit.

Looking at TI's op-amp catalog, it is easy to see that high slew rate devices are usually high bandwidth devices. Because motor drive systems do not usually require passing high frequency signals, using high bandwidth amplifiers comes with some substantial trade-offs, including increased stability concerns and higher cost. Arguably the biggest tradeoff is that high bandwidth devices need higher quiescent current (I_q) making them unsuitable for applications which are power constrained like battery operated tools and drones.

1.1 Trademarks

All trademarks are the property of their respective owners.

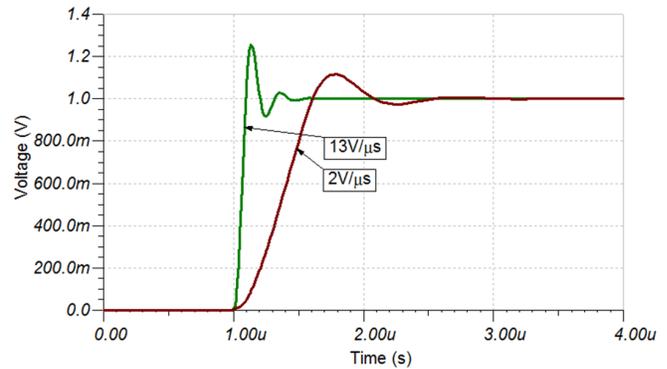


Figure 3. Slew Rate Comparison

TI now has the TLV9052, featuring a 13 V/μs slew rate, 5 MHz bandwidth and only 330 μA I_q . The TLV9052 represents a significant improvement over other low voltage (<7 V supply) op-amps with similar bandwidth, which typically have slew rates ranging from 2 V/μs to 10 V/μs and 400 μA to 2 mA of I_q . This combination of features in the TLV9052 makes operational amplifier an attractive way to extract more performance from a motor drive system while maintaining low system cost and power consumption. If a simpler motor control system is used with only a single shunt, consider using the TLV9002 which has a good trade-off of specifications and price.

1 Related Documentation

For more information on slew rate, bandwidth and stability please see TI Precision Labs Op Amps videos:

- [Slew Rate](#)
- [Bandwidth](#)
- [Stability](#)

More information on designing a low-side current sense amplifier with an op amp can be found in the following TI Circuit Cookbooks:

- [Single Supply Low-Side Current Sensing SBOA215](#)
- [Bidirectional Low-Side Current Sensing SBOA223](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated