

Voltage-to-current (V-I) converter circuit with BJT




Amplifiers

Design Goals

Input			Output		Supply		
V_{iMin}	V_{iMax}	I_{iMax}	I_{oMin}	I_{oMax}	V_{cc}	V_{ee}	V_{load}
0V	10V	200 μ A	0A	1A	15V	0V	36V

Design Description

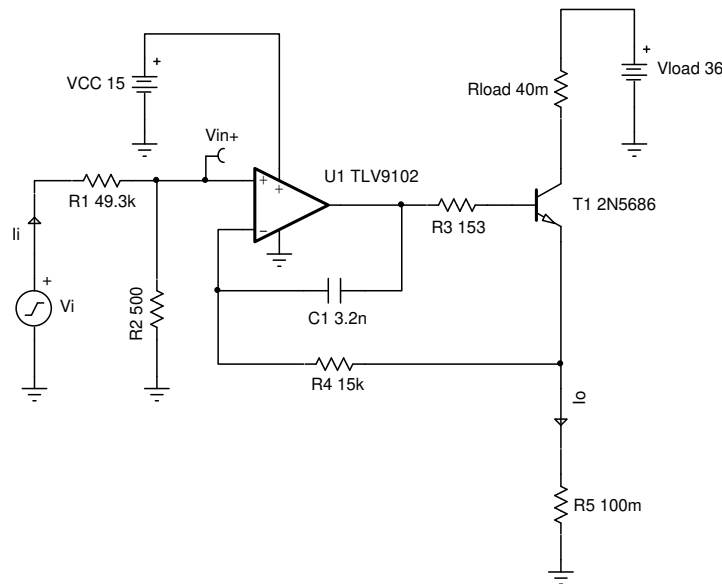This low-side voltage-to-current (V-I) converter delivers a well-regulated current to a load which can be connected to a voltage greater than the op amp supply voltage. The circuit accepts an input voltage from 0V to 10V and converts it to a current from 0A and 1A. The current is accurately regulated by feeding back the voltage drop across a low-side current-sense resistor (R_5) to the op amp.



Design Notes

1. Resistor divider (R_1 and R_2) is implemented to limit the maximum voltage at the non-inverting input, V_{in+} , and sense resistor, R_5 , at full-scale.
2. For an op amp that is not rail-to-rail input (RRI), a voltage divider may be needed to reduce the input voltage to be within the common-mode voltage of the op amp.
3. Use low resistance values for R_5 to maximize load compliance voltage and reduce the power dissipated at full-scale.
4. Using a high-gain BJT reduces the output current requirement for the op amp.
5. Feedback components R_3 , R_4 , and C_1 provide compensation to ensure stability. R_3 isolates the input capacitance of the bipolar junction transistor (BJT), R_4 provides a DC feedback path directly at the current-setting resistor (R_5), and C_1 provides a high-frequency feedback path that bypasses the BJT.
6. Use the op amp in a linear operating region. Linear output swing is usually specified under the A_{OL} test conditions in the device data sheet.

Design Steps

The transfer function of the circuit is:

$$I_o = \frac{R_2}{R_5 \times (R_1 + R_2)} \times V_i$$

1. Calculate the sense resistor, R_5 . The sense resistor should be sized as small as possible to maximize the load compliance voltage and reduce power dissipation. Set the maximum voltage across the sense resistor to 100mV. Limiting the voltage drop to 100mV limits the power dissipated in the sense resistor to 100mW at full-scale output.

$$\text{Let } V_{in-(max)} = 100\text{mV at } I_{oMax} = 1\text{A}$$

$$R_5 = \frac{V_{in-(max)}}{I_{oMax}} = \frac{100\text{mV}}{1\text{A}} = 100\text{m}\Omega$$

2. Select resistors, R_1 and R_2 , for the voltage divider at the input. At the maximum input voltage, the voltage divider should reduce the input voltage to the op amp, $V_{in+(max)}$, to the maximum voltage across the sense resistor, R_5 . R_1 and R_2 should be chosen such that the maximum input current is not exceeded.

$$V_{in-(max)} = V_{in+(max)} = I_{iMax} \times R_2 = 100\text{mV}$$

$$R_2 = \frac{V_{in+(max)}}{I_{iMax}} = \frac{100\text{mV}}{200\mu\text{A}} = 500\Omega \sim 499\Omega \text{ (Standard value)}$$


$$V_{in+(max)} = V_{iMax} \times \left(\frac{R_2}{R_1 + R_2} \right)$$

$$R_1 = 49.5\text{k}\Omega \sim 49.3\text{k}\Omega \text{ (Standard value)}$$


3. See the [Design References](#) section [3] for the design procedure on how to properly size the compensation components, R_3 , R_4 , and C_1 .

Design Simulations


DC Simulation Results

 

AC Simulation Results

 

Transient Simulation Results

 

Design References

1. See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.
2. SPICE Simulation File: [SBOMB58](#).
3. [TI Precision Labs](#)

Design Featured Op Amp

TLV9102	
V_{SS}	$\pm 1.35V$ to $\pm 8V$, 2.7V to 16V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{os}	0.3mV
I_q	120 μ A
I_b	10pA
UGBW	1.1MHz
SR	4.5V/ μ s
#Channels	1, 2, 4
www.ti.com/product/TLV9102	

Design Alternate Op Amp

TLV9152	
V_{SS}	$\pm 1.35V$ to $\pm 8V$, 2.7V to 16V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{os}	125 μ V
I_q	560 μ A
I_b	10pA
UGBW	4.5MHz
SR	20V/ μ s
#Channels	1, 2, 4
www.ti.com/product/TLV9152	

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated