

Make a Precision –10-V Reference

R. Mark Stitt

High-Performance Analog

ABSTRACT

The need for a precision –10.0V reference arises often. This application report provides details for making a precision 10-V reference.

The best way to get a 0V to +10V output from a CMOS MDAC is to use a –10V reference (see [Figure 4](#) through [Figure 6](#)). Although Texas Instruments offers no –10V reference, the REF102 precision +10.0V reference can be accurately converted to a precision –10.0V reference. The circuit is simple and requires no precision components.

The simplest approach for converting a REF102 into a –10.0V reference is shown in [Figure 1](#). The only extra component is a 1kΩ resistor connected to –V_S. This circuit is useful, but has limitations. Maximum expected load current plus maximum reference quiescent current must be supplied by the resistor at minimum –V_S. Changes in current resulting from load and power supply variations must be driven by the reference. The excess current through the reference reduces its accuracy due to drift from self-heating and thermal feedback. Changes in reference output current due to power-supply variations translate into line regulation error. Voltage reference load regulation is not usually as good as line regulation. Finally, the output impedance due to the resistor pull-down causes settling problems with dynamic loads.

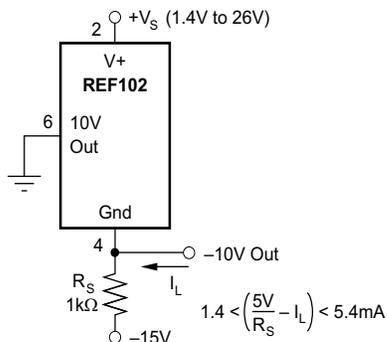


Figure 1. Simple –10-V Reference

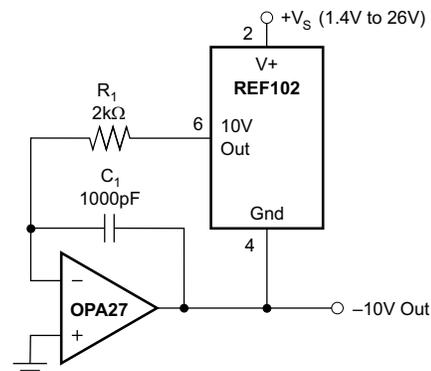


Figure 2. Improved –10-V Reference

The circuit shown in [Figure 2](#) solves these problems. As in [Figure 1](#), no precision resistors are needed. The error contributed by the op amp is negligible (the OPA27 0.6μV/°C V_{OS}/dT adds only 0.06 ppm/°C drift to the –10V reference). As a bonus, the circuit incorporates noise filtering.

To understand how the circuit works, notice that the reference is in the feedback loop of the op amp. The op amp output forces the Gnd connection of the reference to exactly –10.0V so that the voltage at the op amp inverting input is the same as at its noninverting input (ground). Since no current flows into the op amp input, the reference output current remains at zero, eliminating voltage reference thermal feedback or load regulation errors. The R₁, C₁ network assures loop stability and provides noise filtering. Reference noise is filtered by a single pole of $f_{-3dB} = 1/(2 \times \pi \times R_1 \times C_1)$. Bias current flowing through R₁ can produce DC errors and noise. If a lower filter pole is needed, keep R₁ = 2kΩ and increase C₁ to preserve accuracy.

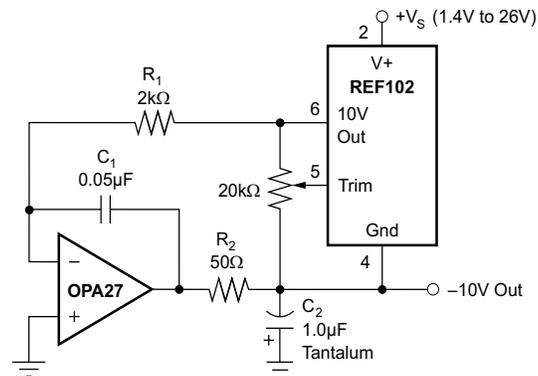


Figure 3. Improved -10V Reference with Improved Filter, with VOUT Trim

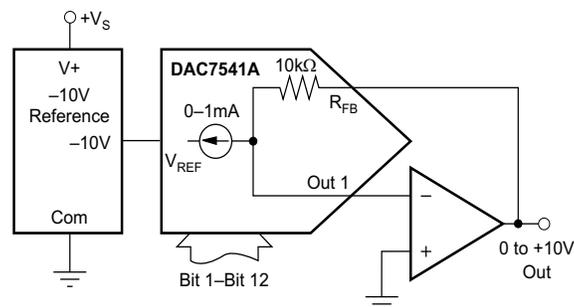


Figure 4. Precision 0V to $+10\text{V}$ Output DAC

Figure 3 shows an improved filter and a provision for output voltage adjustment. The $20\text{k}\Omega$ pot can be used for fine adjustments or to increase the output to -10.24V for 10mV per 10-bit LSB—ideal in many binary DAC applications. The improved filter:

1. Provides low output impedance at high frequency for driving dynamic loads
2. Improves noise filtering
3. Drives large capacitive loads—see AB-003

Figure 4 shows the preferred way to connect a CMOS MDAC for a 0 to $+10\text{V}$ output. This approach is less expensive and provides better accuracy than the other approaches shown below.

The circuit shown in [Figure 5](#) is commonly used to get a 0 to +10V output with a CMOS MDAC. The disadvantage with this circuit is that it requires an extra op amp and pair of precision resistors for each DAC. Also, settling time increases because two amplifiers must settle in the signal path. For good settling time, both amplifiers must be fast settling. Then settling time increases by the square root-of-the-sum-of-the-squares of settling time for each amplifier.

The circuit shown in [Figure 6](#) can also be used to get a 0 to +10V output from a CMOS MDAC. The problem with this circuit is nonlinearity due to code-dependent voltage across the switches within the DAC. Using a 2.5V reference and gain at the output, as shown, mitigates this error, but you still need a pair of precision resistors for each DAC. The appropriate use for this circuit is in +5V single-supply applications. With a 2.5V reference and a unity-gain, single supply buffer, the output will be 0 to +2.5V.

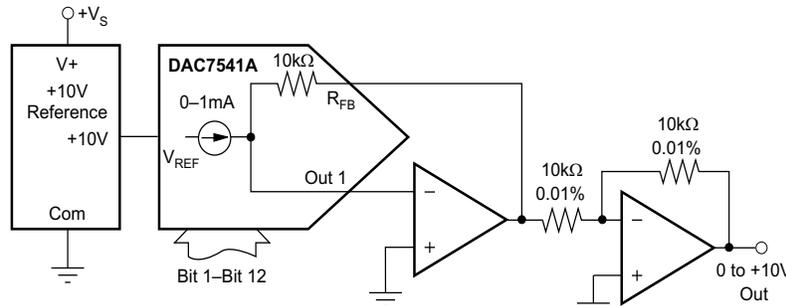


Figure 5. Another 0V to +10V Output DAC

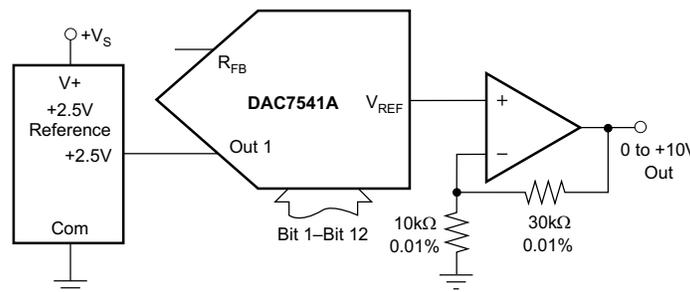


Figure 6. Single Supply 0V to +10V

Revision History

Changes from Original (October 2000) to A Revision	Page
• Changed formatting to standard TI application note.	1

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com