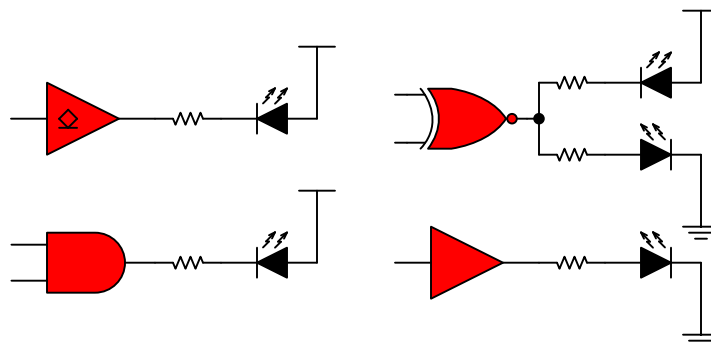


Product Overview

Drive Indicator LEDs



Examples: Using Logic as Indicator LED Drivers

See more about this use case in the *Logic Minute* video [Controlling an Indicator LED](#).

Design Considerations

- Indicator LEDs typically need 1 to 20 mA of drive current to illuminate
- Different LED colors will require different forward voltages

Common LED Forward Voltages by Color

Red	Orange	Yellow	Green	Blue	White
1.8 V	2.0 V	2.2 V	3.5 V	3.6 V	4.0 V

- Series resistors are used to limit the current through the LEDs and can be estimated by the equation:

$$R_{limiting} = \frac{V_{supply} - V_{LED}}{I_{desired}}$$

- Logic functions can be used to provide simple or complex control
- The output voltage of a logic gate (V_{OH} or V_{OL}) is specified at a given test current only
- [\[FAQ\] How do I determine the output voltage or output current of a CMOS logic device?](#)
- Need additional assistance? Ask our engineers a question on the [TI E2E™ logic support forum](#)

Recommended Parts

Part Number	Automotive Qualified	V _{CC} Range	Type	Features	Application
SN74LVC1G07-Q1	✓	1.65 V – 5.5 V	Open-Drain Buffer	Overvoltage tolerant input and output	Open-drain output enables using a 1.8-V signal to control a 5-V powered LED
SN74LVC1G07					
SN74HCS08-Q1	✓	2 V - 6 V	AND Gate	Schmitt-trigger inputs	Control up to 4 LEDs using AND logic
SN74HCS08					
SN74HCS595-Q1	✓	2 V - 6 V	Serial-In Parallel-Out Shift Register	Schmitt-trigger inputs	Drive 8 LEDs per shift register with as few as 3 control inputs
SN74HCS595					

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated