

Protecting Analog Input Channels With Channel Protector With Secondary Rails



Sameer Arora

Multiplexers and Protection Devices

Introduction

The resistance temperature detector (RTD) is an excellent device to measure the signal transition of the temperature with extreme accuracy (more accurate than the thermocouple, and being able to handle higher temperature than the thermistor) helping reduce the external noise. There are various types that use two, three, or four-wire measuring systems depending upon the accuracy level desired and the expected cost. In all of the wire measuring systems, the voltage across R_{RTD} is measured, which is converted to digital format using an analog-to-digital converter (ADC).

This article discusses the overvoltage protection solution for the RTD input systems using the fault-protected multiplexers and channel protectors.

RTD Input Module Using the High-Resolution ADC

The RTD sensor requires an excitation current to produce an output voltage. The excitation current is provided by the ADC containing the multiplexer, PGA, and internal reference. The two-wire system has one wire from each end and the three-wire system has one wire from each end and another wire from any end that goes to the measuring circuit.

Figure 2 shows the basic block diagram for the RTD input system with the $\Delta\Sigma$ ADC and protection using discrete components. As the image shows, the excitation current is provided by the IDAC1/2 for the RTD Sensors.

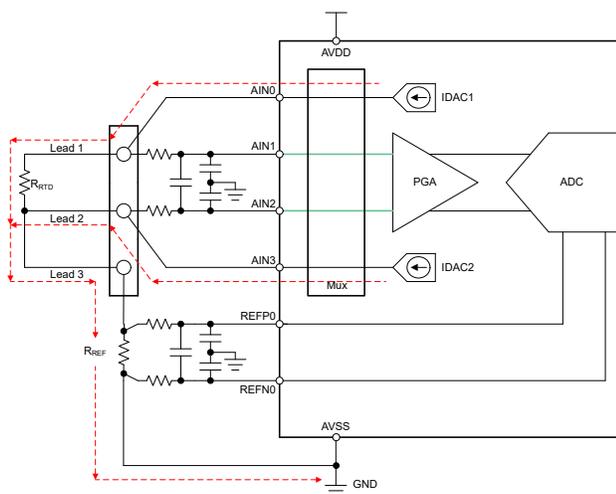


Figure 1. Three-Wire RTD Ratio Metric Measurement Using $\Delta\Sigma$ ADC

There are a number of fault cases that may occur that can be damaging to many of the integrated circuits in the industrial environment. *Such fault conditions may include, but are not limited to, human error from miswiring connections, EOS (transient conditions above standard MUX rating), Latch-up failures, and so forth.* Overvoltage protection is a desirable specification for an RTD module which provides protection to the entire signal conditioning circuit.

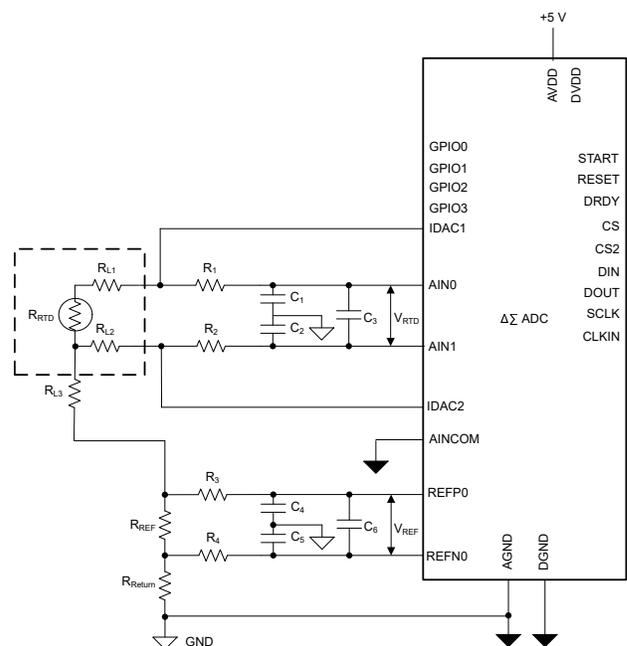


Figure 2. Three-Wire RTD Input System With Discrete Protection

Generally, the discrete components are used in the arrangement in [Figure 2](#) between the source or sense and the ADC. For overvoltage protection, various types of solutions are employed:

- Using series resistors in front of the pins of an ADC can help protect the ADC pins. These pins include analog input and excitation output pins, but the resistors will limit compliance voltage.
- The protection of current source can be realized by discrete components. The current-limiting resistors and the clamping diodes can provide protection against some level of positive and negative voltage.
- Reference resistor for ratio metric measurements can also receive voltage that is too high and get damaged. Here, a limiting resistor and TVS is also required, so that the resistor itself cannot be overloaded.
- The voltage drop has to be limited to a safe level for the ADC or an additional filter network is required with an impedance high enough so that the ADC internal steering diode can handle the current caused by the overvoltage.
- Fault-protected multiplexers like [TMUX7412F](#) and [TMUX7462F](#) can be used to protect the source pins and the analog input channels against the overvoltage events. These parts can provide ± 60 -V fault voltage protection in both the powered and unpowered mode.

[Figure 3](#) illustrates the RTD circuit configuration with the multiplexer.

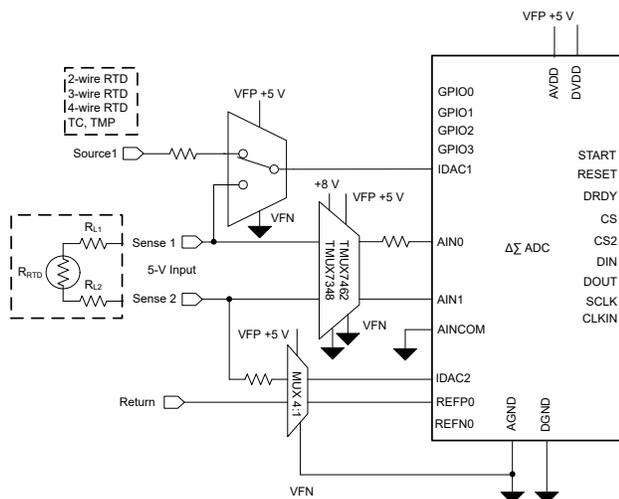


Figure 3. RTD Circuit Configuration With the Multiplexer

The [TMUX7462F](#) is a four-channel protector with adjustable fault threshold, that can be placed on the front end of a signal path to protect analog input pins downstream from damages caused by overvoltage faults. Each of the four channels has

an internal switch that is turned-off autonomously upon occurrence of an overvoltage fault without the need of external controls. This simplifies robust system-level protection designs by removing the need for control signals for each channel of the device. The overvoltage protection is available in powered and powered-off conditions, making the [TMUX7462F](#) suitable for applications with multiple channels that need to be protected simultaneously in an application. For a higher number of channels and multiplexing requirements, the [TMUX7348F](#), an 8:1, 1-channel multiplexer with the adjustable fault threshold (secondary supplies) can also be used as an input multiplexer.

These multiplexers can accept input signals in the range of ± 5 V to ± 22 V and can protect the circuit against high voltage due to potential miswiring risk (outside the VFN, VFP range) up to the protection level of the MUX, that is, ± 60 V.

Using the Secondary Rails for the Protection

V_{FP} and V_{FN} provide the much-needed protection to the ADC in the event that the input RTD is operating at a voltage level higher than the ADC and the high voltage gets exposed to the AIN pin during an overvoltage event. V_{FP} and V_{FN} can be configured to match the ADC supply voltage and can help clamp down the voltage to the supply voltage of the ADC.

Two secondary power supplies on the device, V_{FP} and V_{FN} , are the required secondary power supplies that set the level at which the overvoltage protection comes into play. V_{FP} can be supplied from 3 V up to VDD and V_{FN} can be supplied from VSS to 0 V.

Some of the ADC can have ± 15 V (HV_AVDD, HV_AVSS) for the HV inputs. It has a +5/GND (AVDD, AGND) domain for the REF circuitry and the internal current sources. Introducing fault-protected multiplexers for the IDACs connecting the V_{FP} , V_{FN} to the AVDD/GND domain will work as protection to the IDAC pins and REF inputs.

The switch channels remain in the high-impedance state (regardless of switch input conditions) when the devices power supplies are floating, grounded, or at a level that is below the undervoltage (UV) threshold. If the signal level on any Sx pin exceeds the fault supply (V_{FP} or V_{FN}) by a threshold voltage (V_T), then the Sx pin becomes high impedance and an output fault flag is asserted low to indicate a fault condition under normal operation. The drain pin (Dx) is either pulled to the fault supply voltage that was exceeded or left floating depending on the DR control logic.

Summary

The [TMUX7412F](#) and [TMUX7462F](#) is part of the fault-protected switches and multiplexers family of devices. The ability to protect downstream components from overvoltage events up to ± 60 V and latch-up immunity features makes these switches and multiplexers suitable for harsh environments. Using analog switches and multiplexers in an RTD input system creates ease-of-use and have many advantages including making RTD modules secure from fault voltage, offering low noise and fast settling time.

Reference

- Texas Instruments, [A Basic Guide to RTD Measurements](#) application note
- Texas Instruments E2E™ Forum, [How to design for precision RTD measurements with ADCs](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated