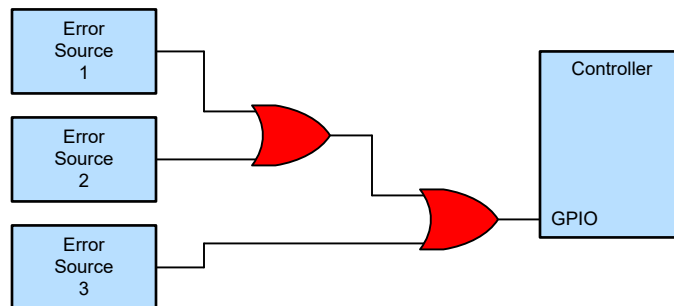


Use Fewer Inputs to Monitor Error Signals



Error source signals can be combined to reduce the number of required inputs to a system controller when it is more important to know *that* an error has occurred than it is to know which device triggered the error. For example, if an overheating condition is detected, it is likely that the system will increase fan speed or shut down operations to respond to the issue regardless of which device signaled the error.



Example Block Diagram for Combining Three Error Sources Into One Error Signal Using OR Gates

See more about this use case in the *Logic Minute* video [Use Fewer Inputs to Monitor Error Signals](#).

Design Considerations

- Ensure that the input signals are digital; analog signals should be converted using a comparator
- Inputs should be active high for this combination method
- [\[FAQ\] How does a slow or floating input affect a CMOS device?](#)
- Ask a question on our [Engineer-to-Engineer forum](#)

Recommended Parts

Part Number	AEC-Q100	V _{CC} Range	Channels	Features
SN74AUP2G32		0.8 V – 3.6 V	2 × 2 input gates	Low power – I _{CC} < 0.9 μA
SN74HCS32		2 V – 6 V	4 × 2 input gates	Schmitt-Trigger input architecture Low power – I _{CC} < 2 μA
SN74HCS32-Q1	✓			
SN74HCS4075		2 V – 6 V	3 × 3 input gates	
SN74HCS4075-Q1	✓			

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated