

Implementation of FSK Modulation and Demodulation using CD74HC4046A

Mahendra Patel
Standard Linear and Logic

ABSTRACT

In telecommunications and signal processing, frequency modulation (FM) is encoding of information on a carrier wave by varying the instantaneous frequency of the wave. Digital data can be encoded and transmitted via carrier wave by shifting the carrier's frequency among a predefined set of frequencies—a technique known as frequency-shift keying (FSK). FSK is widely used in modems, radio-teletype and fax modems, and can also be used to send Morse code.

Frequency-shift keying (FSK) is a frequency modulation scheme in which digital information is transmitted through discrete frequency changes of a carrier wave. This application report discusses logic-level implementation of binary FSK (BFSK) modulator and demodulator using a phase-locked loop PLL device – CD54HC4046A, CD54HCT4046A, CD74HC4046A, and CD74HCT4046A (hereafter in this document referred to as HC/HCT4046A). BFSK is the simplest FSK, using a pair of discrete frequencies to transmit binary information.

Contents

1	Introduction	2
2	Implementation of Modulator	3
3	Implementation of Demodulator	5
4	Test Circuit Waveforms	6
5	Schemes To Realize Modulator – Demodulator Pair	10
6	Conclusion	12

List of Figures

1	Block Diagram of HC/HCT4046A in a Typical PLL Circuit	2
2	Basic Block Diagram of a PLL as a Modulator.....	3
3	Frequency Characteristics of VCO Operating without Offset	3
4	Typical Modulator Schematic.....	4
5	Basic Block Diagram of PLL as Demodulator	5
6	Typical Demodulator Schematic	6
7	Scheme 1	10
8	Scheme 2.....	11
9	Level-Shifter Circuit using LP211	11
10	Simulated Waveforms of Level-Shifter Circuit using LP211	11

List of Tables

1	Modulator Test Circuit Results	4
2	Demodulator Test Circuit Results.....	6
3	Variation in VCO _{OUT} Frequency, Peak-to-Peak Voltage and DEM _{OUT}	7
4	VCO _{IN} (Modulating), VCO _{OUT} (Modulated) and DEM _{OUT} (Demodulated).....	8

1 Introduction

Many measurement applications (for example, electric and gas meters) require a way to communicate electronically with a central office so that measured data can be reported back to the central office and new tariffs can be set in the remote site. ⁽¹⁾ Telephony provides a convenient means of data communication.

This application report discusses logic-level implementation of FSK modulator and demodulator using a PLL device HC/HCT4046A. The HC/HCT4046A, PLL with VCO is a high-speed CMOS IC designed for use in general-purpose PLL applications, including frequency modulation, demodulation, discrimination, synthesis, and multiplication.

Figure 1 illustrates the functional block diagram of a PLL IC, highlighting the following:

- The voltage controlled oscillator (VCO) generates a center frequency locally.
- The center frequency is compared with the incoming signal frequency using a phase comparator (PC)
- The PC generates an error voltage, V_d , which is fed into VCO after a low-pass filter (LPF) shifting the frequency of VCO to lock with the incoming signal.

 


Figure 1. Block Diagram of HC/HCT4046A in a Typical PLL Circuit

⁽¹⁾ Schematics in this report are only for reference. Precise implementation can vary from country to country and based on the application, transmission media, and so forth.

2 Implementation of Modulator

The modulator uses only VCO, as shown in the block diagram illustrated in Figure 2. Values of R1 and C1 determine the frequency range of the VCO and center frequency of operation depends upon VCO input, which is a digital input signal level for a modulator. Hence high (bit1) and low (bit 0) voltage levels of digital input determines actual output frequencies and separation between them.


 


Figure 2. Basic Block Diagram of a PLL as a Modulator

To design a modulator with maximum and minimum frequency of f_{MAX} and f_{MIN} respectively, the following steps are required:

 1. Given f_{MAX} and f_{MIN} , center frequency f_o can be estimated as $(f_{MAX} - f_{MIN}) / 2$, see Figure 3.



$2f_L$ = Frequency Lock Range, f_o = Center Frequency


Figure 3. Frequency Characteristics of VCO Operating without Offset

2. Determine the values of R1 and C1 using figures 11–15 in the device datasheet (SCHS204). Note that the values of these components must satisfy following conditions:
 - (a) $3 \text{ k}\Omega < R1 < 300 \text{ k}\Omega$
 - (b) $C1 > 40 \text{ pF}$
 - (c) $(R1 \parallel R2) > 2.7 \text{ k}\Omega$

Use of R2 to set the offset frequency is optional and can be left open, if not needed.

3. Figure 16–21 of the device datasheet (SCHS204) gives an estimate of separation between frequencies for the given V_{COIN} voltage. $1.0 \text{ V} < V_{COIN} < 0.9 \times V_{CC}$ is recommended to generate proper oscillation from VCO.

- An optional LPF (R3-C2, illustrated in Figure 4) is included to minimize noise at the VCO_{IN} pin. The 3-dB cut off frequency of this filter should be 10 times or higher than the maximum bit rate of the modulating signal.

 
Figure 4. Typical Modulator Schematic

Example:

A test circuit ($V_{CC} = 5\text{ V}$) was implemented to modulate a digital signal with the following component values:

$R1 = 3\text{ k}\Omega$, $C1 = 47\text{ pF}$, $R2 = \text{open}$, $R3 = 0\ \Omega$, $C2 = \text{open}$


Table 1. Modulator Test Circuit Results

	VCO _{IN} (V)	Frequency of VCO _{OUT} (Hz)	VCO _{OUT} peak to peak (V)
1.	1.0	8.22 M	4.6
2.	2.5	17.24 M	3.1
3.	4.5	27.93 M	2.2

Therefore, by choosing logic 0 as 1 V and logic 1 as 4.5 V, a frequency separation of 19.7 MHz can be obtained.

In a practical circuit, frequency separation depends upon the bandwidth availability of the transmission media. Therefore, by choosing an appropriate offset frequency and voltage level of the VCO_{IN} signal, expected modulation can be achieved.

With an increase in VCO_{IN} (CH1) voltage, the frequency of oscillation increases and VCO_{OUT} peak-to-peak voltage (CH2) decreases as shown in [Waveform 1](#).

 

Waveform 1. VCO_{IN} (CH1) Voltage and VCO_{OUT} Peak-to-Peak (CH2) Variation

3 Implementation of Demodulator

The demodulator operates in closed-loop mode with the PC and an external LPF, as shown in [Figure 5](#).

 


Figure 5. Basic Block Diagram of PLL as Demodulator

To design a demodulator with maximum and minimum frequency of f_{MAX} and f_{MIN} , respectively (which is same as that of modulator), the following steps are required:

1. Use the same value of R1 and C1 as that of modulator.
2. While using PC1, the capture range depends on the LPF (R3-C2) characteristics and can be made as large as the lock range. For PC2, capture range is equal to lock range and is independent of the LPF.
3. Since leakage current can affect the $V_{DEMOOUT}$, a load resistor (R5) from this pin to GND in the range of 50 k Ω to 300 k Ω is recommended.

Table 3. Variation in VCO_{OUT} Frequency, Peak-to-Peak Voltage and DEM_{OUT}

 
 
 
	Condition at Modulator	Demodulator Waveforms: CH1: SIG _{IN} and CH2: DEM _{OUT}
1.	VCO _{IN} = 1 V	 <p style="text-align: center;">Waveform 2</p>
2.	VCO _{IN} = 2.5 V	 <p style="text-align: center;">Waveform 3</p>
3.	VCO _{IN} = 4.5 V	 <p style="text-align: center;">Waveform 4</p>

Table 4. VCO_{IN} (Modulating), VCO_{OUT} (Modulated) and DEM_{OUT} (Demodulated)

 
 
 
 
 
 
	VCO _{IN}	DEM _{OUT}	Waveforms: CH1: VCO _{IN} , CH2: VCO _{OUT} , CH3: DEM _{OUT}
1.	Peak to peak (V)=3.44 V, Frequency = 1 kHz	Peak to peak (V) = 3.12 V, Mean (V) = 2.74 V	 <p style="text-align: center;">Waveform 5</p>
2.	Peak to peak (V) = 3.52 V, Frequency = 5 kHz	Peak to peak (V) = 3.20 V, Mean (V) = 2.62 V	 <p style="text-align: center;">Waveform 6</p>
3.	Peak to peak (V) = 3.60 V, Frequency = 10 kHz	Peak to peak (V) = 3.28 V, Mean (V) = 2.64 V	 <p style="text-align: center;">Waveform 7</p>

Table 4. (continued)

	VCO _{IN}	DEM _{OUT}	Waveforms: CH1: VCO _{IN} , CH2: VCO _{OUT} , CH3: DEM _{OUT}
4.	Peak to peak (V) = 3.60 V, Frequency = 20 kHz	Peak to peak (V) = 3.12 V, Mean (V) = 2.69 V	 <p style="text-align: center;">Waveform 8</p>
5.	Peak to peak (V) = 3.52 V, Frequency = 30 kHz	Peak to peak (V) = 3.04 V, Mean (V) = 2.72 V	 <p style="text-align: center;">Waveform 9</p>
6.	Peak to peak (V) = 3.52 V, Frequency = 40 kHz	Peak to peak (V) = 2.88 V, Mean (V) = 2.71 V	 <p style="text-align: center;">Waveform 10</p>

It can be concluded from Waveforms 5 through 9, that it is difficult to use the DEM_{OUT} signal as it is, at higher frequency of modulating signal. Hence, a Schmitt trigger can be used with appropriate threshold and hysteresis to get a clean demodulated signal with sharp rising and falling edges.

5 Schemes To Realize Modulator – Demodulator Pair

This section briefly describes various FSK modulation-demodulation schemes. It is important to consider the limitations of each technique before using it for a specific application. In each case, frequency used to represent digital data after FSK modulation should be hundred folds or higher than that of digital data rate to ensure correct bit duration for each bit after demodulation.

5.1 Scheme 1

In this scheme, VCO at the modulator transmits a particular frequency during occurrences of bit 1 in the digital data and remains idle during occurrence of bit 0. At the demodulator end, the presence or absence of the frequency is tracked by the PLL. PC output followed by LPF, represents the demodulated signal, which is the equivalent of the original digital information.

For this scheme, $V_{CO_{IN}} < 0.6 \text{ V}$ for logic 0 and $V_{CO_{IN}}$ close to $0.9 \times V_{CC}$ for logic 1 is recommended.

Use of PC2 at the demodulator gives good results over a wide range of frequency.

 


Figure 7. Scheme 1

Advantages:

- Power consumption is less at the modulator.
- A burst of frequency is transmitted only during transmission of a specific data bit (either 1 or 0), hence, there is less noise created in the transmission media.
- Single frequency is used; therefore, the bandwidth requirement is smaller.
- Gives better performance even at higher frequencies (200 kbps or higher) of modulating signal (as compared to scheme 2), because of wide separation possible between logic 0 and logic 1 voltages.

Limitations:

- It is difficult to determine if the remote modulator is defunct (versus continuously sending 0's).
- When $V_{CO_{IN}} < 0.6 \text{ V}$ (logic 0), modulator output may either be 0 V or V_{CC} ; however, this does not affect demodulation.

5.2 Scheme 2

In this scheme, VCO at the modulator transmits one particular frequency during occurrences of bit 1 in the digital data and other frequency during occurrence of bit 0. At the demodulator end, the change in the frequency is tracked by the PLL. PC output followed by LPF represents the demodulated signal, which is the equivalent of the original digital information.

For this scheme, $1.0\text{ V} < V_{CO_IN} < 0.9\text{ V}_{CC}$ is required.

Use of PC2 at the demodulator gives good results over a wide range of frequency.

 


Figure 8. Scheme 2

Level shifting of the input digital signal is required to meet the V_{CO_IN} input range which can be achieved using a level-shifter circuit.

 


Figure 9. Level-Shifter Circuit using LP211

 


Figure 10. Simulated Waveforms of Level-Shifter Circuit using LP211

As can be seen from the test waveform in Figure 10, a digital signal V_{in} (0 V–3.3 V) is converted to V_{CO_IN} (1.07 V–4.5 V).

Advantages:

- It is easy to determine if the remote modulator is defunct.

Limitations:

- Power consumption is more at the modulator due to continuous oscillations.
- Requires more bandwidth
- As VCO_{IN} logic 0 and logic1 voltage level separation decreases, noise on the demodulated output appears to increase.

6 Conclusion

This application report described logic-level implementation of BFSK modulator and demodulator using HC/HCT4046A devices.

However, while implementing this circuit for a real-time application, the following important factors must be considered for a reliable communication link:

- Output impedance of the modulator
- Characteristic impedance of the transmission media
- Frequency response of transmission media
- Input impedance of the demodulator

Hence, impedance matching and signal conditioning becomes an important aspect in a practical system.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com