

# **TMDS Clock Detection Solution in HDMI® Sink Applications TS3USB3031, SN65LVDS4, SN65LVDS17**

Gibson Kim

## ABSTRACT

*High-Definition Multimedia Interface (HDMI®) sink applications such as digital TVs, monitors, and other display equipment are able to wake up from standby or sleep mode by detecting Transition-Minimized Differential Signaling (TMDS) clock or signals in HDMI applications.*

### Contents

1	Waking Up an HDMI Sink Device .....	2
2	Communicating Without CEC .....	3
3	Conclusion .....	8

### List of Figures

1	HDMI High-Level Block Diagram .....	2
2	Conceptual Schematic for one TMDS Differential Pair .....	3
3	Implementation Example Block Diagram 1 .....	4
4	Implementation Example Block Diagram 2 - Single-Chip Implementation .....	5
5	Q-Signal Boost Circuitry Suggestion .....	6
6	Q-Signal Boost Circuitry for Simulation .....	6
7	Typical Waveforms From Simulation.....	7
8	Single Remote Controller for Both HDMI Sink and Source .....	8

### List of Tables

1	CEC Operation Codes .....	2
2	Termination Requirement in HDMI Receiver.....	3
3	Summary of Simulation Result for Corner Cases .....	7
4	HDMI Sink can Wake-Up Without CEC.....	8


## Trademarks

Blu-ray Disk is a trademark of Blu-ray Disc Association.  
HDMI is a registered trademark of HDMI Licensing, LLC.  
All other trademarks are the property of their respective owners.

## 1 Waking Up an HDMI Sink Device

HDMI is a defacto interface standard in consumer electronics and the most successful and easiest video and audio connector in the industry. Most digital TVs, monitors, and video display equipment have one or more HDMI ports. Video source equipment such as set-top boxes, gaming consoles, Blu-ray Disk™ players, notebooks, and mobile video sources support HDMI as well.

HDMI supports a supplemental specification, *Consumer Electronics Control* (CEC), to control the HDMI source and sink in HDMI-connected equipment. CEC provides the same 'language' between the HDMI equipment allowing users to easily control them. [Figure 1](#) shows the high-level HDMI interconnection, including a CEC line.

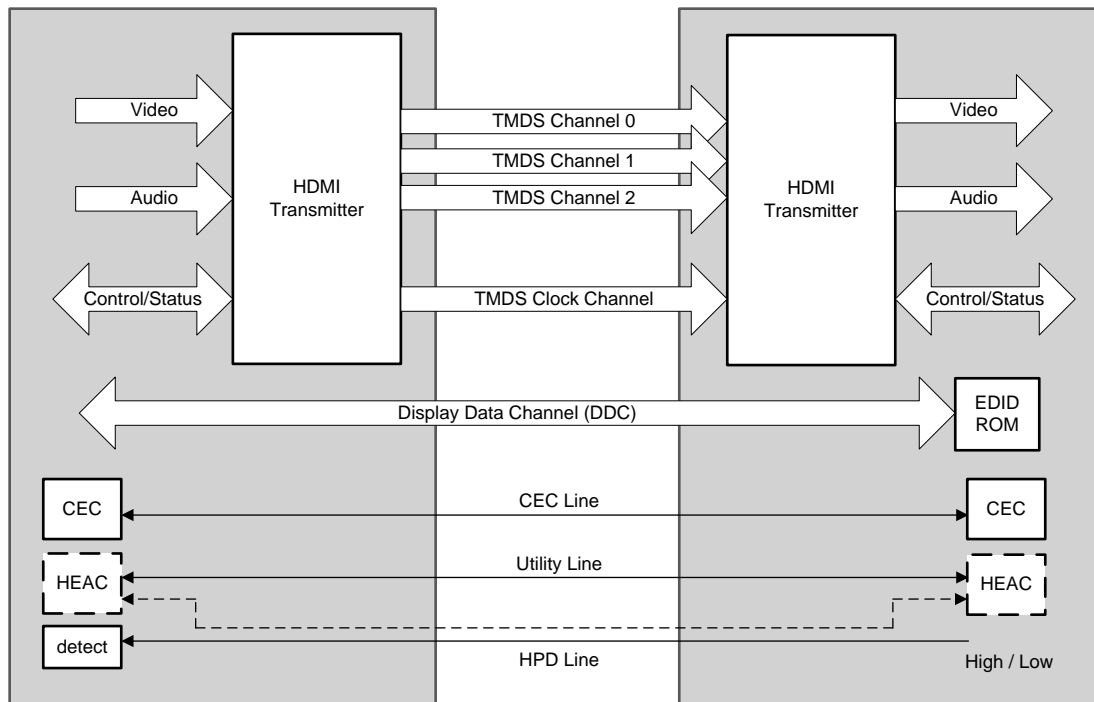

**Figure 1. HDMI High-Level Block Diagram**

CEC is one of the 19 HDMI connector pins and CEC has its own electrical and protocol specification. A number of different messages and operation code (opcode) are used for the best user experience so that users can use only one remote controller to control both HDMI source and HDMI sink devices. For instance, if an HDMI source and sink are in standby mode and the user wants to wake up both of them, the following power-on function code can be used to switch on the HDMI devices by pressing the power button on the remote controller. This will wake up both the HDMI source and sink devices. More advanced user-controlled CEC messages are available, refer to the CEC specification in HDMI 2.0, or older version specifications.

**Table 1. CEC Operation Codes**

UI Command Code	User Operation	Function
0x6C	Power off function	Puts the device into the Standby state. If repeated, the device stays in the Standby state.
0x6D	Power on function	Puts the device into the On (non-Standby) state. If repeated, the device stays in the active state.

### 1.1 Reasons for Wake Up Failure

Although CEC is provided for the control of the HDMI devices, its implementation and operation is not that simple. It is common that HDMI sink users experience the HDMI source is not controllable through a single remote controller as expected, and vice versa. This is because many HDMI sources and sinks do not support CEC, including a few very well-known HDMI source devices and thus there is no simple way to control both the HDMI source and sink devices at once. There are also a number of HDMI devices supporting CEC, but require complicated steps to enable the feature in the equipment. Not as common are some devices that implement vendor-specific codes preventing HDMI source and sink devices from communicating.

## 2 Communicating Without CEC

This section provides examples for making the HDMI sink device detect *Transition Minimized Differential Signaling* (TMDS) clock or signal from an HDMI source device so that the HDMI sink can wake up from its standby state by turning on the HDMI source with a single remote controller.

The HDMI transmitter source detects receiver terminations in HDMI sink. If the HDMI receiver enables the termination resistors, then the transmitter will determine the 3.3-V terminated level and that the receiver is connected and functioning.

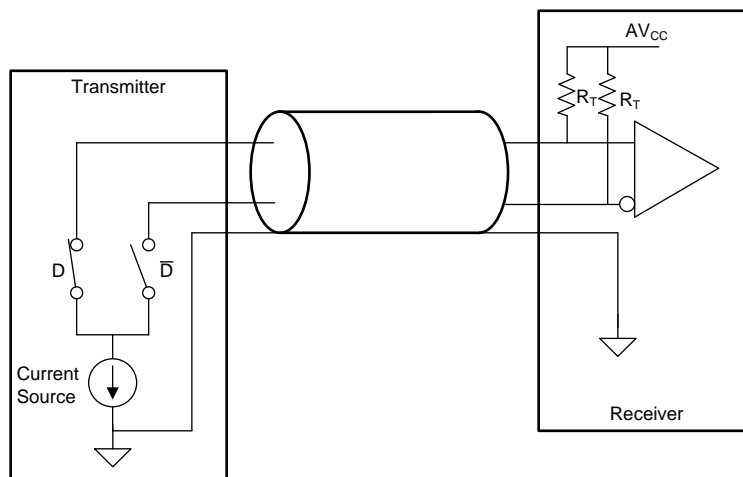



Figure 2. Conceptual Schematic for one TMDS Differential Pair

Table 2. Termination Requirement in HDMI Receiver

Item	Value
Termination supply voltage, $AV_{CC}$	3.3 V $\pm 5\%$
Termination resistance, $R_T$	50 $\Omega$ $\pm 5\%$

When an HDMI sink is in standby mode, most HDMI sinks will disable the termination resistors to save power while enabling a *Hot-Plug Detection* (HPD) signal (high) as long as an HDMI source plug is providing HDMI 5 V. The HDMI source will have no way to provide a TMDS signal and wake up the sink, because they are not terminated.

## 2.1 Implementation Example 1: TS3USB3031, SN65LVDS4

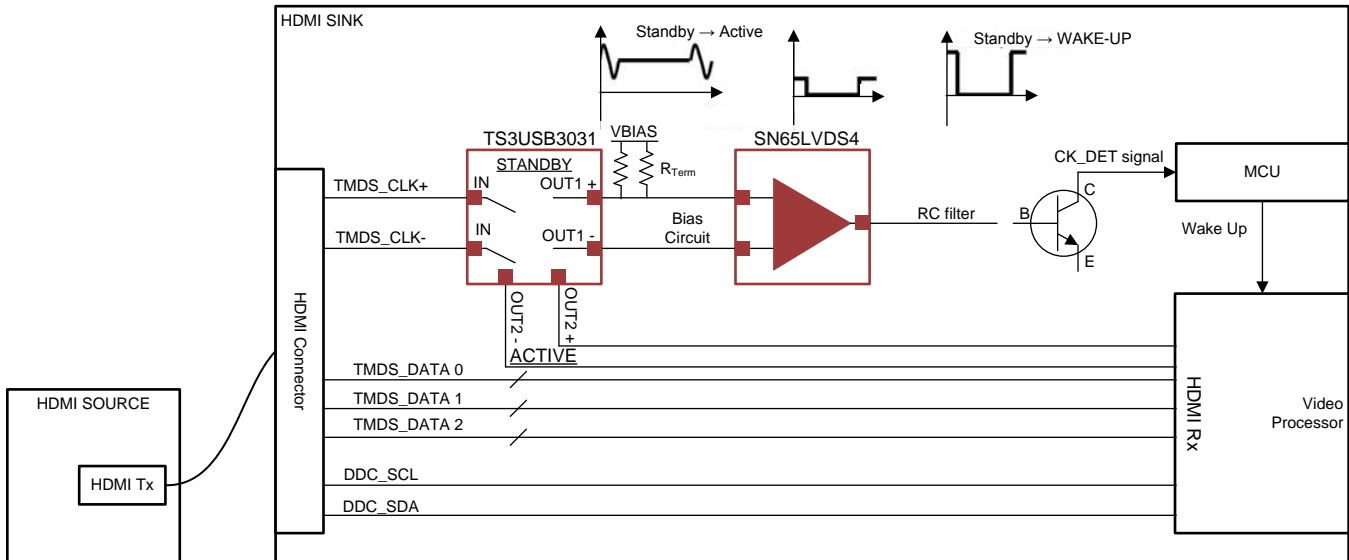

**Figure 3. Implementation Example Block Diagram 1**

This is proven by simulation and actual test board environment for both functionality and HDMI compliance test at different corner cases:

- A high-speed switch can be used to switch or isolate actual TMDS clock path from TMDS clock detection path. In *Active* mode, TMDS clock can be connected to HDMI Rx in a video processor. In *Standby* mode, it is directed to TMDS clock and signal detection circuitry to check if there is an incoming signal or not.
- Use caution when selecting a high-speed switch. In order to fulfill signal integrity and HDMI compliance test, the electrical characteristics of the switch are important. The [TS3USB3031](#) provides a good enough bandwidth and I/O capacitance up to 4K/60fps video conditions. A good layout technique is required to minimize impact to the impedance - HDMI spec:  $100\ \Omega \pm 15\%$  with single excursion of  $100\ \Omega \pm 25\%$  with duration less than 250 ps.
- Proper termination for HDMI source to see  $R_{Term}$  in the standby mode of the HDMI sink is needed.
- Differential to single-ended receiver can be used to convert TMDS clock signals to single-ended TTL or CMOS signals. A proper bias circuitry may be needed for TMDS to the Differential to single-ended receiver. The [SN65LVDS4](#) has a wide-enough bandwidth,  $V_{ID}$  and sensitivity spec so that TMDS clock rates from all video resolutions can be converted to single-ended signal.
- Depending on the MCU or processor that will detect the wake-up signal from SN65LVDS4, a proper RC filtering may be needed to eventually detect the wake-up signal. If the MCU or processor can detect the clock signal itself, this step is not needed.
- A proper transistor may be used to meet I/O spec of the MCU.
- Once the wake-up signal is detected, then the MCU wakes up the video processor and the video processor can enable  $R_{Term}$  in HDMI Rx for normal operation.

## 2.2 Implementation Example 2: SN65LVDS17

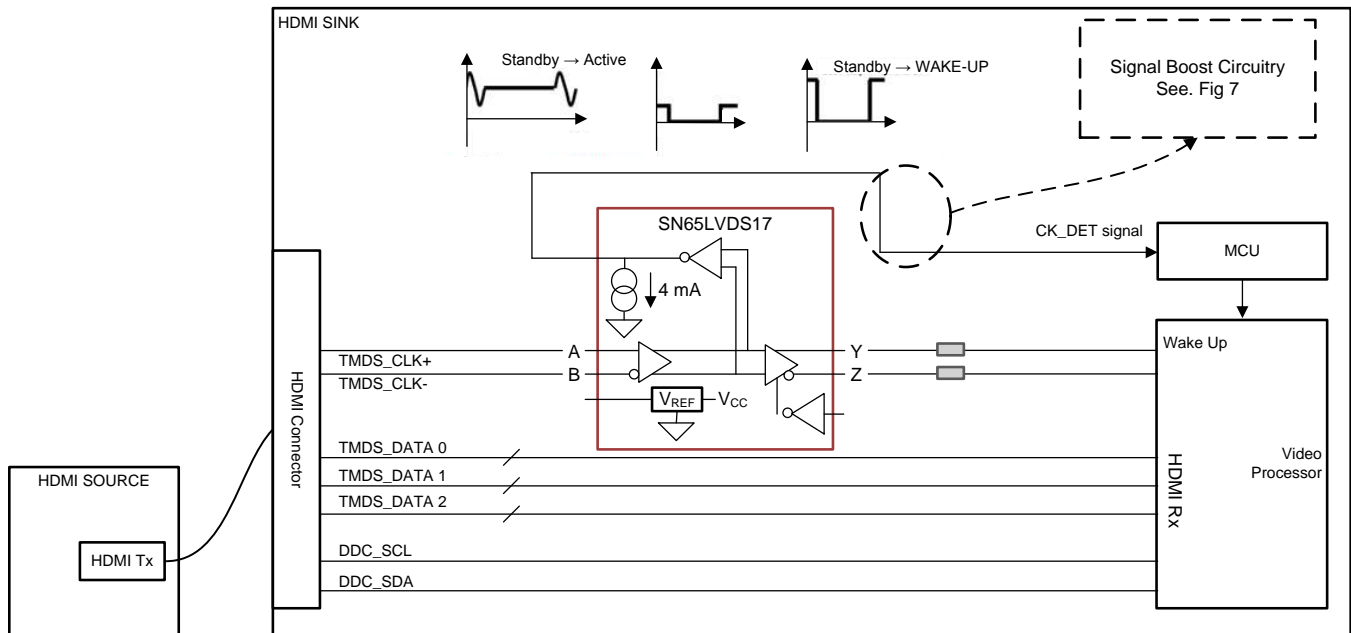


Figure 4. Implementation Example Block Diagram 2 - Single-Chip Implementation

This is proven by simulation and actual test board environment for both functionality and HDMI compliance test at different corner cases.

- Products like the [SN65LVDS17](#) can be used to detect TMDS clock. SN65LVDS17 supports wide enough bandwidth up to 2 GHz for TMDS clock. It senses clock signals and transmits Q output with 575-mV peak-to-peak output voltage.
- Proper termination for HDMI source to see  $R_{Term}$  in standby mode of HDMI Sink is needed. AC coupling caps are required between SN65LVDS17 to HDMI Rx.
- Depending on the MCU or processor that will detect the wake-up signal from SN65LVDS17, a proper circuitry at Q output may be needed to eventually detect the wake-up signal. If the MCU or processor can detect the Q signal of the SN65LVDS17 itself, this step is not needed.
- Once the wake-up signal is detected, then the MCU wakes up the video processor and the video processor can enable  $R_{Term}$  in HDMI Rx for normal operation.

The following list is a circuit suggestion to boost up Q output from [SN65LVDS17](#) and to provide a proper clock detection signal to the MCU. It is required to have transistors with enough bandwidth and accurate pull up and pull down the design (R5 and R6) depending on the transistor (QN2).

- C1 allows decoupling of the LVDS17 output bias to avoid issues from part-to-part variations
- R1 and R2 to bias QN1
- QN1 has to have enough BW to pass a maximum of 340-MHz signals
- R3 and R4 provide gain
- C2 and R5 ensure QN2 is always off and no leakage occurs when there is no clock signal
- QN2 has to have enough BW to pass 340-MHz signals
- R6 and C3 determine how fast the circuit will determine clock presence or absence
- MMBT5179 or similar performance transistors are good choices

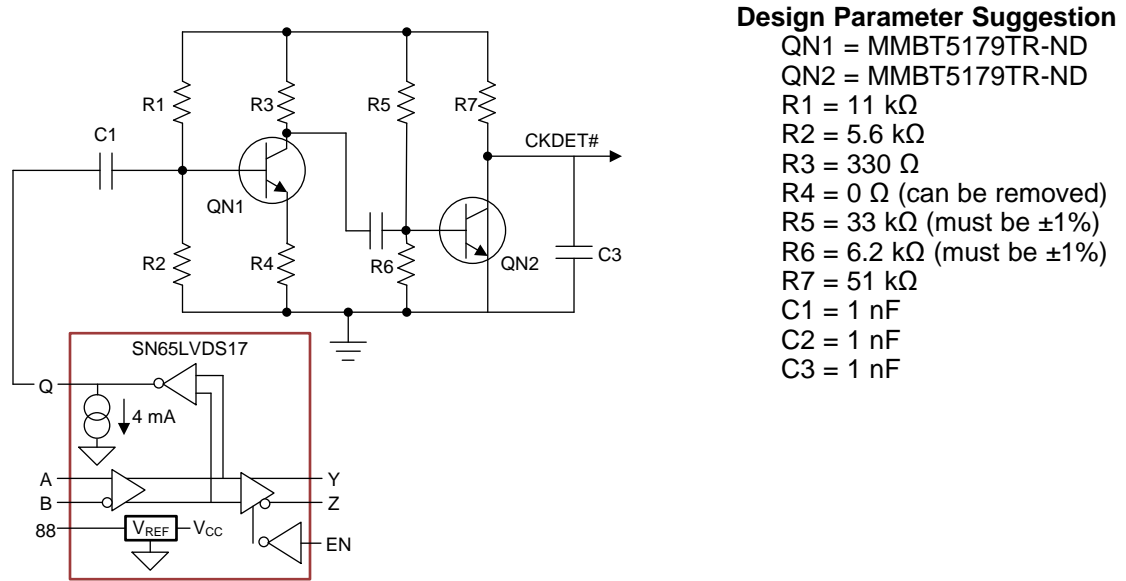


Figure 5. Q-Signal Boost Circuitry Suggestion

Simulation has been done with the circuit shown in Figure 6 at different corner conditions.

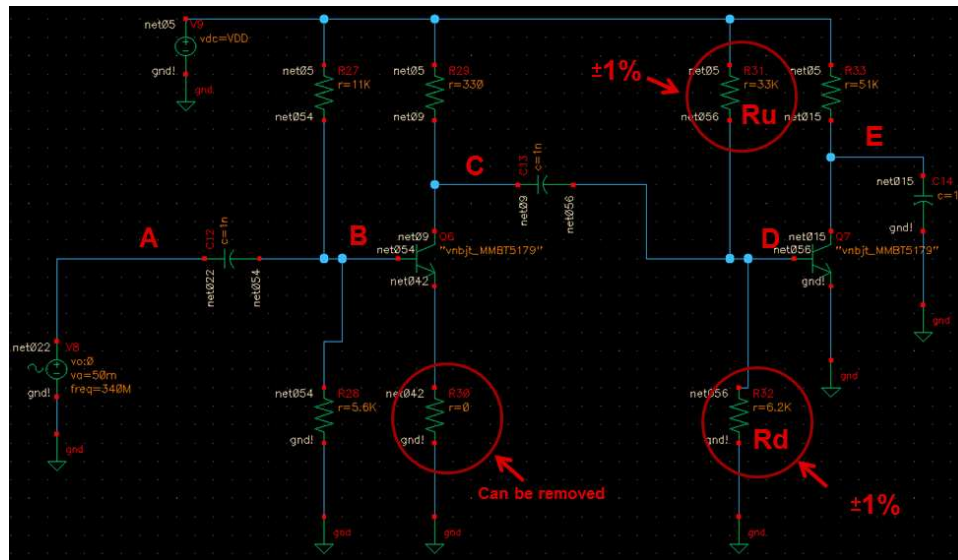


Figure 6. Q-Signal Boost Circuitry for Simulation

Figure 7 shows the waveform from a simulation with a clock input of 70-mV swing under typical temperature and Vcc conditions.

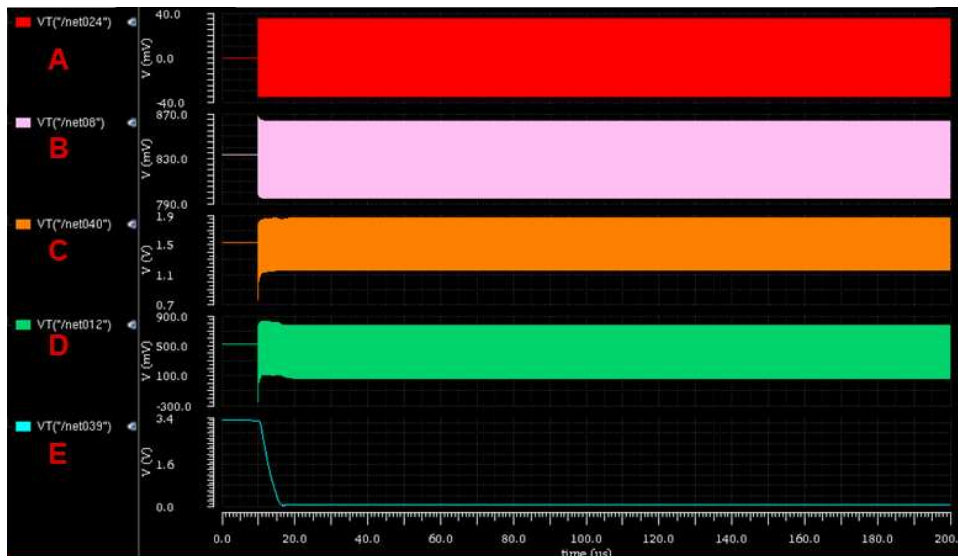


Figure 7. Typical Waveforms From Simulation

TI completed a simulation with corner cases and the results suggest that a well-designed circuit with pullup and pulldown resistors (R5 and R6) and Vcc with 1% tolerance will allow the MCU to detect signals with down to a 70-mV swing level under 0–70°C temperature conditions.

Table 3. Summary of Simulation Result for Corner Cases

		Worst for VOL		Typical			Worst for VOH	
Simulation Condition	Temp	0C	0C	0C	27C	70C	70C	70C
70mV swing at A	VDD	3.3V-10%	3.3V-5%	3.3V-1%	3.3V	3.3V+1%	3.3V+5%	3.3V+10%
	Ru and Rd	Ru+1% Rd-1%	Ru+1% Rd-1%	Ru+1% Rd-1%	/	Ru-1% Rd+1%	Ru-1% Rd+1%	Ru-1% Rd+1%
	Output Level	VOH	2.77V	1.22V	94mV	49mV	38mV	38mV
	VOL	2.97V	3.135V	3.269V	3.298V	3.245V	3.287V	3.202V
		Worst for VOL		Typical			Worst for VOH	
Simulation Condition	Temp	0C	0C	0C	27C	70C	70C	70C
100mV swing at A	VDD	3.3V-10%	3.3V-5%	3.3V-1%	3.3V	3.3V+1%	3.3V+5%	3.3V+10%
	Ru and Rd	Ru+1% Rd-1%	Ru+1% Rd-1%	Ru+1% Rd-1%	/	Ru-1% Rd+1%	Ru-1% Rd+1%	Ru-1% Rd+1%
	Output Level	VOH	1.29V	62mV	43mV	36mV	31mV	31mV
	VOL	2.97V	3.135V	3.269V	3.298V	3.245V	3.287V	3.202V
		Worst for VOL		Typical			Worst for VOH	
Simulation Condition	Temp	0C	0C	0C	27C	70C	70C	70C
130mV swing at A	VDD	3.3V-10%	3.3V-5%	3.3V-1%	3.3V	3.3V+1%	3.3V+5%	3.3V+10%
	Ru and Rd	Ru+1% Rd-1%	Ru+1% Rd-1%	Ru+1% Rd-1%	/	Ru-1% Rd+1%	Ru-1% Rd+1%	Ru-1% Rd+1%
	Output Level	VOH	85mV	43mV	35mV	30mV	26mV	26mV
	VOL	2.97V	3.135V	3.269V	3.298V	3.245V	3.287V	3.202V

### 3 Conclusion

With a TMDS clock or signal-detection circuitry implemented, the HDMI source can determine TMDS receiver termination and transmit clock and signal when the user activates the source from its standby mode, and eventually HDMI sink can detect TMDS clock or signal running and wake up the system without any control.

**Table 4. HDMI Sink can Wake-Up Without CEC**

Device Power State No CEC Supported		Without TMDS Clock Detector		With TMDS Detector	
HDMI Sink	HDMI Source	R <sub>Term</sub>	Source Remote Control Causes Wake-Up	R <sub>Term</sub>	Source Remote Control Causes Wake-Up
Active	Active	Yes	-	Yes	-
Active	Standby	Yes	-	Yes	-
Standby	Active	No	No	Yes	Yes
Standby	Standby	No	No	Yes	Yes



**Figure 8. Single Remote Controller for Both HDMI Sink and Source**



## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated