

Comparison of the silicon-based isolation vs. optocoupler

The control of a larger number of independent GPIO signals by a digital isolator brings the following advantages compared to a per-channel isolation using an optocoupler.

Power consumption

The power consumption is independent of the channel count and the inputs of the digital isolator provide high-impedance inputs. Optocoupler power consumption can be $10 \times$ of a digital isolator when configured in an SPI interface. The current is provided either by a transistor or directly from the control signal of the controller.

Size and height

The digital isolator ISO7741 is available in a small 5-mm \times 6-mm SOIC package; the shift registers in TSSOP packages. The example application requires a board space of about 100 mm² while the same solution with optocouplers (6 devices with 4 channels per package) requires about 275 mm².

Update rate

For this example, the SPI clock speed must be at least $17 \times$ the update rate of the required INx and FAULT# update rate. The delay of a standard optocoupler is in the same ball park and dependent on the load resistance, but also on internal storage, rise and fall times.

Processor resources

Processor resources for the introduced approach are independent of the channel count. Only four processor pins for the SPI are required. Most SPI implementations today are buffered, that is, cycle-accurate back-to-back transfers are possible.

Controller including a direct memory access (DMA) triggered by SPI interrupts reducing the software overhead to a memory read or write. In contrast, each optocoupler requires a separated controller GPIO line. GPIO control by port pin may not be as accurate as software is involved. Even an interrupt-driven implementation normally cannot guarantee a cycle-accurate update of the controller port pins.

Scalability

The solution is expandable in multiples of 8 by adding shift registers to the signal chain. As shown, no review of processor resources is needed if the channels count changes.

BOM count

The BOM is limited to the ISO7741DBQ and one or more serial shift register, one dual-inverter for the input functionality, and some bypass capacitors. The amount of optocouplers is given by the isolating channels, but an optocoupler with multiple channels per device are available. Each optocoupler needs at least a current-limiting resistor at the input and a pullup resistor at the output if an open-collector output is used.

Aging

Digital isolators are more reliable as optocouplers, which is important especially in industrial 24 hours per day, 7 days per week applications with long runtimes.

References

- [ISO7741 product page](#)
- [TPS274160 product page](#)
- [SN74HCS594-Q1 product page](#)
- [SN74HCS165 product page](#)
- [SN74LVC2G14 product page](#)

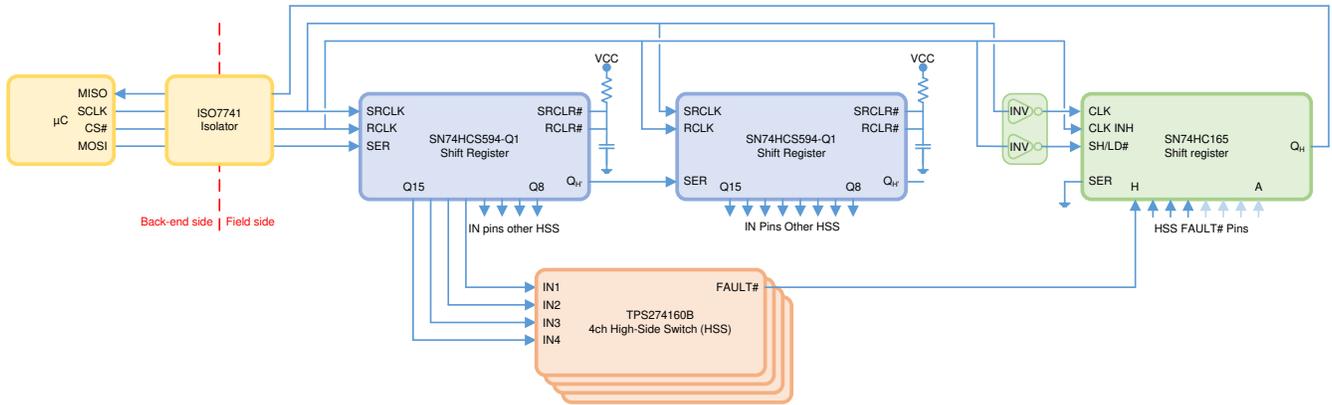


Figure 3. Block Diagram

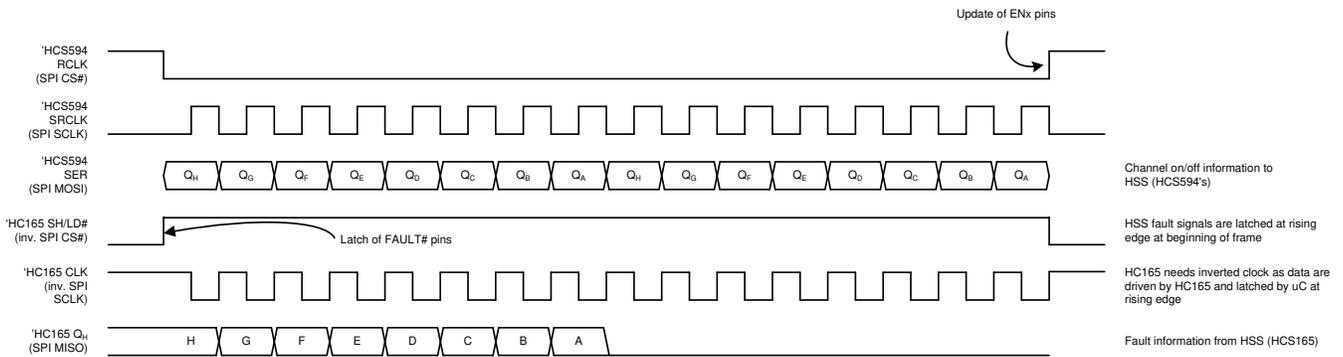


Figure 4. Timings

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated