

7-W Single Stage PFC LED Lighting Design with TRIAC Dimming

Jamie Zhang, Linda Ye and Jimmy Liu

Power Field Applications/China Power Reference Design

ABSTRACT

This report describes a reference design of 7-W AC/DC LED lighting driver with TRIAC dimming. The solution adopts single-stage power factor correction (PFC) flyback topology with primary side constant power control. A thorough analysis and design of the power converter are presented. Finally, the experimental results obtained on 7-W application are provided. The design can be easily modified to be suitable for other applications.

Contents

1	Introduction	2
2	Theory of Operation	2
	2.1 Single-Stage Flyback Converter with Power Factor Correction	2
	2.2 TPS92210 Controller and System Operation	3
3	7-W Off-Line Constant Power LED Lighting Driver Design	5
	3.1 Design Specification	5
	3.2 Schematic.....	6
	3.3 PCB Layout	7
	3.4 Efficiency	8
	3.5 Line Regulation.....	8
	3.6 Power Factor	9
	3.7 TRIAC Dimming Performance	9
4	Conclusion.....	13
	Reference	13

List of Figures

Figure 1.	Single-Stage Flyback Converter	2
Figure 2.	Feedforward Circuit for Primary Side Constant Power Control	4
Figure 3.	T_{on} Time vs. Vin_{rms} and Input Power vs. Vin_{rms}	5
Figure 4.	PMP4304A Schematic.....	6
Figure 5.	Circuit Board Assembly Drawing — Layer 1.....	7
Figure 6.	Circuit Board Assembly Drawing — Layer 2.....	7
Figure 7.	Efficiency vs. Input Voltage	8
Figure 8.	Output Current vs. Input Voltage.....	8
Figure 9.	Power Factor vs. Input Voltage.....	9
Figure 10.	Output Current vs Dimmer Conduction Angle.....	10
Figure 11.	Input Current vs. Input Voltage at Different Conduction Angle.....	12

TABLES

Table 1.	Electrical Design Specification.....	5
Table 2.	Output Current with Different Dimmer Conduction Angle	9

1 Introduction

The reference design, PMP4304A, is a single-stage power factor corrected LED driver with TRIAC dimming using Texas Instrument's TPS92210 LED lighting power controller. The LED application focuses on PAR Bulb replacement with a small form factor, low cost, high PF and high TRIAC dimming performance.

The solution adopt single stage power factor correction (PFC) flyback converter with primary side constant power control. It realizes primary side constant power control in the single stage flyback topology without opto-coupler. The driver can work with highline AC or low-line AC. The output provides a constant current of 350 mA to drive typically 6 LEDs in series.

2 Theory of Operation

2.1 Single-Stage Flyback Converter with Power Factor Correction

This single-stage power factor corrected converter is an isolated flyback AC/DC topology that rectifies the AC input line to a DC output with an input sinusoidal current. The single-stage flyback topology is widely used as an isolated LED solution because this solution has a very low BOM cost and high efficiency.

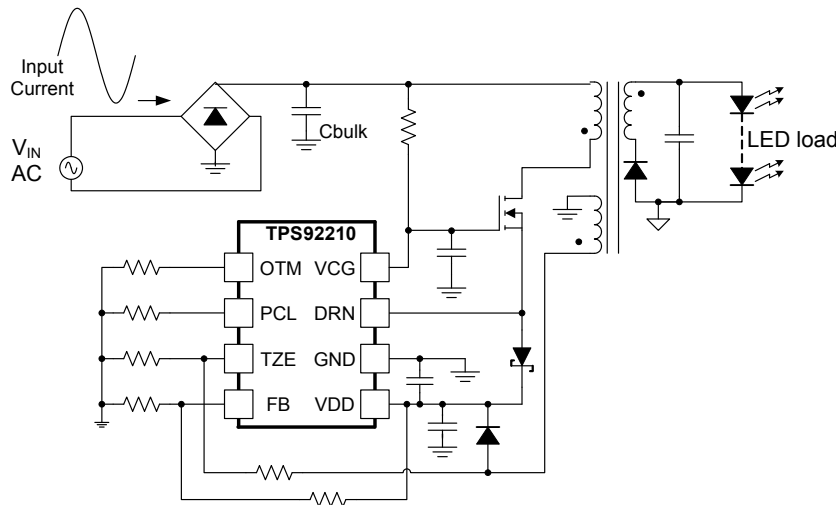


Figure 1. Single-Stage Flyback Converter

Conventional single-stage flyback solution adopt transition mode to regulate the constant on time to implement the PFC function. However, the flyback topology with transition mode is unnatural PFC because the duty cycle and the frequency always changes. So the PF and THD is not highly accurate at this condition.

However, the primary side constant power single-stage flyback is a natural PFC.

First, the input voltage can be set as below:

$$V_{in}(wt) = \sqrt{2} * V_{rms} * \sin(wt) \quad (1)$$

Then the average input current can be calculated as Equation 2.

$$I_{avg}(wt) = \sqrt{2} * V_{rms} * \sin(wt) * \frac{T_{on}}{L} * \frac{1}{2} * T_{on} * f \quad (2)$$

By Equation 1 and 2, the input power can be calculated as below.

$$P_{in} = \frac{\int_0^{\pi/w} \sin^2(wt) * dt}{L} * V_{rms}^2 * T_{on}^2 * f \quad \Bigg/ \quad \frac{\pi}{w} = \frac{1}{2} * \frac{V_{rms}^2 * T_{on}^2}{L} * f \quad (3)$$

In the primary side constant power scheme:

$$V_{rms} * T_{on} = K \quad (4)$$

In Equation 4, K is a constant and the value of K depends the system total power.

When the RMS of V_{in} changes, the duty on time changes reversely. And when the RMS of V_{in} is defined, the duty on time will not be changed again. So when the system is steady, the duty on time and duty are constant.

At the same time, in order to keep the constant power, the system is kept in the same switching frequency.

Because the T_{on} , L , f , and V_{in} are all constant, the input current is a natural sinusoidal from Equation 2.

From the other side, the input power is also constant from Equation 3.

In conclusion, it is seen that the primary side constant power single-stage scheme has some advantage with the conventional scheme in this application. First, the primary side constant power scheme is a natural PFC, its PF and THD are all better than conventional scheme. Second, as its name implies, the primary side constant power scheme can be controlled only on primary side. By this, the opto-coupler can be excluded, allowing for a low-cost BOM.

2.2 TPS92210 Controller and System Operation

For the TPS92210 controller, there is an OTM pin, which can control the ton time by the resistor connected to it; the details are shown below.

$$R_{OTM} = t_{ON} \times \left(2 \times 10^{10} \frac{\Omega}{s} \right) \quad (5)$$

In order to realize the primary side constant power control, the following circuit is used as Figure 2.

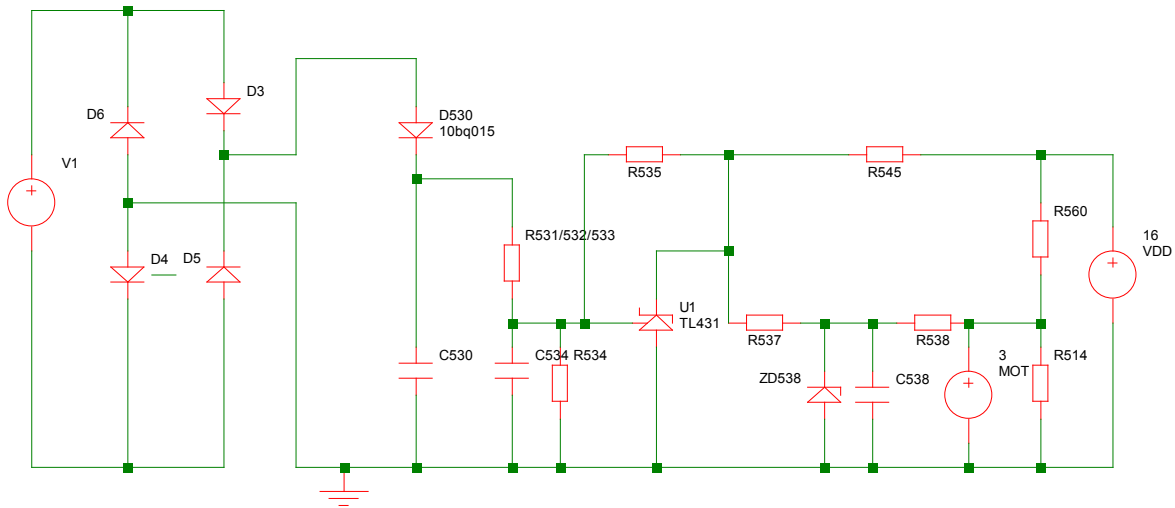


Figure 2. Feedforward Circuit for Primary Side Constant Power Control

Assuming $V_{in_rms} = x$, the relationship between T_{on} and V_{in_rms} can be calculated as below.

$$T_{on}(x) := \frac{\frac{3}{(2 \cdot 10^{10})}}{\frac{3}{R_{514}} - \left(\frac{V_{dd} - 3}{R_{560}} \right) - \frac{V_f + \frac{V_f \cdot R_{535}}{R_{534}} - \frac{(\sqrt{2}x - 35) \cdot R_{535}}{3 \cdot 10^6} - 3}{R_{538} + R_{537}}} \quad (6)$$

If :

$$A = \frac{3}{R_{514}} - \frac{V_{dd} - 3}{R_{560}} - \frac{V_f + \frac{V_f \cdot R_{535}}{R_{534}} + \frac{35 \cdot R_{535}}{3 \cdot 10^6} - 3}{R_{538} + R_{537}}$$

$$B = \frac{\frac{\sqrt{2} \cdot R_{535}}{3 \cdot 10^6}}{R_{538} + R_{537}}$$

$$C = \frac{3}{2 \cdot 10^{10}}$$

Then the formula becomes the simple calculation shown in Equation 7.

$$T_{on}(x) = \frac{C}{A + B * x} \quad (7)$$

To meet the requirements of primary side constant power control ($V_{rms} * T_{on} = K$), $B = 0$ is chosen. At the same time, A and C can be chosen according to the input power.

Figure 3 is a simulation result after the calculation in the 7-W example. The T_{on} time becomes small when the input voltage becomes high. At the same time, the input power must be kept constant.

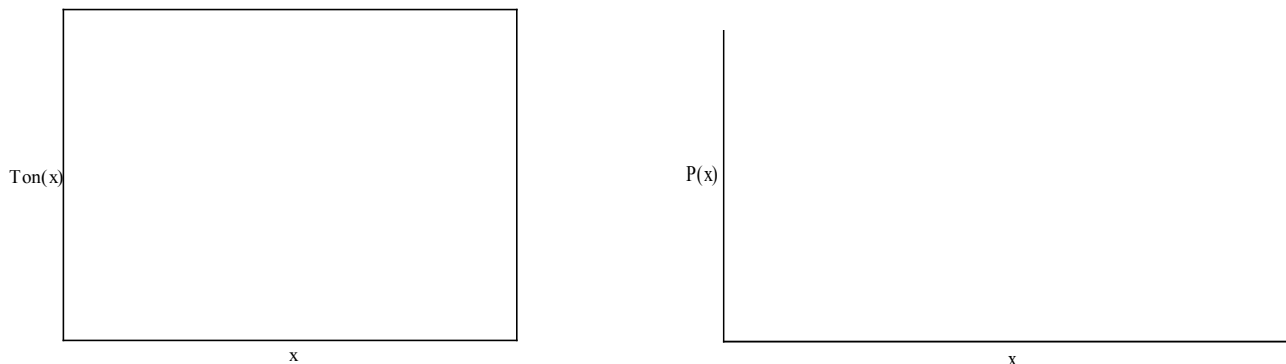


Figure 3. T_{on} Time vs. V_{in_rms} and Input Power vs. V_{in_rms}

3 7-W Off-Line Constant Power LED Lighting Driver Design

3.1 Design Specification

Table 1. Electrical Design Specification

Specification Items	Min	Typical	Max
Input AC voltage	180 V _{ac}	220 A _{ac}	265 V _{ac}
Output current Tolerance	347 mA	356 mA	372 mA
Number of LED		6	
Power Factor	0.975	0.944	0.902
Efficiency without TRIAC dimming	80.90%	81.50%	81.20%

3.2 Schematic

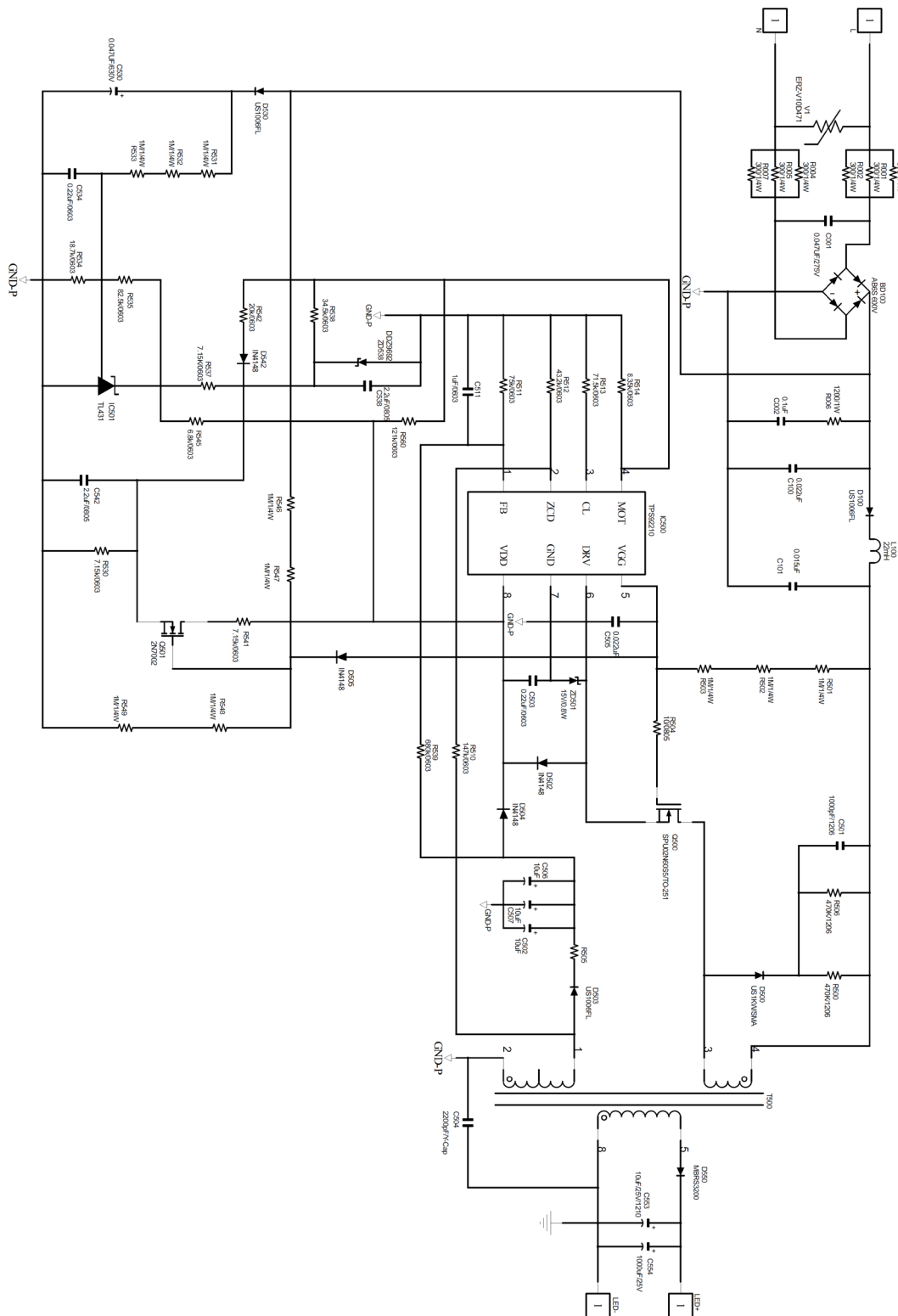


Figure 4. PMP4304A Schematic

3.3 PCB Layout

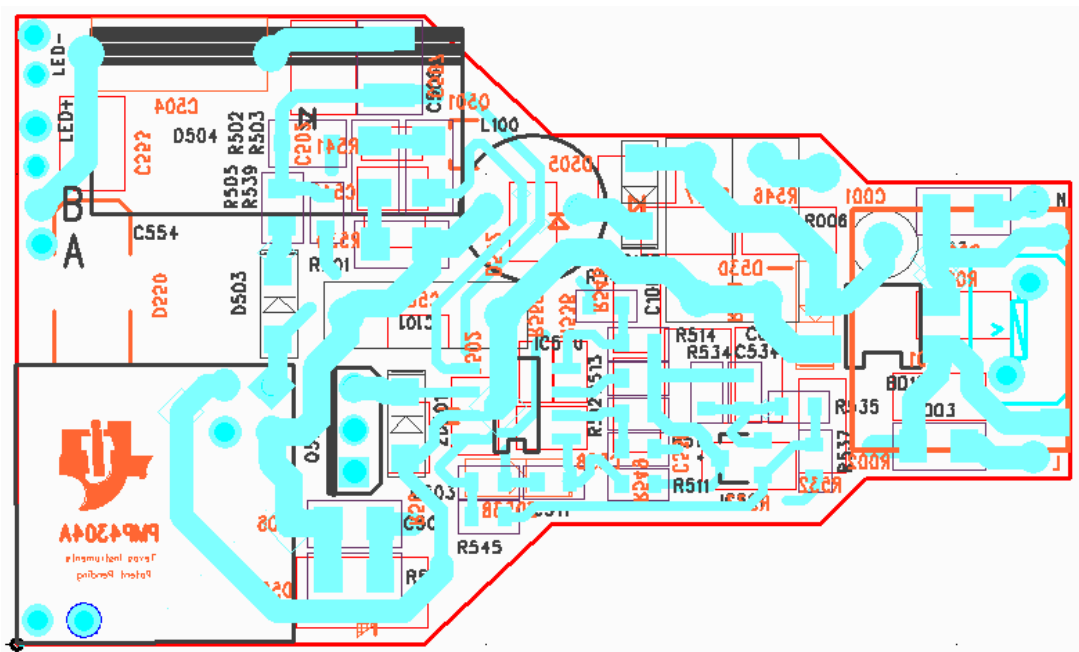


Figure 5. Circuit Board Assembly Drawing — Layer 1

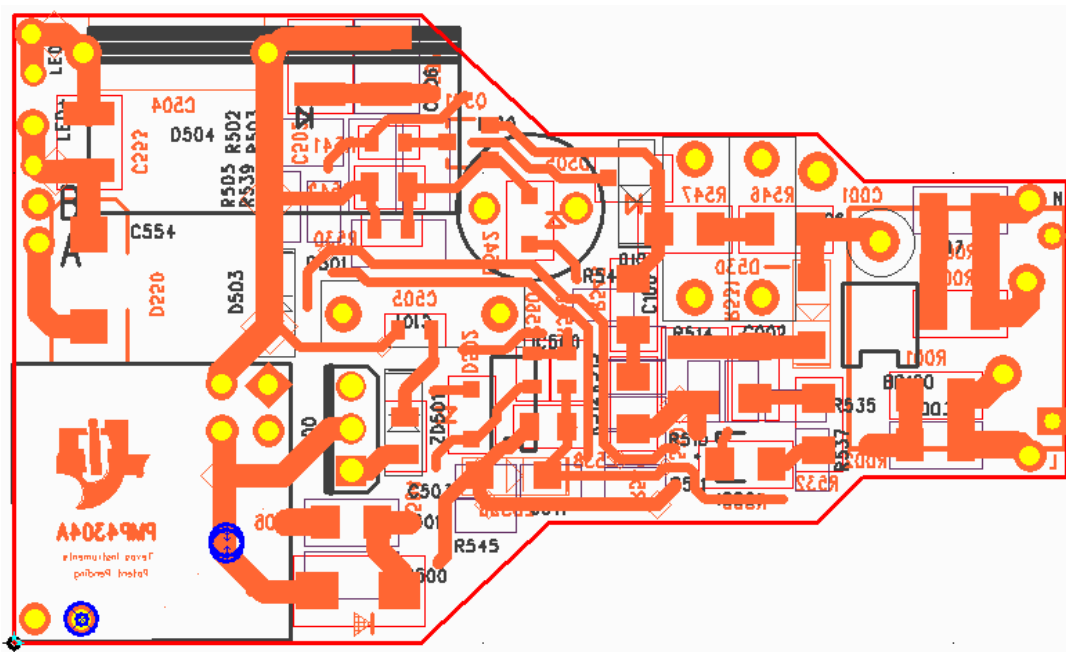


Figure 6. Circuit Board Assembly Drawing — Layer 2

3.4 Efficiency

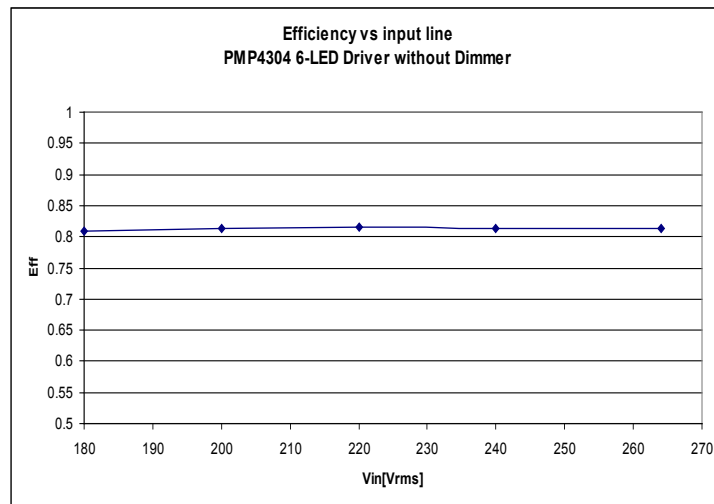


Figure 7. Efficiency vs. Input Voltage

3.5 Line Regulation

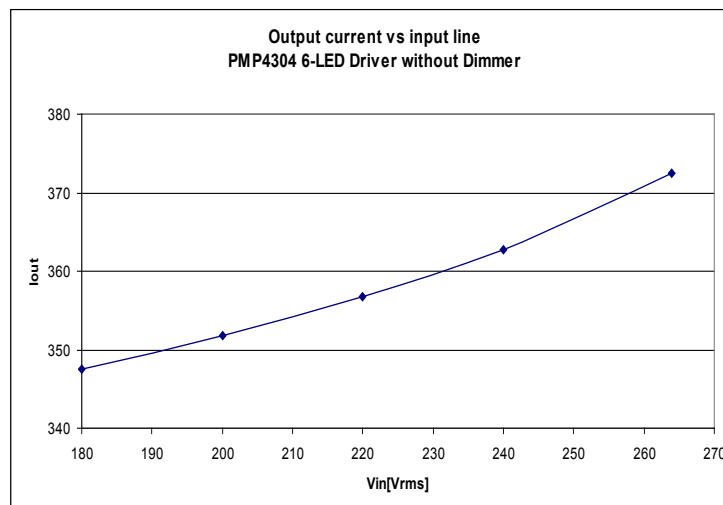


Figure 8. Output Current vs. Input Voltage

3.6 Power Factor

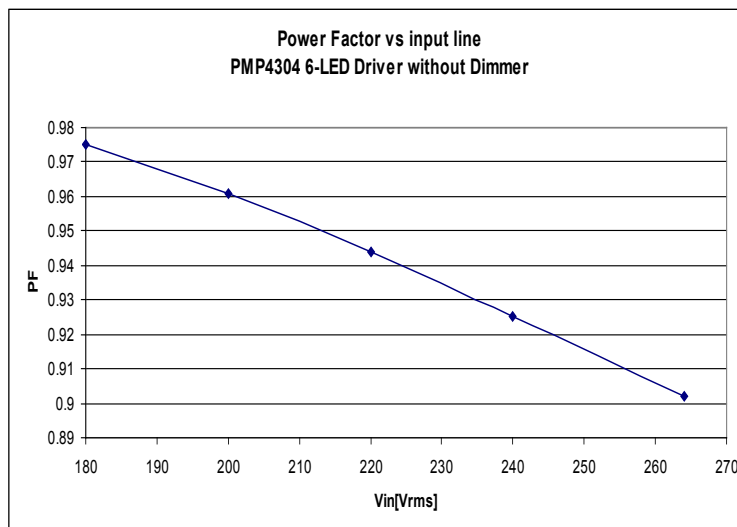


Figure 9. Power Factor vs. Input Voltage

3.7 TRIAC Dimming Performance

Table 2. Output Current with Different Dimmer Conduction Angle

Vin	Io [mA]	T/2 [mS]	Ton [mS]	Angle
220	20	8.333	1.92	41.47366
220	54.79	8.333	2.64	57.02628
220	81.04	8.333	3.24	69.9868
220	107.09	8.333	3.9	84.24337
220	138.8	8.333	4.6	99.36397
220	182.3	8.333	5.2	112.3245
220	236	8.333	5.8	125.285
220	270.71	8.333	6.32	136.5175
220	303.62	8.333	6.8	146.8859
220	333.25	8.333	7.28	157.2543
220	350.66	8.333	7.76	167.6227



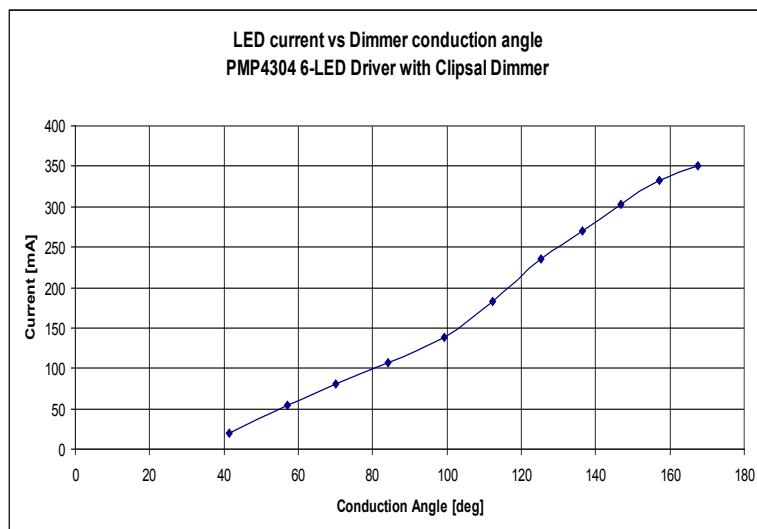


Figure 10. Output Current vs Dimmer Conduction Angle

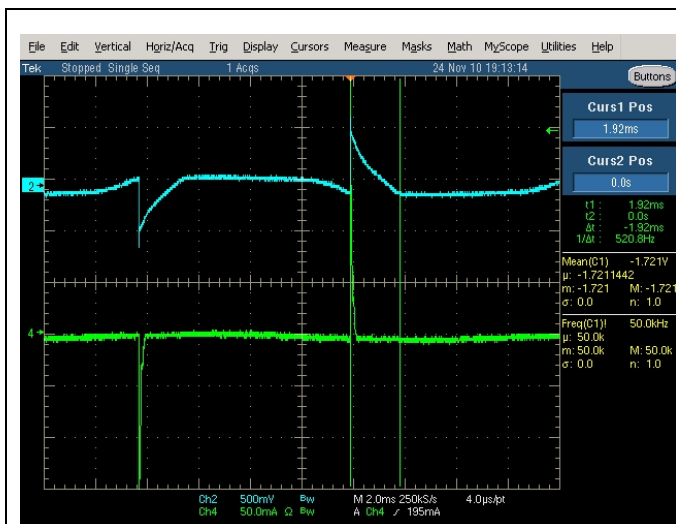


Vin = 220 Vac, Phase = 41.5 deg

Upper: Vin / Lower: Iin

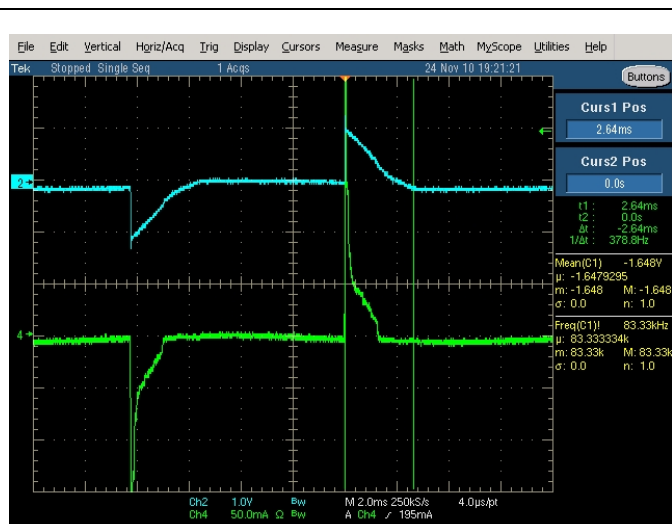


Vin = 220 Vac, Phase = 57 deg

Upper: Vin / Lower: Iin

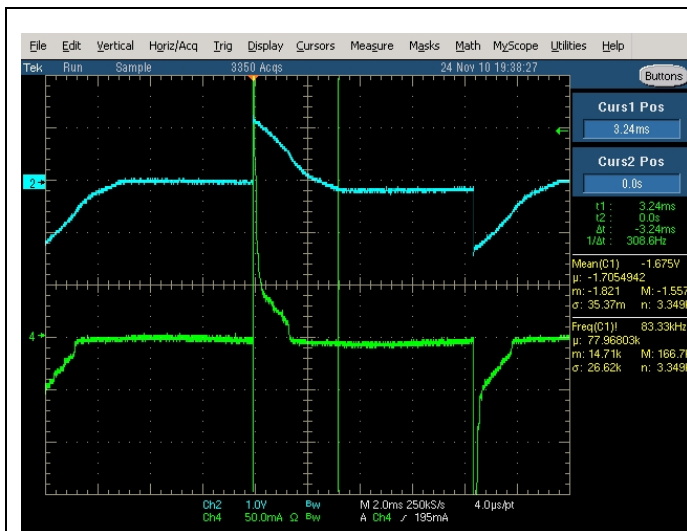


Vin = 220 Vac, Phase = 70 deg

Upper: Vin / Lower: Iin

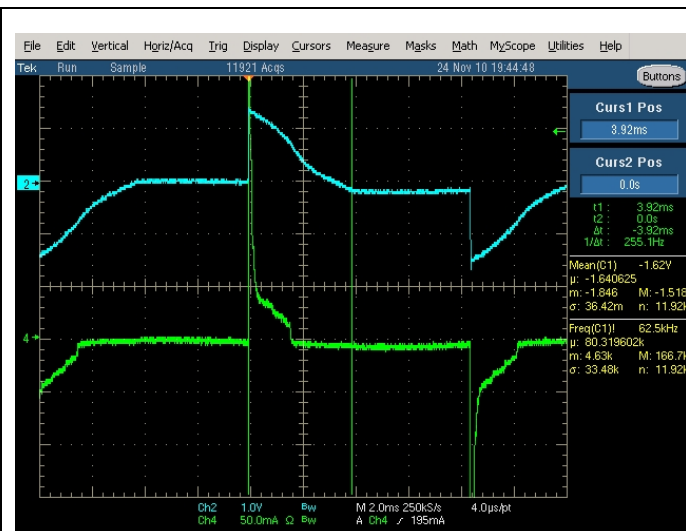


Vin = 220 Vac, Phase = 84 deg

Upper: Vin / Lower: Iin

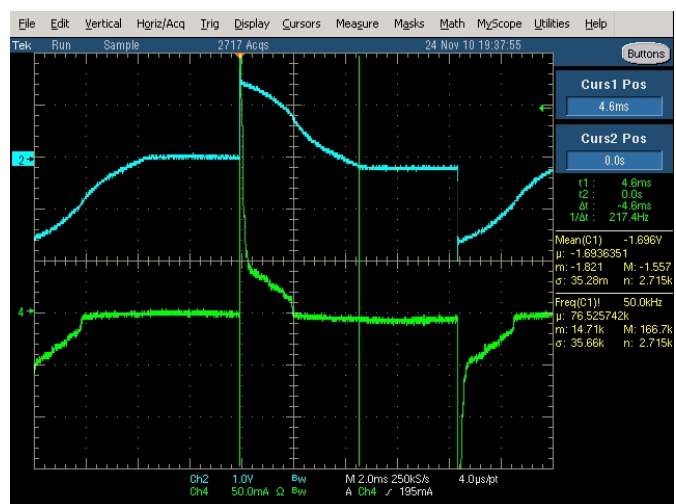


Vin = 220 Vac, Phase = 99 deg

Upper: Vin / Lower: Iin

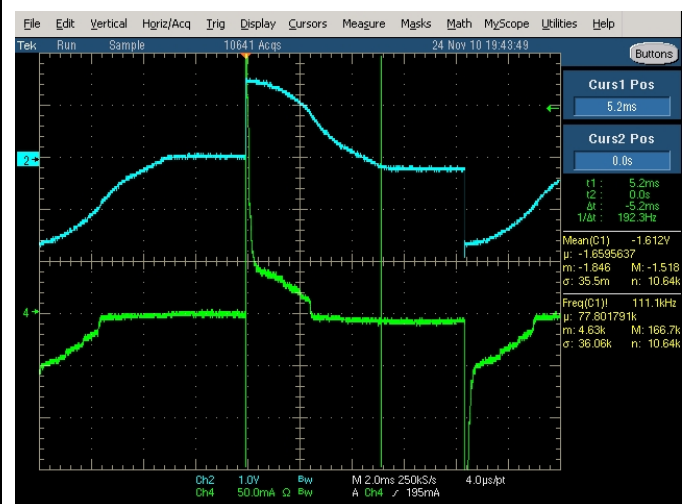


Vin = 220 Vac, Phase = 112 deg

Upper: Vin / Lower: Iin

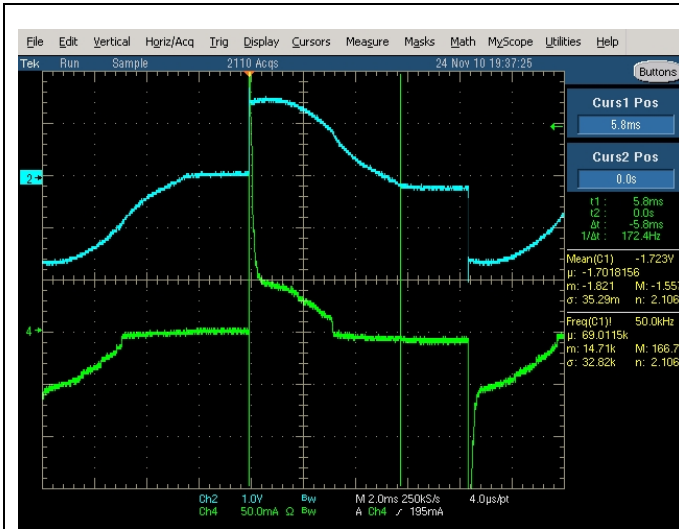


Vin = 220 Vac, Phase = 125 deg

Upper: Vin / Lower: Iin

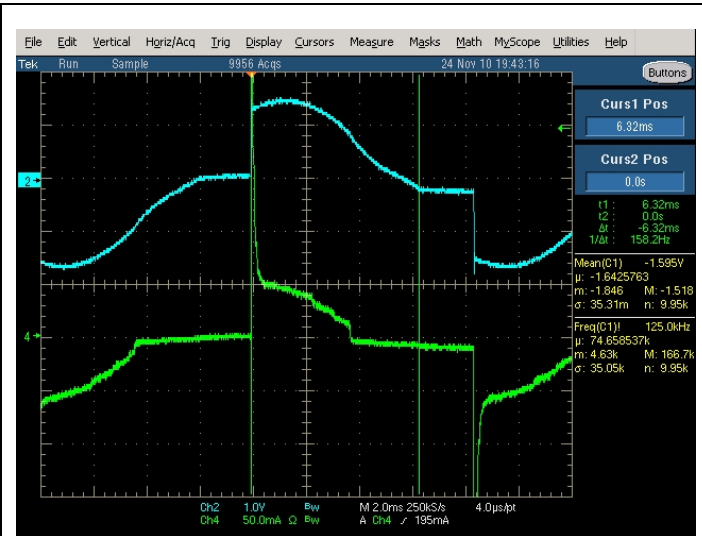


Vin = 220 Vac, Phase = 137 deg

Upper: Vin / Lower: Iin

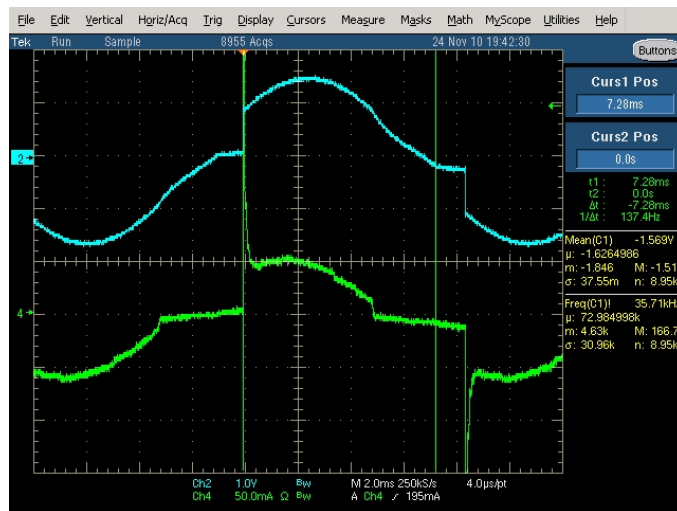

Vin = 220 Vac, Phase = 157 deg

Upper: Vin / Lower: Iin

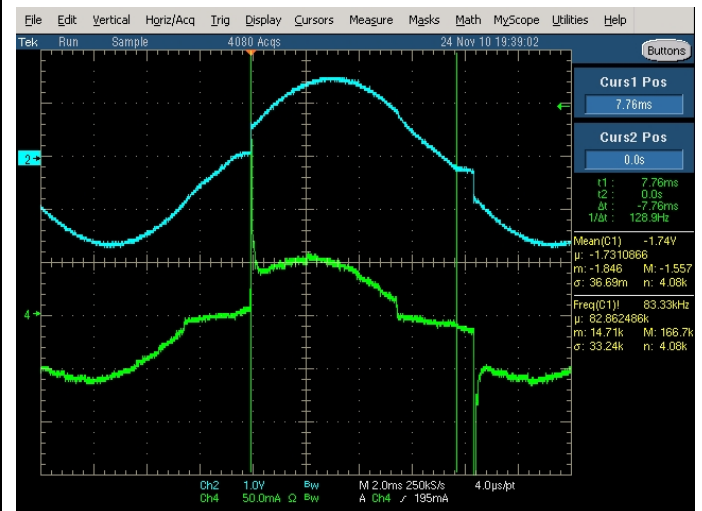

Vin = 220 Vac, Phase = 168 deg

Upper: Vin / Lower: Iin

Figure 11. Input Current vs. Input Voltage at Different Conduction Angle

4 Conclusion

This document shows the analysis of the primary side constant power controlled single stage flyback LED driver, and the benefit of using the primary side control based on the TPS92210. Meanwhile, a practical 7-W design has been implemented. It shows the TPS92210 solution benefits with small form factor, low cost, high PF, and high TRIAC dimming performance.

Reference

1. TPS92210 Datasheet, LED LIGHTING POWER CONTROLLER

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com