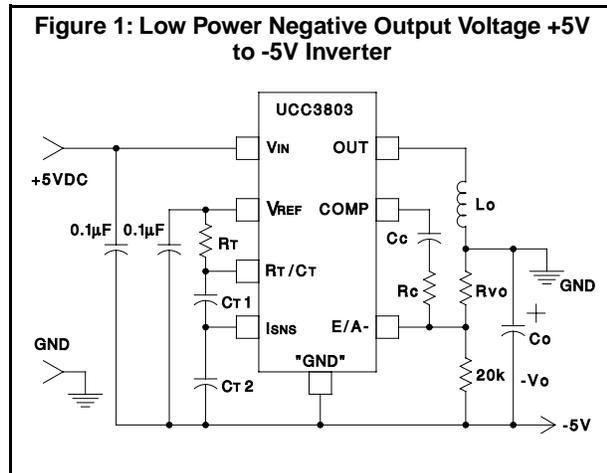


Simple Techniques to Generate a Negative Voltage Bias Supply from a Positive Input Voltage

by Bill Andreycak

Developing a low power negative supply voltage from a positive input supply can be accomplished using some very common PWM control ICs. Typical applications include generating a negative five through twelve volt (-5V to -12V) supply for analog function ICs (OP amps), RS-232 communication circuits, and MOSFET or IGBT gate drives at power levels below a few Watts.

Many PWM ICs contain a high current totem pole output which goes high during the device's ON-time or pulse width. The exact pulse width is modulated to regulate a converter's output voltage during changes in input voltage and output current. The IC's totem pole output can also be used as the main switch in low power applications. One example of this is a Flyback converter configured as shown in Figure 1.



With this arrangement, the inductor (L) charges when the IC output is high and discharges or flies-back when the IC output goes low. Energy stored during the inductors charging time is transferred to the output capacitor (Cout) during the flyback, or OFF portion of the cycle. When a BiCMOS PWM control IC is used, the external diode can be replaced by the MOS channel and body diode of the

IC's lower totem pole transistor thus saving one component. Reverse recovery characteristics are not a concern since current also flows through the MOS transistor channel in parallel with the body diode.

The circuit can be designed for either continuous or discontinuous inductor current operation, depending on the application. Discontinuous mode is generally preferred at lower power levels to minimize inductor size. Continuous inductor current operation is more applicable with higher load currents. High frequency switching and surface mount packaging options minimize overall size.

Conventional duty cycle control (voltage mode) is less complex to implement as the control technique than current mode control. The principal difficulty is sensing the inductor current which is not referenced to the IC's return connection, -Vout instead of ground. Adding a current sense transformer is possible, but will increase cost and complexity. Overcurrent protection is obtained by using the IC's internal maximum current limit at the switch.

Note that the BiCMOS UCC3803 device used in the example circuit of Figure 1. has a maximum low impedance input supply voltage rating of 12VDC. This limits it's applications to less than negative seven volts outputs (-7V max) with a +5V DC input. Higher voltage outputs, for example -12V to -15V, can be obtained by using a UC3843 with a higher maximum input voltage (30VDC). Here too there are some limitations. These fully bipolar ICs draw higher supply current and have higher undervoltage lock-out (UVLO) thresholds, but are acceptable choices for some applications.

The IC datasheet should be referred to for additional information. Application Notes within the IC databook contain general information about the design of the Flyback converter, and others. For further assistance contact a Unitrode Field Application Engineer or the factory.

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF TI PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.