

# Multicell Li-Ion and Li-Polymer Battery Gas-Gauge Application Using the bqJunior™

Bill Jackson

PMP Portable Power

## ABSTRACT


The bqJunior™ series of gas gauges are designed to operate from a single-cell, lithium-ion or lithium-polymer battery. Many applications that could benefit from using these gas gauges use two or more lithium cells in series, where the battery voltage exceeds the operating voltage for the bqJunior™ gas gauges. This application report describes a low-component count solution for using the bq27000, bq27200, or bq27010 with a multicell battery.

## 1 DESIGN APPROACH

A typical approach to a multicell design might be to use a voltage divider across the battery to provide the BAT input to the gas gauge for battery voltage measurement and to use an LDO to provide a regulated Vcc to the gas gauge. The disadvantages of this approach include the additional current drain of the voltage divider and LDO as well as the additional voltage measurement inaccuracy due to the voltage divider resistor tolerance and the loading of the BAT input on the high-impedance voltage divider. An additional design constraint requires keeping the BAT voltage less than or equal to Vcc. For example, if a two-cell, lithium-ion battery is used, the maximum battery voltage may be 8.4 V. A voltage divider of two makes all voltages look like a single cell. The required LDO would need to provide a nonstandard Vcc in the range of 4.2 V to 4.5 V; therefore, an adjustable LDO with external voltage-setting resistors would be needed. However, a design where the BAT voltage can be less than Vcc as the battery is discharged, may cause increased current consumption with some gauges.

The design approach shown in [Figure 1](#) prevents the BAT voltage from exceeding Vcc. A unity-gain operational amplifier is used to buffer the output of a resistive voltage divider and provide a Vcc and BAT voltage that is equal to the voltage divider output. The micro-power operational amplifier generally has a much higher input impedance than the 10-M $\Omega$  impedance of the BAT input and reduces the voltage measurement error due to loading of the voltage divider output. The tolerance of the voltage divider resistors still have a direct impact on the voltage measurement error. The TLV27L1 has a quiescent current of 7  $\mu$ A. Use of a somewhat higher-cost TLV2241 with a quiescent current of 1  $\mu$ A allows implementing a 2-cell design with minimal operating current.

Figure 1 shows RC decoupling of the operational amplifier output to each of the Vcc and BAT inputs. This allows use of appropriate bypass capacitors at the Vcc and BAT inputs, yet does not cause instability of the unity-gain amplifier due to a capacitive load. The BAT input is not tied directly to the Vcc pin to prevent any voltage measurement error due to voltage drop on R3 due to Vcc current.

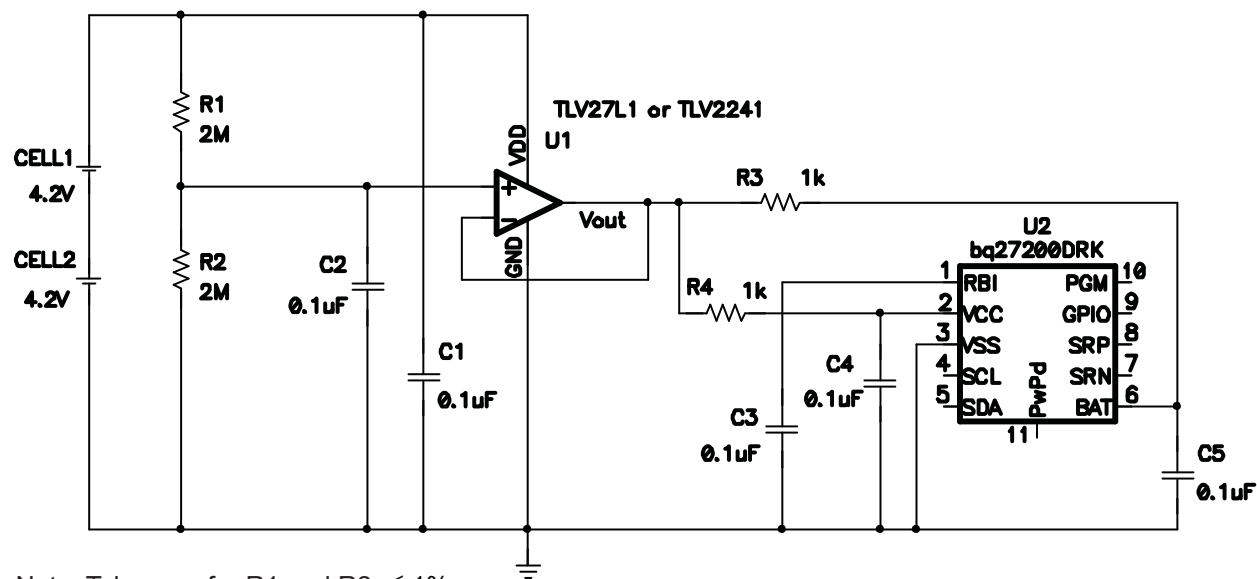

Note: Tolerance for R1 and R2:  $\leq 1\%$

Figure 1. Powering bqJunior™ From an Operational Amplifier

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
		Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
		Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments  
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2006, Texas Instruments Incorporated