

bq20z75/95 Printed-Circuit Board Layout Guide

*Doug Williams**Battery Management*

ABSTRACT

New single-package IC fuel gauges can significantly simplify PCB layout. Attention to layout, however, is critical to the success of any battery management circuit board. The mixture of high-current paths with an ultralow-current microcontroller creates the potential for design issues that can be troublesome. This document presents guidelines that can ensure a stable and well performing project.

Introduction

New single-package integrated circuits (IC) are available that combine the separate fuel gauge and AFE chips into one small package. This configuration can significantly simplify printed-circuit board (PCB) layout, but attention to layout is critical to the success of any battery management circuit board. The mixture of high-current paths with an ultralow-current microcontroller creates the potential for design issues. Careful placement and routing with regard to the principles described in the following discussion can ensure success.

IC Orientation

The orientation of the fuel gauge IC is often driven by the shape of the board. Some pack designs have severe dimensional constraints, such as only allowing for a 10-mm width. This leaves no choice but to mount the bq20z75/95 IC in such a manner that no space is available for decoupling/filter capacitors to be placed next to the IC pins. In that case, adequate decoupling can be provided by mounting the capacitors on the other side of the board, as shown in [Figure 1](#).

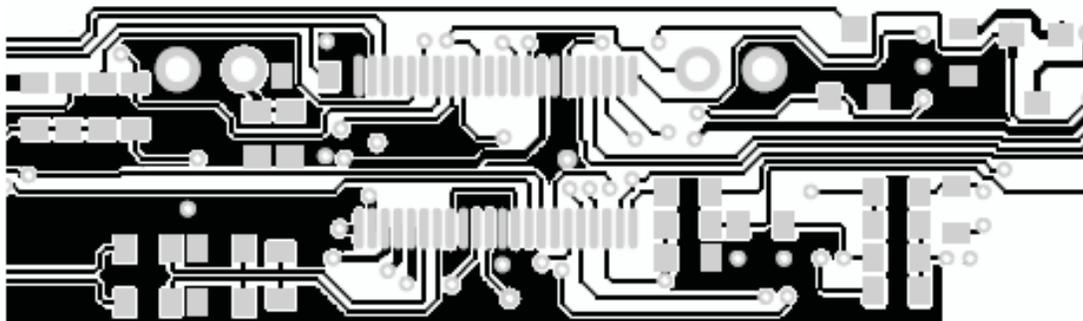


Figure 1. Typical Narrow Board Design Where Most Decoupling/Filter Capacitors Are Located on Other Side.

bq20z75/95 Power Supply Decoupling Capacitor

Fortunately, only one capacitor needs to be extremely close to the IC. The power supply decoupling from REG to VSS is very important for optimal operation of the bq20z75/95 advanced gas gauge. For the bq20z95, this is the 1- μ F ceramic capacitor from pin 32 to pins 31 and 34. Ensure that a heavy copper trace is between pins 31 and 34. For the bq20z75, the capacitor is from REG pin 26 to VSS pins 25 and 28. This is C15 in the reference schematic in [Figure 10](#).

Ground System

To keep the loop area small, place both terminals of this capacitor within 3 mm of the IC, and centered around pin 32 (bq20z95) or pin 26 (bq20z75). Use the shortest possible traces. A large loop area renders the capacitor useless and forms a little loop antenna for noise pickup.

Ground System

The bq20z75/95 requires a low-current ground system separate from the high-current PACK(-) path. Refer to the ground symbols in the bq20z75/95 reference designs, and provide the separate low-current ground system accordingly. It is important that the low-current ground system only connects to PACK(-) at the sense resistor Kelvin pick-off point as shown in Figure 2. The use of an optional inner layer ground plane is recommended, but not required, for the low-current ground system.

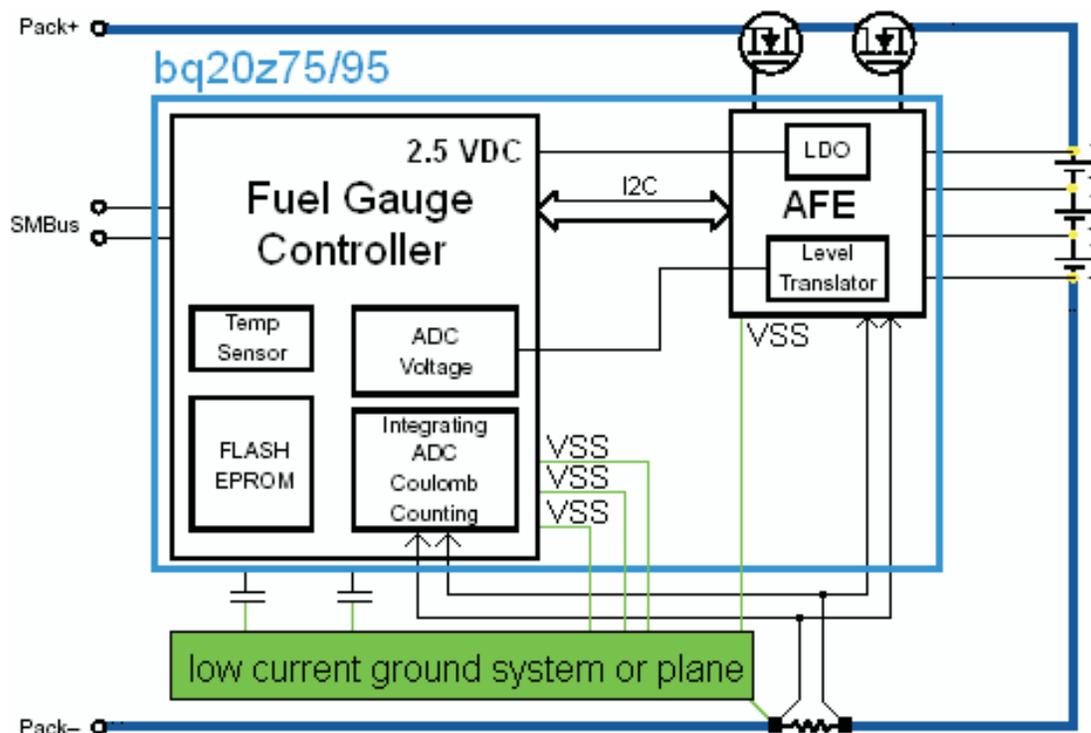


Figure 2. Diagram Showing bq20z75/95 Using Low-Current Ground System for Its Vss Pins and Associated Components

Kevin Connections

Kelvin voltage sensing is extremely important in order to accurately measure current and top and bottom cell voltages. [Figure 3](#) and [Figure 4](#) demonstrate *correct* and *incorrect* techniques, respectively.

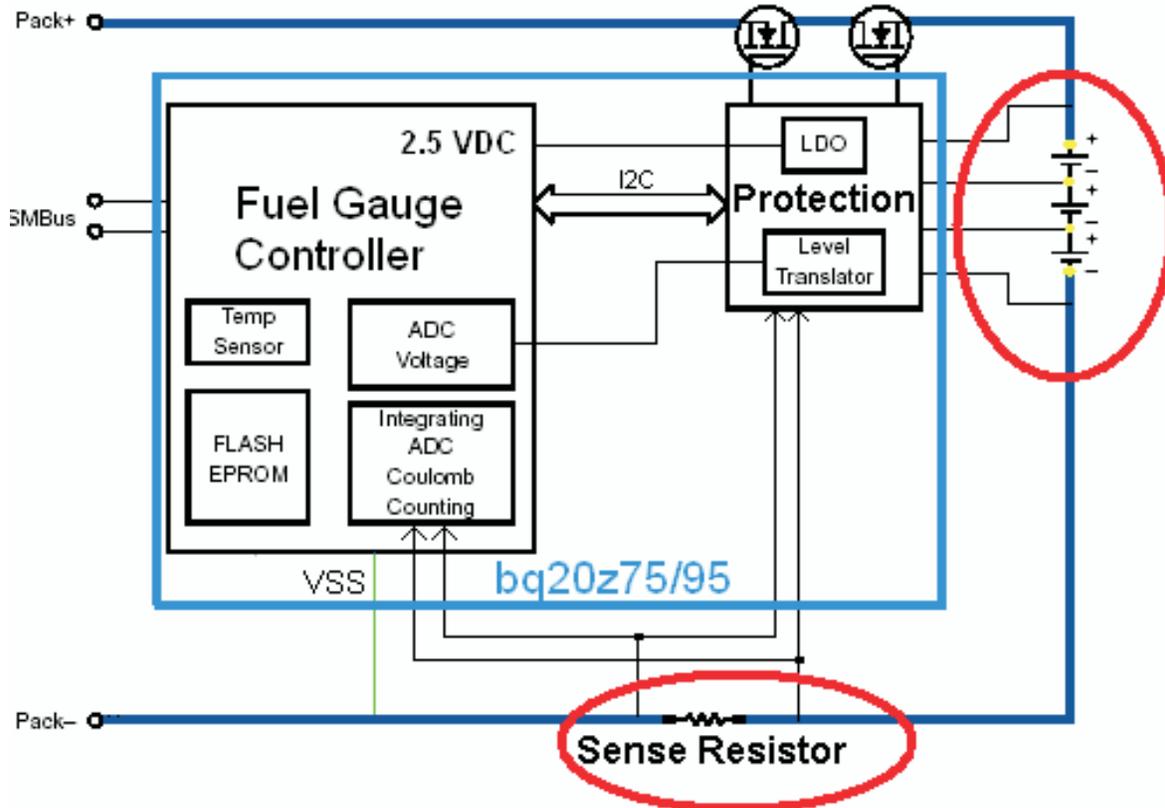


Figure 3. Incorrect Kelvin Voltage Sensing Technique

In [Figure 3](#), sensing through high-current copper traces produces measurement errors.

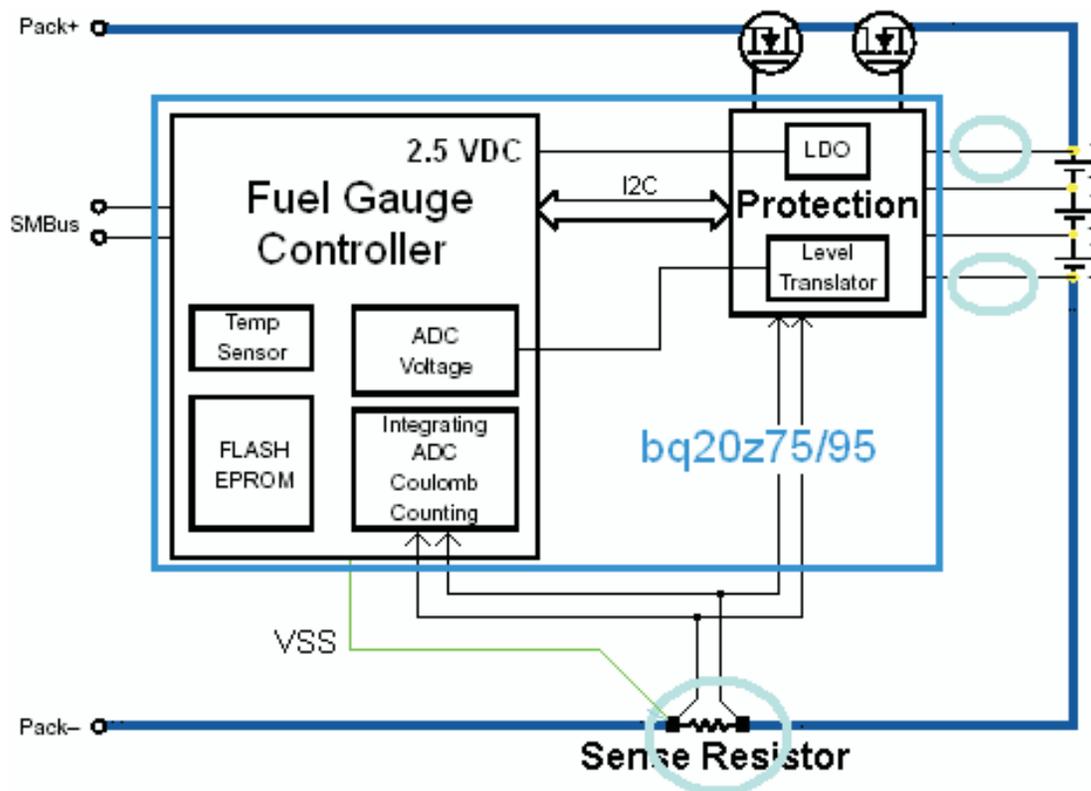


Figure 4. Correct Kelvin Voltage Sensing Technique

As Figure 4 shows, in some cases, the top and bottom cell voltage sensing may be extended out to the cells.

RBI and LED Capacitors

The 3.3-V LEDOUT (pin 8) output requires a 4.7- μ F ceramic capacitor when LEDs are used, but still requires 2.2 μ F capacitance for loop stability when LEDs are not used, as with the bq20z75. This capacitor also should be placed as close to the IC as is practical, but several millimeters of copper trace is not a problem.

Placement of the RBI capacitor is not as critical. It can be placed further away from the IC.

MRST Connection

RESET and MRST are connected to allow the internal AFE to control the gas gauge reset state. The connection between these pins must be as short as possible in order to avoid any incoming noise. The recommended direct interconnection presents no problem. If unwanted resets are found, one or more of the following solutions may be effective:

- Add a 0.1- μ F capacitor between MRST and ground.
- Provide a 1-k Ω pullup resistor to 2.5 V at RESET.
- Surround the entire circuit with a ground pattern.

Normally, these steps are not required. If a test pin is added at MRST, provide it with a 10-k Ω series resistor.

Communication Line Protection Components

The 5.6-V zener diodes, used to protect the communication pins of the bq20z75/95 from ESD, should be located as close to the pack connector as possible. Return the grounded end of these zener diodes to the Pack(-) node, rather than to the low-current digital ground system. In this manner, ESD is diverted away from the sensitive electronics as much as possible.

Protector FET Bypass and Pack Terminal Bypass Capacitors

The general principle is to use wide copper traces to lower the inductance of the bypass capacitor circuits. In [Figure 5](#), an example layout demonstrates this technique.

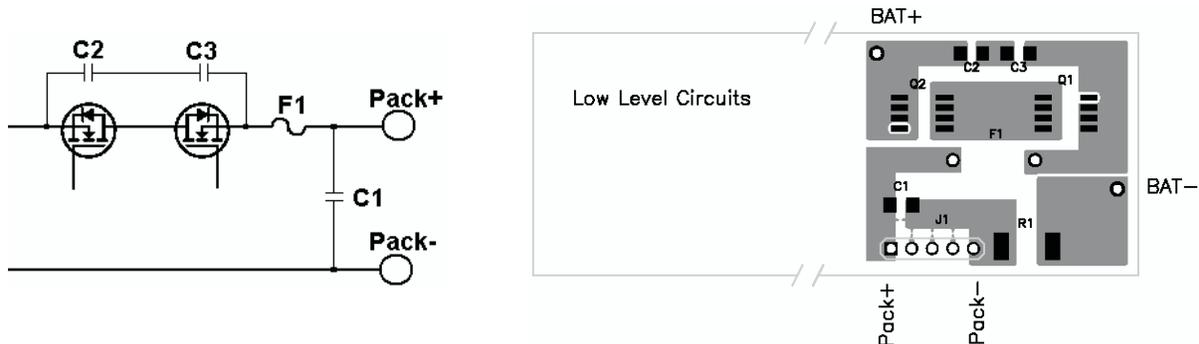


Figure 5. Using Wide Copper Traces Lowers the Inductance of Bypass Capacitors C1, C2, C3

Board Offset Considerations

Although the most important component for board offset reduction is the decoupling capacitor for REG (2.5 V REG), additional benefit is possible by using this recommended pattern for the Coulomb Counter differential low-pass filter network. Maintain the symmetrical placement pattern shown for optimum current offset performance. Use symmetrical shielded differential traces, if possible, from the sense resistor to the 100-Ω resistors as shown in [Figure 6](#). If the current sense leads are long, ensure that the 100-Ω resistors are within 10–15 mm from the IC.

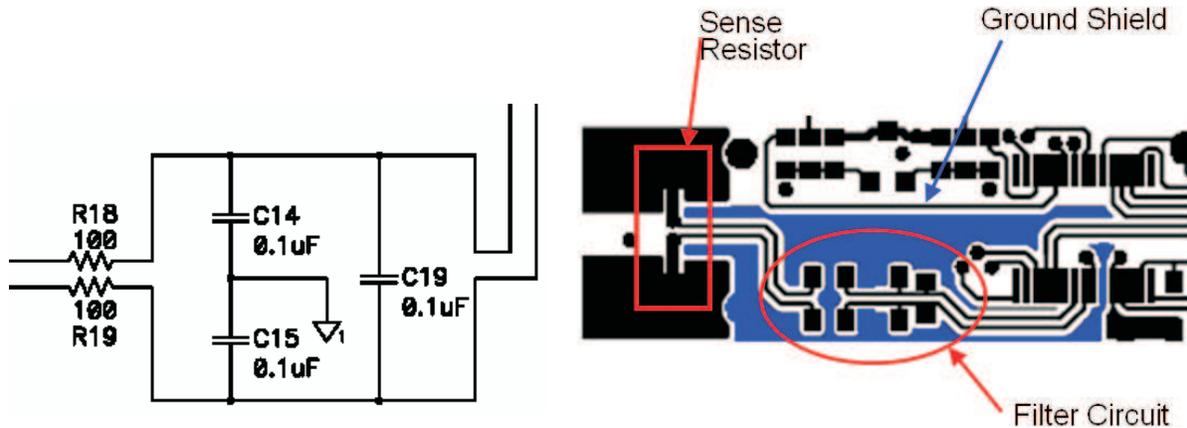


Figure 6. Differential Filter Components With Symmetrical Layout

ESD Spark Gap

Protect SMBus Clock, Data, and other communication lines from ESD with a spark gap at the connector. The pattern shown in [Figure 7](#) is recommended, with 0,2-mm spacing between the points.

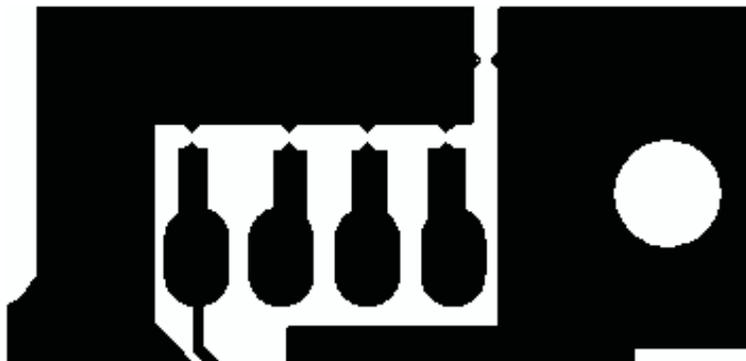


Figure 7. Recommended Spark Gap Pattern Helps Protect Communication Lines From ESD

Radio Frequency Interference

Normally, strong RF signals have no effect on gas gauge performance. However, any silicon structure can rectify RF signals, producing unwanted voltages and currents at critical nodes. In fact, any copper trace or battery connection has a frequency where it becomes an effective half-wave or quarter-wave receiving antenna. For example, the 1900-MHz cell phone band has a quarter wavelength of only 3,9 cm. A 3-watt cell phone, held next to a battery management circuit board, can induce significant errors under the right conditions. Full sweep RF testing for every new design is strongly recommended. Layout modification and/or the use of small bypass capacitors can usually mitigate the problem.

The most vulnerable node on the bq20z75/95 reference design is the SAFE output, which feeds into a signal diode, followed by a FET gate and shunt capacitor. This type of network demodulates an RF signal and can produce enough DC on the gate of the fuse ignition FET to actually ignite the chemical fuse. The solution is to keep the trace from the SAFE output to the diode as short as possible to reduce its effectiveness as an antenna. Alternately, both sides of the trace can be guarded with grounded copper.

Unwanted Magnetic Coupling

A battery fuel gauge circuit board is a challenging environment due to the fundamental incompatibility of high-current traces and ultralow-current semiconductor devices. The best way to protect against unwanted trace-to-trace coupling is with a component placement such as that shown in [Figure 8](#), where the high-current section is on the opposite side of the board from the electronic devices. This is not possible in many situations due to mechanical constraints; nevertheless, every attempt should be made to route high-current traces away from signal traces, which enter the bq20z75/95 directly.

IC voltage references and registers can be disturbed and, in rare cases, damaged due to magnetic and capacitive coupling from the high-current path. Note that during surge current and ESD events, the high-current traces appear inductive and can couple unwanted noise into sensitive nodes of the gas gauge electronics, as illustrated in [Figure 9](#).

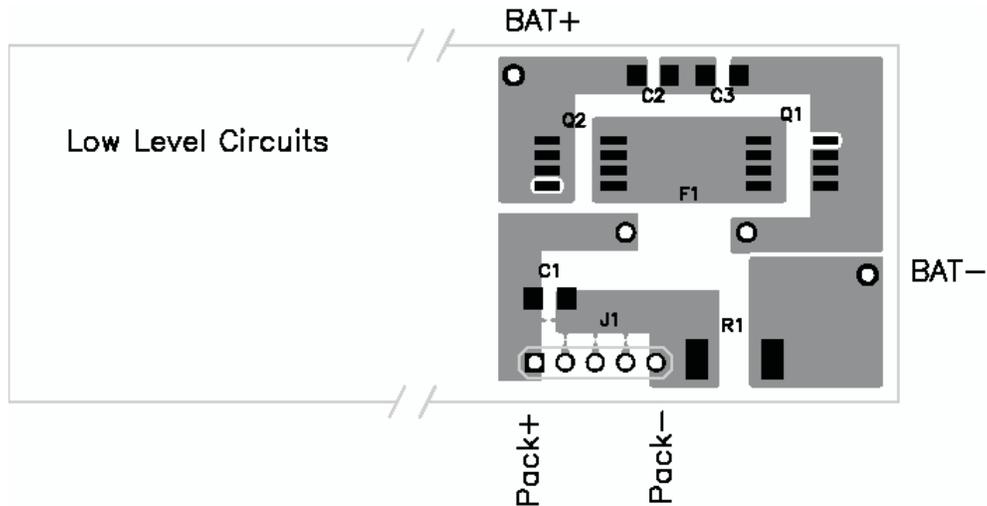


Figure 8. Separating High- and Low-Current Sections Provides an Advantage in Noise Immunity

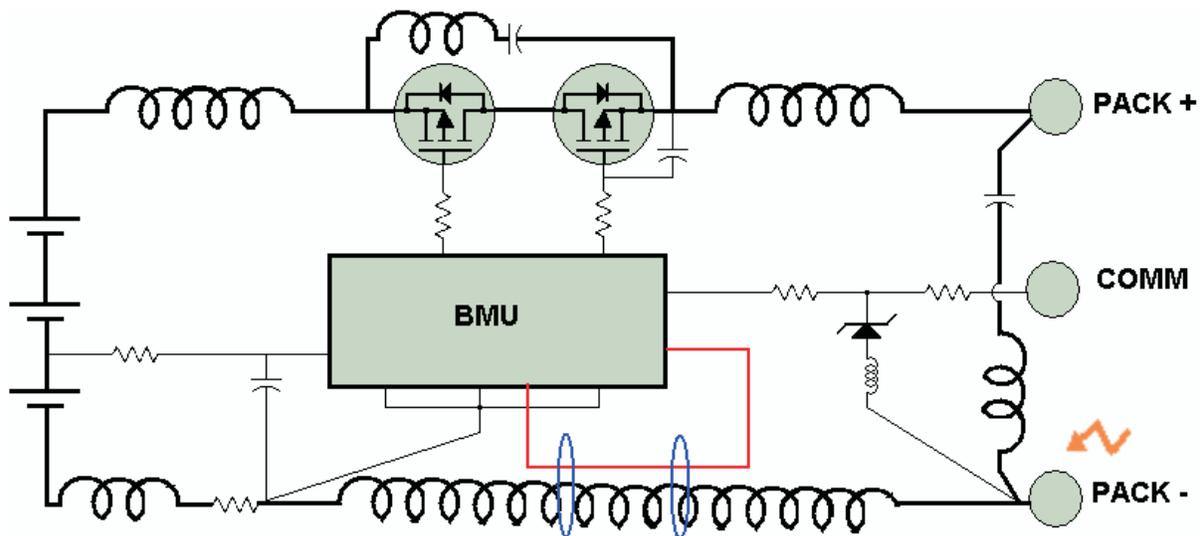


Figure 9. Avoiding Close Spacing Between High-Current and Low-Level Signal Lines

Thermal Considerations

Avoid thermal problems by placing the sense resistor, protection FETS, and high-current traces well away from the ICs.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Telephony	www.ti.com/telephony
Low Power Wireless	www.ti.com/lpw	Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated