

Analysis of Start-Up Performance for UCC28700

Max Han
Power Management/Field Application

ABSTRACT

The UCC28700 device is a primary controlled fly-back power supply controller, which provides both constant voltage and constant current regulation. The device has high resolution for voltage and current regulation, and it has very low no-load power consumption and good start-up performance. As a result, the UCC28700 device is highly suited for low-power adapter and auxiliary power supply application. Compared with other competitors, the UCC28700 device has better performance and needs a smaller V_{DD} capacitor. A customer may experience a situation in which the UCC28700 device cannot start a constant current full load, but can start at resistance full load. The real reason is that the value of the V_{DD} capacitor is not sufficient and primary peak current is designed too small. This paper analyzes the design of primary peak current and V_{DD} capacitor. An experiment result validates the theoretical analysis.

Contents

1. Introduction	2
2. Analysis	2
3. Design	4
4. Experiment	6
5. Conclusion	8
6. References	8

Figures

Figure 1. UCC28700 Application Circuit	2
Figure 2. UCC28700 Secondary Side Circuit	3
Figure 3. Transformer Current	4
Figure 4. UCC28700 Start-up Waveform	6
Figure 5. UCC28700 Start-up Waveform with $C_{DD} = 4.7 \mu\text{F}$, $R_{CS} = 2.05 \Omega$	7
Figure 6. UCC28700 Start-up Waveform with $C_{DD} = 4.7 \mu\text{F}$, $R_{CS} = 1.8 \Omega$	7
Figure 7. UCC28700 Start-up Waveform with $C_{DD} = 1 \mu\text{F}$, $R_{CS} = 1.8 \Omega$	8

Tables

Table 1. Parameters Comparison Table	6
---	----------

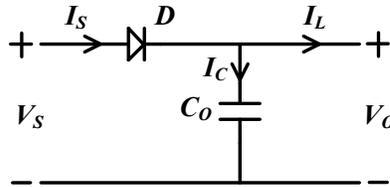


Figure 2. UCC28700 Secondary Side Circuit

To C_{DD} , C_O , and the transformer, the following equations are achieved. In Equation 4, a 1-mA current margin is provided.

NOTE: N_P is primary turns of transformer, N_S is secondary turns, and N_A is auxiliary turns.

$$I_C = I_S - I_L \quad (1)$$

$$V_{OCC} = V_{DD(off)} \frac{N_S}{N_A} \quad (2)$$

$$t_a = C_O \frac{V_{OCC}}{I_C} \quad (3)$$

$$\Delta V_{DD} = \frac{(I_{run} + 1mA)}{C_{DD}} t_a \quad (4)$$

$$V_{DD} = V_{DD(on)} - \Delta V_{DD} \quad (5)$$

Where:

- $V_{DD(off)}$ is UVLO turn-off voltage.
- $V_{DD(on)}$ is UVLO turn-on voltage.
- I_{run} is supply current on the V_{DD} pin when UCC28700 works.
- V_{DD} is the voltage of C_{DD} .
- ΔV_{DD} is the decreased voltage on C_{DD} .
- t_a is the time that output voltage ramps up from 0 to V_{OCC} .

According to the preceding equations, if the value of I_S is low, I_C will be small, so t_a becomes a long time when output voltage ramps up to V_{OCC} ; however, during this period, V_{DD} may decrease below $V_{DD(off)}$ and the UCC28700 device may enter UVLO state and stop switching. Then the current through R_{STR} charges C_{DD} ; when V_{DD} is higher than $V_{DD(on)}$, the device restarts. Although faulty startup continues, the UCC28700 device cannot enter normal state.

In Equation 4, if C_{DD} is large enough, ΔV_{DD} will be small for certain t_a . So, both a large value C_{DD} and a high primary peak current can make the UCC28700 device start well. However, large value C_{DD} means higher price and larger size, and high primary peak current increases power loss and increases transformer size. Consequently, choosing C_{DD} and primary peak current is a trade-off.

In normal operation, auxiliary winding voltage dominates V_{DD} . If V_O reaches its maximum value, V_{DD} will also match its maximum value. The relation is shown in Equation 6.

$$V_{DD\max} = V_{O\max} \frac{N_A}{N_S} \quad (6)$$

From Equation 2, 3, and 6, if N_A increases, t_a is reduced, that's good for UCC28700 starting up. So a large value should be chosen for N_A , and it also must provide voltage margin for V_{DD} .

3. Design

All device values, except C_{DD} and R_{CS} , are the same as the UCC28700EVM-068 5-W USB adapter ^[1] schematic. Figure 3 is shown in the UCC28700 data sheet ^[2]. I_S is deduced as Equation 7, where η_{XFMR} is estimated transformer efficiency.

Transformer efficiency is influenced by the core and winding losses, leakage inductance ratio, and bias power ratio to rated output power. For a 5-V, 1-A charger example, bias power of 1.5% is a good estimate ^[1]. An overall transformer efficiency of 0.9 is an approximate estimate to include 3.5% leakage inductance, 5% core and winding loss, and 1.5% bias power ^[1].

Maximum primary peak current I_{PP} is achieved at the beginning of startup, and the UCC28700 device enters constant current regulation with maintaining constant secondary diode conduction duty cycle, 0.425.

The transformer is WE 750312723 on EVM, $N_P/N_S = 15.33$, $N_P/N_A = 3.83$, and saturation current is 440 mA.

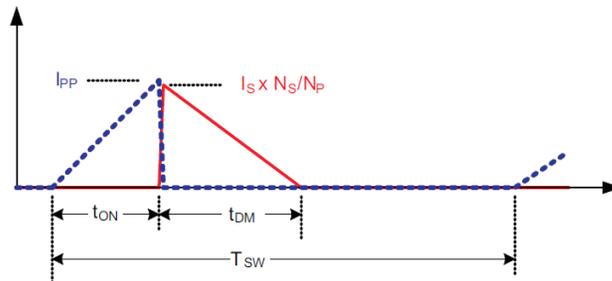


Figure 3. Transformer Current

$$I_S = \frac{I_{PP} N_P t_{DM}}{2 N_S T_{SW}} \eta_{XFMR} \quad (7)$$

At the beginning of startup, average charging current of output capacitor is positive, the charge current equals $(I_S - I_L)$ as Equation 1 shows. Before V_O ramps up to V_{OCC} , the auxiliary turn voltage is lower than V_{DD} , and C_{DD} cannot be charged by auxiliary turns. However, C_{DD} is discharged by I_{run} and gate drive current during this period; if V_{DD} is lower than $V_{DD(off)}$, the UCC28700 device shuts down. To ensure the device starts up well, V_{DD} must be larger than $V_{DD(off)}$ during t_a . In Equations 8 and 9, a critical condition is applied; t_{start} is the time that V_O ramps up from 0 to V_{OCC} . Equation 2 shows the relation of V_{OCC} and $V_{DD(off)}$. An estimated 1 mA of gate-drive current exists in Equation 8 and 1 V of margin is added to V_{DD} . V_{CST} is chip select threshold voltage. At the beginning of startup, voltage on the UCC28700 VS pin is low, so V_{CST} stays at its maximum value.

$$C_{DD} = \frac{t_{start}(I_{run} + 1mA)}{(V_{DD(on)} - V_{DD(off)}) - 1V} \quad (8)$$

$$t_{start} = \frac{C_O V_{OCC}}{I_S - I_L} \quad (9)$$

$$R_{CS} = \frac{V_{CST}}{I_{PP}} \quad (10)$$

In the UCC28700 device, $V_{DD(on)} = 21$ V, $V_{DD(off)} = 8.1$ V, so according to Equation 2, $V_{OCC} = 2.02$ V. $I_{run} = 2.1$ mA in data sheet, C_{DD} is chosen as $4.7 \mu\text{F}$, $t_{start} = 18.04$ ms is deduced by Equation 8. UCC28700 EVM is 5-V, 1-A adapter, so full load current I_L is 1 A. Output capacitors are two paralleled $560\text{-}\mu\text{F}$ capacitors, so $C_O = 1120 \mu\text{F}$. t_{start} , I_L , and C_O are substituted into Equations 7 and 9, I_{PP} is obtained as 383.85 mA. From Equation 10, $R_{CS} = 1.95 \Omega$. To add margin on V_{DD} , 1.8Ω is selected for R_{CS} .

As shown in Table 1, the UCC28700 device has better constant current (CC) regulation performance; a higher max operation frequency, which can minimize the solution size; standby power is less than 30 mW, which is for 5-star rating; and higher max V_{DD} , which can reduce V_{DD} capacitor value. Of the three products highlighted in Table 1, the UCC28700 device is the best choice when designing 5-V adapters. The UCC28700 device can choose higher N_A/N_S because it has higher max V_{DD} according to Equation 2, and smaller t_{start} is achieved (see Equation 9). In Equation 8, t_{start} is proportional to C_{DD} , so smaller C_{DD} is required during design.

Table 1. Parameters Comparison Table

Product Number	UCC28700	OB2520M	iW1680
CV (constant voltage)	5%	5%	null
CC (constant current)	5%	6%	null
Max Operation Frequency	130 kHz	100 kHz	72 kHz
Standby Power	<30 mW	<200 mW	<30 mW
Max V_{DD}	38 V	28 V	25 V

4. Experiment

To validate the preceding analysis, a UCC28700EVM-068 5-W USB adapter is used. All device values are kept the same except C_{DD} and R_{CS} , $C_{DD} = 4.7 \mu\text{F}$, $R_{CS} = 1.8 \Omega$. The load is constant current as 1 A.

Figure 4 is a UCC28700 start-up waveform. CH1 is a MOSFET gate-drive signal and CH3 is output voltage. The device starts up smoothly, with no overshoot and audible noise. The figure shows the UCC28700 device has a very good start-up performance. In Figure 4, t_{start} approximates 18 ms, which meets the calculated result.

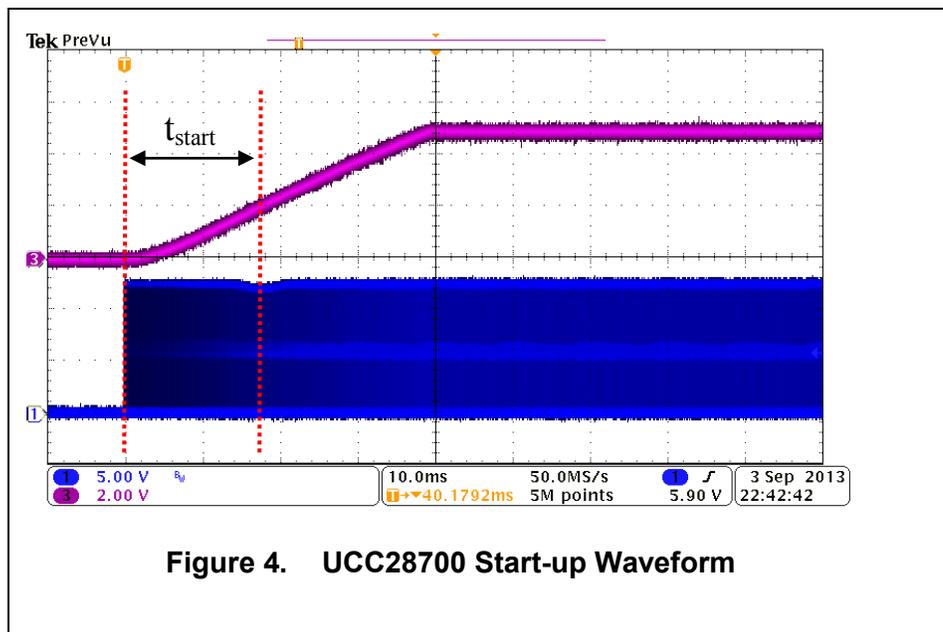


Figure 5, Figure 6, and Figure 7 represent a compared experiment. CH1 is V_{DD} voltage and CH3 is output voltage.

- In Figure 5, $C_{DD} = 4.7 \mu\text{F}$, $R_{CS} = 2.05 \Omega$: because primary peak current is not large enough, V_{DD} decreases below $V_{DD(\text{off})}$, thus the UCC28700 device cannot start.
- In Figure 6, $C_{DD} = 4.7 \mu\text{F}$, $R_{CS} = 1.8 \Omega$: primary peak current is increased, so a good start-up performance is observed.
- In Figure 7, $C_{DD} = 1 \mu\text{F}$, $R_{CS} = 1.8 \Omega$: the UCC28700 device cannot start because C_{DD} is not large enough to provide sufficient energy.

The results of the experiment reveal that both high primary peak current and large volume C_{DD} can make the UCC28700 device start successfully at constant current full load. These findings verify the preceding analysis.

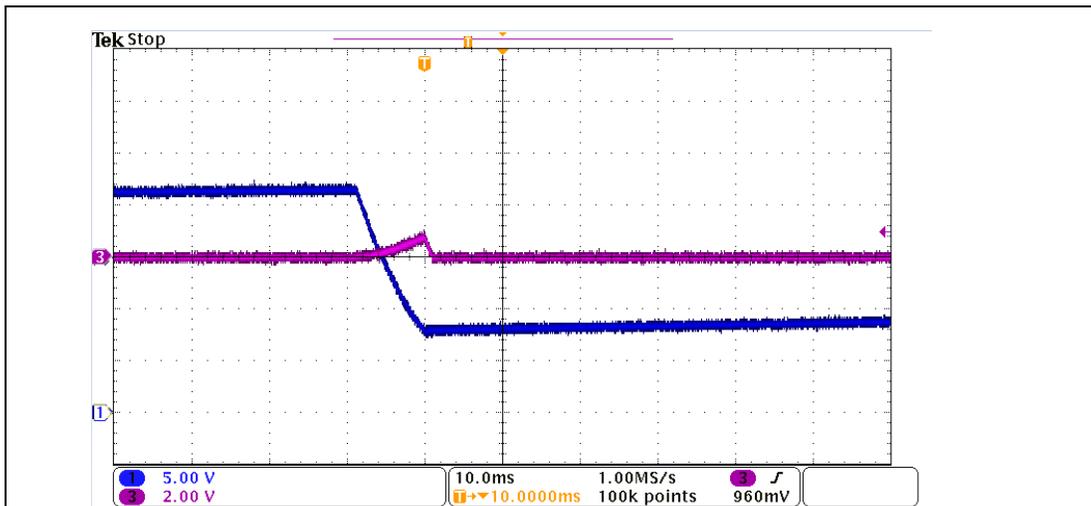


Figure 5. UCC28700 Start-up Waveform with $C_{DD} = 4.7 \mu\text{F}$, $R_{CS} = 2.05 \Omega$


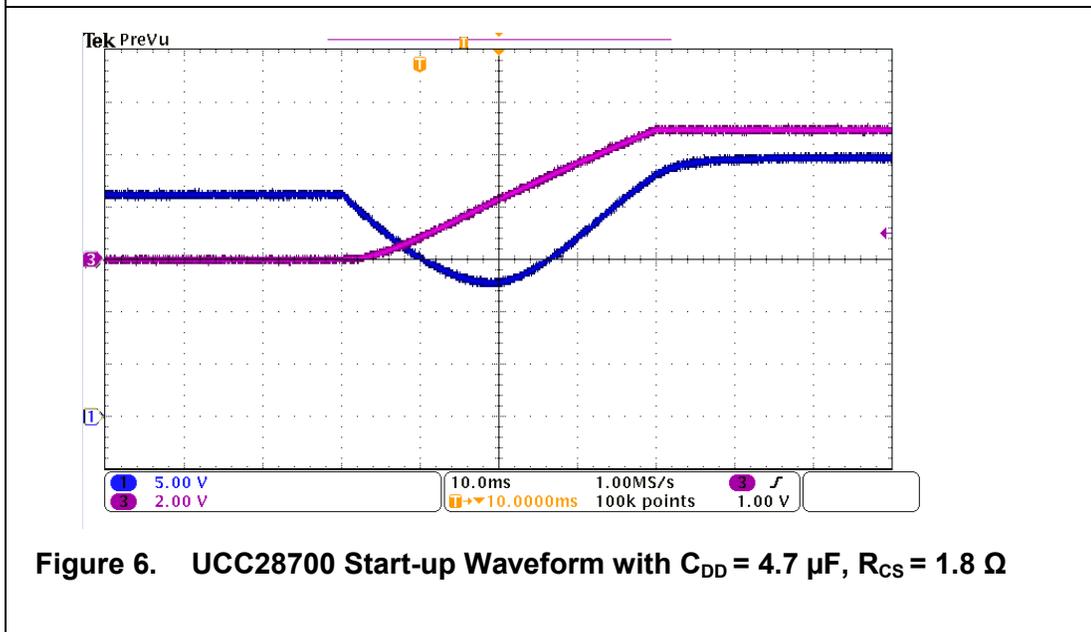


Figure 6. UCC28700 Start-up Waveform with $C_{DD} = 4.7 \mu\text{F}$, $R_{CS} = 1.8 \Omega$

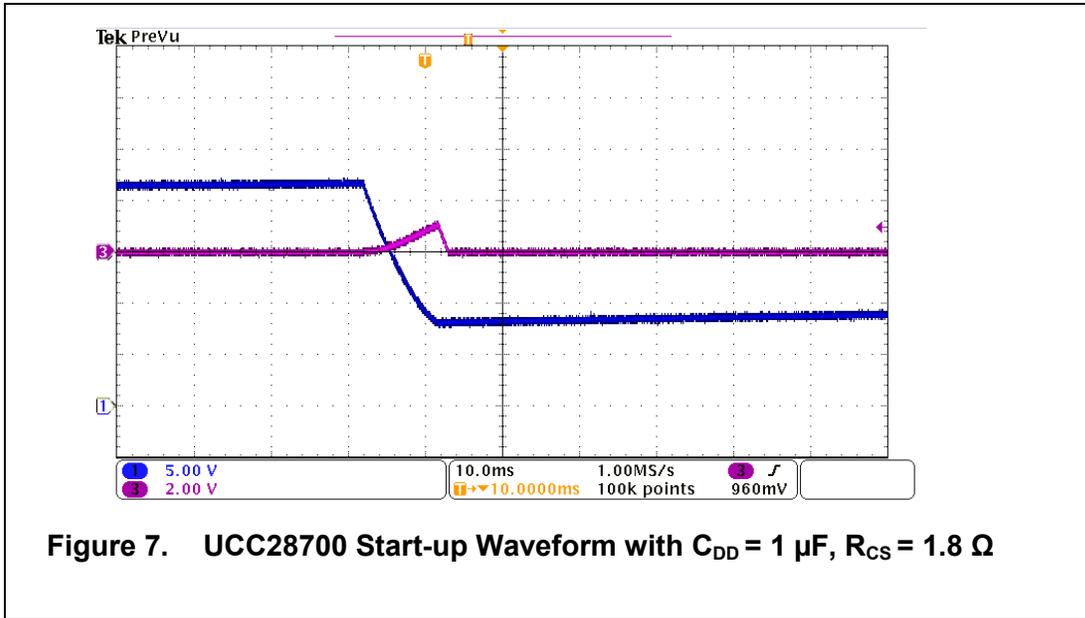

5. Conclusion

Comparison results indicate the UCC28700 device has better performance in CV and CC regulation, solution size, standby power, and V_{DD} capacitor value. In the course of this study, primary peak current and V_{DD} capacitor were analyzed and calculated. Proper parameters were chosen according to equations, and the analysis was verified by experiment results.

6. References

- [1] *UCC28700EVM-068 5-W USB Adapter*. Texas Instruments User's Guide, SLUU968, July 2012
- [2] *Constant-Voltage, Constant-Current Controller With Primary-Side Regulation*. Texas Instruments UCC2870x data sheet, SLUSB41, July 2012

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com