

# **TPS53319 DCAP Mode With Ripple Injection Modeling Design Consideration**

Tony Huang

Power Management/Field Applications

## **ABSTRACT**

TPS53319 is high-current buck converter with DCAP mode. To use all the ceramic output capacitors, the DCAP mode buck converter can be configured with external ripple injection. This paper discusses a novel small-signal model and loop frequency response analysis. An example is implemented to verify the modeling and compensation.

## **Contents**

<b>1</b>	<b>TPS53319 Introduction .....</b>	<b>1</b>
<b>2</b>	<b>DCAP Mode Small-Signal Circuitry.....</b>	<b>2</b>
<b>3</b>	<b>DCAP Model Buck Converter Modeling Analysis .....</b>	<b>3</b>
<b>4</b>	<b>TPS53319 Design Example.....</b>	<b>7</b>
<b>5</b>	<b>Conclusion .....</b>	<b>8</b>
<b>6</b>	<b>References.....</b>	<b>8</b>

## **Figures**

<b>Figure 1.</b>	<b>TPS53319 Internal Block Diagram.....</b>	<b>2</b>
<b>Figure 2.</b>	<b>Control Block Diagram for COT Mode Buck Converter .....</b>	<b>3</b>
<b>Figure 3.</b>	<b>DCAP Mode Buck Converter .....</b>	<b>3</b>
<b>Figure 4.</b>	<b>Equivalent Control Circuitry .....</b>	<b>4</b>
<b>Figure 5.</b>	<b>Small-Signal Implementation From Control to Output.....</b>	<b>6</b>
<b>Figure 6.</b>	<b>TPS53319 Buck Converter With 5.0-V, 10-A Output.....</b>	<b>7</b>
<b>Figure 7.</b>	<b>Simulation Results With the Bode Plot Based on the Modeling .....</b>	<b>8</b>

## **1 TPS53319 Introduction**

TPS53319 is a 14-A synchronous switcher with DCAP mode and integrated MOSFETs. The device is designed for ease of use, low external component count, and space-conscious power systems. These devices feature accurate 1%, 0.6-V reference, and integrated boost switch. A sample of competitive features include: a conversion input voltage range of 1.5 V wide to 22 V wide, very low external component count, DCAP mode control for superfast transient, auto-skip mode operation, internal soft-start control, selectable frequency, and no need for compensation. The conversion input voltage range is 1.5 to 22 V, the supply voltage range is 4.5 V to 25 V, and the output voltage range is 0.6 V to 5.5 V, as shown in Figure.1.

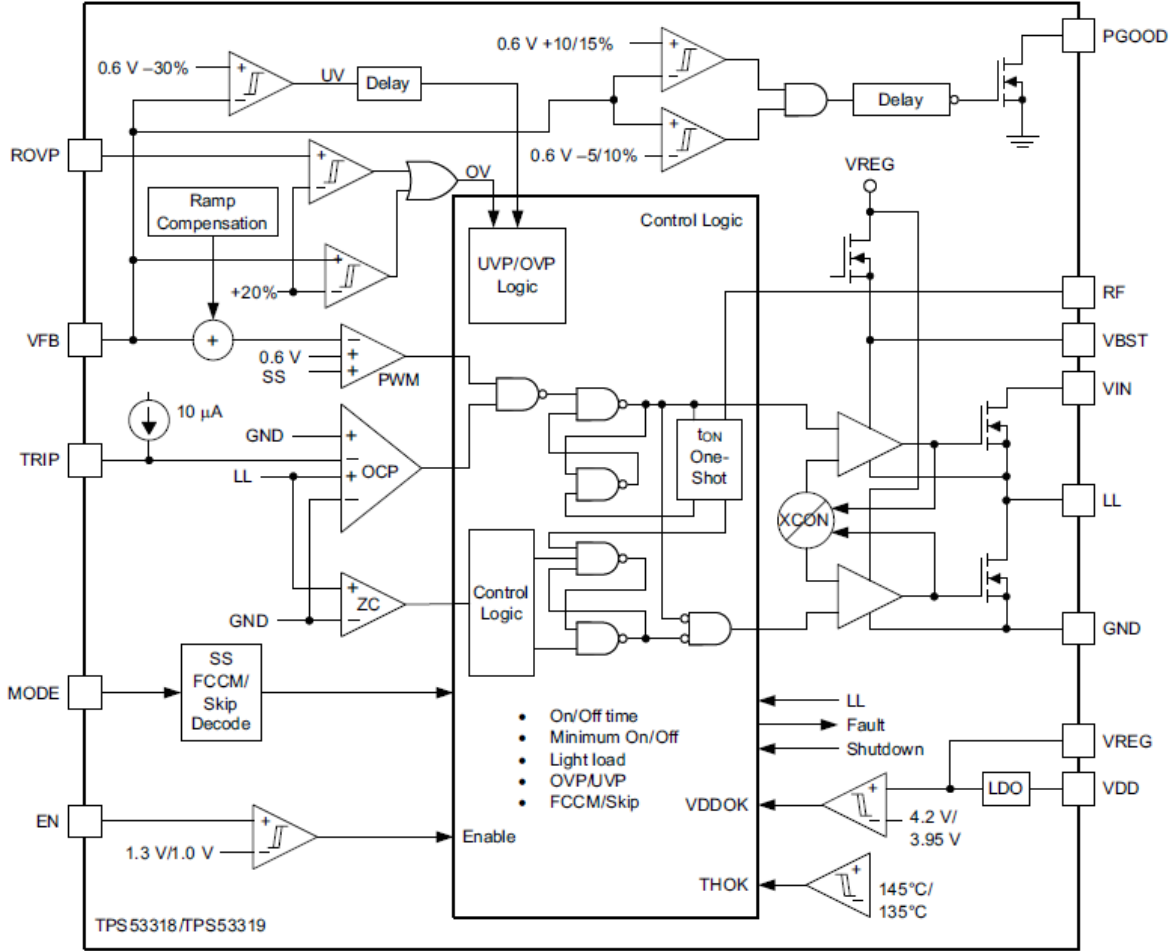


Figure 1. TPS53319 Internal Block Diagram

## 2 DCAP Mode Small-Signal Circuitry

For a Buck converter with constant on time control mode, a sampling function as below can be introduced to describe the function of constant on time sampling-hold control.

$$H_e(s) = \frac{1 - e^{-s \times t_{on}}}{s \times t_{on}} \approx \frac{1}{1 + \frac{s}{2/t_{on}} + \frac{s^2}{\pi^2/t_{on}^2}} ; \tag{1}$$

Define:

$$G_a(s) = \frac{1}{sR_1C_1} ; G_b(s) = \frac{(s^2R_1R_2C_1C_2 + sR_1C_1 + sR_2C_2 + 1)}{s^2R_1R_2C_1C_2} \tag{2}$$

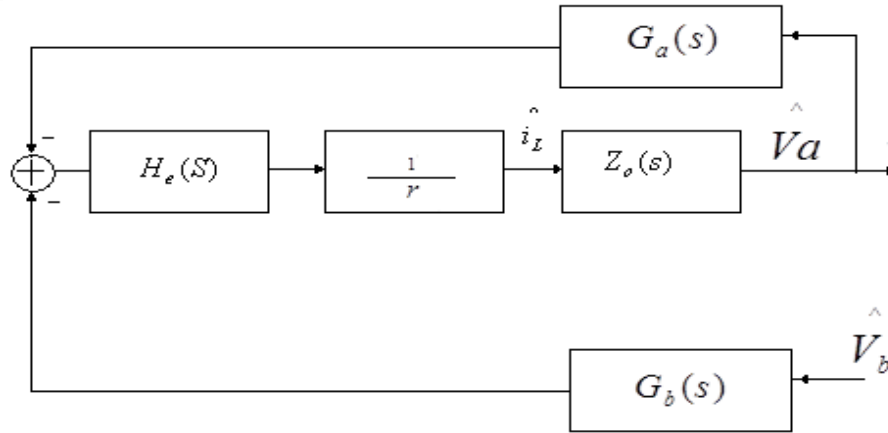


Figure 2. Control Block Diagram for COT Mode Buck Converter

### 3 DCAP Model Buck Converter Modeling Analysis

Figure 3 shows circuitry for a DCAP mode converter. Figure 4 shows equivalent control circuitry.

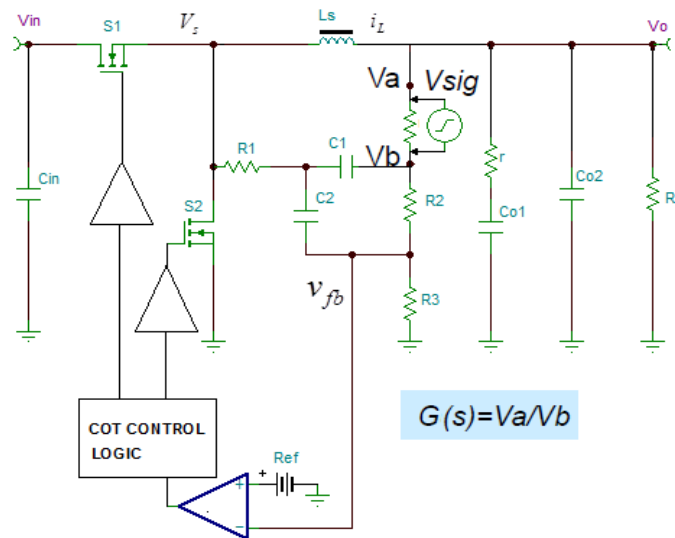


Figure 3. DCAP Mode Buck Converter

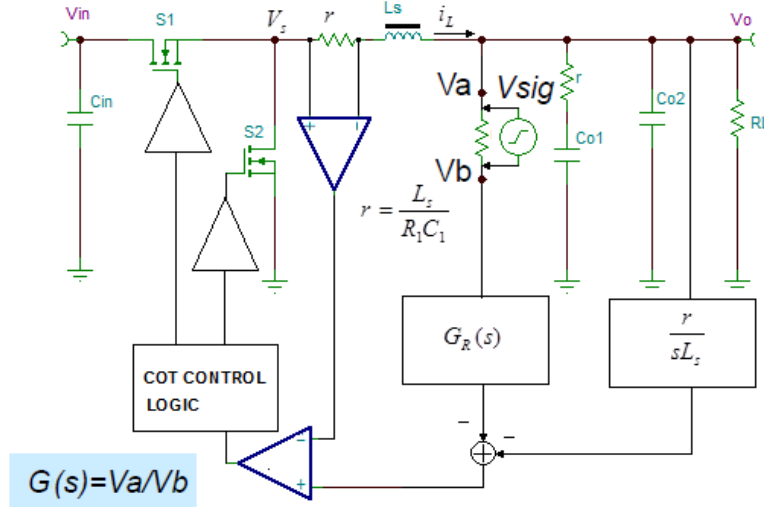


Figure 4. Equivalent Control Circuitry

$$G_2(s) = \frac{(1 + sR_1C_1)(1 + \frac{R_2}{R_3} + sR_2C_2) + sR_1C_2(1 + \frac{R_2}{R_3})}{sR_2C_2} \quad (3)$$

$$G_1(s) = \frac{s^2R_1R_2C_1C_2 + s(R_1C_1 + R_1C_2) + 1}{(1 + sR_1C_1)(1 + \frac{R_2}{R_3} + sR_2C_2) + sR_1C_2(1 + \frac{R_2}{R_3})} \quad (4)$$

Then:

$$\frac{\langle V_s \rangle - \langle V_o \rangle + \langle V_o \rangle + \langle V_b \rangle G_1(s)G_2(s)}{G_2(s)} = \langle V_{fb} \rangle \quad (5)$$

Considering:

$$\langle V_s \rangle - \langle V_o \rangle = sL_s \langle i_L \rangle, \quad (6)$$

Meanwhile, defining:

$$r = \frac{L_s}{R_1C_1} \quad (7)$$

Then:

$$\left[ \frac{\langle i_L \rangle r + \langle V_o \rangle \frac{r}{sL_s} + \langle V_b \rangle \frac{G_1(s)G_2(s)}{sR_1C_1}}{G_2(s)} \right] sR_1C_1 = \langle V_{fb} \rangle \quad (8)$$

With small-signal transaction, then:

$$r \hat{i}_L + \hat{V}_o \frac{r}{sL_s} + \hat{V}_b \frac{G_1(s)G_2(s)}{sR_1C_1} = 0 \quad (9)$$

And define:

$$Z_o(s) = Z_c(s) = \frac{R_L(1 + sEsrC_{o1})}{(1 + sR_L(C_{o1} + C_{o2}))} \quad (10)$$

Considering the COT control with sampling-hold function  $H_e(s)$ , the loop gain can be described as shown in Equations 11 through 13.

$$\begin{aligned} G(s) &= -\frac{[G_1(s)G_2(s)]}{srR_1C_1} \frac{H_e(s)}{\left[1 + \frac{H_e(s)}{sL_s}\right]} Z_o(s) \\ &= -\frac{(s^2R_1R_2C_1C_2 + sR_1(C_1 + C_2) + 1)}{s^2R_1R_2C_1C_2} \frac{H_e(s)}{\left[1 + \frac{H_e(s)}{sL_s}\right]} \frac{R_L(1 + sEsrC_{o1})}{r(1 + sR_L(C_{o1} + C_{o2}))} \end{aligned} \quad (11)$$

$$G(s) = -\frac{\left(\frac{s^2}{\omega_a^2} + \frac{s}{\omega_a Q_a} + 1\right)}{\frac{s^2}{\omega_a^2}} \frac{H_e(s)}{\left[1 + \frac{H_e(s)}{sL_s}\right]} \frac{R_L(1 + sEsrC_{o1})}{r[1 + sR_L(C_{o1} + C_{o2})]} \quad (12)$$

$$\omega_a = \frac{1}{\sqrt{R_1R_2C_1C_2}}; Q_a = \frac{\sqrt{R_1R_2C_1C_2}}{R_1(C_1 + C_2)} \quad (13)$$


From this previous analysis, it is critical that we can use the COT current mode to simulate the loop function. We can define the following parameters:

$$L_a = L_s; C_a = \frac{t_{on}^2}{\pi^2 L_s}; R_a = \frac{2L_s}{t_{on}} \quad (14)$$

$$L_c = R_1R_2C_2; R_c = R_1\left(1 + \frac{C_2}{C_1}\right) \quad (15)$$

$$G_m = \frac{1}{r}; G_a = G_c = G_{v1} = 1 \quad (16)$$

With the previous definition, Figure 5 shows a small-signal circuitry implementation:

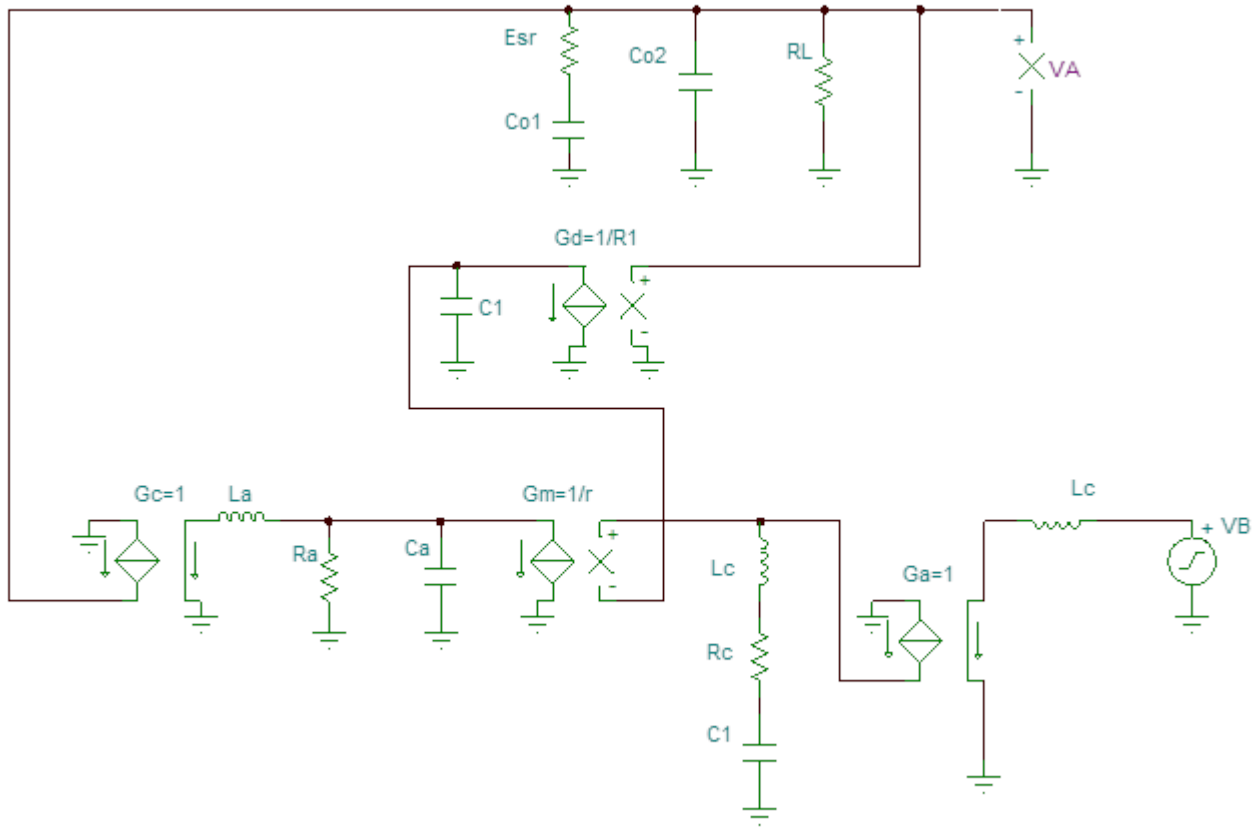

**Figure 5. Small-Signal Implementation From Control to Output**

For the COT mode with ripple injection, according to Routh Criterion, the related stability criteria as in Equation 17:

$$\frac{R_1 R_2 C_1 C_2}{R_1 (C_1 + C_2) + R_2 C_2} > \frac{L_s}{R_1 C_1} C_{out} > \frac{T_{on}}{2} \tag{17}$$

The simplified criteria as in Equation 18:

$$C_2 < C_1; R_2 > R_1; f_{sw} > \frac{1}{2\pi\sqrt{L_s C_{out}}} > \frac{1}{2\pi R_2 C_2}; \frac{L_s C_{out}}{R_1 C_1} > \frac{T_{on}}{2} \tag{18}$$

Defining the gain function of the ripple injection circuitry:

$$G_R(s) = -\frac{(s^2 R_1 R_2 C_1 C_2 + s R_1 (C_1 + C_2) + 1)}{s^2 R_1 R_2 C_1 C_2} = -\frac{\frac{s^2}{\omega_a^2} + \frac{s}{\omega_a Q_a} + 1}{\frac{s^2}{\omega_a^2}} \tag{19}$$

Therefore, the closed-loop gain function as in Equation 20:

$$G(s) = G_R(s) \frac{H_e(s)}{\left[1 + \frac{H_e(s)}{sL_s}\right]} \frac{R_L(1 + sEsrC_{o1})}{r(1 + sR_L(C_{o1} + C_{o2}))} \quad (20)$$

The closed-loop gain and phase have the following additional impact:


$$|G_R(j2\pi f_c)| \approx \frac{\omega_a}{2\pi f_c Q_a}; \quad PhaseDelay \approx -A \tan\left(\frac{\omega_a}{2\pi f_c Q_a}\right) \quad (21)$$

Then, without loading and ignoring the Esr resistor, the crossover frequency and phase margin can be approximately deduced as follows:

$$f_c \approx \frac{\sqrt{\frac{\omega_a}{rQ_a C_{out}}}}{2\pi}; \quad PhaseMargin \approx 90^\circ - A \tan\left(\frac{\omega_a}{2\pi f_c Q_a}\right) \quad (22)$$


### 4 TPS53319 Design Example

Based on the COT buck converter schematic design (see Figure 6), using the small-signal analysis, we can get the overall simulation model according to Figure 5. Figure 7 shows the simulated Bode plot results.

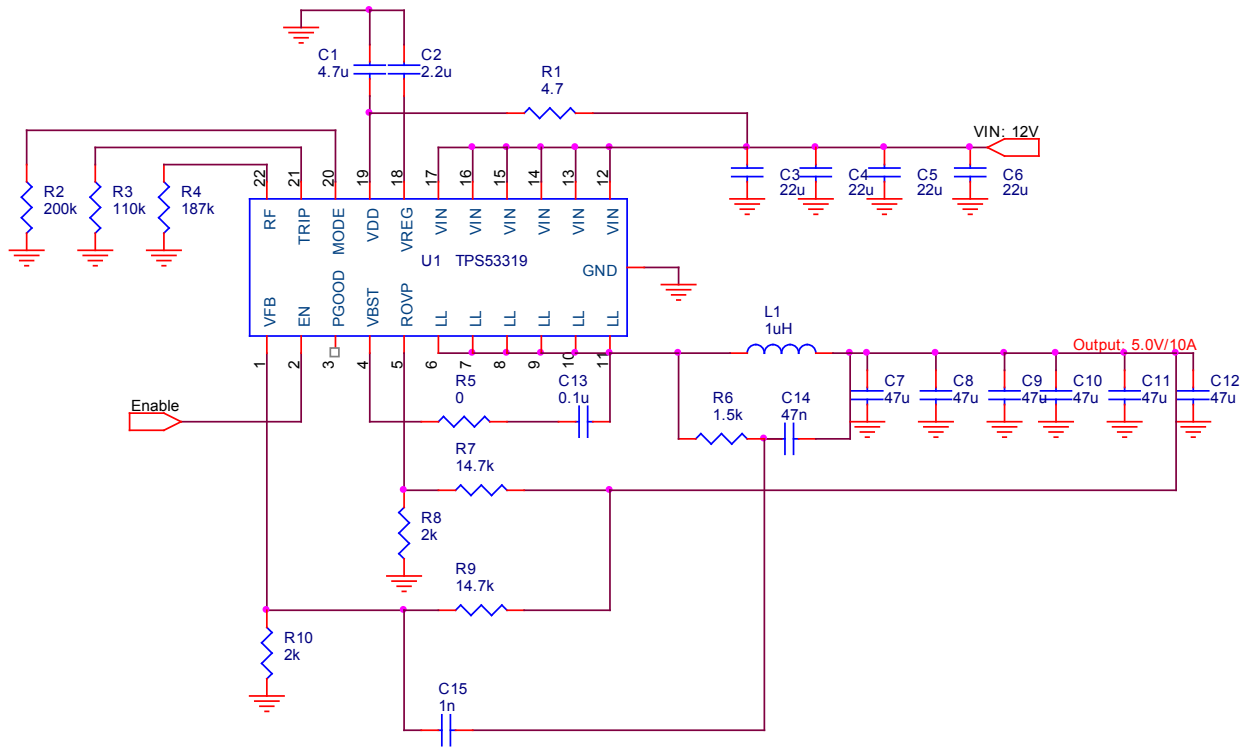

**Figure 6. TPS53319 Buck Converter With 5.0-V, 10-A Output**

The test results showed the crossover frequency, 41.3 kHz, and the phase margin, 63.1 degrees.

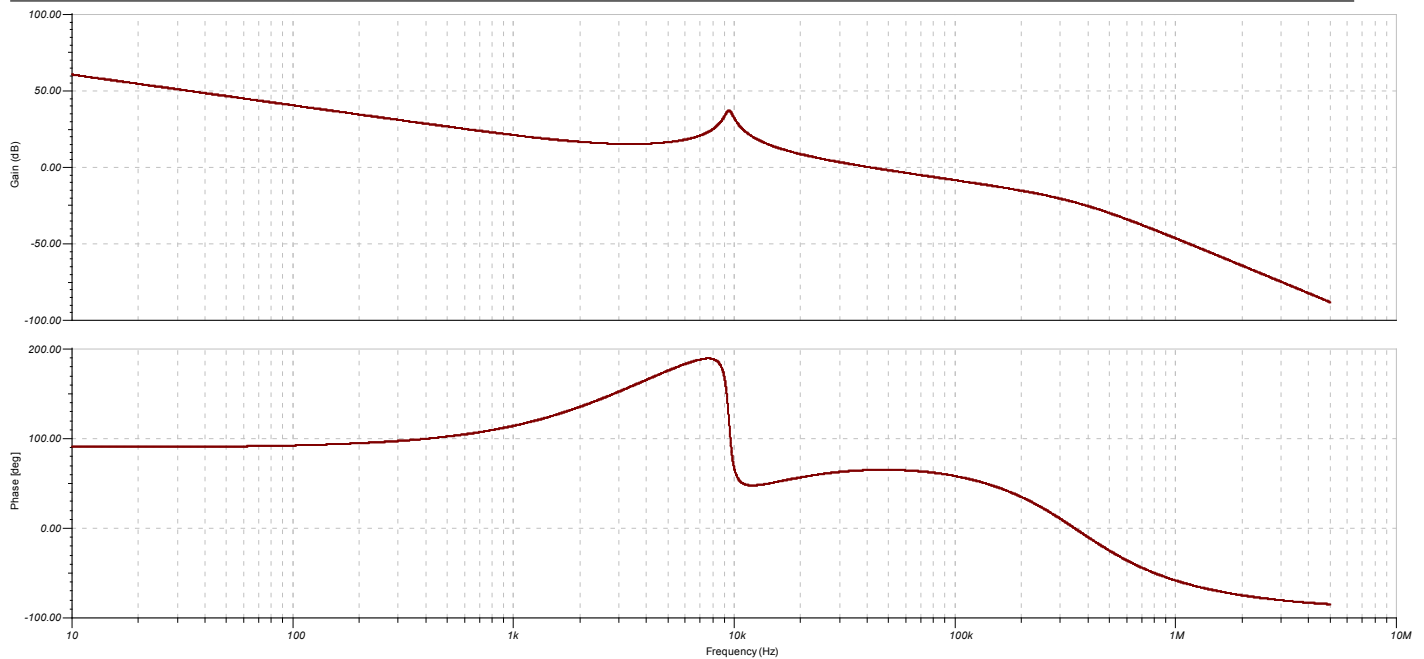

**Figure 7. Simulation Results With the Bode Plot Based on the Modeling**

## 5 Conclusion

The analysis has shown that novel modeling and analysis is effective and critical to the design of the DCAP mode converter. In addition, this paper has provided the control block diagram and the simulation circuitry.

## 6 References

1. Texas instruments, SLUSAY8B, TPS53319 data sheet.
2. Texas instruments, SLVU728, TPS53319 EVM-136 User's Guide



## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)