

Bootstrap Circuitry Selection for Half-Bridge Configurations



Mamadou Diallo

High Power Drivers

ABSTRACT

Driving MOSFETs in half-bridge configurations present many challenges for designers. One of those challenges is generating bias for the high-side FET. A bootstrap circuit takes care of this issue when properly designed.

This document uses UCC27710, TI's 620V half-bridge gate driver with interlock to present the different components in a bootstrap circuit and how to properly select them in order to ensure predictable switching of the power FETs.

Table of Contents

1 Introduction	2
2 Basic Operation of Bootstrap Circuit	2
3 Bootstrap Components Selection	3
3.1 Bootstrap Capacitor.....	3
3.2 VDD Bypass Capacitor.....	4
3.3 External Bootstrap Diode.....	4
3.4 Bootstrap Resistor.....	6
4 Layout Considerations for Bootstrap Components	7
5 Summary	8
6 References	8
7 Revision History	8

List of Figures

Figure 2-1. Bootstrap Charging Path.....	2
Figure 2-2. Bootstrap Capacitor Discharging Path.....	2
Figure 3-1. Reverse Recovery Losses due to Bootstrap Diode Reverse Recovery Time.....	4
Figure 3-2. Reverse Recovery Losses due to Bootstrap Diode Reverse Recovery Time (Zoomed Out).....	5
Figure 3-3. HB_HS Ringing Effects on Switch Node.....	5
Figure 3-4. VDD/HB-HS Fast Ramp Up ($R_{boot} = 0\Omega$).....	6
Figure 3-5. VDD/HB-HS Fast Ramp Up ($R_{boot} = 2.2\Omega$).....	7
Figure 4-1. Layout Example using UCC27710.....	7

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

When using half-bridge configurations, it is necessary to generate high-side bias to drive the gate of the high-side FET referenced to the switch node. One of the most popular and cost effective way for designers to do so is the use of a bootstrap circuit which consists of a capacitor, a diode, a resistor and a bypass capacitor.

This application report will explain how this circuit works, the key components of the bootstrap circuits and their impact in the gate drive. This app note will put emphasis on half-bridge gate drives using drivers with no built-in bootstrap diode, which gives designers flexibility and reduces power dissipation in the gate driver IC. Additionally, it will discuss the layout considerations for the different components of this circuit.

2 Basic Operation of Bootstrap Circuit

A bootstrap circuit is used in half-bridge configurations to supply bias to the high-side FET. Figure 2-1 shows the charging path of a bootstrap circuit in a simplified half-bridge configuration using UCC27710, TI's 620V half-bridge driver with interlock. When the low-side FET is on (high-side FET is off), the HS pin and the switch node are pulled to ground; the VDD bias supply, through the bypass capacitor, charges the bootstrap capacitor through the bootstrap diode and resistor.

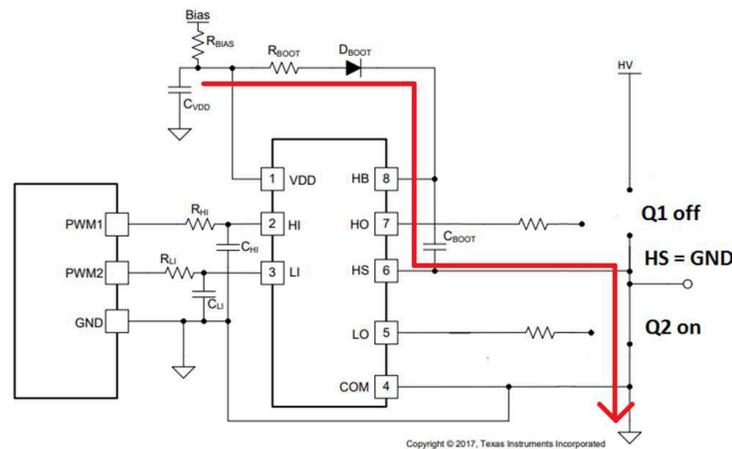


Figure 2-1. Bootstrap Charging Path

When the low-side FET is turned off and the high-side is on, the HS pin of the gate driver and the switch node are pulled to the high voltage bus HV; the bootstrap capacitor discharges some of the stored voltage (accumulated during the charging sequence) to the high-side FET through the HO and HS pins of the gate driver as shown in Figure 2-2.

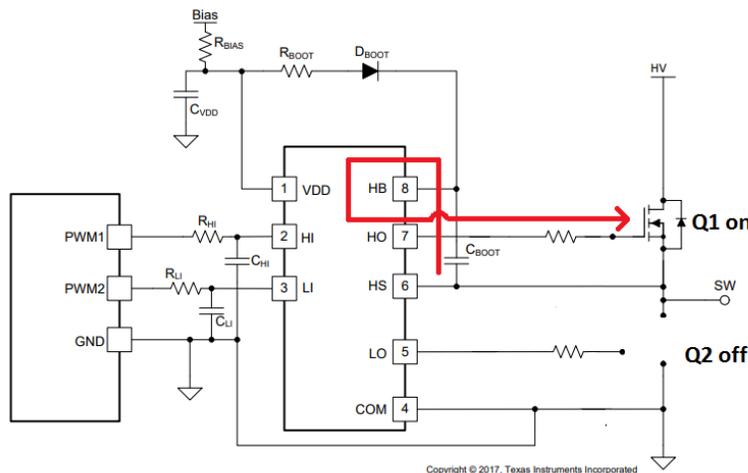


Figure 2-2. Bootstrap Capacitor Discharging Path

3 Bootstrap Components Selection

This section discusses each component's role and its impact in the gate drive.

3.1 Bootstrap Capacitor

From a design perspective, this is the most important component because it provides a low impedance path to source the high peak currents to charge the high-side switch. As a general rule of thumb, this bootstrap capacitor should be sized to have enough energy to drive the gate of the high-side MOSFET without being depleted by more than 10%. This bootstrap cap should be at least 10 times greater than the gate capacitance of the high-side FET. The reason for that is to allow for capacitance shift from DC bias and temperature, and also skipped cycles that occur during load transients. The gate capacitance can be determined using [Equation 1](#):

$$C_g = \frac{Q_g}{V_{Q1g}} \quad (1)$$

where Q_g : gate charge (MOSFET's datasheet)

$$V_{Q1g} = V_{DD} - V_{\text{BootDiode}}$$

where $V_{\text{BootDiode}}$: forward voltage drop across the boot diode.

Once the gate charge determined, the minimum value for the bootstrap capacitor can be estimated using [Equation 2](#):

$$C_{\text{boot}} \geq 10 \times C_g \quad (2)$$

Alternatively, a more detailed calculation of the minimum bootstrap capacitor value can be done using [Equation 3](#):

$$C_{\text{boot}} \geq \frac{Q_{\text{total}}}{\Delta V_{\text{HB}}} \quad (3)$$

$$Q_{\text{total}} = Q_G + I_{\text{HBS}} \times \frac{D_{\text{max}}}{f_{\text{sw}}} + \frac{I_{\text{HB}}}{f_{\text{sw}}}$$

where:

- Q_G = Total MOSFET gate charge (MOSFET's datasheet)

- I_{HBS} = HB to VSS leakage current (gate driver's datasheet)

- D_{max} = Maximum duty cycle

- I_{HB} = HB Quiescent current (Gate driver's datasheet)

And

$$\Delta V_{\text{HB}} = V_{DD} - V_{\text{DH}} - V_{\text{HBL}}$$

where:

- V_{DD} = Supply voltage of the gate driver IC

- V_{DH} = Bootstrap diode forward voltage drop (Bootstrap diode datasheet)

- V_{HBL} = HB UVLO falling threshold (Gate driver datasheet)

It is important to note that values below the minimum required bootstrap capacitor value could lead to activation of the driver's UVLO therefore prematurely turning off the high-side FET. On the flip side, higher values of the bootstrap capacitor lead to lower ripple voltage and longer reverse recovery time in some conditions (when initially charging the bootstrap cap or with a narrow bootstrap charging period) as well as higher peak current through the bootstrap diode. [Equation 4](#) relates the bootstrap cap and the peak currents through the bootstrap diode.

$$I_{\text{peak}} = C_{\text{boot}} \times \frac{dv}{dt} \quad (4)$$

It is generally recommended to use low ESR and ESL surface mount multi-layer ceramic capacitors (MLCC) with good voltage ratings (2xVDD), temperature coefficients and capacitance tolerances.

3.2 VDD Bypass Capacitor

The charge to replenish the bootstrap capacitor must come from some larger bypass capacitor, usually the VDD bypass capacitor. As a rule of thumb, this bypass capacitor should be sized to be at least 10 times larger than the bootstrap capacitor so that it is not completely drained during the charging time of the bootstrap capacitor. This allows the bootstrap capacitor to be properly replenished during the charging sequence. This 10x ratio results in 10% maximum ripple on the VDD capacitor in worst case conditions.

$$C_{VDD} \geq 10 \times C_{Boot} \tag{5}$$

3.3 External Bootstrap Diode

In order to minimize losses associated with the reverse recovery properties of the diode and ground noise bouncing, a fast recovery diode or Schottky diode with low forward voltage drop and low junction capacitance is recommended. Using Schottky diodes reduce the risk associated with charge supplied back to the gate driver supply from the bootstrap capacitor and minimize leakage current. Figure 3-1, shows the reverse recovery losses when using diodes with reverse recovery times on HB-HS(Ch1). We can observe large amount of over and undershoot on the HB-HS pin which can trigger the driver's UVLO and shutdown the gate driver.

When the HS pin (switch node) is pulled to a higher voltage, the diode must be able reverse bias fast enough to block any charges from the bootstrap capacitor to the VDD supply. This bootstrap diode should be carefully chosen such that it is capable of handling the peak transient currents during start-up; and such that its voltage rating is higher than the system DC-link voltage with enough margins.

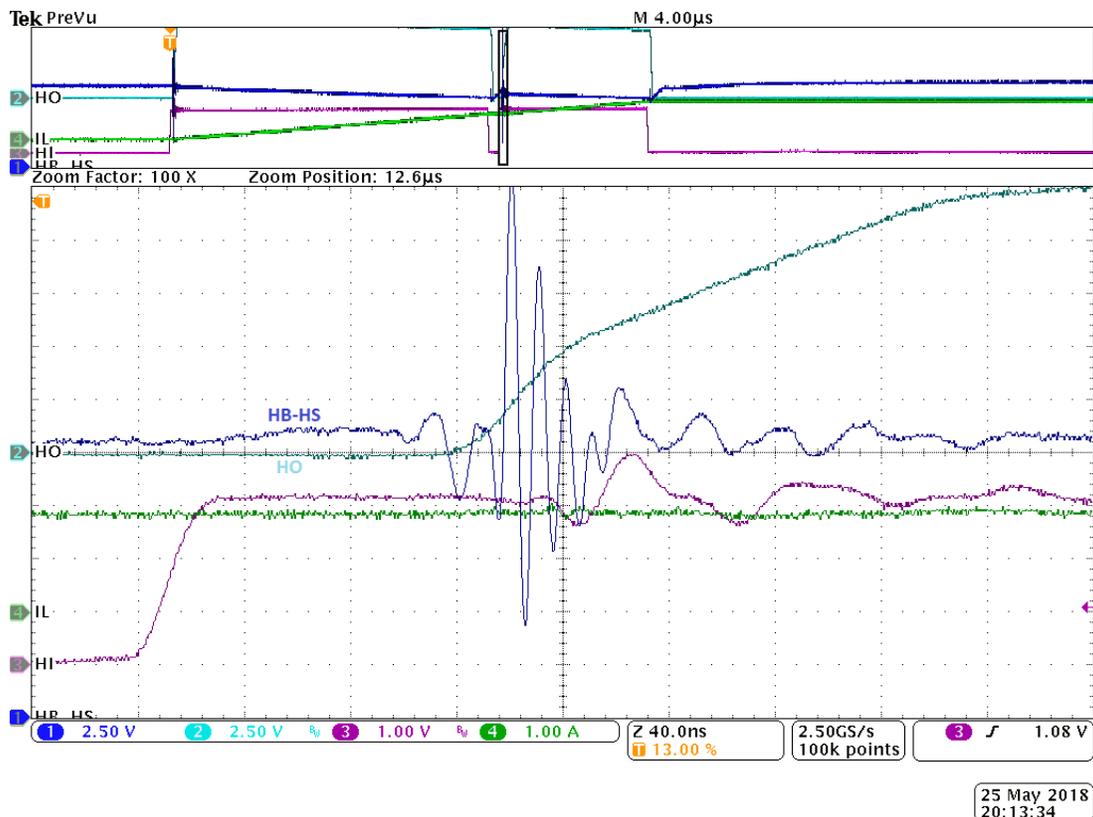


Figure 3-1. Reverse Recovery Losses due to Bootstrap Diode Reverse Recovery Time

Figure 3-2 below shows a reverse recovery condition created (channel 1) by setting up the timing to specifically force the switch node high with the diode current flowing.

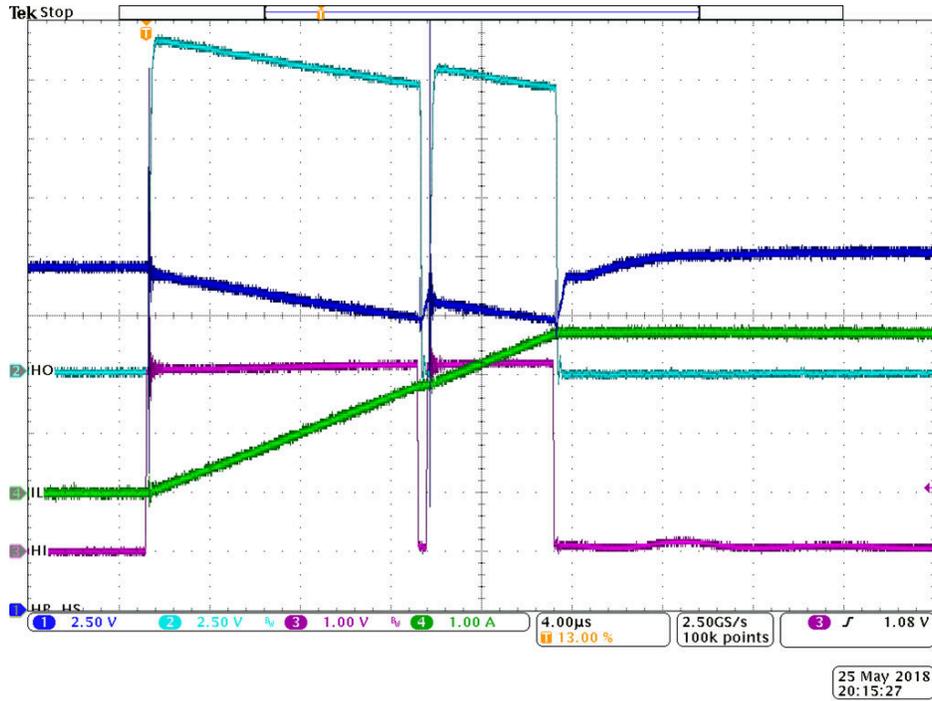


Figure 3-2. Reverse Recovery Losses due to Bootstrap Diode Reverse Recovery Time (Zoomed Out)

Figure 3-3 shows the effects of the losses on the HB-*HS* pin which can trigger the switch node and potentially damage the driver.

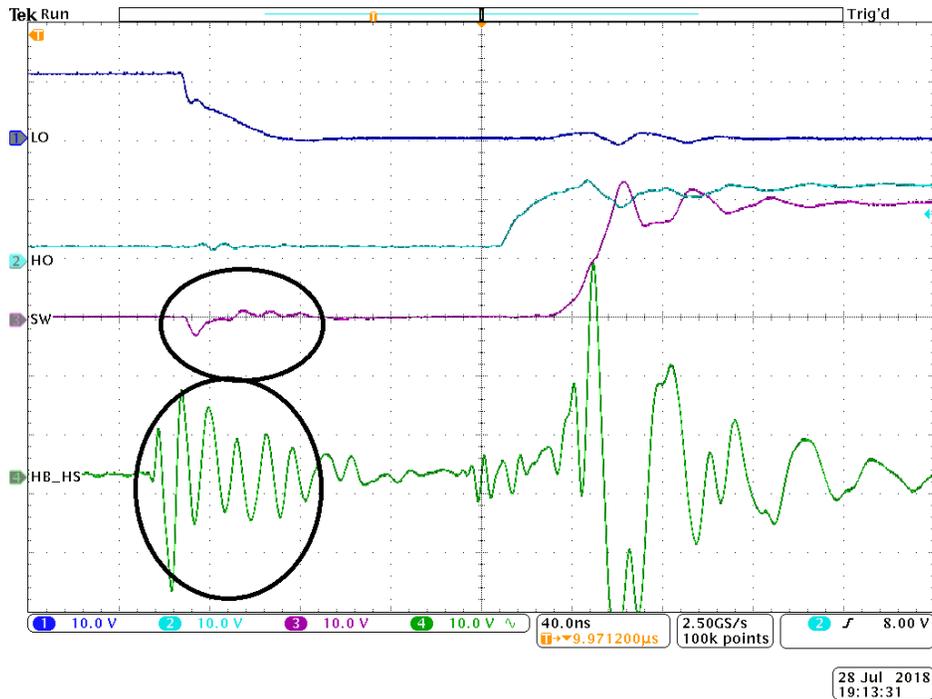


Figure 3-3. HB-*HS* Ringing Effects on Switch Node

3.4 Bootstrap Resistor

The role of the bootstrap resistor is to limit the peak currents at the bootstrap diode during start-up, it should therefore be carefully selected as it introduces a time constant with the bootstrap capacitor given by Equation 6:

$$\tau = \frac{R_{\text{Boot}} \times C_{\text{Boot}}}{\text{Duty Cycle}} \quad (6)$$

This time constant occurring during the high-side off time explains the dependency on duty cycle. This duty cycle being constant, the bootstrap resistor and bootstrap capacitor should be tuned appropriately to achieve the desired start-up time. Increasing the bootstrap resistor values will increase the time constant leading to slower start-up time.

Additionally, the bootstrap resistor chosen must be able to withstand high power dissipation during the first charging sequence of the bootstrap capacitor. This energy can be estimated by Equation 7:

$$\frac{1}{2} \times C_{\text{boot}} \times V_{\text{Cboot}}^2 \quad (7)$$

This energy is dissipated during the charging time of the bootstrap capacitor and can be estimated using Equation 8:

$$E \cong 3 \times C_{\text{boot}} \times R_{\text{boot}} \quad (8)$$

This resistor is essential in limiting the peak currents through the bootstrap diode at start-up and limiting the dv/dt of HB-HS (high-side floating supply to the return high-side floating supply). The peak current through this resistor can be calculated using Equation 9:

$$I_{\text{pk}} = \frac{V_{\text{DD}} - V_{\text{BootDiode}}}{R_{\text{boot}}} \quad (9)$$

Figure 3-4 shows the fast ramp up on VDD (CH4) and HB-HS (CH1) when using a 0-Ohm resistor which leads to undesired change in voltage on LO(CH3) and HO(CH2).

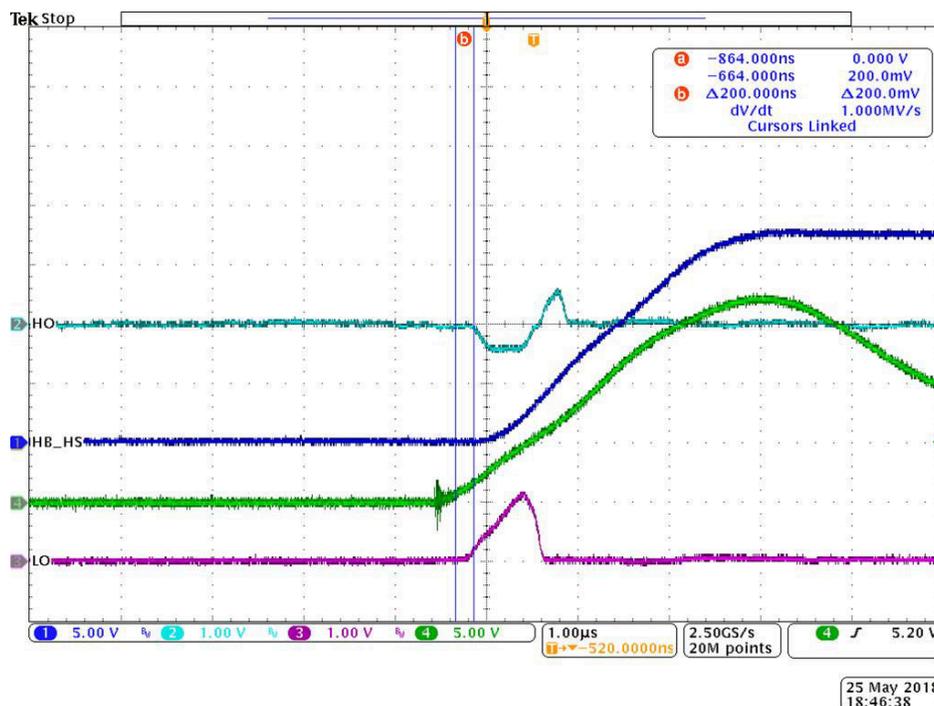


Figure 3-4. VDD/HB-HS Fast Ramp Up ($R_{\text{boot}} = 0\text{Ohms}$)

Figure 3-5 shows how using slightly higher resistor value ($R_{boot} = 2.2\Omega$) solve this issue. It is important to note that the bias rising rate observed in Figure 3-5 does not apply to all drivers.

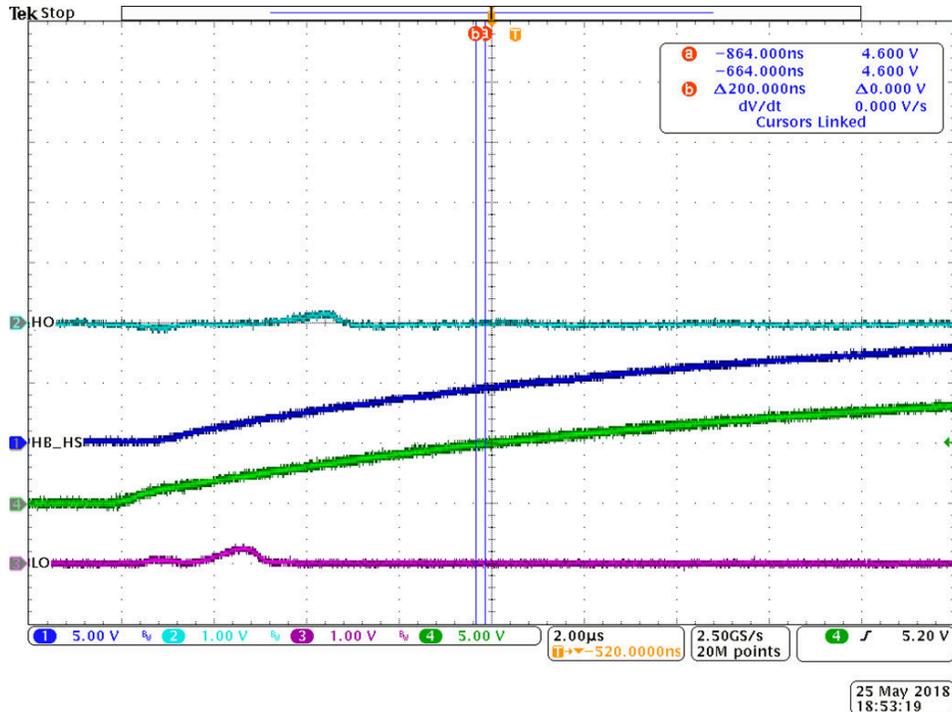


Figure 3-5. VDD/HS Fast Ramp Up ($R_{boot} = 2.2\Omega$)

4 Layout Considerations for Bootstrap Components

Once all bootstrap components appropriately selected, it is important to carefully place these components in order to minimize parasitic inductances and reduce high current trace length. This high current path includes the bootstrap capacitor, the bootstrap diode, the ground-referenced VDD bypass capacitor of the driver, and the low-side power switch. It is therefore important to reduce that path and keep that loop as small as possible. The bootstrap capacitor and bypass capacitor should be placed as closed as possible to the gate driver supply pins. Figure 4-1 below shows a good layout example using UCC27710 with all bootstrap components located near the gate driver IC minimizing any effects of parasitic inductances and reducing the high peak currents path of the bootstrap circuit. It is also important to separate high voltage power and low voltage signal traces.

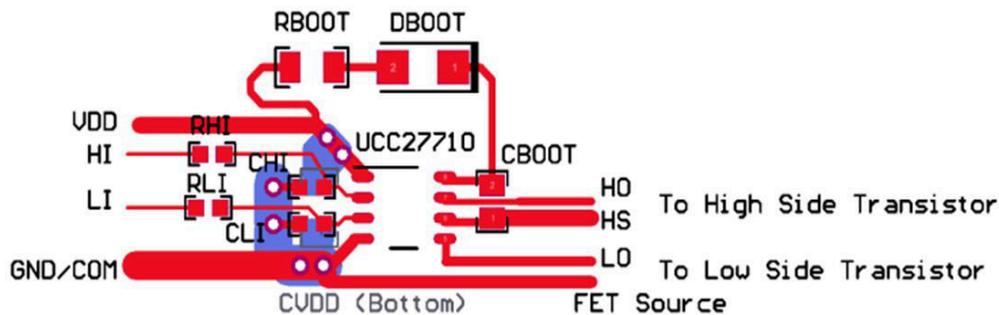


Figure 4-1. Layout Example using UCC27710

5 Summary

This application report used UCC27710, TI's 600V family of half-bridge drivers to discuss the basic operation of a bootstrap circuit in a half-bridge configuration. It also discussed the role and importance of each bootstrap components required to generate bias for the high-side FET in half-bridge configurations. It showed a detailed calculation method as well as a general rule of thumb estimation for the bootstrap capacitor. Additionally, it discussed how to properly place these components on a PCB layout once all the components are appropriately selected.

6 References

- [UCC27710 Product Folder](#)
- [UCC27710 Datasheet](#)
- [UCC27710 Evaluation Module](#)
- [Half-bridge Driver Products](#)
- [Fundamentals of MOSFET and IGBT Gate Driver Circuits](#)

7 Revision History

Changes from Revision * (August 2018) to Revision A (September 2023)	Page
• Updated the numbering format for tables, figures, and cross-references throughout the document.....	1

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated