

Extending the Input Voltage Range of an LDO Regulator

Jeff Falin

PMP Systems Power

ABSTRACT

This application report explains how to use a FET to overcome the input voltage limitation of a linear regulator.

All IC's have an input voltage limitation due to the manufacturing process. This limitation is cumbersome when trying to step down a high-supply voltage to a lower, regulated voltage using a dc/dc converter such as a linear regulator. Adding a FET to the input of a linear regulator creates a dc/dc converter with a wider input voltage range than the range of the regulator alone. The excess voltage (and therefore power) is dropped across the FET. Figure 1 shows an IRF7601 N-channel MOSFET on the input of a TPS79228 2.8-V, 100-mA, low-noise, high-PSRR LDO regulator. The two resistors provide a bias voltage to the gate of the MOSFET and the load current determines the voltage at the source of the MOSFET (i.e., the FET's on resistance adjusts to meet the load current). The MOSFET is selected based on three criteria: drain to source breakdown voltage, gate drive requirements, and power dissipation capabilities. In this example, the maximum power-supply voltage is 15 V, but the TPS79228 has a maximum recommended operating input voltage of 5.5 V, so a MOSFET with a 20-V breakdown voltage is selected.

To determine the minimum bias voltage for the gate of the MOSFET, the MOSFET's drain current (I_D) vs gate-source voltage (V_{GS}) data sheet curve is required. For the IRF7601, the curves indicate that the device needs V_{GS} slightly below 1.5 V for a 100-mA output current. Since the maximum dropout of the regulator is 100 mV at 100 mA, the regulator's input voltage must stay above 2.9 V. Therefore, the gate of the MOSFET must be biased to at least $1.5 \text{ V} + 2.9 \text{ V} = 4.4 \text{ V}$, so that when the MOSFET is providing 100 mA, its source voltage does not drop below 2.9 V. The maximum gate bias voltage is simply the maximum recommended operating voltage for the regulator, or 5.5 V. This voltage provides more than enough gate drive to provide the regulator's 1 μA of quiescent current while in shutdown mode. Although the gate can be biased between 4.4 V and 5.5 V, a bias voltage of 5.0 V is selected to account for variations in the threshold voltage. Maximum power dissipation for the FET is:

$$100 \text{ mA} \times (15 \text{ V} - 2.9 \text{ V}) = 1.21 \text{ W}$$

which the IRF7601 in a Micro 8 package can handle for $T_A = 55^\circ\text{C}$. So, a low noise, low ripple 2.8-V output voltage is generated from a 15-V supply using the TPS79228 and a MOSFET.

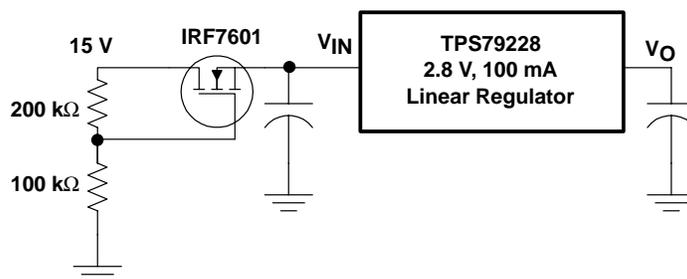


Figure 1. MOSFET Switch Used to Expand the Regulator's Input Voltage

Figure 2 is slightly more complicated but may be necessary if the input voltage varies significantly. A Zener diode replaces the bottom resistor in Figure 1 and provides a fixed gate drive to the MOSFET. The output voltage of the Zener is selected in a manner similar to that explained previously.

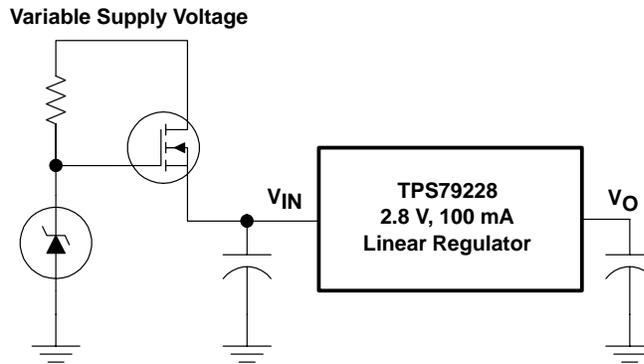


Figure 2. MOSFET Switch Biased With Zener Diode Used to Expand Regulator's Input Voltage

Either method is acceptable for creating a dc/dc converter with a wider input voltage range than the converter IC allows. The single MOSFET solution is the simplest and cheapest solution. The MOSFET biased with a Zener diode is the best choice when the supply is unregulated.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Mailing Address:

Texas Instruments
Post Office Box 655303
Dallas, Texas 75265