

White Light LED Driver With Gradual Dimming

S.K. Loo, Michael Day

PMP/Portable Power DC-DC Applications

ABSTRACT

Many consumer products using white light LEDs for illumination and backlighting provide gradual LED illumination at turnon and turnoff. This gradual illumination is usually achieved with the aid of a microprocessor that provides PWM dimming control. This circuit uses the Texas Instruments TPS61040 white light LED driver to provide gradual illumination at turnon and turnoff without the use of a microprocessor.

The following circuit generates a 101mA constant current to drive up to 6 white LEDs for portable applications such PDAs and digital cameras. The input operating range is 1.8 V to 6 V, which covers two-cell alkaline and NiMh inputs (1.8 V to ~3 V), three-cell alkaline and NiMh inputs (2.7 V to ~4.8 V), and single-cell Li-Ion inputs (3 V~4.2 V). This boost converter uses R1 to set a constant current through the LEDs. A detailed description of this circuit can be found in the TPS61040 data sheet ([SLVS413](#)).

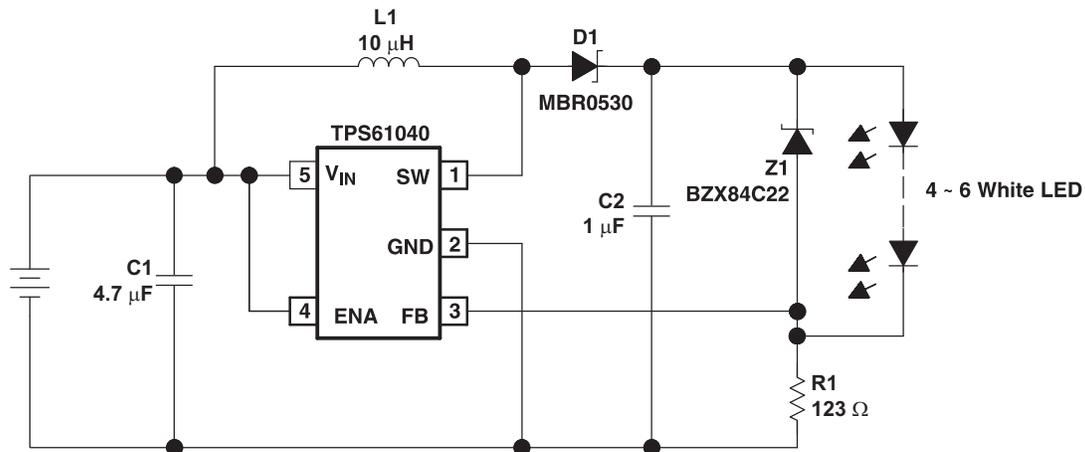


Figure 1. Constant Current LED Drive Supply

The circuit shown in [Figure 1](#) instantly produces the maximum programmed load current at turnon and instantly goes to zero current at turnoff. The circuit shown in [Figure 2](#) slowly (1–2 seconds) increases and decreased the LED brightness at turnon and turnoff. Only a slight modification of the original circuit is required to produce this effect.

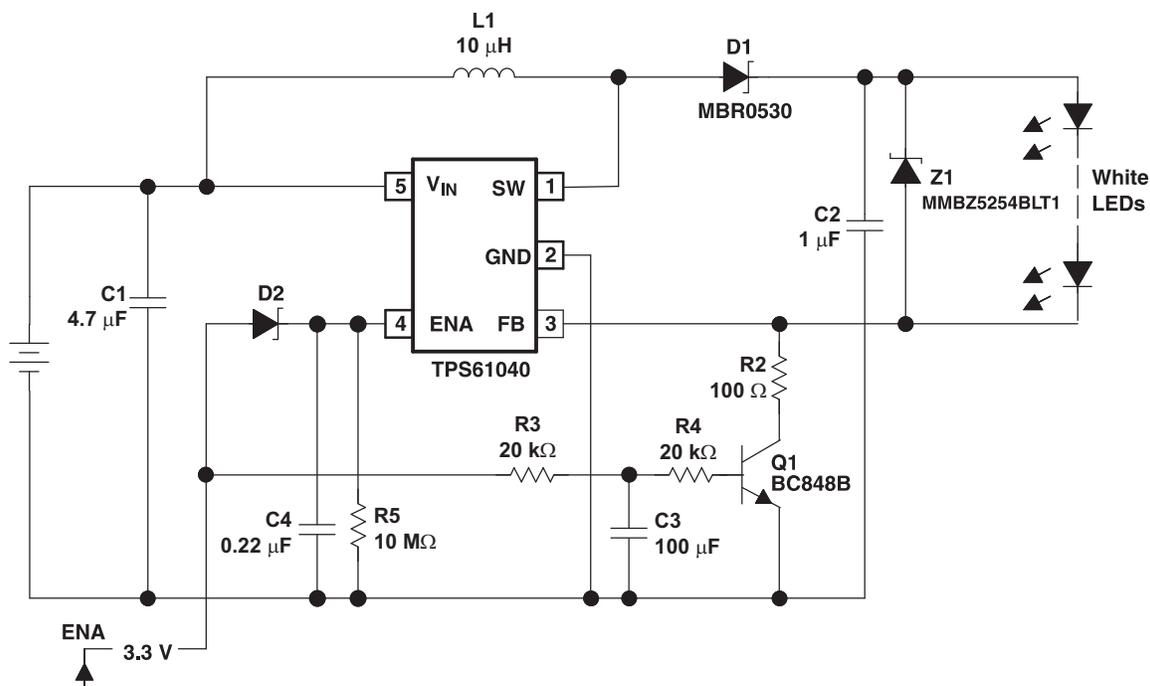


Figure 2. Additional Components Provide Gradual Turnon and Turnoff of LED Current

On application of the enable signal, R3 slowly charges C3, which slowly turns on Q1. The TPS61040 is immediately enabled through D2. During turnon, the initial resistance from FB to ground is extremely high, limiting the LED current to 0 mA. As Q1 slowly turns on, the effective resistance gradually drops. The drop in resistance directly correlates to a rise in LED current. The LEDs transition from 0% brightness to 100% brightness in 1–2 seconds, depending on the time constants chosen. Figure 3 shows the relevant waveforms during turnon.

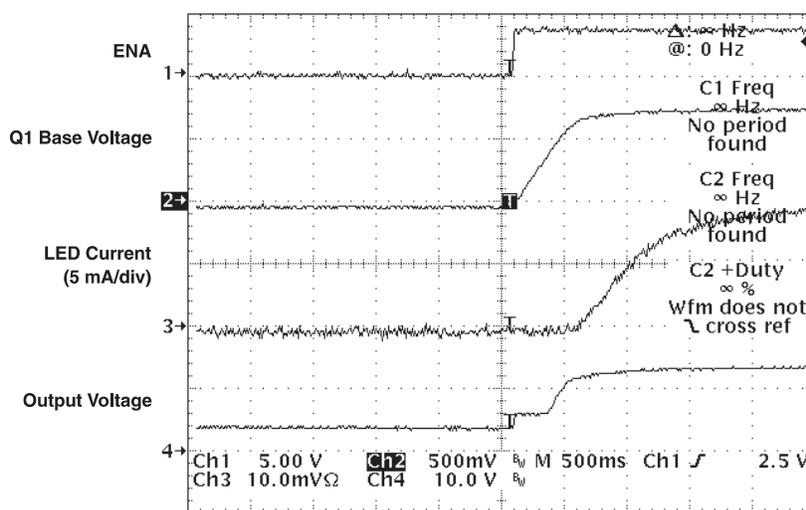


Figure 3. Waveform During Turnon

When ENA goes low during turnoff, D2 prevents C4 from discharging. The TPS61040 remains enabled until C4 discharges through R5. While the TPS61040 is still enabled, C3 begins to discharge through R3 and R4. As the available base current to Q1 drops, the effective resistance of Q1 starts to increase. The LED current drops in proportion to the increase in the total resistance seen at the FB pin. Figure 4 shows the relevant waveforms during turnoff.

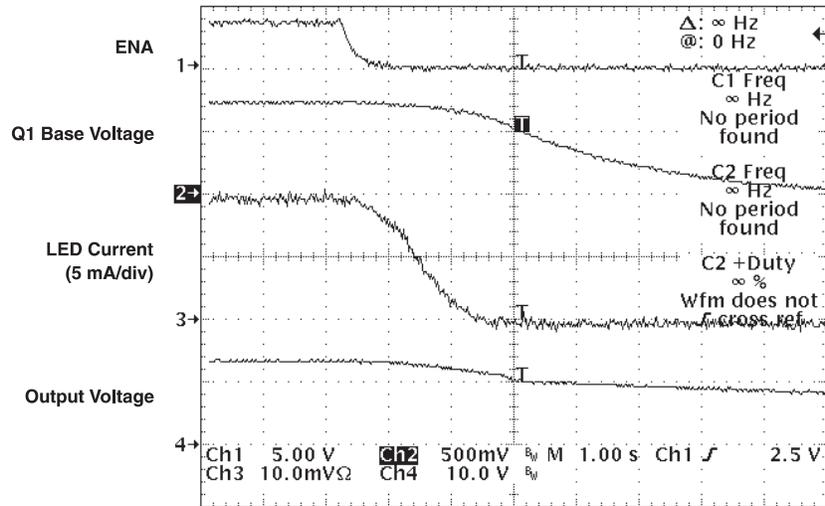


Figure 4. Waveforms During Turnoff

At turnon, a short delay occurs between the ENA signal going high and the start of the current flowing through the LEDs. This occurs because Q1 does not start to conduct until its base voltage reaches approximately 0.7 V. The addition of a 3.3-k Ω resistor, R6 shown in Figure 5, causes the base voltage to immediately jump to about 0.5 V at turnon. This reduces the start-up delay from 500 ms to about 100 ms. Turnon and turnoff waveforms with R6 added are shown in Figure 6 and Figure 7.

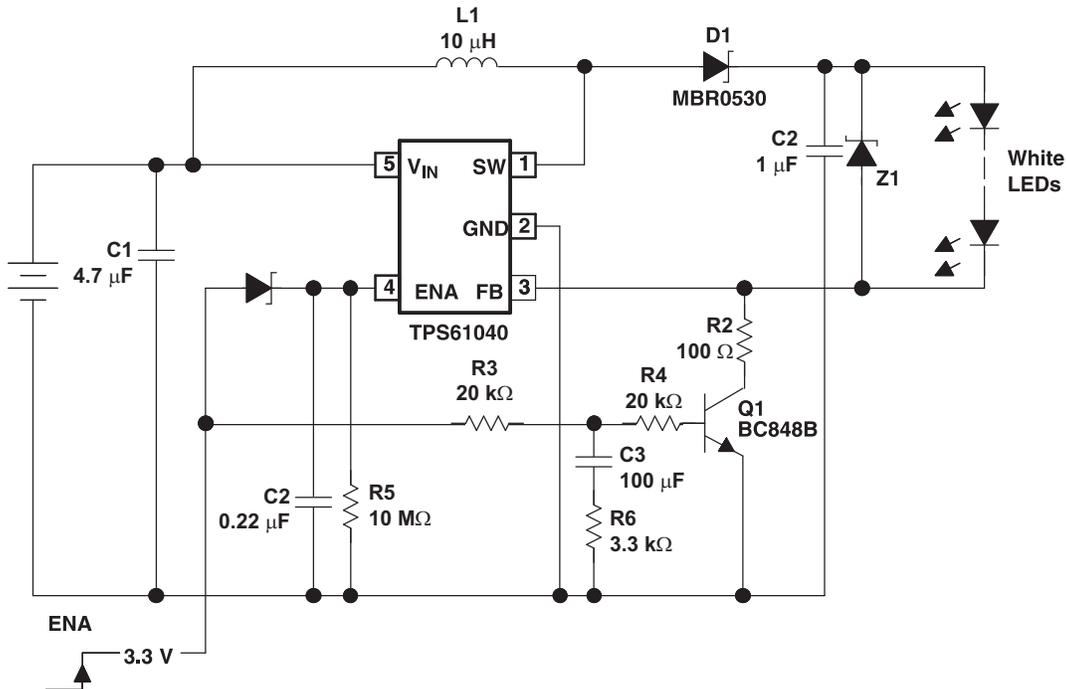


Figure 5. Modification to Reduce Turnon Delay

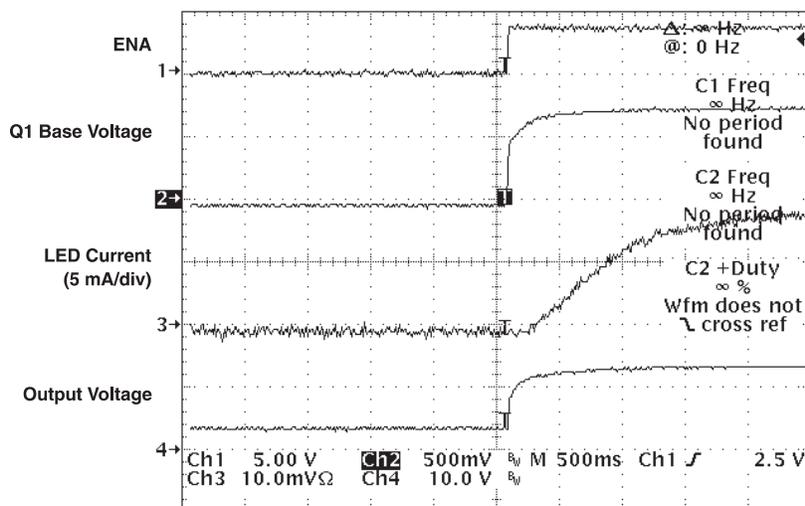


Figure 6. Reduced Delay Turnon

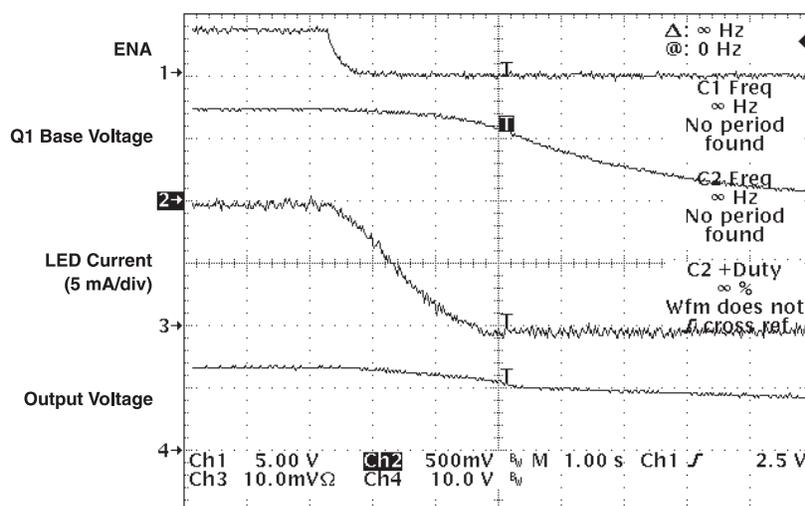


Figure 7. Reduced Delay Turnoff

This application report has shown how to provide a gradual turnon and turnoff of white light LEDs without the use of microprocessor control.

References

1. *TPS61040* data sheet ([SLVS413](#))
2. *TPS61040EVM-002* users guide ([SLVU068](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
Low Power Wireless	www.ti.com/lpw

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265