

Doubling the Power With Ganged TPS2062/TPS2066

Heping Dai

PMP Systems Power

ABSTRACT

The TPS2062 and TPS2066 devices are dual-channel, 1-A, power-distribution switches that are intended for applications where heavy capacitive loads and short circuits are likely to be encountered. These devices incorporate 70-m Ω , N-channel MOSFET power switches for power-distribution systems that require multiple power switches in a single package. When the output load exceeds the current-limit threshold or a short is present, the device limits the output current to a safe level by switching into a constant-current mode, pulling the overcurrent logic output low. The current limit for each power switch is set at 1.5 A, typically. When continuous heavy overloads and short circuits increase the power dissipation in the switch, causing the junction temperature to rise, a thermal protection circuit shuts off the switch to prevent damage. Recovery from a thermal shutdown is automatic once the device has cooled sufficiently. Internal circuitry ensures that the switch remains off until valid input voltage is present.

While the 1-A continuous current for one switch can provide up to 5 W of power to the switch output, it may still not be enough for some applications. A simple solution is to gang the two power switches in one package by connecting the two output pins together. Mathematically, this can double the power to a load. However, if voltage drops, switch impedances, and/or thermal distributions are different between the two channels, the currents in the two power switches will be imbalanced. A current imbalance could cause one power path to run away until breakdown or over-heating occurs. This application report shows that the TPS2062 and TPS2066 switches can share the current almost equally when the switches are ganged and effectively double the power outage compared to an individual single switch.

Contents

| | | |
|----------|-------------------------------------|----------|
| 1 | Doubling Power to Load | 2 |
| 2 | Statistic Product Data | 3 |
| 3 | Layout Considerations | 5 |
| 4 | Conclusions | 5 |
| 5 | Reference | 5 |

List of Figures

| | | |
|---|-------------------------------------------------------------------------------------------------------------------|---|
| 1 | Paralleling Two Power Switches of TPS2062 | 2 |
| 2 | Power Switch Currents With $R_L = 2 \Omega$ (ch1: \overline{OC} ; ch3:lout1; ch4:lout2) | 2 |
| 3 | Power Switch in Current Limiting and Thermal Shutdown With $R_L = 1 \Omega$ (M1:lout; ch3:lout1; ch4:lout2) | 3 |
| 4 | A Overcurrent Load (1 Ω) Connected to Powered Output (ch1: \overline{OC} ; ch3:lout1; ch4:lout2) | 3 |
| 5 | Statistical Current-Limit Test Results of Power Switch 1 | 4 |
| 6 | Statistical Current-Limit Test Results of Power Switch 2 | 4 |
| 7 | Statistical Current-Limit Test Results of Ganged TPS2062 | 5 |

1 Doubling Power to Load

Because the bias voltage for the two switches of the TPS2062 or the TPS2066 are the same as their inputs are tied together internally in the device, the major factors that affect current sharing are the turnon resistance (R_{dson}), thermal sensing circuits, and the layout of the two power switches of the device. Due to the symmetrical layout design of the devices, the R_{dson} of the two switches match well, as does the thermal sensing (based on simulation and product test results). In order to verify the ganging performance, a test circuit was developed, as shown in Figure 1.

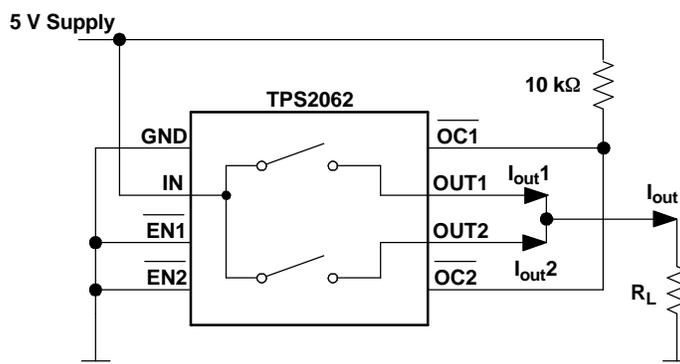


Figure 1. Paralleling Two Power Switches of TPS2062

During testing, the load resistance R_L was adjusted to find where the current limit takes place. A 2- Ω resistor on the load has an equivalent 2.5-A load current to the device. Figure 3 shows the testing result of the individual current for each of the two power switches (Iout1 and Iout2). It is clear that the two power switches share the load well as Iout1 = 1.2 A and Iout2 = 1.2 A.

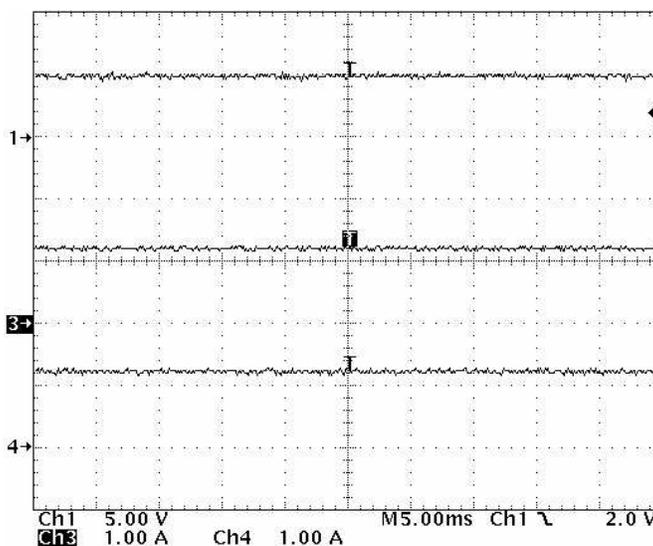


Figure 2. Power Switch Currents With $R_L = 2 \Omega$ (ch1:OC; ch3:Iout1; ch4:Iout2)

The test results show that the TPS2062 can deliver at least 2-A of continuous current to the load when the power switch outputs are tied together.

The TPS2062 has current limiting and thermal protection. To trip the current limit and thermal protection in the device, reduce the load resistance to 1 Ω . Figure 3 shows the individual current on each switch and the total load current. As shown, the current limits on both switches are always triggered at the same time and go to thermal shutdown (the period with 0-A current) at the same time as well.

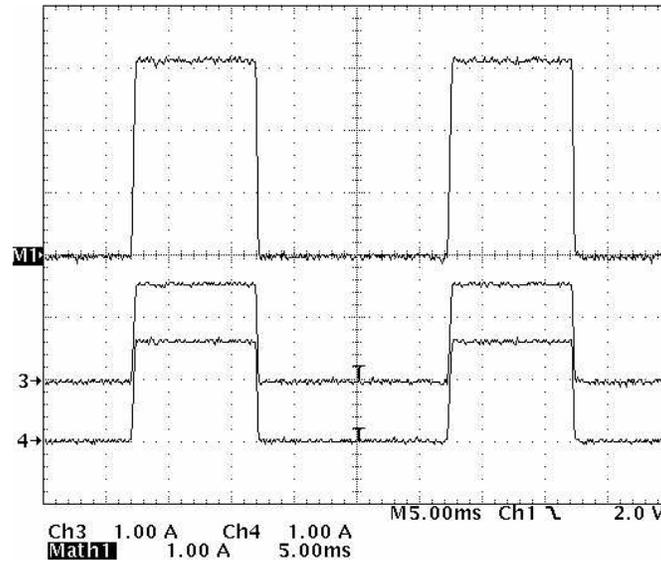


Figure 3. Power Switch in Current Limiting and Thermal Shutdown With $R_L = 1 \Omega$ (M1:lout; ch3:lout1; ch4:lout2)

Figure 4 shows the combined overcurrent flag output (\overline{OC}) of the two power switches and the switch currents. It shows the \overline{OC} is asserted about 8 ms after the overcurrent trip due to the internal \overline{OC} deglitch.

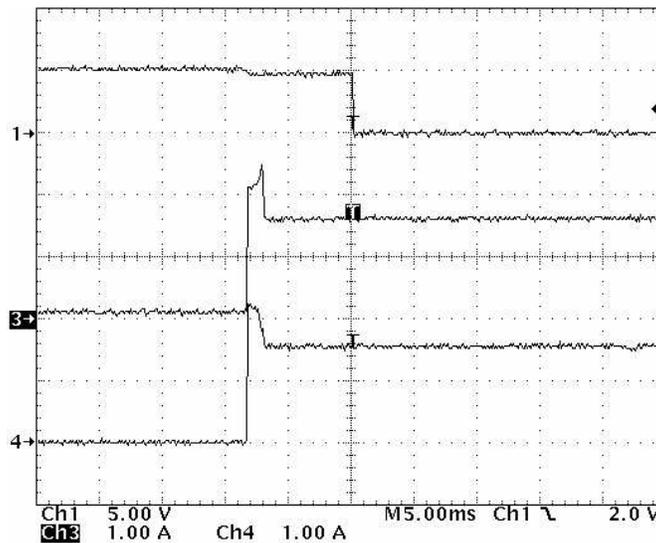


Figure 4. A Overcurrent Load (1Ω) Connected to Powered Output (ch1: \overline{OC} ; ch3:lout1; ch4:lout2)

2 Statistic Product Data

A more thorough investigation of ganging the TPS2062 power switch outputs was performed by testing a large quantity of TPS2062 devices. Statistical current-limit data was generated. For the individual power switches in the TPS2062/TPS2066, their statistics current limits are shown in Figure 5 and Figure 6 with minimum (-6σ), mean, and maximum ($+6 \sigma$) data.

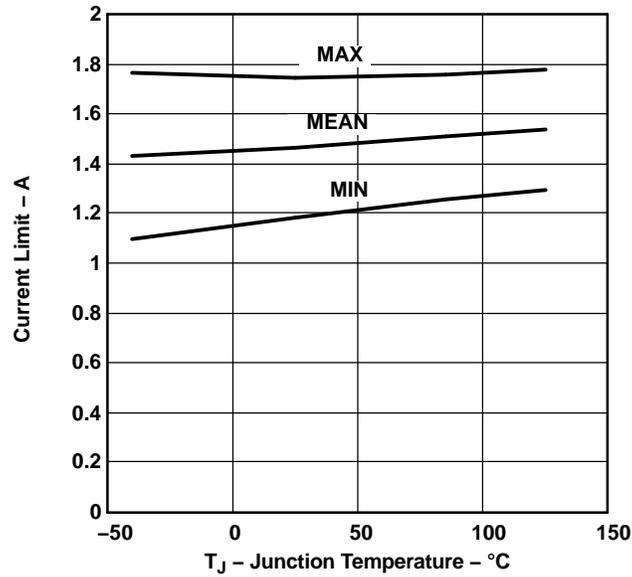


Figure 5. Statistical Current-Limit Test Results of Power Switch 1

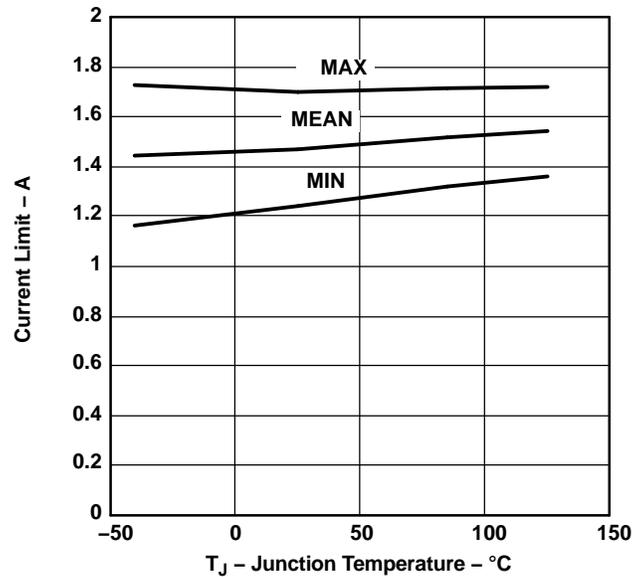


Figure 6. Statistical Current-Limit Test Results of Power Switch 2

The data show that the two power switches have almost equal current-limit distribution (minimum, mean, and maximum) due to the symmetrical power switch layout of the TPS2062.

When the two power switches are ganged, by connecting the two output pins together, the ganged current limit is also tested and its statistical results are shown in [Figure 7](#).

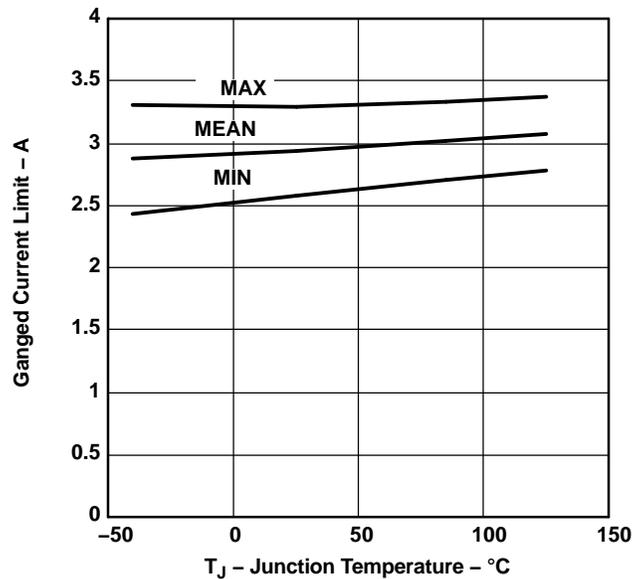


Figure 7. Statistical Current-Limit Test Results of Ganged TPS2062

The data in [Figure 7](#) show that the ganged current limit is equal to the addition of the two individual current limits of the power switches from the minimum to the average and to the maximum. The results show that the ganged power switch can at least conduct 2 A of continuous current, and the typical current limit is about 3 A.

3 Layout Considerations

In order to have the best possible current sharing between the two internal power switches, not only do the power switches have to be laid out exactly the same, but all the external connections must be also symmetrical between the two channels. The best approach is to short the two outputs at the pins with enough copper plane underneath the output pins. The traces from the input power supply or connector to the TPS2062/TPS2066 input pin and from the ganged output pins to load or an output connector should be wide and short so that the trace impedance is small. A large bulk capacitor and a small ceramic capacitor (at least 0.1 μ F) placed close to the input pin are recommended.

4 Conclusions

Due to its internal symmetrical layout, the TPS2062/TPS2066 becomes a power switch that has twice the current rating of its individual power switches when its two outputs are connected together. The current limit and thermal protection work the same way as in an individual TPS2062/TPS2066 power switch but with doubled, current-trip threshold and current limit. Therefore, the TPS2062/TPS2066 with two power switches ganged can provide twice the power to a load than that of an individual power switch.

5 Reference

1. *TPS2062, TPS2066, Dual, Current-Limited, Power-Distribution Switches* data sheet ([SLVS490](#)), Texas Instruments.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | | Applications | |
|------------------|--------------------------------------------------------------------|---------------------|--------------------------------------------------------------------------|
| Amplifiers | amplifier.ti.com | Audio | www.ti.com/audio |
| Data Converters | dataconverter.ti.com | Automotive | www.ti.com/automotive |
| DSP | dsp.ti.com | Broadband | www.ti.com/broadband |
| Interface | interface.ti.com | Digital Control | www.ti.com/digitalcontrol |
| Logic | logic.ti.com | Military | www.ti.com/military |
| Power Mgmt | power.ti.com | Optical Networking | www.ti.com/opticalnetwork |
| Microcontrollers | microcontroller.ti.com | Security | www.ti.com/security |
| | | Telephony | www.ti.com/telephony |
| | | Video & Imaging | www.ti.com/video |
| | | Wireless | www.ti.com/wireless |

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2004, Texas Instruments Incorporated