

Ceramic Capacitors Replace Tantalum Capacitors in LDOs

Jeff Falin

PMP Portable Power

ABSTRACT

With the proper considerations, ceramic output capacitors can be used with low dropout linear regulators (LDO) and DC/DC switching converters that require tantalum output capacitors.

Many internally compensated linear regulators and switching converters require some equivalent series resistance (ESR) in the output capacitor, C_{OUT} . The control loop for these tantalum C_{OUT} -only converters relies on the zero that is created by the product of the output capacitance, C_{OUT} , and the ESR for stability. Converter data sheets typically provide a minimum (and possibly maximum ESR) value for a given output capacitance or the required frequency of the zero. For example, the data sheet for the TPS769xx family of linear regulators provides a curve of ESR versus output current for different output voltages (Figure 1).

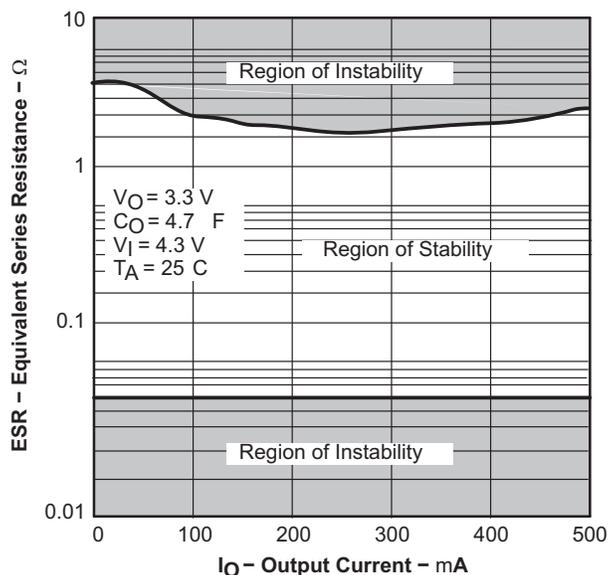


Figure 1. Typical Region of Stability ESR Versus Output Current

For various reasons including lower cost, smaller size, and/or reliability, some system engineers prefer to use ceramic capacitors instead of tantalum capacitors in their applications. A low-ESR ceramic output capacitor with a discrete series resistor can be used to replace a tantalum output capacitor. The schematic in Figure 2 shows such an implementation, using a 0.060- Ω series resistor and 4.7- μF ceramic output capacitor. This series combination of parts meets the TPS76933 ESR requirements shown in Figure 1; therefore, the linear regulator will be stable over the load range. No further testing is required. While a 1/4-watt resistor is acceptable for simulating the output capacitor ESR of most linear regulators, a resistor with larger power rating may be necessary for switching converters because the inductor ripple current, ΔI , flows through the resistor, dissipating $\Delta I^2 \cdot R$ watts of power in the resistor.

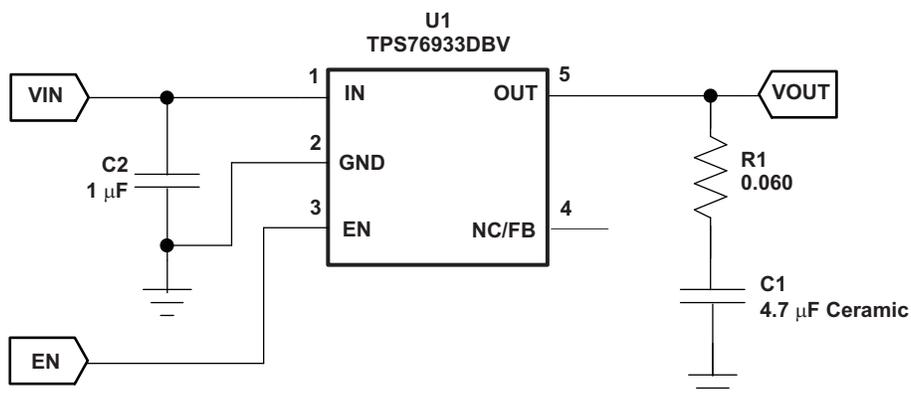


Figure 2. TPS76933 Implementation using R1 to provide ESR

To minimize load transient dips caused by ESR, use only the smallest required ESR. In this example, even though the minimum ESR was 0.050 Ω , a 0.060- Ω resistor was selected to allow some margin for resistor tolerance over temperature. Because it is the ESR and C_{OUT} product that is important, choosing a larger C_{OUT} allows a smaller ESR to be chosen.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
Low Power Wireless	www.ti.com/lpw	Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265