

Ballast Resistors Allow Load Sharing Between Two Paralleled DC/DC Converters

Jeff Falin

PMP Portable Power

ABSTRACT

This application report explains one method for minimizing the size of the ballast resistors between two identical dc/dc converters that are tied, through these resistors, to the same load.

In some applications, it may be more cost effective or thermally beneficial to parallel two lower current dc/dc converters to drive a single high-current load instead of using a single higher current-rated converter. However, all dc/dc converters regulate their output voltage to a dc set point (V_{DCx}) plus and minus a tolerance percentage (TOL_{DCDC}) up to their maximum-rated current. Therefore, simply tying the outputs of the two converters to the same load does not always result in equal current sharing below each converter's maximum-rated current because the converter that is regulating high at $V_{DCx} \times (1+TOL_{DCDC})$ attempts to provide all of the load current until reaching its current limit. As shown in [Figure 1](#), load-sharing (ballast) resistors, R_{SHARE} , located between each converter's regulated output and the load are necessary in order to accommodate the difference in each converter's regulated output voltage. This application report explains one method for minimizing the size of the ballast resistors between two identical dc/dc converters that are tied, through these resistors, to the same load. Minimizing the ballast resistors is important for minimizing power lost in the resistors as well as minimizing $V_{DROP} = I_{DCx} \times R_{SHARE}$ which reduces the voltage seen by the load, V_O . The following assumptions were used to develop the design equations:

1. Both dc/dc converters are the same and are set to the same nominal output voltage. Due to internal voltage reference tolerances and external feedback resistor tolerances for adjustable devices, each converter's regulated output voltage is different.
2. Both dc/dc converters only source current, i.e., neither dc/dc converter can sink current, less than or equal to their maximum-rated currents.
3. Both R_{SHARE} resistors are the same value.

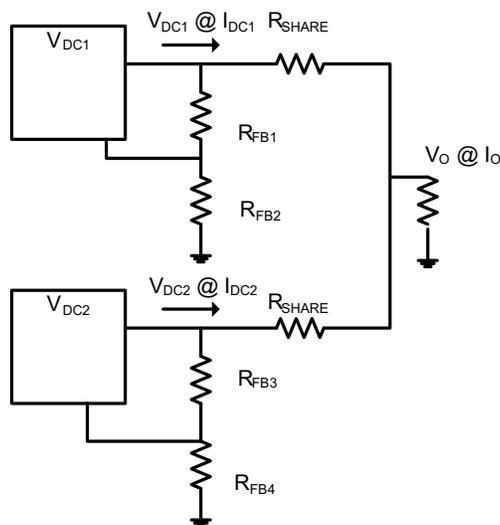


Figure 1. Using Load-Sharing Resistors

If it is assumed that dc/dc converter 1 regulates at the high end of its tolerance while dc/dc converter 2 regulates at the low end of its tolerance, then Equation 1 gives the minimum share resistor value to ensure that neither converter exceeds its maximum-rated current.

$$R_{\text{SHARE}} = \frac{V_{\text{DC}} \times (2 \times \text{TOL}_{\text{DCDC}})}{2 \times I_{\text{DCMAX}} - I_{\text{OMAX}}} \quad (1)$$

Where

V_{DC} = the nominal output of each converter

$$\text{TOL}_{\text{DCDC}} = \text{TOL}_{V_{\text{REF}}} + 2 \times \left(1 - \frac{V_{\text{REF}}}{V_{\text{DC}}} \right) \times \text{TOL}_{R_{\text{FB}}}$$

$\text{TOL}_{V_{\text{REF}}}$ = the tolerance of the dc/dc converter's internal reference

V_{REF} = the nominal value of the dc/dc converter's internal reference

$\text{TOL}_{R_{\text{FB}}}$ = the tolerance of the external feedback resistors

I_{DCMAX} = the maximum-rated current of the dc/dc converter

I_{OMAX} = the maximum load current to be shared

The absolute minimum output voltage occurs in the unlikely event that both converters are regulating at the low end of their tolerance and therefore are equally sharing the output load current. The equation below computes this value:

$$V_{\text{OABSMIN}} = V_{\text{DC}} \times (1 - \text{TOL}_{\text{DCDC}}) - \frac{I_{\text{OMAX}}}{2} \times R_{\text{SHARE}} \times (1 + \text{TOL}_{R_{\text{SHARE}}}) \quad (2)$$

Where $\text{TOL}_{R_{\text{SHARE}}}$ = the tolerance of the R_{SHARE} .

Choosing a value for R_{SHARE} is an iterative process in which V_{DC} is selected then V_{OABSMIN} is computed. If V_{OABSMIN} is too low, V_{DC} is incremented and R_{SHARE} recomputed until V_{OABSMIN} is above the minimum regulated voltage required by the application. Choosing converters and resistors with tighter tolerances reduce the value of R_{SHARE} and increase V_{OABSMIN} .

Due to the various combinations of the tolerances of each component, the actual output voltage varies from board to board. Using the preceding equations to compute R_{SHARE} ensures that V_{O} is between $V_{\text{DC}} \times (1 + \text{TOL}_{\text{DCDC}})$ at no load and V_{OABSMIN} at full load.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright 2008, Texas Instruments Incorporated