

Cyclone™ III FPGA Starter Kit Power Reference Design


Matthew Borne

PMP - DC/DC Converters


ABSTRACT

This power supply was designed to power the 3C25F324 starter kit. This reference design has many benefits over the existing power supply found on the starter kit demonstration board.

Altera™ Starter Kit Block Diagram

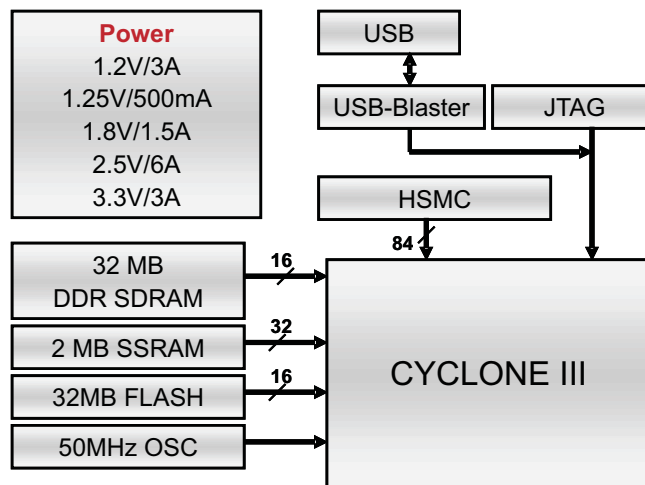

Power Reference Design Details

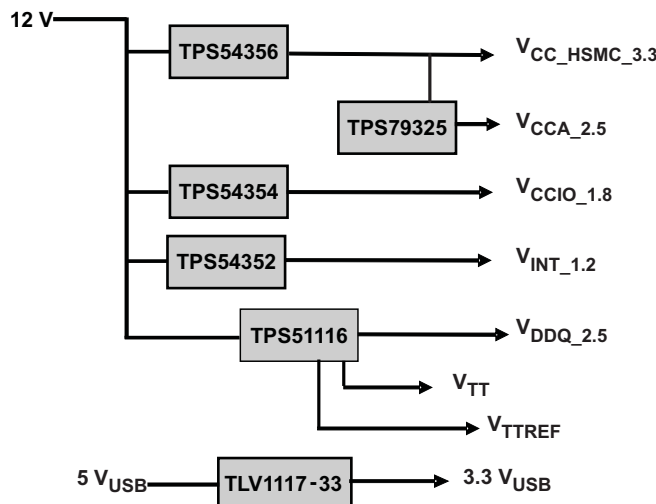


Cyclone, Altera are trademarks of Altera Corporation.

Power Reference Board Top Assembly View

POWER RAILS	VOLTAGE	LOAD
Vcc5.0	5 V	DDR bias, USB
Vcc3.3	3.3 V	HSMC, GPIO, Clock, LED, SRAM
Vcc2.5	2.5 V	DDR SRAM, SRAM, FLASH, VCCIO_ALL, VCCA_ALL
Vcc1.8	1.8 V	FLASH
Vcc1.2	1.2 V	VINT ,VCCD_ALL
Vcc1.25	1.25 V	DDR ref


Power Reference Board Top Assembly View

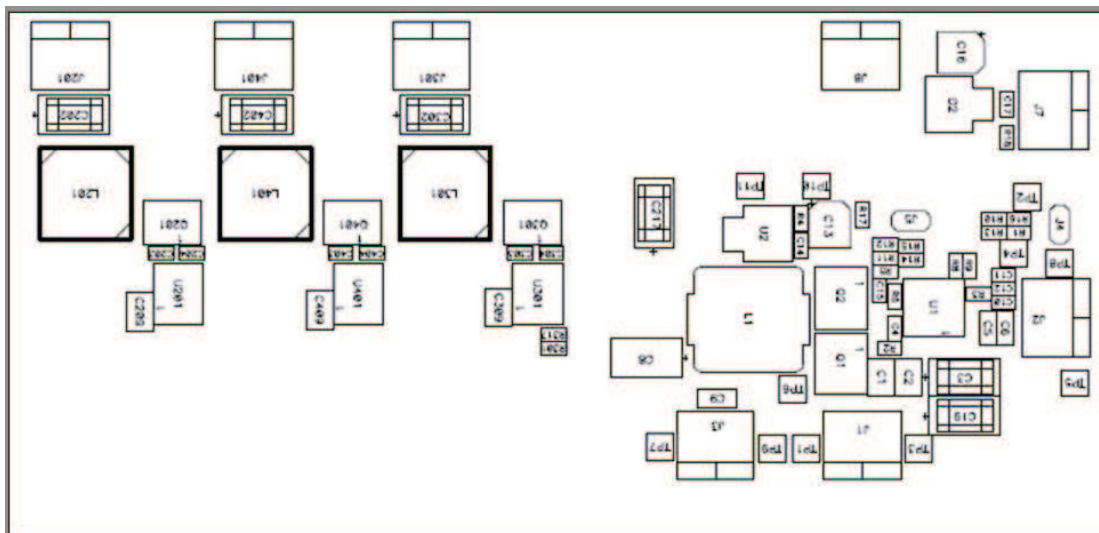

Full load at all buck converters

- U1, TPS51116, 2.5 V at 6 A
- U201, TPS54356, 3.3 V at 3 A
- U301, TPS54352, 1.2 V at 3 A
- U401, TPS54354, 1.8 V at 1.5 A

Cyclone™ III Thermal Board Image

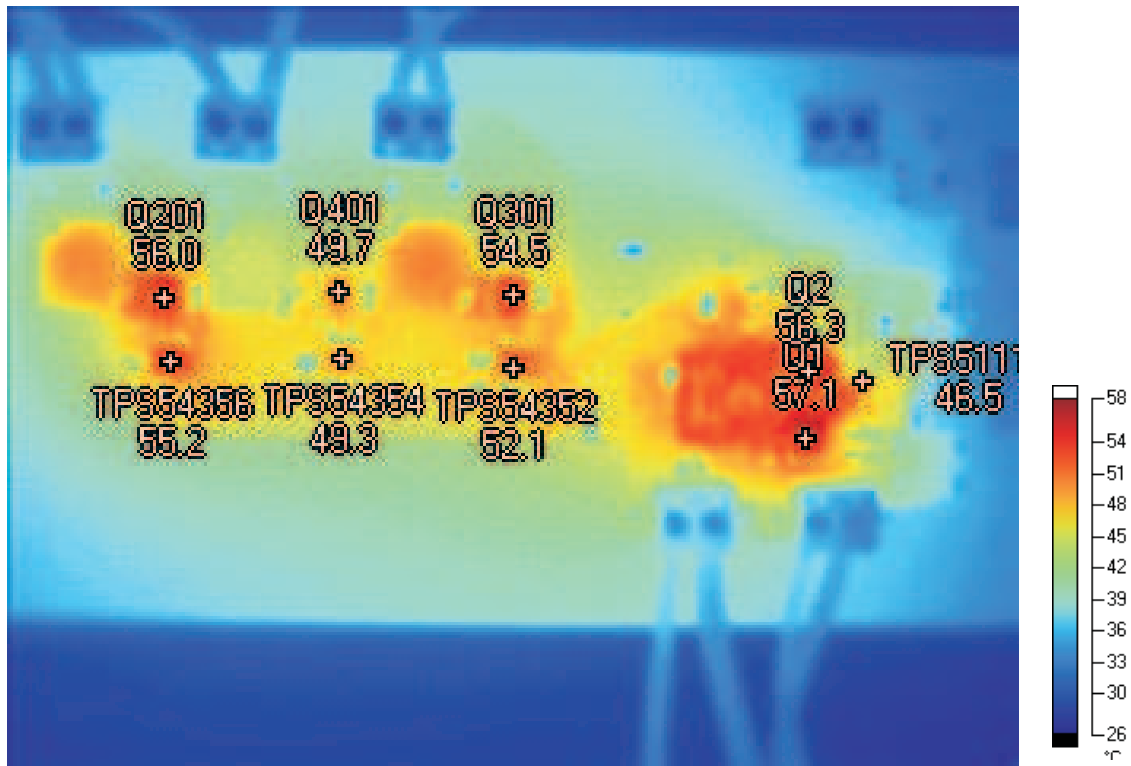

Markers

LABEL	TEMPERATURE	EMISSIVITY	BACKGROUND	
Q1	57.1°C	0.95	24°C	
Q2	56.3°C	0.95	24°C	
TPS51116	46.5°C	0.95	24°C	2V5
Q301	54.5°C	0.95	24°C	
TPS54352	52.1°C	0.95	24°C	1V2
Q401	49.7°C	0.95	24°C	
TPS54354	49.3°C	0.95	24°C	1V8
Q201	56°C	0.95	24°C	
TPS54356	55.2°C	0.95	24°C	3V3

→ Hot Spot Q1 w/ 57.1°C, so max. dT = +33.1

TI Design Benefits

- DDR supply with one single controller; TI saves one complete DC/DC converter
- Existing starter kit catch diodes are overloaded
- TI does not use power modules
- TI offers higher efficiency
- TI offers a low-cost complete discrete solution

Available Material From TI


Available Material From TI

- Schematic for DDR supply (could be either DDR1 or DDR2)
- Schematic for I/O – core – FPGA voltages
- Bill of Materials – low parts count for total PSU
- Gerber files
- Test Results



Request Additional Power Support

fpgasupport@list.ti.com


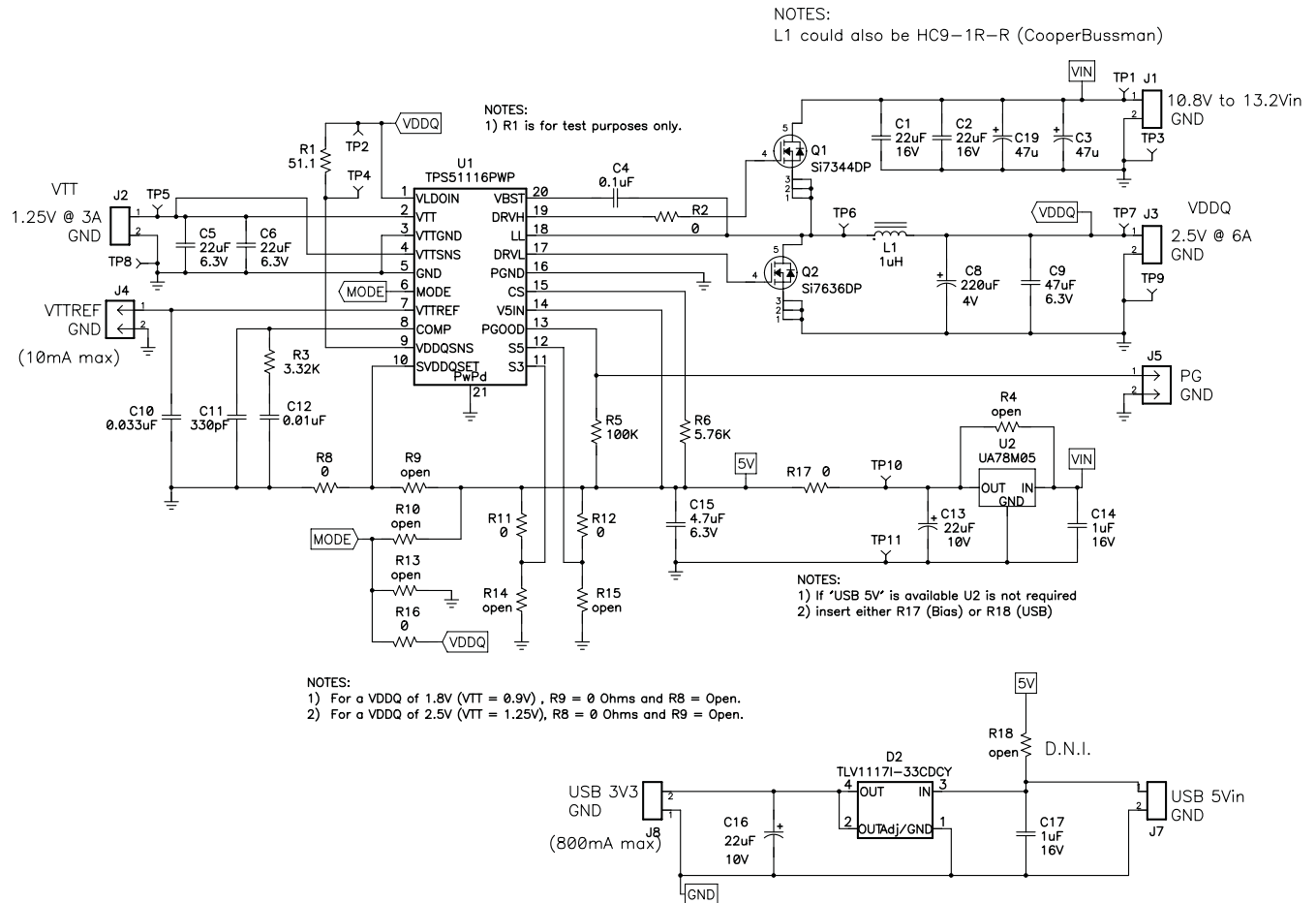
Circuit Diagram DDR1, 2V5 and 1V25 (USB 3V3)



Circuit Diagram PoL, 3V3, 2V5, 1V8, 1V2

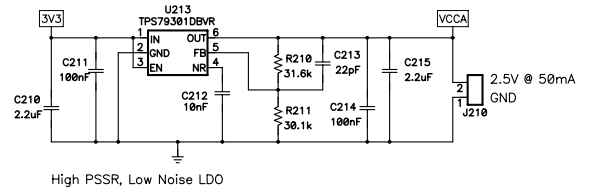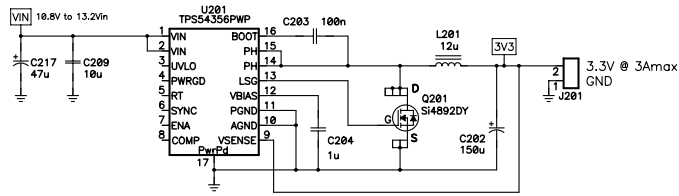

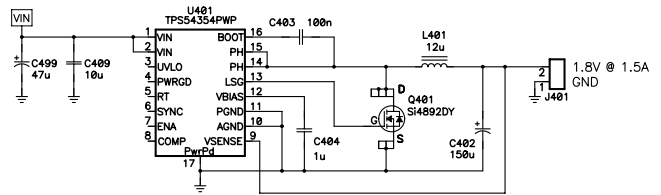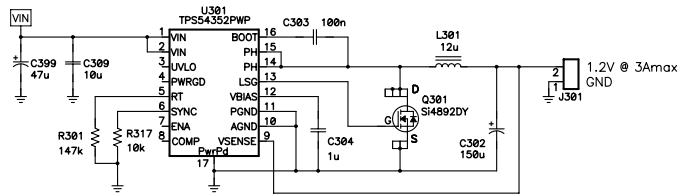maximum effcy. w/ TPS54550 at 3Amps out;
use fsw 250kHz at 1V2 and 500kHz at 3V3.



NOTES:
1) Fsw 350kHz by R301, R317

Reference Design Bill of Materials

Count	Part Number	Description	Value	MFR
7	5000	Test Point, Red, Thru Hole Color Keyed	5000	Keystone
4	5001	Test Point, Black, Thru Hole Color Keyed	5001	Keystone
5	Std	POSCAP 16TQC47M	47 μ	Sanyo
1	Std	Capacitor, Ceramic, 0.01 μ F, 25V, X7R, 10%, 0603	0.01 μ F	Std
1	Std	Capacitor, Ceramic, 0.10 μ F, 25V, X7R, 10%, 0603	10 nF	Std
1	Std	Capacitor, Ceramic, 22 pF, 25V, X7R, 10%, 0603	22 pF	Std
1	Std	Capacitor, Ceramic, 0.033 μ F, 16V, X7R, 10%, 0603	0.033 μ F	Std
1	Std	Capacitor, Ceramic, 0.1 μ F, 50V, X7R, 10%, 0603	0.1 μ F	Std
2	Std	Capacitor, Ceramic, 100 nF, 50V, X7R, 10%, 0603	100 nF	Std
2	Std	Capacitor, Ceramic, 2.2 μ F, 50V, X7R, 10%, 0603	2.2 μ F	Std
3	Std	Capacitor, Ceramic, 1 μ F, 16V	1 μ	Std
1	Std	Capacitor, Ceramic, 330 pF, 50V, NPO, 10%, 0603	330 pF	Std
3	Std	Capacitor, Ceramic, vvV, [temp], [tol]	100 n	Std
1	Std	Resistor, Chip, 147 k Ω , 1/16W, 1%	147 k	Std
6	Std	Resistor, Chip	0	Std
1	Std	Resistor, Chip	30.1 k	Std
1	Std	Resistor, Chip	31.6 k	Std
1	Std	Resistor, Chip	open	Std
1	Std	Resistor, Chip, 100 k Ω , 1%, 0603	100 K	Std
1	Std	Resistor, Chip, 10k, 0603, 1/16W, 1%	10 k	Std
1	Std	Resistor, Chip, 3.32 k Ω , 1%, 0603	3.32 K	Std
1	Std	Resistor, Chip, 5.76 k Ω , 1%, 0603	5.76 K	Std
1	Std	Resistor, Chip, 51.1 Ω , 1%, 0603	51.1	Std
3	4TPE150MI	POSCAP, TPE, 150 μ F, 4V, 18 m Ω	150 μ	Sanyo
1	C1608X5R0J475KT	Capacitor, Ceramic, 4.7 μ F, 6.3V, X5R, 10%, 0603	4.7 μ F	TDK
2	C1608X5R1C105KT	Capacitor, Ceramic, 1 μ F, 16V, X5R, 10%, 0603	1 μ F	TDK
2	C2012X5R0J226MT	Capacitor, Ceramic, 22 μ F, 6.3V, X5R, 20%, 0805	22 μ F	TDK
1	C3216X5R0J476MT	Capacitor, Ceramic, 47 μ F, 6.3V, X5R, 20%, 1206	47 μ F	TDK
3	C3225X5R1C106M	Capacitor, Ceramic, 10 μ F, 16V, X5R, 20%	10 μ	TDK
2	C3225X7R1C226MT	Capacitor, Ceramic, 22 μ F, 16V, X5R, 20%, 1210	22 μ F	TDK
4	D120/2DS	Terminal Block, 2-pin, 15-A, 5,1 mm	(blank)	OST
2	ECE-Vxxxvvz	Capacitor, Aluminum, xxV, 20%	22 μ F	Panasonic
5	ED1609	Terminal Block, 2-pin, 15-A, 5,1 mm	ED1609-ND	OST
1	EEFCX0G221R	Capacitor, Aluminum, 220 μ F, 4V, 5 m Ω	220 μ F	Panasonic
3	ELLCTV120M	SMD Choke Coil, 12 μ H, 26 m Ω , 3.7A	12 μ	Panasonic
1	IHLP5050EZRZ1R0M01	Inductor, SMT, 1 μ H, 29A, 0.0025 Ω	1 μ H	Vishay Dale
2	PTC36SAAN	Header, 2-pin, 100mil spacing, (36-pin strip)	PTC36SAAN	Sullins
3	Si4892DY	Trans, N-ch, 30V, 7A, 20 m Ω , Qg=10.5nC	Si4892DY	Vishay
1	Si7344DP	MOSFET, N-Ch, 20V, 14A, 0.012 Ω	Si7344DP	Vishay
1	Si7636DP	MOSFET, N-Ch, 30V, 25A, 0.0048 Ω	Si7636DP	Vishay
1	TLV1117I-xxCDCY	IC, vvV, 800 mA LDO Voltage Regulators	TLV1117I-33CDCY	Texas Instruments
1	TPS51116PWP	IC, Synchronous VDDQ Controller w/ VTT LDO	TPS51116PWP	Texas Instruments
1	TPS54352PWP	IC, 4.5-V to 20-V Input, 3-A Synchronous Converter	TPS54352PWP	Texas Instruments
1	TPS54354PWP	IC, 4.5-V to 20-V Input, 3-A Synchronous Converter	TPS54354PWP	Texas Instruments
1	TPS54356PWP	IC, 4.5-V to 20-V Input, 3-A Synchronous Converter	TPS54356PWP	Texas Instruments
1	TPS79301DBVR	IC, UltraLow-Noise, High PSRR, 200 mA, LDO	TPS79301DBVR	Texas Instruments
1	UA78M05IDCY	IC, Voltage Regulator, 5V, 500 mA	UA78M05	Texas Instruments

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2008, Texas Instruments Incorporated