

# **Adding Hysteresis to Supply Voltage Supervisor**

Sureena Gupta

PMP - Linear Power Applications

## **ABSTRACT**

Some applications require supply voltage hysteresis to keep a supply voltage supervisor (SVS) from falsely resetting the system due to voltage dips and glitches. This application report presents one solution for adding hysteresis to an SVS. The solution schematic is given along with component selection criteria and equations, such that readers can appropriately scale the solution to their own requirements. The document also includes a sample design implementation along with captured waveforms.

## **Contents**

1	Introduction .....	1
2	Design Solution .....	2
3	Circuit Analysis.....	2
4	Design Example .....	3
5	Conclusion.....	5
6	Reference.....	5

## **List of Figures**

1	General Schematic for a Supervisor With Increased Hysteresis .....	2
2	Simplified Sensing Schematic With RESET Pin Voltage Set to Zero .....	2
3	Simplified Sensing Schematic With RESET Pin Voltage Pulled Up to V2 via Rp.....	3
4	Schematic of Supervisor TPS3808 With External Hysteresis Resistor.....	4
5	Output Waveform Indicating Input Voltage and RESET Pin Voltage .....	5

## **1 Introduction**

As the input voltage to a system dips below the minimum required voltage for operation, the supply voltage supervisor (SVS) asserts a reset signal to turn off the system. When the system is turned off, current flow stops, and the voltage to the SVS may rise due to the decreased IR drop. The SVS then falsely turns the system back on. This erroneous reset lasts as long as the input voltage spikes exceed the threshold voltage, or the voltage dips fall below the threshold voltage. This condition can be undesirable for various applications. In order to avoid this undesirable condition due to erratic change in input voltage caused by a discharging battery or perhaps a noisy power supply, hysteresis can be added to the SVS circuitry. The addition of hysteresis implies that the SVS is turned off when the input voltage falls below the threshold voltage, but it is not turned back on until the input voltage rises above another predetermined threshold voltage. For instance, it can be equivalent to the voltage supplied by a newly replaced battery for a battery-supplied input voltage source.


For example, the TPS3808 inherently has some internal sensing voltage hysteresis, but the amount of hysteresis provided is not adequate to avoid the aforementioned erratic condition and needs external components to further add the required hysteresis. This application report presents the design procedures to be followed to add hysteresis to a SVS circuitry.

## 2 Design Solution

The internal hysteresis voltage of a TPS3808 is 6 mV on the sense pin (the hysteresis calculation is shown in [Section 4](#)), and it may not be adequate to meet the customer requirements. Hence, additional input voltage hysteresis can be added to the SVS.

The required additional input voltage hysteresis can be obtained by adding a feedback/hysteresis resistor at the sensing voltage node as shown in the solution schematic, [Figure 1](#).

The hysteresis resistor ( $R_h$ ) helps increase the hysteresis of input voltage by increasing the threshold voltage when the input voltage is increasing and helps decrease the threshold voltage when the input voltage is decreasing. This phenomenon is explained with simplified circuits in the next section.

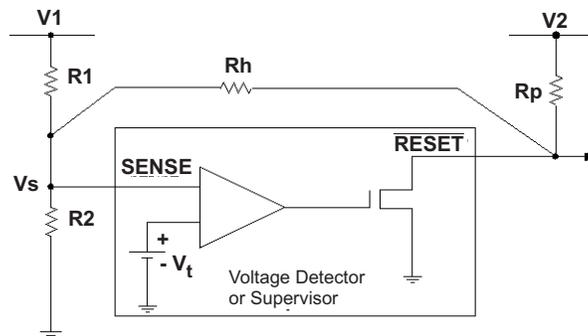

**Figure 1. General Schematic for a Supervisor With Increased Hysteresis**

Where:


- V1 is the input supply voltage;
- V2 is the voltage used that the output is pulled up to;
- Vs is the voltage at the sense pin;
- Vt is the threshold voltage or reference voltage;
- Rp is used as a pullup on the  $\overline{\text{RESET}}$  output;
- Rh is a resistor used to increase the hysteresis.

## 3 Circuit Analysis

The circuit operates in two conditions. The first condition is when the supplied input voltage ( $V_1$ ) is increasing, and the second condition is when the supplied input voltage is decreasing. Let the '+' sign indicate increasing voltage case and the '-' sign indicate decreasing voltage case.

### 3.1 CASE 1 – Input Voltage Increasing

The supplied input voltage increases during power up and is denoted by  $V_{1+}$ . In this case, the supervisor begins with an active low  $\overline{\text{RESET}}$  signal, so the voltage at the RESET pin is close to zero volt. For this case, assume it is zero volt, so the entire sensing schematic simplifies as shown in [Figure 2](#).

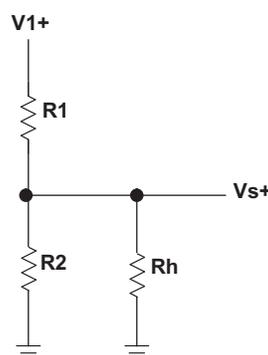

**Figure 2. Simplified Sensing Schematic With  $\overline{\text{RESET}}$  Pin Voltage Set to Zero**

When  $V_{s+}$  increases beyond  $V_{t+}$  (internal reference or threshold voltage), the supervisor lets  $\overline{\text{RESET}}$  float. The equation for the point at which the supervisor stops driving  $\overline{\text{RESET}}$  low is:

$$\frac{V_{1+} - V_{s+}}{R1} = \frac{V_{s+}}{R2} + \frac{V_{s+}}{R_h} \quad (1)$$

### 3.2 CASE 2 –Input Supply Voltage decreasing

The supplied input voltage decreases when the battery is discharging or due to a droop in supplied voltage and is denoted by  $V_{1-}$ . In this case, the supervisor is not asserting an active low  $\overline{\text{RESET}}$  signal, so the voltage at the  $\overline{\text{RESET}}$  pin is pulled up to  $V_2$  via  $R_p$ , and the sensing schematic simplifies as shown in Figure 3.

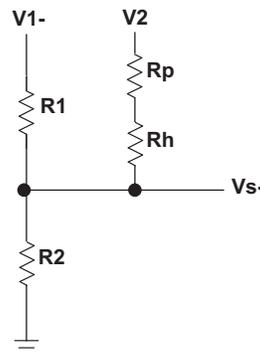


Figure 3. Simplified Sensing Schematic With  $\overline{\text{RESET}}$  Pin Voltage Pulled Up to  $V_2$  via  $R_p$

The equation for the trip point in this case is:

$$\frac{V_{1-} - V_{s-}}{R1} + \frac{V_2 - V_{s-}}{R_h + R_p} = \frac{V_{s-}}{R2} \quad (2)$$

## 4 Design Example


The aforementioned cases and equations can be illustrated using the TPS3808 as an example. This device has some inherent hysteresis; the two different threshold voltages depend on whether the supplied input voltage is increasing or decreasing. When the input voltage is increasing, the internal sensing threshold voltage is denoted by  $V_{s+}$  and when the input voltage is decreasing, the internal sensing threshold voltage is denoted by  $V_{s-}$ .

These threshold voltage values are listed in the data sheet ([SBVS103](#)). The data sheet indicates that the internal reference voltage  $V_t$  is set to 0.4 V, and the typical hysteresis is set at 1.5%  $V_t$ . Hence, the values can be deduced as:

$$\begin{aligned} V_{s-} &= 0.4 \text{ V} \\ V_{s+} &= 0.406 \text{ V} \end{aligned}$$

The amount of inherent hysteresis provided can be calculated as  $(V_{s+}) - (V_{s-})$ . For the TPS3808, the inherent internal hysteresis is approximately 6 mV. The amount of hysteresis (from the battery perspective) is  $(V_{1+}) - (V_{1-})$ , which is simply  $(V_{s+}) - (V_{s-})$  gained up through the resistor divider formed by  $R_1$  and  $R_2$ . This equates to 27 mV of hysteresis on a 1.8-V battery voltage ( $V_{1-}$ ).

Assume that a system powered by two AA batteries needs to be reset when the battery voltage falls below 1.8 V. Also, assume that the system must not come out of reset until the battery voltage is above 2 V. This condition requires 200 mV of hysteresis, which is much greater than the 27-mV hysteresis provided by the TPS3808 device. Hence, additional hysteresis is required. The remaining section demonstrates the procedure to be followed to implement the required additional hysteresis.

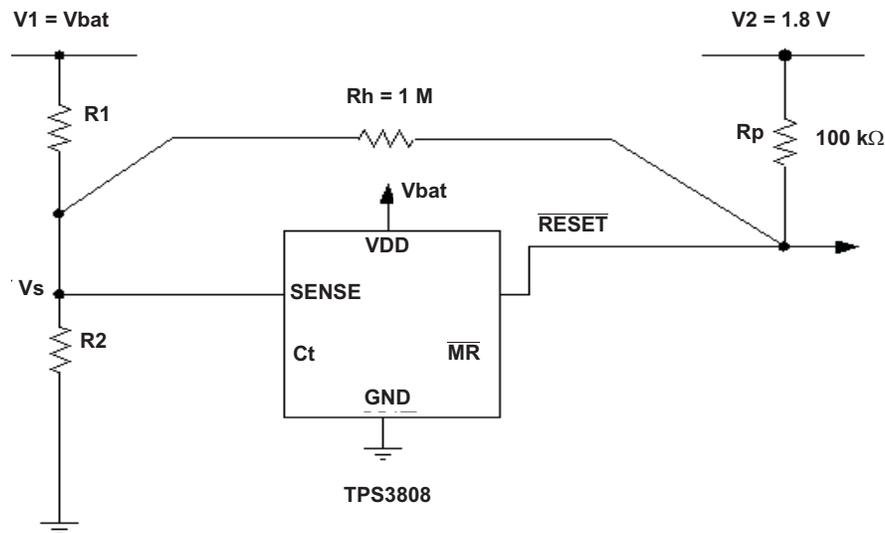

**Figure 4. Schematic of Supervisor TPS3808 With External Hysteresis Resistor**

Using the SVS TPS3808, the circuit was connected as shown in [Figure 4](#). The values for different components were selected as per the requirements and are listed as follows:

$$\begin{aligned} V1+ &= 2 \text{ V} \\ V1- &= 1.8 \text{ V} \\ V2 &= 1.8 \text{ V} \end{aligned}$$

To solve the design problem, consider the seven variables and two equations. Five of the seven variables were selected in order to solve the two equations.

$V1+$  and  $V1-$  were selected to create the desired input supply voltage hysteresis as required by the system.

$V2$  was selected to pull up the output of the  $\overline{\text{RESET}}$  pin to the desired logic voltage levels.

$R_p$  is typically selected in tens of  $k\Omega$ .

Any other resistor can be selected out of the remaining three. Usually,  $R_h$  is a good choice with values in single-digit  $M\Omega$ . Typically,  $R_h$  is a large value.

When designing the resistors  $R_h$  and  $R_2$ , consider that as  $R_2$  increases,  $R_h$  increases. Typically,  $R_h$  is a large-valued resistor (can be more than  $1 M\Omega$ ). Because resistors larger than  $1 M\Omega$  are uncommon and cost more than regularly available resistors, it is a good practice to design  $R_h$  as  $1 M\Omega$  and then calculate resistor  $R_1$  and  $R_2$  values by simultaneously solving [Equation 1](#) and [Equation 2](#). On the other hand, selecting  $R_2$  with a higher resistance can help further reduce the quiescent current, which improves the device efficiency. However, a higher  $R_2$  resistance implies a large-valued resistor  $R_h$  ( $R_h > 1 M\Omega$ ). For this example, the following values were selected:

$$\begin{aligned} R_p &= 100 \text{ k}\Omega. \\ R_h &= 1 \text{ M}\Omega \end{aligned}$$

By solving [Equation 1](#) and [Equation 2](#), deduce the values for  $R_1$  and  $R_2$ .

After solving,

$$\begin{aligned} R_1 &= 102 \text{ k}\Omega \\ R_2 &= 26.7 \text{ k}\Omega \end{aligned}$$

The designed components were implemented on a printed-circuit board, and the output waveform was recorded as shown in Figure 5. The input voltage V1 is ramped between 1 V and 3 V, so that the designed operations can be observed. When  $V1+ = 2\text{ V}$ , (the circuit operation is initialized and after certain predetermined time delay  $T_d$  (20 ms in this case), the RESET pin voltage rises from 0 V to 1.8 V (V2). When the input voltage is decreasing and  $V1-$  falls below 1.8 V, the RESET pin voltage falls back to 0 V.

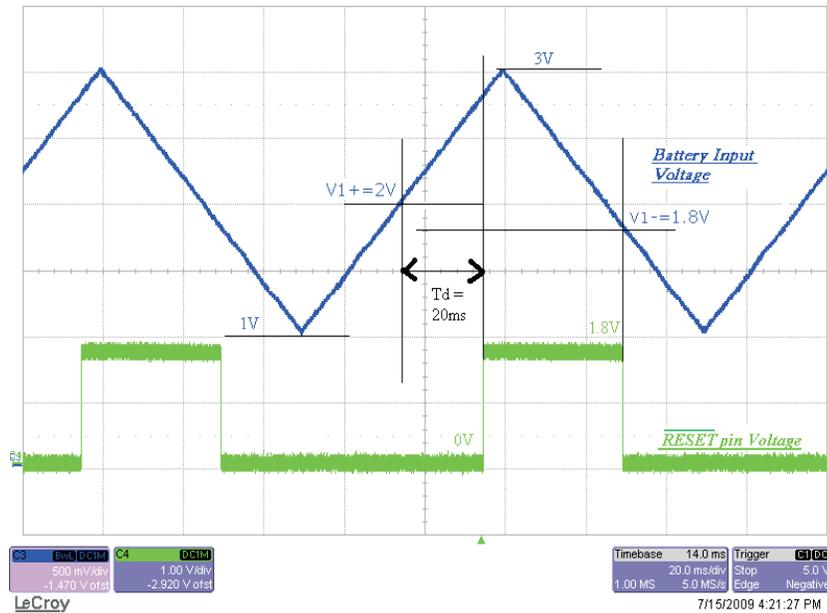


Figure 5. Output Waveform Indicating Input Voltage and RESET Pin Voltage

## 5 Conclusion

This application report presents a solution schematic for adding external hysteresis to the supply voltage supervisors, along with the circuit analysis to clarify how to configure an SVS for this kind of application. Along with the appropriate equations, the design process can assist designers in tailoring a solution based on the required applications. A sample module using the TPS3808 was designed and implemented to guide the user through the procedure. A screen shot from the oscilloscope displays the required results.

In summary, this application report helps designers add supply voltage hysteresis to the SVS to meet customer application requirements.

## 6 Reference

TPS3808-EP, *Low Quiescent Current, Programmable Delay Supervisory Circuit* data sheet ([SBVS103](#))

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2009, Texas Instruments Incorporated