

TPS61020 Boost Converter Start-Up and Precharge

Bill Johns

PMP/Portable Power DC-DC Applications

ABSTRACT

The TPS61020 is a highly integrated, low-power, boost converter ideally suited for portable battery-powered equipment. To improve start-up performance from a power-limited source such as a battery, the TPS6102x family uses different steps and modes to reduce demand on the battery. This prevents the battery bus from sagging during start-up and improves start-up operation at low voltage.

Typical start-up behavior for a boost converter requires a large amount of current from the input bus to charge the output capacitor up to the output voltage, even with no load on the output. During no-load start-up, a typical boost converter operates at the main power-switch current limit to charge the output capacitor quickly. The TPS61020 main power-switch current limit is 1.5 A, which results in a 1.5-A input current at start-up. An input current this large presents problems for some input power sources.

Batteries have some internal resistance because resistance increases as the battery is discharged. This internal resistance combined with large peak currents at start-up causes the battery voltage to drop at start-up. If the battery bus voltage decreases below undervoltage lockout for the converter, the converter shuts down.

To prevent this large start-up current, the TPS6102x family uses a controlled start-up sequence with four operating phases to provide smooth start-ups.

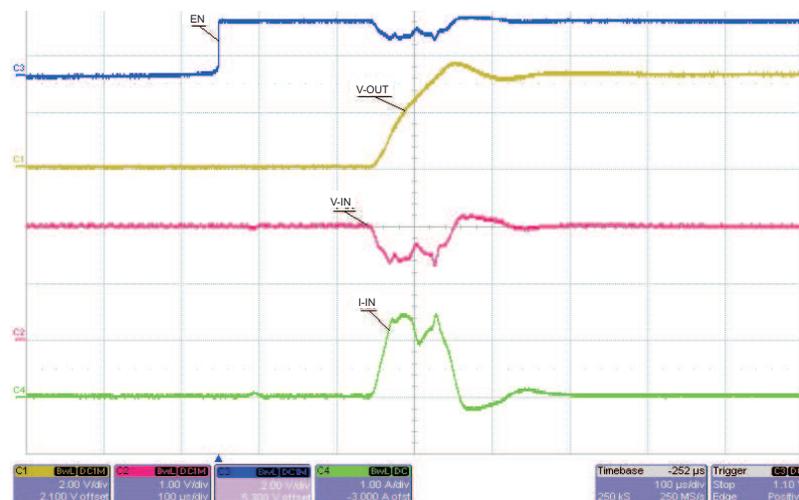


Figure 1. Standard Boost Converter Without Controlled Start-Up

Figure 1 shows a typical boost converter start-up from a battery at 2 V. This is a no-load condition; the output capacitor is the only load. A 0.5-Ω resistor has been added to the power supply input to simulate battery impedance. Note that the input current increases to 1.5 A for 100 μs, and the bus voltage decreases in response to the load.

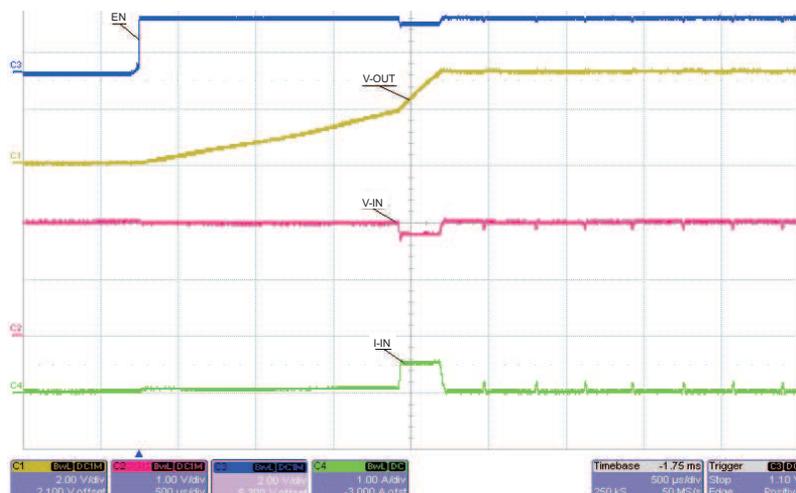


Figure 2. TPS61020 Start-Up Current

Figure 2 shows the start-up of a TPS61020 converter in the same set up as Figure 1, with an input voltage of 2 V and a battery impedance of 0.5 Ω . Note that the TPS61020 soft-start circuitry keeps the peak input current below 600 mA, thereby minimizing the input bus voltage drop.

Start-Up Phases

The TPS61020 implements four distinct operating modes during start-up. These modes are designed to minimize current draw from the input bus during start-up. Each of the phases provides limited output current to reduce input current. As output voltage increases, the converter switches to the next phase. The subsequent phases have higher output current in the final phase, when the device transition to full current limit output voltage is near the set point.

Table 1. Start-Up Phases for TPS61020

PHASE	ENTER	EXIT	COMMENT
Phase 1	EN or UVLO	Vout ~ Vin	Limited current to output capacitor
Phase 2	Vout ~ Vin	Vout ~1.4 V	Switching starts at fix 50% duty cycle
Phase 3	Vout ~ 1.4 V	Set point -1.6%	Switch current limit reduce to 40%
Normal operation	Set point - 1.6%		Switch current limit to normal

Phase 1 Precharge

Precharge is the first phase of start-up. During precharge, the TPS61020 delivers a constant current to its output capacitor. The constant current linearly charges up the output capacitor to approximately V_{in} . The TPS61020 does not switch during precharge. This eliminates the large inrush currents present in standard boost converters when the input bus is directly connected to the output capacitor through the synchronous rectifier. Precharge is implemented by setting the internal synchronous rectifier FET connected between the SW pin and the Vout pin into its linear region. TPS61020 enters precharge after the device is enabled from EN or UVLO. The TPS61020 remains in precharge until the output voltage increases near the input voltage, approximately at input voltage of 0.1 V.

Precharge current is not a fixed value but is determined by input voltage and to a lesser degree by output voltage.

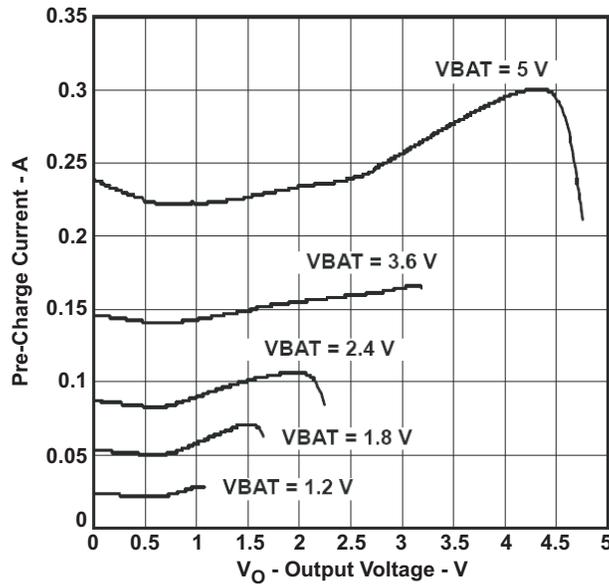


Figure 3. Short-Circuit Precharge Current

Phase 2 Fixed 50% Duty Cycle

Fixed 50% duty cycle is the second phase of start-up; this is an optional step that does not have to be used. During this mode, the converter begins switching but at a fixed 50% duty cycle. Output voltage during this phase increases from V_{in} to 1.4 V. By switching at a fixed 50% duty cycle, an inherent current limit is set by the rate of rise of the inductor current and rate of discharge of the inductor current. If the input voltage is above 1.4 V, then Phase 1 increases output voltage to 1.4 V and Phase 2 is not required; the device switches directly from Phase 1 to Phase 3.

Phase 3 SW-Limit to 40%

SW Limit to 40% is the third and final phase of start-up. This mode starts at about 1.4 V and ends when output voltage is at 1.6% of the set point. Phase 1 or Phase 2 has increased the output voltage, and it has reached a minimum of 1.4 V. The main power switch current limit is reduced to 40% of nominal value, from 1.5 A to 600 mA.

Normal Operation — V_{out} is within 1.6% of the set point, and the switch current limit is set to normal.

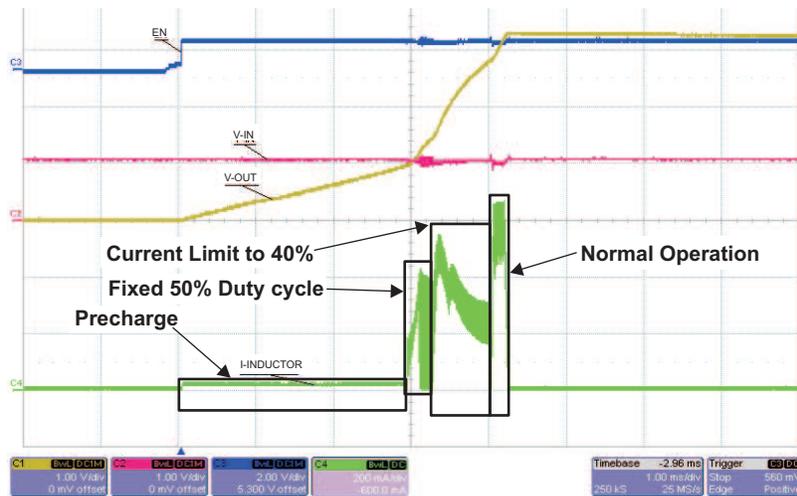


Figure 4. TPS61020 Start-Up From 1 V

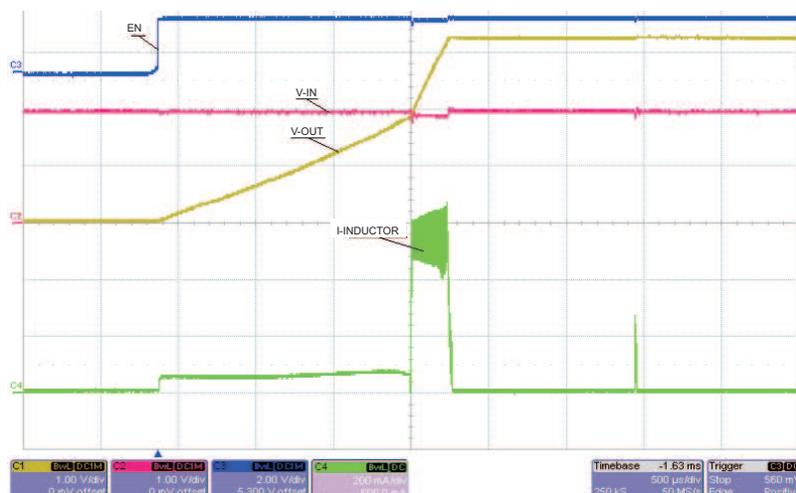


Figure 5. TPS61020 Start-Up From 2 V

Down Mode Start-Up

The TPS61020 down mode is used when V_{in} is higher than V_{out} . This is normally a condition when a buck converter is used to regulate the output, but the mode allows the TPS61020 to operate both above and below output voltage. For start-up in this condition, only the precharge phase mode is used. Normal mode and switching starts when output voltage is within 1.6% of set point. During precharge, the current into the output is approximately 100 mA.

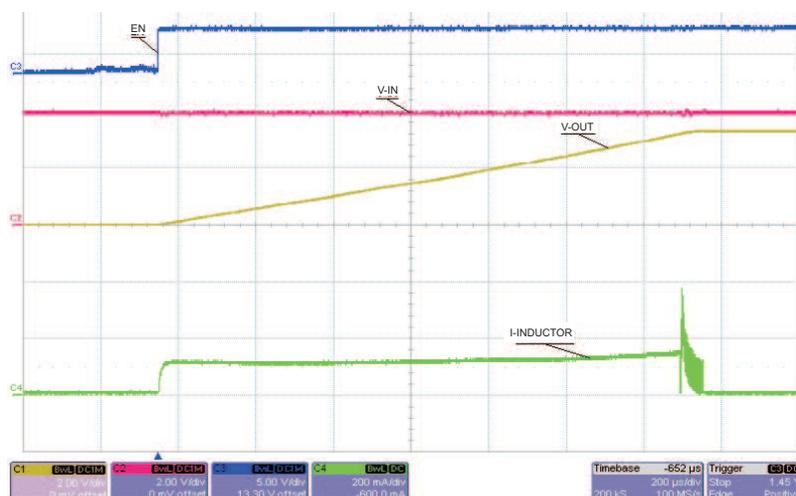


Figure 6. Down Mode Start-Up

Return to Precharge:

If an output overload occurs during normal operation, the converter returns to precharge, preventing an input bus overload. If output voltage decreases below the input voltage by more than 100 mV, the converter returns to the first start-up phase which is precharge. This restarts the start-up sequence again and the original entry and exit requirements apply.

During Down mode, an overload condition and return to precharge is a decrease in output voltage of 10% below set point.

Potential Problems:

To exit start-up and enter normal operation, the output voltage must rise to complete each phase and then move to the next. If the output voltage does not increase, the converter can become stuck in start-up mode. This problem often occurs due to a load on the output during start-up; the limited current is not enough to increase the output voltage to the next level. None of these phases has a time limit or timeout circuit with which to trigger shutdown or exit.

This problem has been seen most often in the precharge start-up phase where the converter acts as a current source. Typically, a resistive load on the output draws additional current and prevents the output from rising to the input. This problem is worst at low input voltage due to precharge current decreasing as input voltage decreases (see [Figure 3](#)).

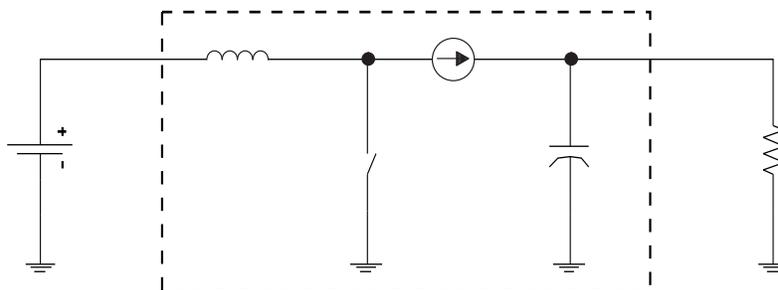


Figure 7. Configuration for Precharge

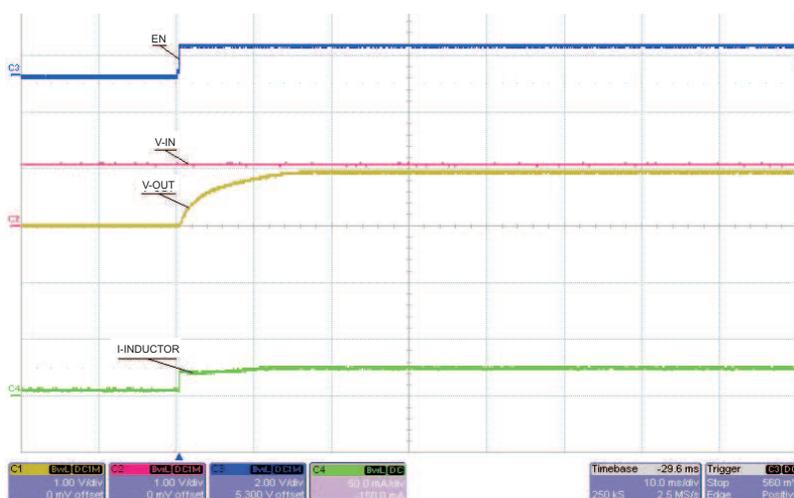


Figure 8. TPS61020 Start-Up Stuck in Precharge, Load 45 Ω

Possible Solutions:

Disconnection circuits have been used in some cases to resolve the start-up problem. These circuits disconnect the output load until the converter output voltage has increased. Often, it is unnecessary to hold the switch off the entire start-up cycle but only the precharge phase. This simplifies the control logic for the output MOSFET.

Conclusion

The TPS61020 provides a graceful start-up from a power-limited source. This is a good solution for some applications. However, the mechanism used to achieve this may present problems in other application and output-load conditions.

References

- (A) *TPS61020/24/25/26/27/28/29, 96% Efficient Synchronous Boost Converter* data sheet ([SLVS451](#))
- (B) *TPS61020EVM, High-Efficiency Synchronous Boost Converters User's Guide* ([SLVU100](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated