

Powering the Freescale™ i.MX25 Using the TPS65051

Sanjay Pithadia and Christian Hoefling

Power Management Products

ABSTRACT

This application report details the power requirements of the Freescale™ i.MX25 processor and how to power it using the [TPS65051](#), a highly-integrated power management unit (PMU) device from Texas Instruments. With its 3.3-V to 6.0-V input voltage range, output current up to 600 mA, and excellent efficiency (up to 95%), the TPS65051 PMU is an excellent choice to meet the requirements of the i.MX25.

Contents

1	Introduction	2
2	i.MX25 Requirements	2
3	Powering Freescale i.MX25 with the TPS65051: Reference Design	4
4	Detailed Design Information	8
5	Measurement Results	9
6	References	10

List of Figures

1	Recommended Power-Up Sequence	3
2	TPS65051 PMU Block Diagram	4
3	Reference Design Schematic	6
4	Power-Up Sequence: DCDC1, DCDC2, LDO1, LDO2.....	9
5	Power-Up Sequence: LDO1, LDO2, LDO3, LDO4	9
6	Efficiency (DCDC1).....	10
7	Efficiency (DCDC2).....	10

List of Tables

1	i.MX25 Voltage Requirements.....	2
2	TPS65051 Assignment of Converter Output Rails	5
3	List of Materials	7

1 Introduction

The reference design discussed in this report applies to the entire Freescale™ i.MX25 processor family. It provides all required analog and logic supply rails and the sequencing necessary to power up an i.MX25 processor.

2 i.MX25 Requirements

Table 1 lists the voltage requirements of the i.MX25 processor.

Table 1. i.MX25 Voltage Requirements⁽¹⁾

Parameter	Symbol	Min	Typ	Max	Units
Core supply voltage (at 266 MHz)	QV _{DD}	1.15	1.34	1.52	V
Core supply voltage (at 400 MHz)	QV _{DD}	1.38	1.45	1.52	V
Coin battery	V _{DD_BAT}	1.15	—	1.55	V
I/O supply voltage GPIO1 (NFC, CSI, SDIO)	NV _{DD_GPIO1}	1.75	—	3.6	V
I/O supply voltage GPIO2 (CRM, LCDC, JTAG, MISC)	NV _{DD_GPIO2}	3.0	3.3	3.6	V
I/O supply voltage DDR (Mobile DDR mode) (EMI1, EMI2)	NV _{DD_MDDR}	1.75	—	1.95	V
I/O supply voltage DDR (DDR2 mode) (EMI1, EMI2)	NV _{DD_DDR2}	1.75	—	1.9	V
I/O supply voltage DDR (SDRAM mode) (EMI1, EMI2)	NV _{DD_SDRAM}	1.75	—	3.6	V
USBPHY1 supply (HS) (USBPHY1_VDDA_BIAS, USBPHY1_UPLL_VDD, USBPHY1_VDDA)	V _{DD_USBPHY1}	3.17	3.3	3.43	V
USBPHY2 supply (FS) (USBPHY2_VDD)	V _{DD_USBPHY2}	3.0	3.3	3.6	V
OSC24M supply (OSC24M_VDD)	V _{DD_OSC24M}	3.0	3.3	3.6	V
PLL supply (MPLL_VDD, UPLL_VDD)	V _{DD_PLL}	1.4	—	1.65	V
Supply of touch screen ADC (NVCC_ADC)	V _{DD_TSC}	3.0	3.3	3.6	V
External reference of touch screen ADC	V _{REF}	2.5	V _{DD_tsc}	V _{DD_tsc}	V
Fusebox program supply voltage (FUSE_VDD)	FUSEV _{DD}	—	3.6	—	V

⁽¹⁾ See [Reference 1](#) for complete information.

2.1 Power-Up/-Down Sequencing

The i.MX25 processor consists of four major sections for the power-supply voltage: digital logic domains (V_{DDn}); I/O power supplies (NV_{DDx}); analog power supplies; and the fuse voltage supply ($FUSEV_{DD}$). These voltage groups can be integrated in several ways, depending on the operating mode and the requirements of the i.MX processor, as well as the specific application.

2.1.1 Power-Up Sequencing

The recommended power-up sequence for the processor follows this order:

- Step 1. Assert Power-On-Reset (POR) (POR = low)
- Step 2. Turn on the core supply voltages and I/O power supplies (NV_{CCx})
- Step 3. Turn on all analog power supplies (V_{DDx}) and $FUSEV_{DD}$
- Step 4. Release POR (POR = high)

Figure 1 illustrates the recommended power-up sequence.

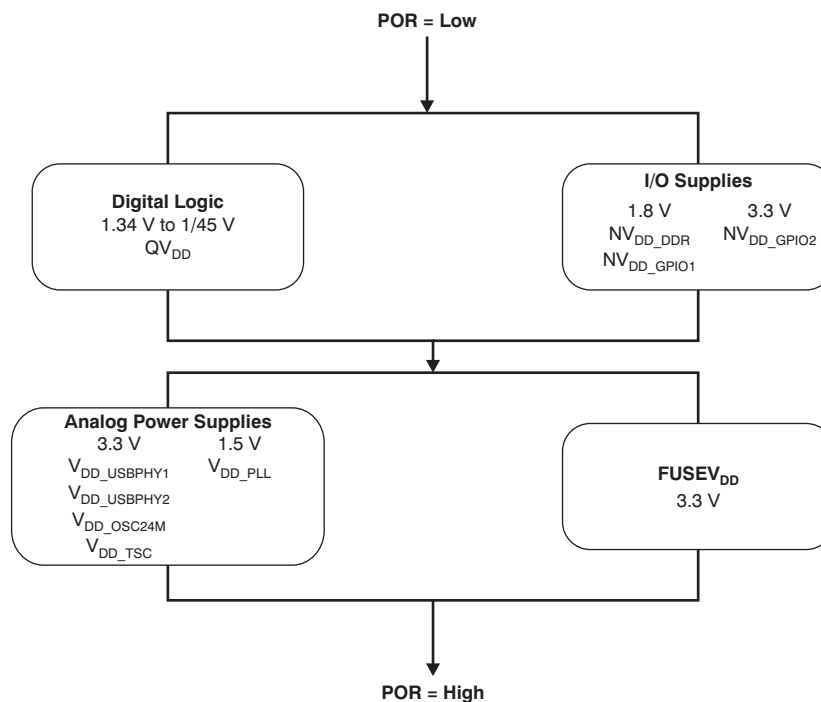


Figure 1. Recommended Power-Up Sequence

2.1.2 Power-Down Sequencing

The power-down sequence has no special requirements.

3 Powering Freescale i.MX25 with the TPS65051: Reference Design

The TPS65051 is an integrated power management device, suitable for applications that require multiple power rails. The TPS65051 provides two highly efficient, 2.25-MHz step-down converters as well as four low dropout (LDO) regulators. The block diagram of the TPS65051 is shown in Figure 2.

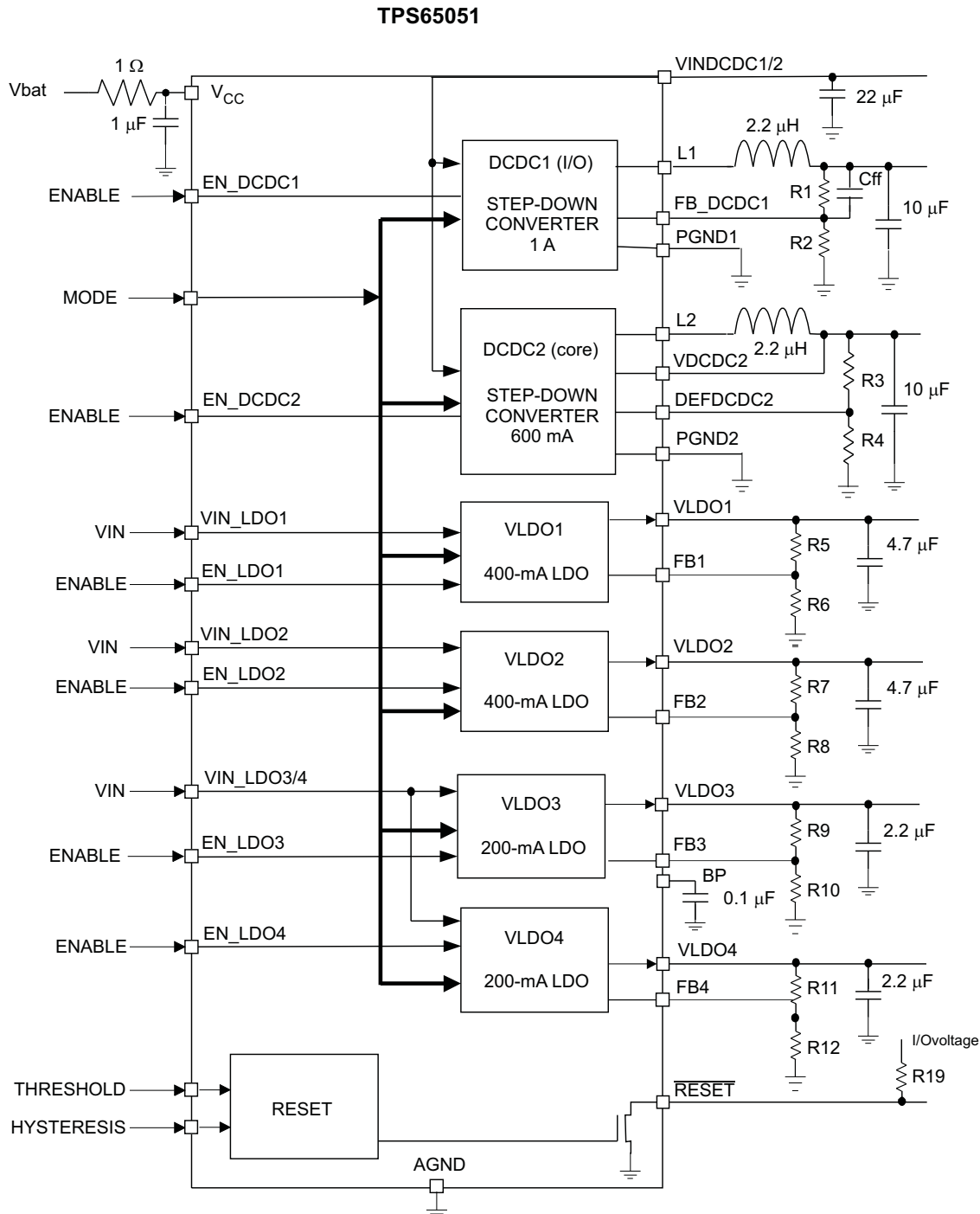


Figure 2. TPS65051 PMU Block Diagram

Following the pattern shown in [Figure 1](#), a power-up sequence that consists of two groups was configured and applied in the power reference design conceived for this report.

The first group in the power-up sequence consists of all rails supplied by DCDC1, DCDC2, and the LDO LDO1. The second group contains LDO2, LDO3, and LDO4. [Table 2](#) describes the converter output rail assignments for the TPS65051.

Table 2. TPS65051 Assignment of Converter Output Rails

Supply Rail		Voltage (V)	TPS65051 Output	Sequencing Order
QV _{DD}	Core	1.45	DCDC1	1
NV _{DD_GPIO1} , NV _{DD_GPIO2} , NV _{DD_SDRAM}		3.3	DCDC2	1
NV _{DD_MDDR} , NV _{DD_DDR2}		1.8	LDO1	1
V _{DD_USBPHY1} , V _{DD_USBPHY2} , V _{DD_OSC24M} , V _{DD_TSC} , V _{REF}		3.3	LDO2	2
FUSEV _{DD}		3.6	LDO3	2
V _{DD_PLL}		1.6	LDO4	2

Figure 3 illustrates the reference design schematic.

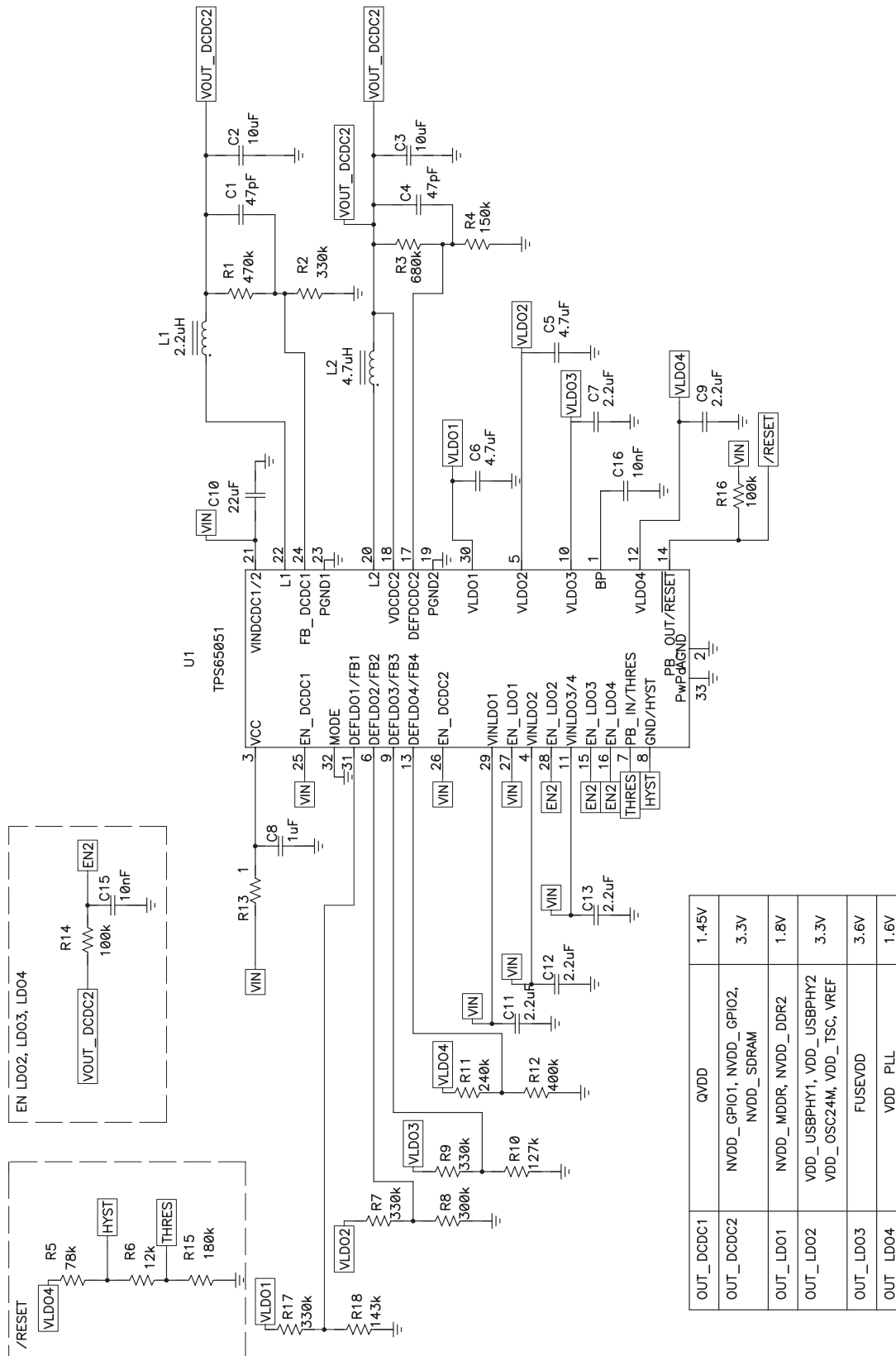


Figure 3. Reference Design Schematic

Table 3 provides the parts list for the reference design.

Table 3. List of Materials

Count	Ref Des	Value	Description	Size	Part No	Mfr
2	C1, C4	47 pF	Capacitor, ceramic, 50V, COG, 5%	0603	C1608C0G1H470J	TDK
1	C10	22 μ F	Capacitor, ceramic, 6.3 V, X5R, 20%	0805	GRM21BR60J226ME39L	Std
2	C15, C16	10 nF	Std	0805	Std	muRata
2	C2, C3	10 μ F	Capacitor, ceramic, 10 V, X5R, 20%	0805	GRM188R60J106ME47D	muRata
2	C5, C6	4.7 μ F	Capacitor, ceramic, 10 V, X5R, 10%	0805	GRM21BR61A106KE19L	muRata
5	C7, C9, C11, C12, C13	2.2 μ F	Capacitor, ceramic, 6.3 V, X5R, 10%	0805	GRM188R60J225KE01D	muRata
1	C8	1 μ F	Capacitor, ceramic, 25 V, X5R, 10%	0805	GRM188R61E105KA12D	muRata
1	L1	2.2 μ H	Inductor, SMT, 1.3 A, 130 m Ω	0.118 x 0.118 inch	LPS3015-332ML	Coilcraft
1	L2	4.7 μ H	Inductor, SMT, 1.3 A, 130 m Ω	0.118 x 0.118 inch	LPS3015-332ML	Coilcraft
1	R1	470 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R10	127 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R11	240 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R12	400 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R13	1 Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
2	R14, R16	100 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R15	180 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R18	143 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
4	R2, R7, R9, R17	330 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R3	680 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R4	150 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R5	78 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R6	12 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	R8	300 k Ω	Resistor, chip, 1/16W, 1%	0603	Std	Std
1	U1	TPS65051	IC, 2.25-MHz Dual Step-Down Converter with Four Low-Input Voltage LDOs	QFN-32	TPS65050/51	TI

4 Detailed Design Information

QV_{DD} (1.45 V)

This rail is supplied by DCDC1.

The output voltage of DCDC1 is adjustable using an external voltage divider. Using Equation 4 from the [TPS65051 data sheet](#), for an output voltage of 1.45 V, the external voltage divider values can be calculated as shown:

$$R1 = 470 \text{ k}\Omega, R2 = 330 \text{ k}\Omega, C_{FF} = 47 \text{ pF}$$

QVDD is part of the first sequencing group. Therefore, the EN DCDC1 pin can be directly connected to VIN.

NV_{DD_GPIO1}, NV_{DD_GPIO2}, NV_{DD_SDRAM} (3.3 V)

This rail is supplied by DCDC2.

The output voltage of DCDC2 is also adjustable using an external voltage divider. Using Equation 5 from the [TPS65051 data sheet](#), for an output voltage of 3.3 V, the external voltage divider values can be calculated in the following way:

$$R3 = 680 \text{ k}\Omega, R4 = 150 \text{ k}\Omega, C_{FF} = 47 \text{ pF}$$

The rails NVDD_GPIO1, NVDD_GPIO2, and NVDD_SDRAM are part of the first sequencing group. EN DCDC2 can thus be directly connected to VIN.

NV_{DD_MDDR}, NV_{DD_DDR2} (1.8 V)

These rails are supplied by LDO1.

The output voltage of LDO1 is adjustable using an external voltage divider. Using Equation 9 from the [TPS65051 product data sheet](#), for an output voltage of 1.8 V, the external voltage divider values can be calculated in this way:

$$R5 = 240 \text{ k}\Omega, R6 = 300 \text{ k}\Omega$$

The rails NVDD_MDDR and NVDD_DDR2 are part of the first sequencing group. EN LDO1 can be directly connected to VIN.

V_{DD_USBPHY1}, V_{DD_USBPHY2}, V_{DD_OSC24M}, V_{DD_TSC}, V_{REF} (3.3 V)

These rails are supplied by LDO2.

The output voltage of LDO2 is adjustable using an external voltage divider. Using Equation 9 from the [TPS65051 product data sheet](#), for an output voltage of 3.3 V, the external voltage divider values can be calculated as shown:

$$R17 = 330 \text{ k}\Omega, R18 = 143 \text{ k}\Omega$$

The rails V_{DD_USBPHY1}, V_{DD_USBPHY2}, V_{DD_OSC24M}, V_{DD_TSC}, and V_{REF} are part of the second sequencing group. EN LDO2 is connected to the output of DCDC2. In addition there is an RC filter connected on EN LDO2 to make sure the second sequencing groups starts after DCDC2.

Generation of FUSEV_{DD} (3.6 V)

These rails are supplied by LDO3.

The output voltage of LDO3 is adjustable using an external voltage divider. Using Equation 9 from the [TPS65051 data sheet](#), for an output voltage of 3.6 V, the external voltage divider values can be calculated as following

$$R9 = 470 \text{ k}\Omega, R10 = 180 \text{ k}\Omega$$

The rail FUSEV_{DD} is part of the second sequencing group. EN LDO3 is connected to the output of DCDC2. In addition, there is an RC filter connected on EN LDO3 to ensure that the second sequencing groups starts after DCDC2.

Generation of V_{DD_PLL} (1.6 V at 200 mA)

These rails are supplied by LDO4.

The output voltage of LDO4 is adjustable using an external voltage divider. Using Equation 9 from the [TPS65051 product data sheet](#), for an output voltage of 1.6 V, the external voltage divider values can be calculated as shown:

$$R11 = 220 \text{ k}\Omega, R12 = 360 \text{ k}\Omega$$

The rail FUSEV_{DD} is part of the second sequencing group. EN LDO4 is connected to the output of DCDC2. In addition, there is an RC filter connected on EN LDO4 to make sure the second sequencing groups starts after DCDC2.

POR

The reset signal for the processor is generated using the integrated SVS onboard the TPS65051 PMU. The SVS monitors the last rail coming up in the power sequence. The last rail is OUT_LDO4 (that is, VDD_PLL). In the design, this rail is monitored; once it reaches 0.3 V, the RESET signal is generated.

5 Measurement Results

This section presents some of the measured performance results for this configuration.

 


Figure 4. Power-Up Sequence: DCDC1, DCDC2, LDO1, LDO2

 


Figure 5. Power-Up Sequence: LDO1, LDO2, LDO3, LDO4

 


Figure 6. Efficiency (DCDC1)

 


Figure 7. Efficiency (DCDC2)

6 References

1. i.MX25 Power Management Using the MC34704. (2009). Application note AN3820. Freescale Semiconductor, Inc.
2. [TPS65051](#) product data sheet. Texas Instruments ([SLVS710A](#)). Revised August, 2007.

Revision History

Changes from Original (February, 2010) to A Revision	Page
• Updated Figure 3	6
• Replaced Bill of Materials	7
• Corrected resistor names indicated is calculation of external voltage divider value	8

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated