

Using the TPS23753A (and family) with an External Error Amplifier

Jesus Efrain Gaxiola-Sosa/Martin Patoka

Power Interface

ABSTRACT

The TPS23753A, TPS23754, TPS23756, and TPS23757 are intended for applications that have primary-secondary isolation, because of this they do not contain an internal (control loop) error amplifier. Despite the lack of an internal error amplifier, it may be advantageous to use these parts in applications which do not require isolation due to their mix of features. These features include adapter ORing support, 12V supply operation, wider duty cycle, and multiple gate drivers. This Application Report shows how to use the common TLV431 as an error amplifier in conjunction with the this family of parts in a non-isolated flyback converter application.

Contents

| | | |
|---|--|----|
| 1 | Introduction | 2 |
| 2 | Converter Analysis | 2 |
| | 2.1 Isolated Converter | 2 |
| | 2.2 Non-Isolated Converter | 7 |
| 3 | Isolated vs. Non-Isolated Comparison | 10 |
| 4 | Conclusions | 11 |
| 5 | References | 11 |

List of Figures

| | | |
|----|---|----|
| 1 | TPS23753AEVM-001 Schematic | 3 |
| 2 | Isolated Circuit Transient Response..... | 4 |
| 3 | Isolated Circuit Startup | 4 |
| 4 | Power Stage Phase/Gain | 5 |
| 5 | Set up for the Power Stage Phase/Gain Measurement Using the Venable Windows Software 4.0 For MODEL 3120, Venable Instruments®, 2006 | 5 |
| 6 | Setup for EVM Phase/Gain Measurement..... | 6 |
| 7 | Isolated Circuit Phase/Gain..... | 6 |
| 8 | TL431 Error Amplifier Direct Interface..... | 7 |
| 9 | Modified TPS23753AEVM-001 Schematic | 8 |
| 10 | Non-isolated Circuit Transient Response | 9 |
| 11 | Non-isolated Circuit Startup | 9 |
| 12 | Non-isolated Circuit Phase/Gain | 10 |
| 13 | Isolated vs Non-isolated Transient Response | 10 |
| 14 | Isolated vs Non-isolated Circuit Startup | 11 |

1 Introduction

The TPS23753A and TPS23757 provide an IEEE 802.3-2008 (or IEEE 802.3at type 1) Power over Ethernet (PoE) interface and dc/dc controller for Powered Devices (PDs) that use up to 13 W. Examples of PDs are Voice-over-IP (VoIP) Phones and wireless access points (WAP). The TPS23754 and TPS23756 provide an IEEE 802.3at type 2 Power over Ethernet (PoE) interface and dc/dc controller for Powered Devices (PDs) that use up to 25.5 W. The most common dc/dc converter topologies used in PDs are the isolated flyback converter, and active-clamp forward converter.

Isolation between the Ethernet wiring and all other potentials is required by IEEE 802.3 (functional requirement), and isolation of customer accessible potentials from the Ethernet wiring is required by the IEC60950 standard (safety). Isolation is usually included to strictly meet the requirements, or for its implied added safety margin in cases where it is not certain. There are some applications that are clearly able to meet the requirements without isolation; an example would be an active-message sign that did not have any metallic I/O ports besides the Ethernet. Removing the isolation is perceived as reducing part count and thus cost. This application note shows how to use the TLV431 as an external error amplifier with this family of parts.

The TPS23753AEVM-001 (HPA304) board is used as a readily available tool to demonstrate the adaptation of an isolated topology to a non-isolated one. The stock EVM control is characterized, then modifications are made and the same characteristics are measured. We have selected load transient response, startup, and loop gain/phase as our criteria. The general technique applies to the whole family as they all use the same control (CTL) and pulse-width-modulation topology.

2 Converter Analysis

2.1 Isolated Converter

[Figure 1](#) is the schematic for the TPS23753A-001 EVM. This design is a 250kHz, 7 W flyback converter with a diode output rectifier. It operates in both continuous and discontinuous modes depending on the output loading. The TPS23753A, U1, provides the pulse-width modulation (PWM), primary MOSFET current sense comparator, and slope compensation for current-mode stability. The TLV431, U3, acts a reference and error amplifier to provide the 5 V output regulation. The control-loop isolation is provided by U2, an optocoupler. Control loop compensation is provided by C11, C13, R16, R12, R11, R21, and C12. A softstart circuit comprised of R13, D9, C14 controls the turn-on rate and eliminates output voltage overshoot at turn-on.

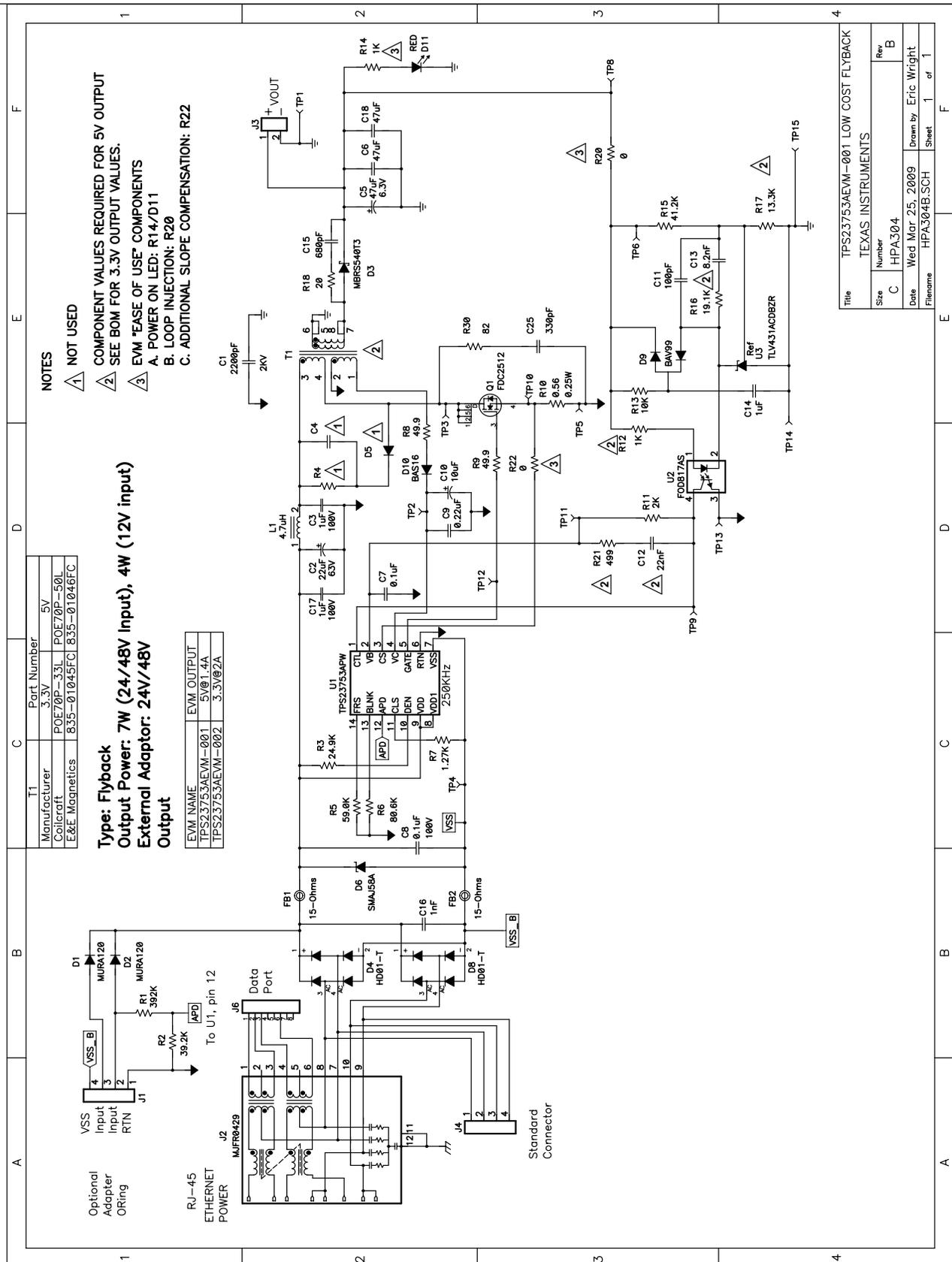


Figure 1. TPS23753AEVM-001 Schematic

Figure 2 shows the transient response of the isolated flyback converter with an input voltage of 57V and 200Hz pulsed load current (I_{LOAD}). The two cases are a 0.6 A to 1.4 A load step to show Continuous Conduction Mode (CCM) operation and 0.1 A to 0.6 A step to show the behavior of the circuit in and out of Discontinuous Conduction Mode (DCM).

As can be observed V_{OUT-PP} , is 240 mV in CCM and 220 mV in DCM about the desired output voltage for their respective I_{LOAD} changes. When I_{LOAD} steps up (down) V_{OUT} goes down (up) as a result of the ESR and ESL of the output capacitor, current-mode operating point, and loop response. V_{OUT} returns into regulation once the feedback loop responds and corrects the perturbation. Transient response is often used as an indication of loop stability.

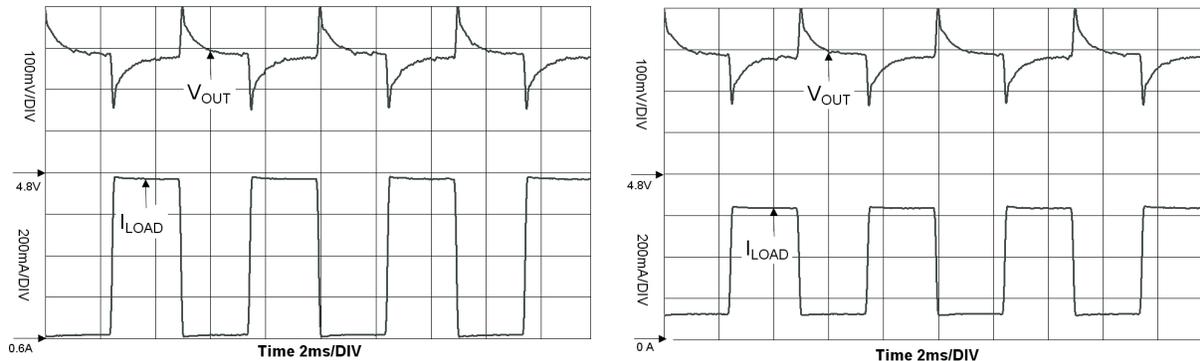


Figure 2. Isolated Circuit Transient Response

Figure 3 shows the converter output voltage during startup at 48 V in, for an I_{LOAD} of 1.4 A in the left hand side plot and at no-load in the right hand side plot. This test shows the ability of the error amplifier to control the output during startup and the action of the softstart circuit to avoid overshoots. Systems typically prefer monotonic rising supply voltages to avoid ambiguous states during startup. With maximum I_{LOAD} and with zero I_{LOAD} the circuit responds in a similar way and with the same speed (about 2 ms). The well controlled and smooth startup shows the system has adequate phase margin and controllability.

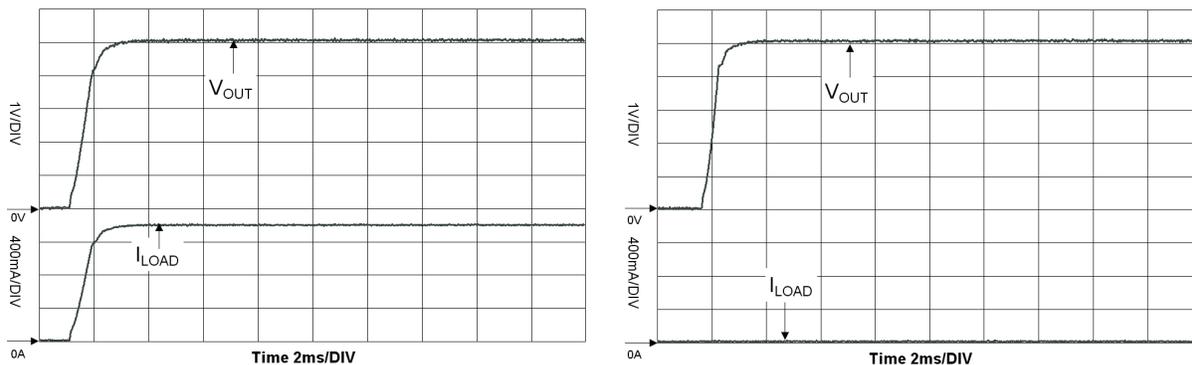


Figure 3. Isolated Circuit Startup

The Gain and Phase response of the Power Stage was obtained and is shown on Figure 4. Setup block diagrams used to perform these measurements are shown in Figure 5 and Figure 6. The box named "Power Stage" in Figure 6 includes part of the TPS23753A, input filter, flyback transformer, output filter, bias supply capacitors, and current sensing circuitry. The box named "PoE Interface" includes part of the TPS23753A, hotswap, Ethernet port, diode bridges, and PoE programming resistors. As shown in Figure 5, the gain/phase analyzer V1 input should be connected to TP9 and V2 to TP8. R20 is replaced by a 50Ω resistor and the two pins of the isolated oscillator interface are connected to TP8 and TP6 in order to add the test source oscillator. The ground of the primary and the secondary winding of the flyback transformer should be tied together as the test set voltage probes are referenced to the same ground.

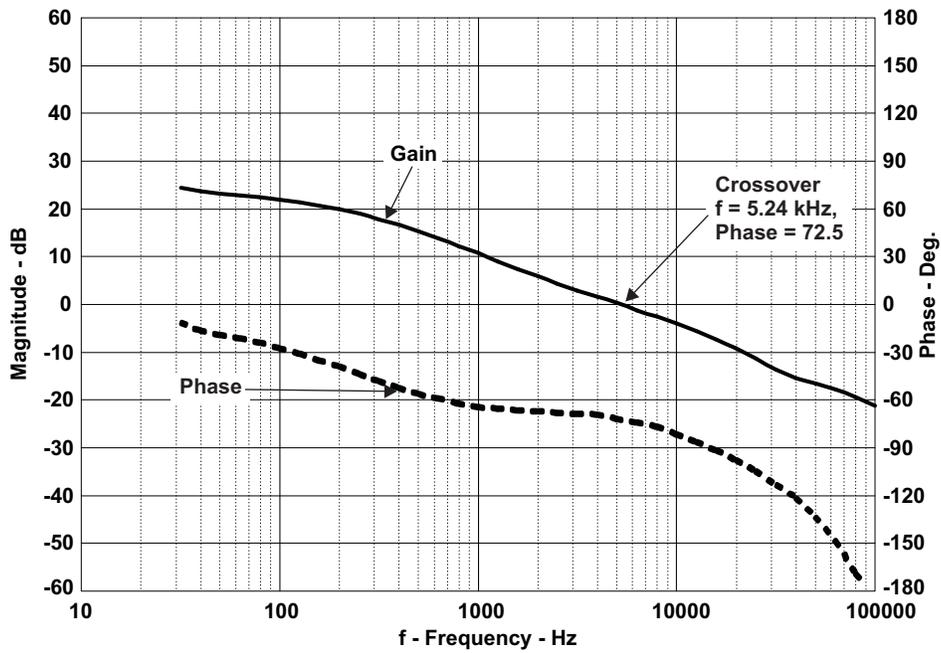


Figure 4. Power Stage Phase/Gain

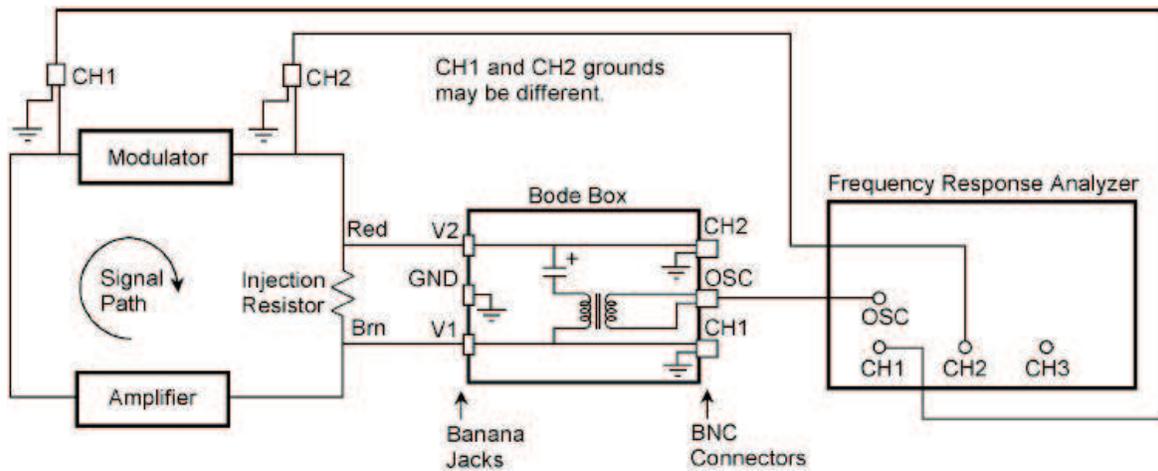


Figure 5. Set up for the Power Stage Phase/Gain Measurement Using the Venable Windows Software 4.0 For MODEL 3120, Venable Instruments®, 2006

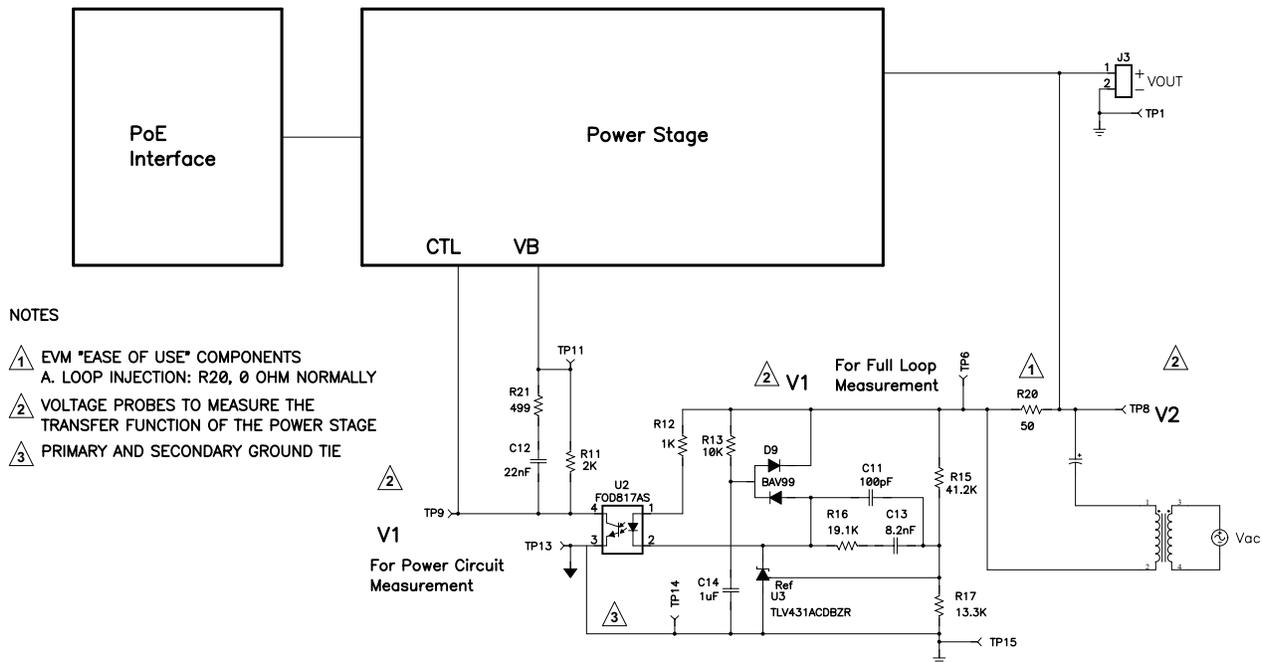


Figure 6. Setup for EVM Phase/Gain Measurement

Figure 7 shows the Gain and Phase response of the complete isolated converter with an input voltage of 57 V and a load current of 1 A. This was obtained with the setup of Figure 5 and Figure 6 by placing the analyzer V1 and V2 probes at TP6 and TP8 respectively. This plot is used to determine the crossover frequency and the stability of the circuit. The phase margin of the system at the gain crossover frequency (0 dB) is used as a measure of relative stability. This figure is a complement to the "quick" stability conclusions that can be made from the step response presented above. The designer should pick a phase margin that offers a good trade-off between speed and stability such as a critically damped 45° (second order system). In this case, the phase margin was 49.3° and the crossover frequency was 7.74 kHz. This means that the system is stable with a phase margin that is consistent with the step response.

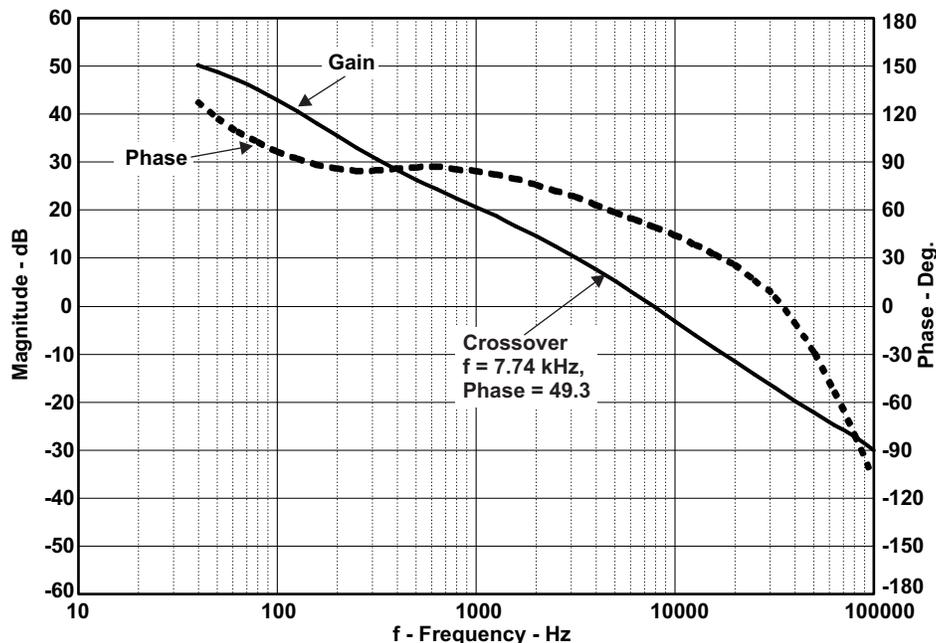


Figure 7. Isolated Circuit Phase/Gain

2.2 Non-Isolated Converter

In the non-isolated circuit, the error amplifier (U3) output is connected directly to the TPS23753A CTL input with no isolating optocoupler. This connection is shown in Figure 8. The optocoupler previously seen in the stock EVM has been removed, and the TLV431 has been directly interfaced to the TPS23753A.

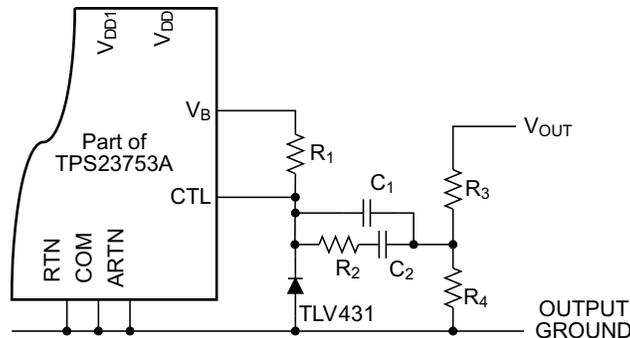


Figure 8. TL431 Error Amplifier Direct Interface

These modifications were made to the stock circuit of Figure 1, and are shown in Figure 9. The changes made are enclosed in the box to the lower right portion of the schematic. Q2 was added, and a number of part-type values were changed.

The new version of the softstart circuit includes Q2, D9, R13, and C14. This non-isolated topology allowed removal of R21 and C12 because the direct V_{OUT} to CTL signal feedback through the optocoupler has been eliminated. This simplifies the analysis and implementation of the compensation. The results of Figure 4 were used to select the compensation elements C11, R16, C13.

An important point in this implementation is that the TPS23753A minimum zero duty cycle threshold is 1.3V. The regulation voltage of the TLV431, when connected with the adjust pin to the output (cathode) is 1.25 V typical and 1.258 V maximum. This permits the TLV431 to apply the full range of control to the TPS23753A CTL input.

The softstart circuit was redesigned to be responsive to the output voltage rise. To accomplish this, Q2 and C14 were added. D19 is a fast discharge for C14 when the output collapses, ensuring rapid reset of the softstart circuit.

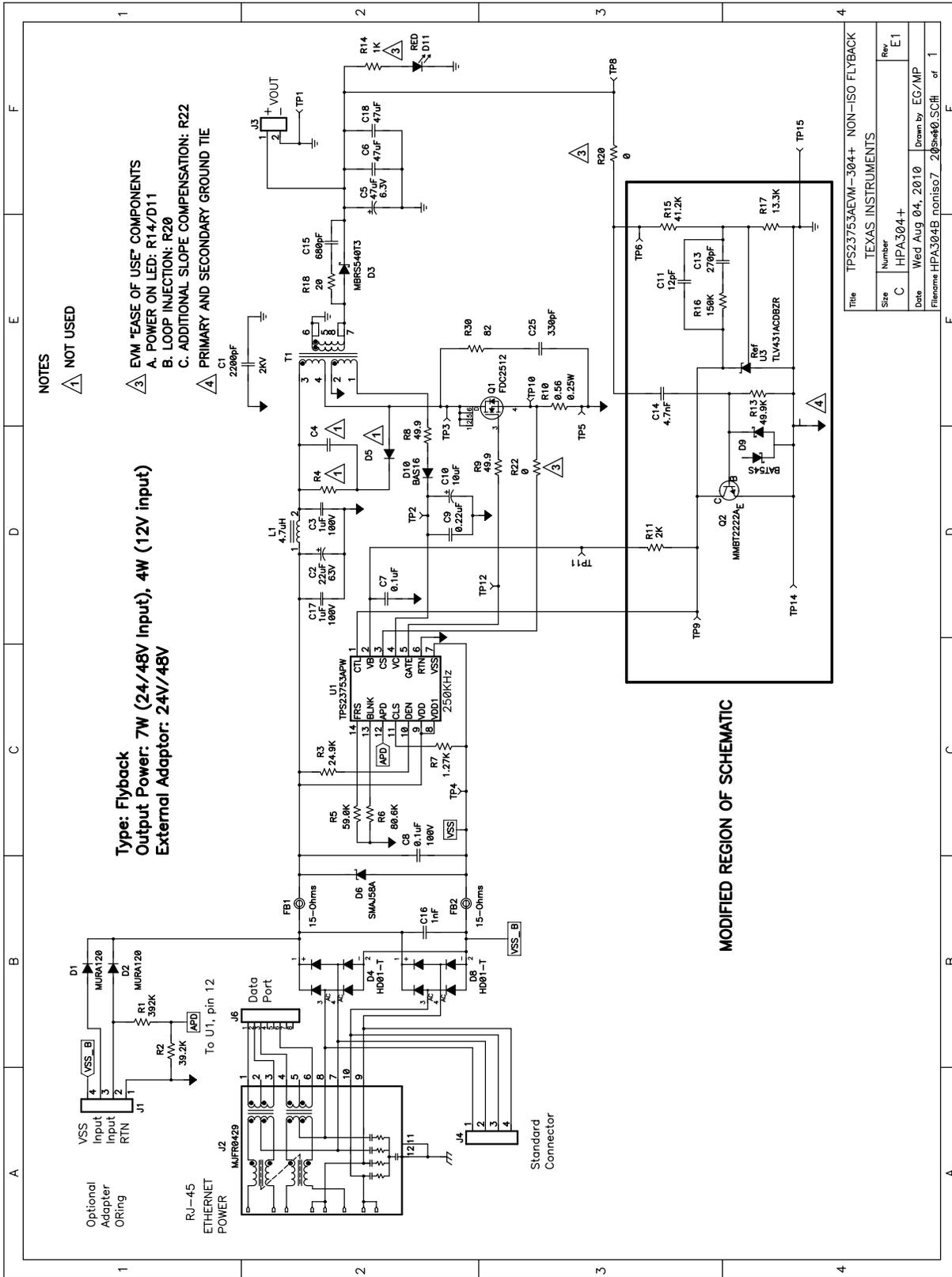


Figure 9. Modified TPS23753AEVM-001 Schematic

Figure 10 shows the transient response of the non-isolated flyback converter with an input voltage of 57 V and 200 Hz pulsed load current (I_{LOAD}). As in Figure 2, these measurements are done to show the behavior of the circuit in CCM and DCM. The figure on the left side shows a V_{OUT-PP} of 45 mV for a 0.6 A to 1.4 A I_{LOAD} step in CCM while the right hand side plot shows a V_{OUT-PP} of 40 mV for a 0.1 A to 0.6 A I_{LOAD} step.

The elimination of the isolating stage and its bandwidth limitations, along with somewhat more aggressive phase margin choices, results in substantially reduced transients from the isolated version of the preceding section.

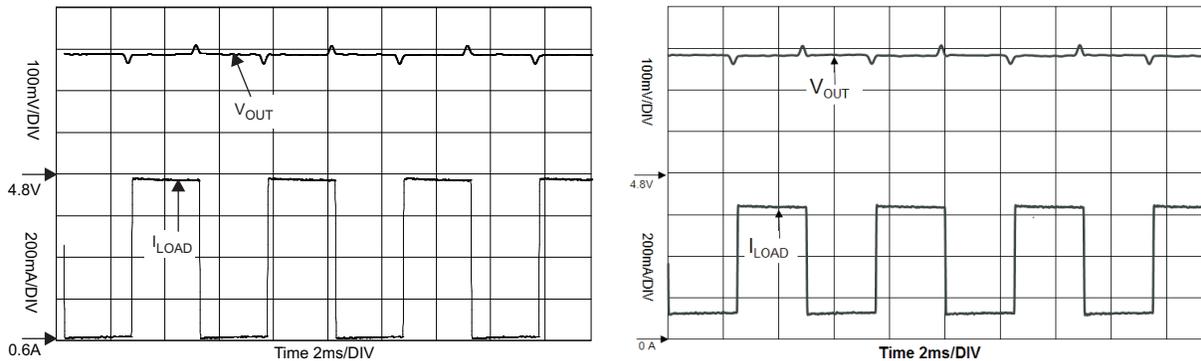


Figure 10. Non-isolated Circuit Transient Response

Figure 11 shows the converter output voltage during startup at 48 V in, for an I_{LOAD} of 1.4 A in the left hand side plot and at no-load in the right hand side plot. The results show a slightly faster rise of 1.5 ms vs. 2ms and sharper entry into regulation than those of Figure 3. The new compensation and the new start-up circuits improve the step response and start-up behavior.

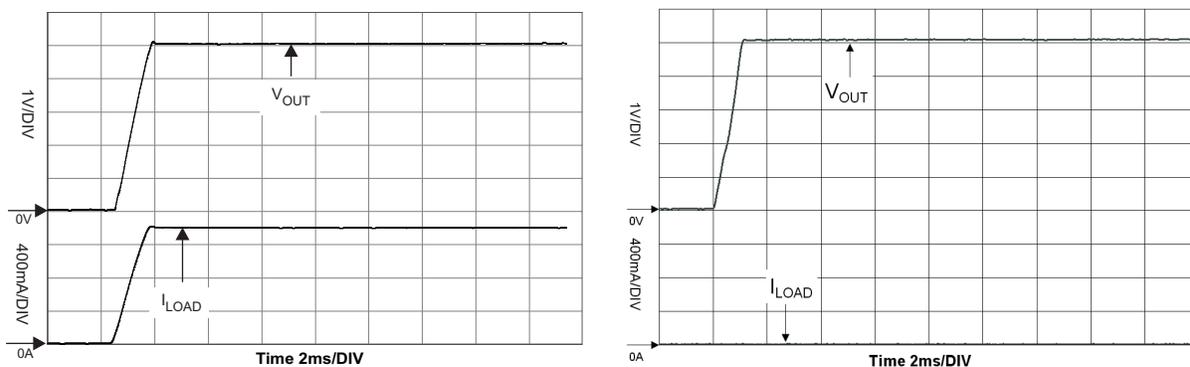


Figure 11. Non-isolated Circuit Startup

Figure 12 shows the Gain and Phase response of the system for an input voltage of 57 V and a load current of 1A. This plot is used to determine the crossover frequency and the stability of the circuit. In this case, the phase margin was 39.23° and the crossover frequency was 14.93 kHz. Notice that the crossover frequency is the double of the isolated case.

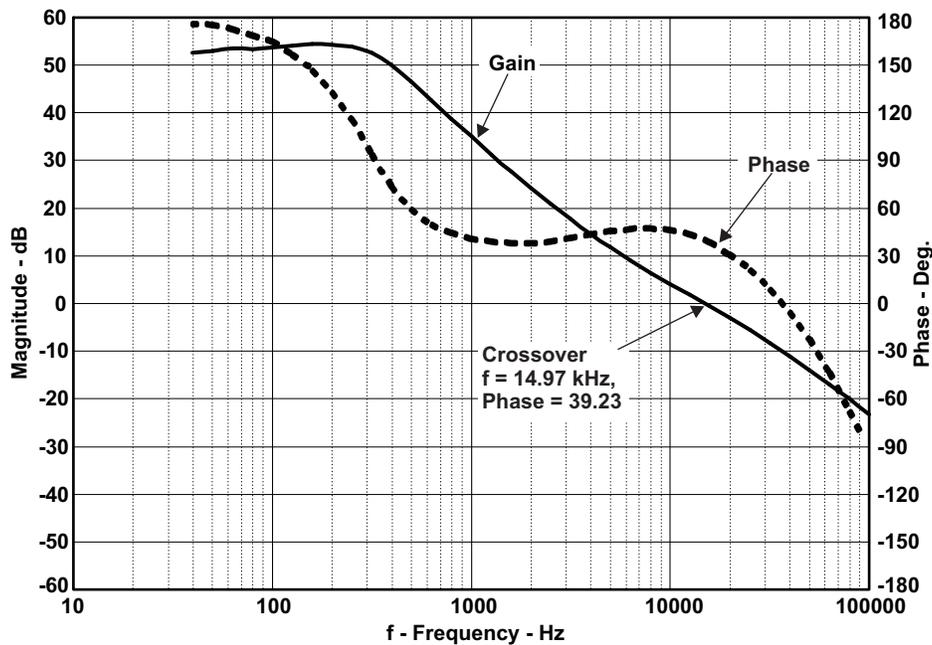


Figure 12. Non-isolated Circuit Phase/Gain

3 Isolated vs. Non-Isolated Comparison

This section compares the behavior of the circuit before (V_{OUT1}) and after (V_{OUT2}) the modifications applied to remove isolation.

Figure 13 shows the transient response with an input voltage of 57 V and 200 Hz pulsed load current (I_{LOAD}) from 0.6 A to 1.4 A (CCM) for the isolated (V_{OUT1}) and non-isolated (V_{OUT2}) converters in the left hand side plot. The plot on the right side shows the same response for I_{LOAD} pulsed from 0.1 A to 0.6 A (DCM).

Figure 14 shows the startup transient response (step response) for I_{LOAD} equal to 1.4 A for the isolated (V_{OUT1}) and non-isolated (V_{OUT2}) converters on the left side plot. The right-side plot shows the same response for the no load (I_{LOAD} equal to 0 A) case. Startup settling time is faster on the non-isolated circuit as can be expected from the wider bandwidth. This can be modified by tuning the startup circuit if desired.

A final recommendation is to make sure that the control block composed by the TLV431 and the associated components are isolated from any possible source of noise such as the drain of the switch or the anode of the output diode. When modifying the EVM, it became apparent that switching noise coupling into the TLV431 circuit was creating problems such as oscillations, dc offsets in the output, and erroneous phase/gain readings.

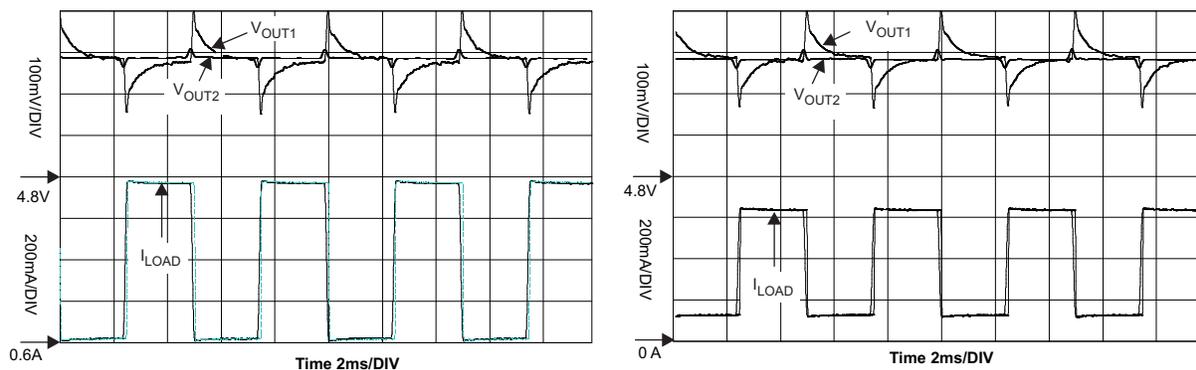


Figure 13. Isolated vs Non-isolated Transient Response

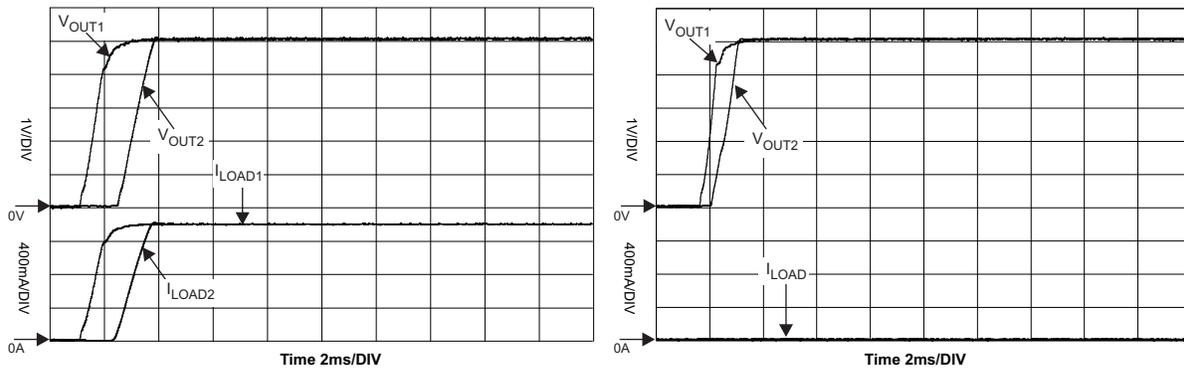


Figure 14. Isolated vs Non-isolated Circuit Startup

4 Conclusions

This application report demonstrates that the TLV431 can be used as an error amplifier for the family of parts including the TPS23753A. A comparison of the performance shows that a faster circuit is possible with the non-isolated configuration. In addition, a slightly different softstart circuit is demonstrated for use in the non-isolated design. This external error amplifier technique permits utilization of features unique to the TPS23753A, TPS23754, TPS23756, and TPS23757 such as adapter ORing support, 12V supply operation, wider duty cycle, and multiple gate drivers to be used in non-isolated converters.

5 References

1. *TPS23753AEVM-001 Evaluation Module for TPS23753A* ([SLVU315](#))
2. *TPS23753A IEEE 8.2.3 PoE Interface and Converter Controller with Enhanced ESD Immunity* ([SLVS933](#))
3. *TLV431 ... Low-Voltage Adjustable Precision Shunt Regulator* ([SLVS139](#))
4. *IEEE Std 802.3at™-2009*, IEEE, 2009
5. *IEC 60950-1, Information Technology Equipment – Safety – Part 1: General Requirements, Second Revision*, IEC, Geneva Switzerland, 2009
6. *Using the Venable Windows Software 4.0 For MODEL 3120*, Venable Instruments®, 2006

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | | Applications | |
|-----------------------------|--|----------------------------|--|
| Amplifiers | amplifier.ti.com | Audio | www.ti.com/audio |
| Data Converters | dataconverter.ti.com | Automotive | www.ti.com/automotive |
| DLP® Products | www.dlp.com | Communications and Telecom | www.ti.com/communications |
| DSP | dsp.ti.com | Computers and Peripherals | www.ti.com/computers |
| Clocks and Timers | www.ti.com/clocks | Consumer Electronics | www.ti.com/consumer-apps |
| Interface | interface.ti.com | Energy | www.ti.com/energy |
| Logic | logic.ti.com | Industrial | www.ti.com/industrial |
| Power Mgmt | power.ti.com | Medical | www.ti.com/medical |
| Microcontrollers | microcontroller.ti.com | Security | www.ti.com/security |
| RFID | www.ti-rfid.com | Space, Avionics & Defense | www.ti.com/space-avionics-defense |
| RF/IF and ZigBee® Solutions | www.ti.com/lprf | Video and Imaging | www.ti.com/video |
| | | Wireless | www.ti.com/wireless-apps |

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated