

Efficiency Evaluation TPS65381-Q1

Michael Wendt

ABSTRACT

The TPS65381 is a multi-rail power supply designed to supply microcontrollers in safety critical applications, such as those found in automotive functions. The device supports Texas Instruments' TMS570LS series 16/32-Bit RISC Flash MCU and other microcontrollers with dual-core lockstep (LS) or loosely coupled (LC) architectures .

The TPS65381 integrates multiple supply rails to power the MCU, CAN, or FlexRay, and an external sensor. An asynchronous buck switch-mode power-supply converter with an internal FET converts the input battery voltage to a 6-V pre-regulator output. This 6-V output supplies the other regulators. Furthermore, the device supports wake-up from IGNITION or wake-up from a CAN transceiver. A fixed 5-V linear regulator with internal FET is integrated as a CAN supply. A second linear regulator with an internal FET regulates the 6 V output to a selected 5-V or 3.3-V MCU IO voltage. The TPS65381 is comprised of a linear-regulator controller with external FET and resistor divider, regulating the 6 V output to an externally adjustable core voltage between 0.8 V and 3.3 V.

For more information see the TPS65381-Q1 datasheet, [SLVSBC4](#).

The efficiency of the buck and boost regulators is important for the efficiency and thermal design of the system. The results of the efficiency measurement are shown in [Section 5](#).

Contents

1	Efficiency Test TPS65381	2
2	Efficiency Test Setup	2
	2.1 Efficiency Test Setup VDD6 BUCK	2
3	The Test Flow	2
4	Application Data Overview	3
5	Test Results	3
	5.1 VDD6 BUCK Efficiency	3
6	Efficiency Test Summary	3

List of Figures

1	Efficiency Test Setup for VDD6 BUCK.....	2
2	Efficiency Results VDD6 BUCK.....	3

1 Efficiency Test TPS65381

The efficiency of a DC-DC converter is the output power divided by the input power and typically provided as a percentage. The TPS65381 has a buck regulator, VDD6 BUCK. An external power supply, such as a car battery, supplies this buck regulator. The output of the VDD6 BUCK regulator is the supply of the regulators VDD5, VDD3/5, VDD1 and is also used to supply VSOUT1.

The standard method is used to measure the efficiency of the VDD6 BUCK regulator. This method calculates the efficiency by a standard way by measuring the input power and the output power. Because the VDD5, VDD3/5, and VDD1 regulators are supplied from VDD6 BUCK, the efficiency measurement includes the current consumption of the VDD5, VDD3/5 and VDD1. These regulators cannot be separated because the TPS65381 is a safety device. The regulators have a minimum internal-load current to ensure the stability of the regulator without external load. This load current creates a failure in the efficiency measurement of the VDD6 Buck regulator and results in a lower efficiency than when the VDD6 BUCK regulator measured without internal load.

2 Efficiency Test Setup

2.1 Efficiency Test Setup VDD6 BUCK

Figure 1 shows the test set up.

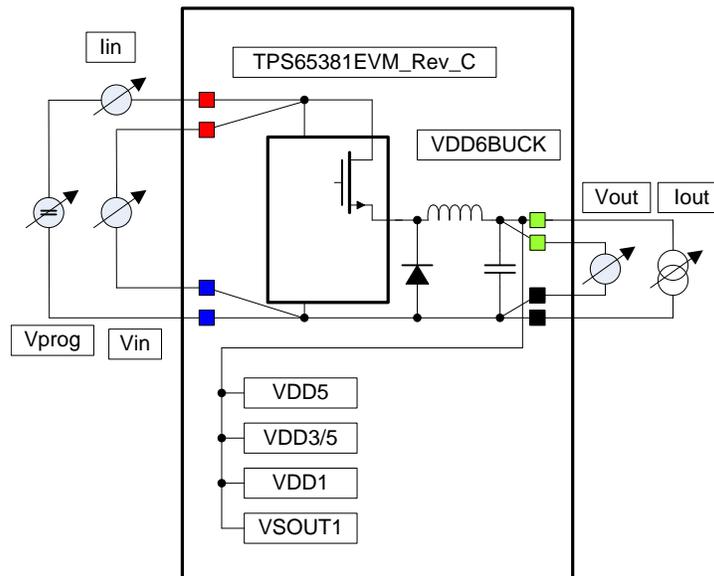


Figure 1. Efficiency Test Setup for VDD6 BUCK

3 The Test Flow

In order to perform the test, the device is placed on the TPS65381EVM (see the EVM user's guide, [SLVU847](#)).

An external lab supply, V_{prog} , supplies the board and DUT. The input current is measured with an ammeter I_{in} . To ensure the correct input voltage measurement an additional voltmeter is used to measure V_{in} .

A source meter creates the load current I_{out} . While another voltmeter the output voltage measures V_{out} .

While changing the output load current I_{out} from 0 to the maximum current (1.3 A), the input voltage (V_{in}), the input current (I_{in}), and the output voltage (V_{out}) are measured. Out of the measurement results the efficiency was calculated for every operation point. The efficiency was tested at three different input voltages for V_{prog} : 7 V, 13.8 V, and 28 V.

Figure 2 shows the test results.

4 Application Data Overview

Board		TPS65381EVM_Rev_c
Vprog		7 V 13.8 V 28 V
Temperature		Room temperature at approximately 25°C
VDD6 Buck	Vout	6 V
	Iload	0 A to 1.3 A
VDD5	Vout	5 V
	Iload	0 A
VDD3/5	Vout	5 V
	Iload	0 A
VDD1	Vout	1.8 V
	Iload	0 A
VSOUT1	Vout	5 V
	Iload	0 A

5 Test Results

5.1 VDD6 BUCK Efficiency

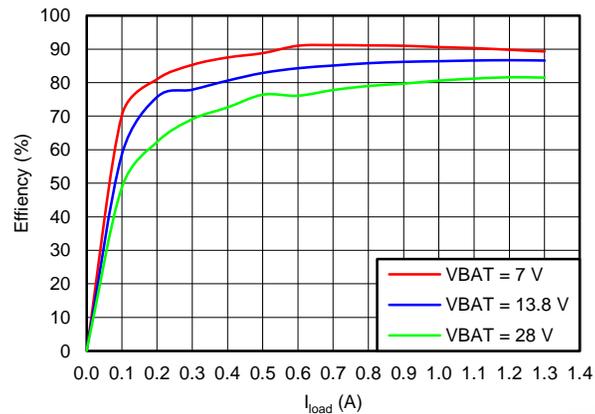


Figure 2. Efficiency Results VDD6 BUCK

6 Efficiency Test Summary

The efficiency tests of the VDD6 BUCK regulator as part of the TPS65381 device was performed with the following results:

- The buck regulator has an efficiency of 86% at a nominal operation point (Vprog = 13.8 V, Iload = 75% of Imax = 1A).
 - The real efficiency is higher because the VDD6 regulator is the supply of low-dropout regulators (LDOs). These LDOs cannot turn off and always use some load current which is not taken into consideration with this test.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com