

Device Behavior Under Slow VBAT Ramp-Down and Ramp-Up

*Samir Camdzic**Automotive, Safety and Industrial*

ABSTRACT

This application report explains device behavior under slow battery-supply voltage ramp-up and ramp-down conditions, based on device supply-rail configuration. Laboratory test results and device simulations results are included to support the analysis and device behavior.

Contents

| | | |
|---|-------------------------------|---|
| 1 | Undervoltage Transients | 2 |
|---|-------------------------------|---|

List of Figures

| | | |
|---|---|---|
| 1 | Battery Slow Ramp-Down Bench Measurement Result | 2 |
| 2 | Battery Slow Ramp-Down Simulation Result | 2 |
| 3 | Battery Slow Ramp-Up Bench Measurement Result | 3 |

1 Undervoltage Transients

Undervoltage transients can be observed on regulated supply outputs when one of the following occurs:

- The power-supply input (VBAT) of the device ramps down at a slow rate and reaches a voltage level of 6.3 V.
- The power-supply input (VBAT) of the device ramps up at a slow rate and reaches a voltage level of 6.6 V.

These transient impact the following regulated supplies:

- VDD5
- VDD3/5 when configured at 5 V
- VSOUT when configured as 5 V or higher

The VDD3/5 undervoltage transient causes a system-reset event (the NRES output is driven low) and disables the EN_DRV output.

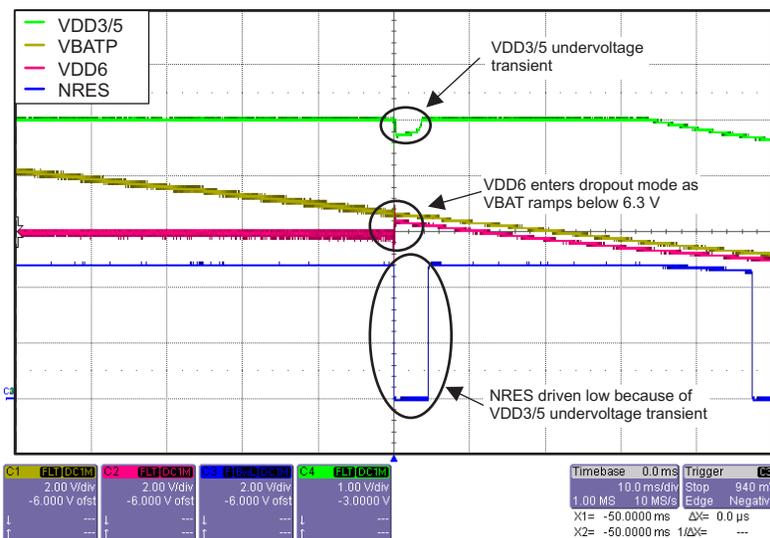


Figure 1. Battery Slow Ramp-Down Bench Measurement Result

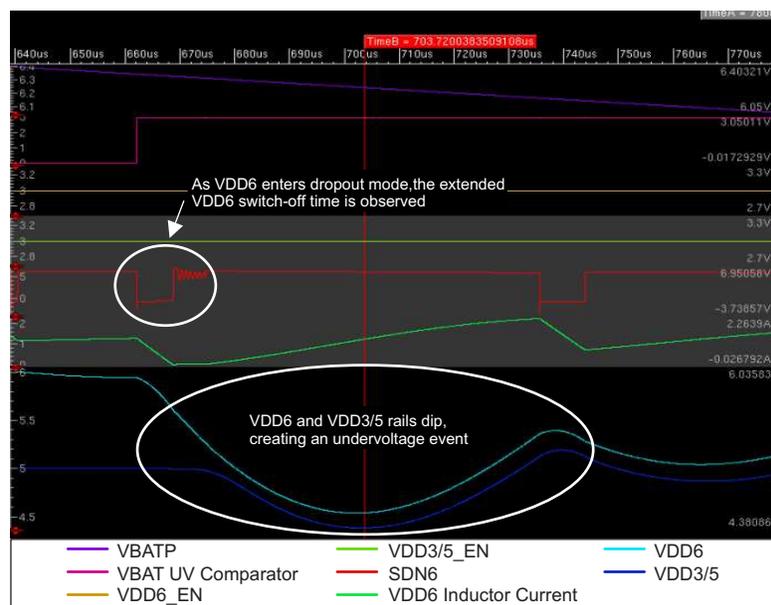


Figure 2. Battery Slow Ramp-Down Simulation Result

The VDD6 capacitor is discharged because of the extended VDD6 switch node off-time which causes a strong decrease of inductor current. Small difference between the VDD6 and VBAT terminals result in a slow increase of inductor current when the VDD6 switch node turns on.

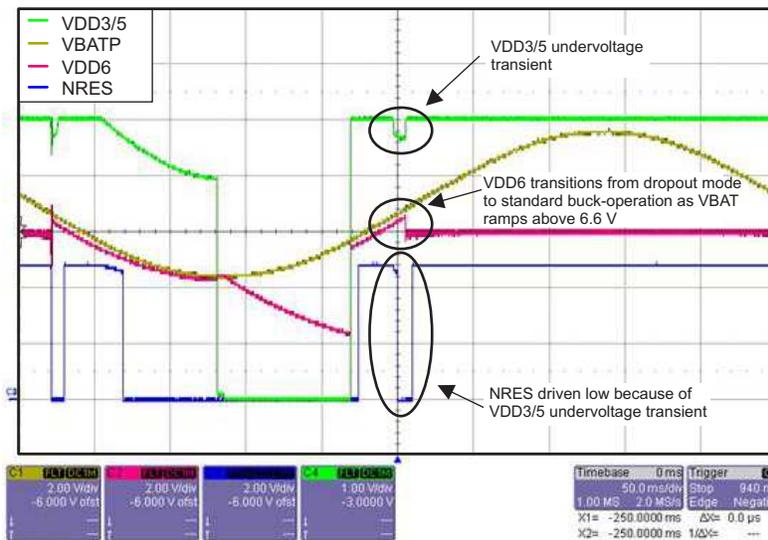


Figure 3. Battery Slow Ramp-Up Bench Measurement Result

The VDD6 terminal transitions from dropout mode to standard buck operation as the VBAT terminal ramps-up and reaches 6.6 V. In the standard buck-operation mode, when the VDD6 terminal is at 6.6 V, it is above the regulation target. Therefore the high-side (HS) switch turns off until the VDD6 terminal drops to 6 V.

During the off-period, the inductor current reduces to 0 with a rate of 200 mA/μs (for a 33-μH inductor), after which the load current on the VDD6 terminal is provided through VDD6 capacitor until the VDD6 terminal drops down to 6 V.

When turning on the VDD6 HS switch with $I_{ind} = 0$, the current can only increase at a rate of 18mA/μs (for a 33-μH inductor and slow battery ramp-up). Until $I_{ind,avg}$ reaches I_{VDD6} , I_{VDD6} remains supplied through C_{VDD6} and the voltage decreases.

The voltage drop on the VDD6 terminal (and thus on the VDD3/5 terminal when the VDD6 terminal is less than 5 V) causes the undervoltage event on the VDD3/5 terminal which leads to NRES being driven low.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

| | |
|------------------------------|--|
| Audio | www.ti.com/audio |
| Amplifiers | amplifier.ti.com |
| Data Converters | dataconverter.ti.com |
| DLP® Products | www.dlp.com |
| DSP | dsp.ti.com |
| Clocks and Timers | www.ti.com/clocks |
| Interface | interface.ti.com |
| Logic | logic.ti.com |
| Power Mgmt | power.ti.com |
| Microcontrollers | microcontroller.ti.com |
| RFID | www.ti-rfid.com |
| OMAP Applications Processors | www.ti.com/omap |
| Wireless Connectivity | www.ti.com/wirelessconnectivity |

Applications

| | |
|-------------------------------|--|
| Automotive and Transportation | www.ti.com/automotive |
| Communications and Telecom | www.ti.com/communications |
| Computers and Peripherals | www.ti.com/computers |
| Consumer Electronics | www.ti.com/consumer-apps |
| Energy and Lighting | www.ti.com/energy |
| Industrial | www.ti.com/industrial |
| Medical | www.ti.com/medical |
| Security | www.ti.com/security |
| Space, Avionics and Defense | www.ti.com/space-avionics-defense |
| Video and Imaging | www.ti.com/video |

TI E2E Community

e2e.ti.com