

Understanding the Start-up Behavior of the TPS61178x

Jasper Li

ABSTRACT

This application report details the start-up behavior of the TPS61178x device. It also characterizes the start-up timing and proposes a method to reduce the start-up inrush current. The proposed method is confirmed by bench test measurements.

Contents

1	Introduction	2
2	Start-up Behavior Description	2
3	Summary	5

List of Figures


1	Typical Schematic of TPS61178x	2
2	Start-up Waveform of the TPS61178 EVM at $V_{IN} = 7.2\text{ V}$	3
3	P-FET Driving Circuitry	3
4	Start-up Waveform at $C_{GATE} = 47\text{ nF}$	4
5	Method to Reduce the Start-up Current	4
6	Start-up Waveform With Proposed Method	5

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

For the conventional synchronous boost converter, the output voltage follows the input voltage when the converter is disabled. This behavior increases power loss due to the leakage current flowing through the feedback divider and the post-load. The TPS61178x device is a 20-V, 10-A boost converter that integrates a circuitry to drive an external P-FET to isolate the output side from the input side. Figure 1 shows a typical schematic of the TPS61178x. Because the output voltage drops to zero after the TPS61178x shuts down, the leakage current in the output also decreases to zero. The start-up circuitry of TPS61178x is designed to prevent the power supply from overloading when output increases from zero to the setting value.

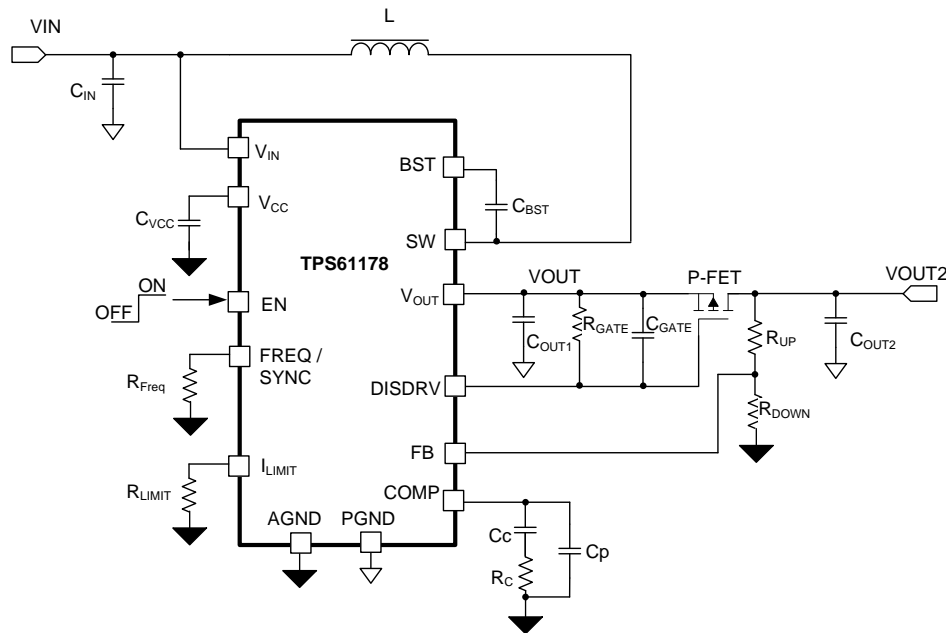

Copyright © 2017, Texas Instruments Incorporated

Figure 1. Typical Schematic of TPS61178x

2 Start-up Behavior Description

The start-up procedure of the TPS61178x device is divided into precharge phase and soft-start phase. The precharge phase is the period when the output voltage (VOUT2) increases from zero to 10% higher than V_{IN} ($1.1 \times V_{IN}$); the soft-start phase is the period from $1.1 \times V_{IN}$ to the setting output voltage.

Figure 2 shows the start-up waveform measured in TPS61178x evaluation module (EVM) at 7.2-V input voltage. In the waveform, CH1 is VOUT2 (after P-FET) shown in Figure 1; CH2 is the TPS61178x VOUT pin (before P-FET); CH3 is the EN pin voltage; and CH4 is the input current of the boost converter. The behavior of the waveform is explained as follows:

- Before t_0 , the EN pin is logic low, and the TPS61178x shuts down. The voltage at the VOUT pin is $(V_{IN} - V_D)$, where V_D is the body diode voltage. The DISDRV pin is in high impedance to turn off the external P-FET.
- At t_0 , the EN pin becomes logic high. After a short delay, the TPS61178x starts switching and boosts the voltage at the VOUT pin to $1.1 \times V_{IN}$. At the same time, the DISDRV pin discharges to ground with a typical 55- μ A current source, as shown in Figure 3. The gate-to-source voltage V_{GS} of the P-FET decreases. The slew rate is determined by Equation 1, where I_{GATE} is typical 55 μ A; τ is $R_{GATE} \times C_{GATE}$.

$$V_{GS} = -I_{GATE} \times R_{GATE} \left(1 - e^{-\frac{t}{\tau}} \right) \quad (1)$$

- At t_1 , the V_{GS} becomes lower than the threshold voltage of the P-FET. The P-FET turns on, and charges the output capacitor to $1.1 \times V_{IN}$.

- At t_2 , the precharge phase finishes and the device enters soft-start phase. The period from t_0 to t_2 is called precharge phase, which is approximately 2.6 ms. After t_2 , the rising rate of the FB pin voltage is internally controlled by Equation 2, where V_{REF} is typical 1.198 V and $t_{startup}$ is typical 3.2 ms

$$V_{FBSS} = \frac{V_{REF}}{t_{startup}} \quad (2)$$

- At t_3 , the FB voltage reaches 1.198 V, and the soft-start phase finishes. The period from t_2 to t_3 can be calculated by Equation 3, where V_{OSET} is the setting output voltage.

$$t_{boost_SS} = t_{startup} \times \left(1 - \frac{1.1 \times V_{IN} \times R_{DOWN}}{(R_{UP} + R_{DOWN}) \times V_{REF}} \right) = t_{startup} \times \frac{V_{OSET} - 1.1 \times V_{IN}}{V_{OSET}} \quad (3)$$

 


Figure 2. Start-up Waveform of the TPS61178 EVM at $V_{IN} = 7.2 V$

 


Figure 3. P-FET Driving Circuitry

The R_{GATE} in Figure 3 is used to clamp the V_{GS} not higher than $-I_{GATE} \times R_{GATE}$. Make sure the $|V_{GS}|$ is high enough to drive the P-FET while lower than the maximum voltage rating. In the TPS61178x EVM, the R_{GATE} is 100 k Ω to get $-5.5 V$ for the CSD25404Q3.

In the precharge phase, an inrush current charges the output capacitor when the P-FET turns on. Increasing the C_{GATE} can reduce the charging current because the V_{GS} slope rate becomes slower. However, the P-FET must effectively turn on before the precharge phase finishes, otherwise the output voltage will be out of control as the FB pin voltage comes from VOUT2. Taking CSD25404Q3 as example, this MOSFET effectively turns on at $V_{GS} = -1.5 V$ from its "Transfer Characteristics". Therefore, the V_{GS} should be lower than $-1.5 V$ before the precharge phase finishes. Because the minimum precharge time is 1.8 ms, the maximum C_{GATE} can be calculated by Equation 4

$$C_{GATE_MAX} = \frac{t_{PRE_CHARGE}}{-\ln\left(1 + \frac{V_{GS}}{I_{GATE} \times R_{GATE}}\right) \times R_{GATE}} = \frac{1.8 \text{ m}}{-\ln\left(1 - \frac{1.5}{55 \mu \times 100 \text{ k}}\right) \times 100 \text{ k}} = 56 \text{ nF} \quad (4)$$

As showed in Figure 4, the inrush current during the precharge phase reduces to 2 A if the C_{GATE} increases from 22 nF to 47 nF, and the P-FET fully turns on within 1.8 ms.

 


Figure 4. Start-up Waveform at $C_{GATE} = 47 \text{ nF}$

To increase C_{GATE} further, add a resistor in series with C_{GATE} , as shown in Figure 5. When the TPS61178x is enabled and the voltage of C_{GATE} is zero, the V_{GS} is defined by Equation 5. As the minimum threshold voltage of the CSD2540Q3 is 0.65 V, the R_{G_A} is set to approximately 13.4 k Ω to void the P-FET turning on at the beginning.

 


Figure 5. Method to Reduce the Start-up Current

$$V_{GS} = -I_{GATE} \frac{R_{GATE} \times R_{G_A}}{R_{GATE} + R_{G_A}} \quad (5)$$

After adding R_{G_A} , the V_{GS} is defined by Equation 6 after the TPS61178x is enabled, where τ is $(R_{G_A} + R_{GATE}) \times C_{GATE}$. The maximum value of C_{GATE} can be calculated by Equation 7.

$$V_{GS} = -I_{GATE} \times R_{GATE} \left(1 - e^{-\frac{t}{\tau}}\right) - I_{GATE} \times R_{GATE} e^{-\frac{t}{\tau}} \times \frac{R_{G_A}}{R_{GATE} + R_{G_A}} \quad (6)$$

$$C_{GATE_MAX} = \frac{t_{PRE_CHARGE}}{-\ln\left(\frac{V_{GS} + I_{GATE} \times R_{GATE}}{I_{GATE} \times R_{GATE}} \times \frac{R_{GATE} + R_{G_A}}{R_{GATE}}\right) \times (R_{GATE} + R_{G_A})}$$

$$= \frac{1.8 \text{ m}}{-\ln\left(\frac{-1.5 + 55 \mu \times 100 \text{ k}}{55 \mu \times 100 \text{ k}} \times \frac{100 \text{ k} + 13.4 \text{ k}}{100 \text{ k}}\right) \times (100 \text{ k} + 13.4 \text{ k})} = 82 \text{ nF} \quad (7)$$

Selecting the R_{G_A} to be 13.4k and C_{GATE} to be 68 nF, the start-up waveform is shown in Figure 6. The input inrush current reduces to 1.5 A, and the P-FET fully turns on within 1.8 ms after the EN pin becomes logic high.

 


Figure 6. Start-up Waveform With Proposed Method

3 Summary

This application report described the soft-start timing and behavior of the TPS61178x device. Theoretic analysis and bench tests show that the input inrush current during start-up is determined by the driver circuitry of the external P-FET. Suitable selection of the circuitry components can help reduce the inrush current.

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Original (December 2017) to A Revision	Page
• Changed "1n" to "ln" in Equation 4	3
• Changed "1n" to "ln" in Equation 7	5

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated