

Headphone Jack Detection in Personal Electronics Using Comparators



Electronic devices from cell phones to laptop computers usually include a stereo headphone jack. When an external headphone is plugged in, the built-in speaker must be disconnected and the audio output switched to the external device. The switching process must be free of any clicking noise and may also provide additional user experience features such as audio volume fading in and out, pausing the music player, and so forth.

The output switching process is commonly accomplished through dedicated control circuitry. It may require constant power even after the host device is in sleep mode because these device would still register and respond to the user's actions while in this state. In this case, low quiescent current (I_Q) becomes a key requirement.

The control circuitry is commonly built with comparators at its core. The newly introduced nano-power and small size open-drain TLV7041 comparator is designed for these applications.

The **TLV7041** comparator includes the following benefits:

1. 335-nA typical quiescent supply current
2. 3-pA typical input bias current
3. Input protection and flexible output pullup options (1.6 V to 6.5 V)
4. Small package dimensions (0.8 mm × 0.8 mm × 0.4 mm)

To meet these requirements, the audio output must be switched to the external device only when the headphone jack is fully seated. This is normally accomplished by the confirmation that both the tip and ground (G) of the headphone plug are connected.

Figure 1 shows the connection terminals of a typical headphone plug (left) and its matching socket (right). In this configuration, two dedicated terminals GND_detect and L_detect are responsible for the state detection. When the headphone jack is fully engaged, GND_detect is connected to GND and the L_detect to L (left audio channel) through the conductor segments

of the headphone plug (left). When L_detect is connected, the headphone jack is considered fully seated based on the fact that the L_detect terminal and plug tip L are situated at the far end of the headphone plug.


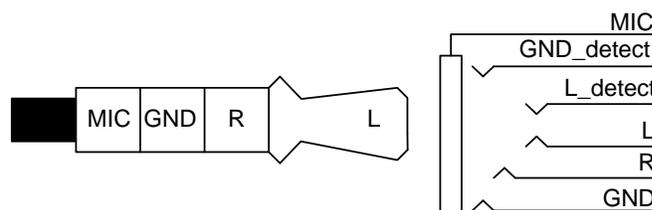


Figure 1. Headphone plug (Left) and Socket

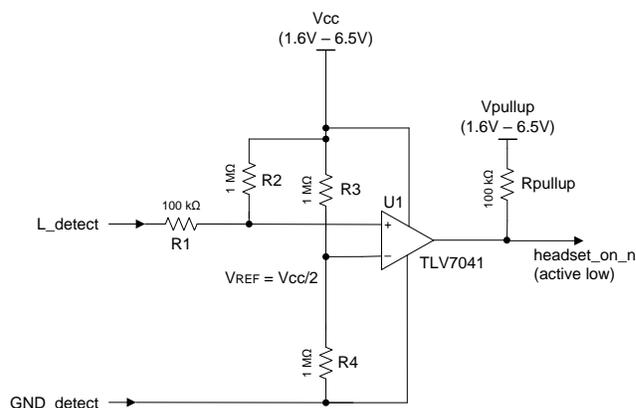The control circuit uses GND_detect and L_detect terminals to determine the plugged-in state, and the circuit sets the output headset_on_n (active low) accordingly. **Figure 2** shows a complete schematic of the circuit based on a single TLV7041.



Copyright © 2017, Texas Instruments Incorporated

Figure 2. Headphone Detection Circuit

The resistor network (R3 and R4) establishes a reference V_{REF} at $V_{CC}/2$ which feeds to the inverting input of TLV7041. R2 pulls the noninverting input to V_{CC} when the headphone jack is not engaged, causing the open-drain output pulled high to V_{pullup} . Thanks to TLV7041's low input bias current (typically at 3 pA), larger resistance values can be used for R2, R3, and R4 (all three resistors are 1 MΩ) without compromising accuracy, which helps reduce total power consumption.

Notice that the V_{EE} of the comparator is connected to the GND_detect instead of to GND. When the headphone jack is not engaged, V_{EE} is pulled to the same level as V_{CC} through R3 and R4 and consequently the comparator is not powered. This causes the output headset_on_n pulled high to V_{pullup} , which indicates an inactive state.

When a user plugs in the headphone jack, the V_{EE} of the comparator is first connected to GND through the GND_detect to power the comparator. This *floating ground* design technique is made possible thanks to the TLV7041 robust input and output protection and design features. For further details, refer to the *Application and Implementation* section of the [TLV7041](#) data sheet.

When the headphone jack is fully seated, the L_detect terminal is connected to L by the conductor tip of the headphone plug. Consequently, the lower impedance of the headphone coil (through R1) pulls the noninverting input below V_{REF} , which brings the output (headset_on_n) to low (active state) to indicate the headphone has been plugged in.

R1 is used to limit the maximum current fed into the TLV7041 input. Before GND_detect is robustly connected to GND, the device's V_{EE} is pulled to V_{CC} . During which, if L_detect is momentarily pulled low, the input level could potentially be below V_{EE} . In this case, R1 limits the current flowing through the input ESD diode (now turned on).

The example uses a separate V_{pullup} to support a load that is powered with a different supply. If that is not the case, a common supply can be used for both V_{CC} and V_{pullup} , and the sister push-pull output feature of the [TLV7031](#) may also be an option.

If you have questions on comparator application, please visit the [E2E](#) forum on ti.com.

[Table 1](#) shows the truth table of the circuit.

Table 1. Headphone Jack Detection Truth Table

INPUT		OUTPUT	HEADPHONE JACK STATE
GND_detect	L_detect	headset_on_n	
Open	Open	high	not plugged in
GND	Open	high	not plugged in
Open	L	high	not plugged in
GND	L	low	plugged in

In summary, the TLV7041 comparator provides several benefits such as low quiescent current, virtually negligible input bias current, small package size, and robust input and output protection engineers can use in power-conscious portable applications.

Table 2. Alternative Open-Drain Device Recommendations

Device	Optimized Parameters	Performance Trade-Off
TLV7081	$I_Q = 370$ nA, 4-pin WCSP (0.7 × 0.7 mm ²) Package	Prop Delay = 4 μs
TLV7021	Prop Delay = 260 ns, 5-pin X2SON (0.8 × 0.8 mm ²) Package	$I_Q = 5$ μA
TLV3691	$I_Q = 75$ nA, 4-pin X2SON (1 × 1 mm ²) Package	Prop Delay = 24 μs

Table 3. Adjacent Tech Notes

SNOA981	Nano-Power Battery Monitoring in Personal Electronics
SNVA808	Low Power Comparator for Signal Processing and Wake-Up Circuit in Smart Meters
SCEA055	Designing and Manufacturing with TI's X2SON Packages

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated