

Application Brief

eFuses in Smart Electricity Meters



Introduction

Communication modules allow for electricity meters to transmit energy readings back to a central data concentrator either through a wireless or wired transmission to eliminate costly on-site readings. To ensure this data transmission functionality does not interfere with the metrology of the electricity meter, many countries have adopted standards such as the IR46 and the Dutch P1 Companion Standard to specify protection requirements with regards to the external communications module. To comply with these standards, TI eFuses can be used to provide a low cost and compact solution to meet the different protection requirements that exist around the world.

separate the internal metrology module from an external communication module malfunction.

During a power outage, the emeter must also be able to switchover to a super capacitor to provide a “last gasp” transmission to record the latest energy usage and to alert the grid of the outage. For topologies 1 and 2, the power MUX and ideal diode block provides robust reverse current blocking, preventing current from flowing back into the meter while the power path switches to the super capacitor.

Similarly in topology 3, TI also offers integrated eFuse solutions with a back for robust reverse current blocking. An integrated eFuse with reverse current blocking such as the TPS25947 simplifies power path designs for the external communications module.

Common Smart eMeter Topologies

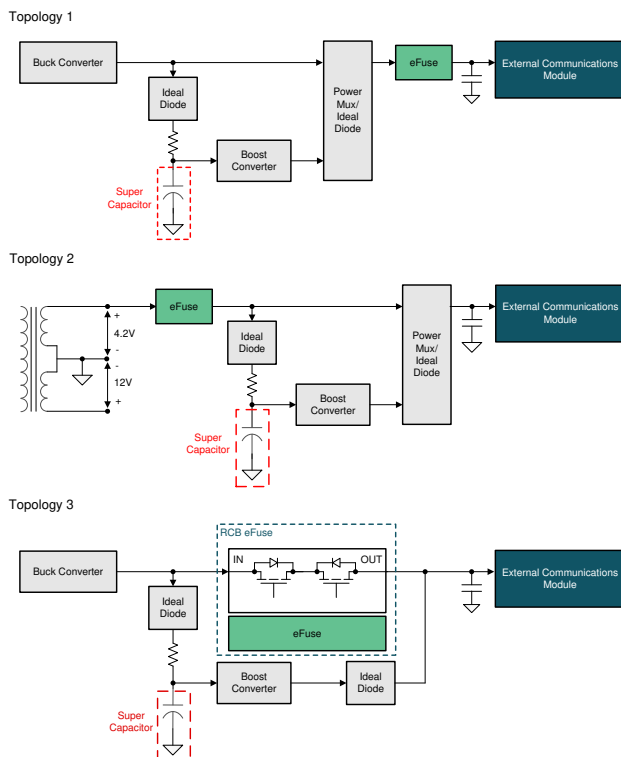


Figure 1. Common smart eMeter topologies

Figure 1 shows three common smart electricity topologies where an eFuse can be utilized to protect the system from external communication module failures and tampering events. The eFuse provides a number of protection features to help electrically

Benefits of eFuse and its Protection Functions

TI eFuses offer compact, low R_{ON} solutions with multiple protection functions such as:

- Overvoltage protection (OVP)
- Current limiting (ILIM)
- Inrush current control (dv/dt)
- Reverse current blocking (RCB)

Depending on the topology that is used some or all of these protection functions could be required. eFuses offer the flexibility of having each of these protection functions in a single, low-cost device so it can be used in multiple designs. Table 1 highlights TI’s recommended eFuse devices for emeter applications based on the different protection functions that may be required.

Table 1. Recommended eFuse Devices

Device	V_{IN} (V)	I_{LIM} (A)	R_{ON} (m Ω)	OVP	dv/dt	RCB	Package
TPS2596	2.7–19	0.12–2	89	✓	✓		SOIC (8) 5 mm × 6 mm
TPS2595	2.7–18	0.5–4	34	✓	✓		WSON (8) 2 mm × 2 mm
TPS25947	2.7–23	0.5–6	27	✓	✓	✓	QFN (10) 2 mm × 2 mm

Overvoltage Protection

Topology 2 highlights an emeter architecture where power is derived from two different tap points off of an AC/DC. In this scenario, there is a potential for overvoltage transients to damage the system. Having a solution to detect the overvoltage and limit it is important. TI eFuses offer overvoltage protection to provide this function. Depending on the eFuse it can have two options; overvoltage clamping or overvoltage cutoff.

Overvoltage clamping will clamp the output to a certain voltage until the device reaches the thermal shutdown threshold which will in turn disable the device to protect itself from being damaged due to overheating. Overvoltage cutoff on the other hand will immediately disable the eFuse when the overvoltage threshold is reached to protect the downstream components.

Current Limiting and Short-Circuit Protection

The external connector of the communication module introduces a number of scenarios that could cause short-circuit or overcurrent events in a system such as damaged cabling or connectors, meter tampering, or water and humidity seepage.

Should any of the above scenarios occurs, it is important that the meteorology portion of the system remains functional so the emeter can continue to log the energy usage of the unit and there is no loss in billing.

TI eFuses offer adjustable short-circuit and current limiting functions to protect the emeter from these external faults. Short-circuit and current limiting levels can be adjusted to fit the needs of the different communication protocol. [Figure 2](#) shows the performance of the fast-trip short-circuit protection of TPS2596 when the output experiences a hot short.

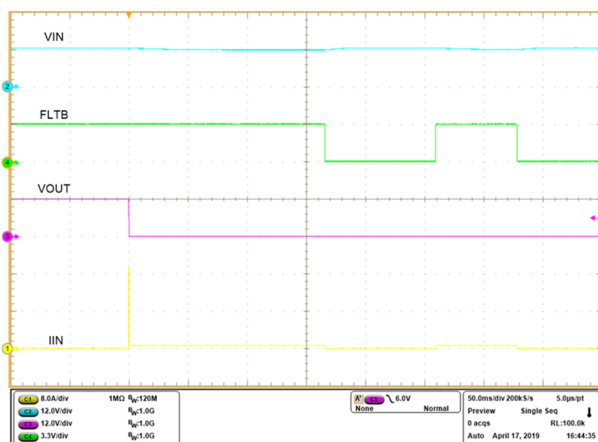


Figure 2. Short-Circuit Response of TPS2596

Once a short-circuit event is detected, the eFuse immediately turns off, disconnecting the load from the power supply. The shut off happens rapidly before the shorted load is able to draw too much current from the power supply.

Inrush Current Control

As mentioned previously, inrush current control is important to charge up the large bulk capacitance that can sit on the input of the communications module. TI eFuses have adjustable slew rate control which allows the user to program the output slew rate of the device to linearly control the amount of inrush current ($I = C \times dv/dt$) when the module initially powers up. [Figure 3](#) shows how the TPS2596 controls the inrush current when powering up a 220- μ F capacitor on its output.

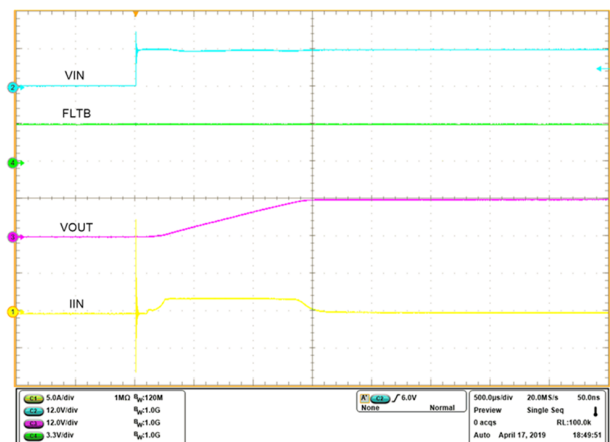


Figure 3. Inrush Current Hotplug Response of TPS2596

The adjustable slew rate of the device controls the VOUT to slowly ramp up at a desired rate. Without inrush current control, the initial inrush current can easily damage the switch that is used to turn on the communications module.

Conclusion

TI eFuses offer an integrated solution for power protection in smart emeters to prevent the system from overvoltage and short-circuit events. Additionally, TI eFuses have low R_{ON} which minimizes the voltage drop on the power path to stay within the tight voltage tolerance of the external communications module. Without proper power protection, both the emeter and the external communications module are susceptible to common fault events which can permanently damage the whole system which can result in energy billings being lost.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated