

# Current Sense Amplifiers in Class-D Audio Subsystems

Arjun Prakash, Current Sensing Products




CLASS-D audio amplifiers provide output power with an efficiency of over 90% as compared to CLASS-AB amplifiers that can provide an output efficiency of <50%. CLASS-D amplifiers are implemented in portable personal audio systems that provide quality sound output enabling longer battery life. A widely used CLASS-D amplifier in automotive systems are for E-call systems that provide critical audio feedback to the driver in case of a driver emergency. In E-call systems discrete current sensing is often implemented for continuous diagnostics to ensure speaker is operational at all times.

Current sensing in audio subsystems are widely used in conjunction with CLASS-D amplifiers for diagnostics or to provide speaker current feedback to the DSP for speaker enhancement to emulate smartamp. The most expensive component in the audio subsystem is the speaker. The impedance of the speakers ranges from 2Ω for subwoofer to a 8Ω for stereo speakers. Exceeding the current flowing through the speakers has a potential to create excessive heat in the voice coil which can lead to permanent damage of the speakers.

CLASS-D amplifier subsystem is as show in [Figure 1](#). High power, high voltage class-d systems are often built discretely as integrated class-d amplifiers with silicon FETs do have limitations in terms of thermal limitations. High voltage class-d systems with GaN FETs are widely being accepted due to its advantages in efficiency and ability to switch at higher frequency. As integrated class-d amplifiers do have integrated

over current protection that protects the class-d and speaker from exceeding currents however with discrete class-d implementation discrete current sensors is needed for implementing over current protection to provide diagnostics for speaker protection.

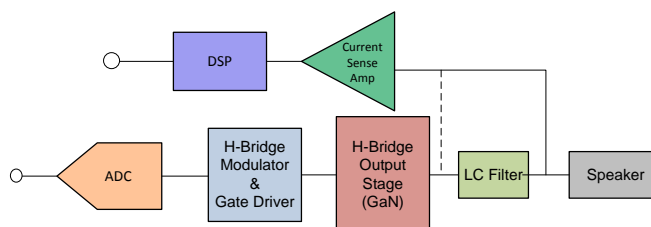

**Figure 1. Discrete CLASS-D System Block Diagram**

Current sensing in a CLASS-D could be realized with either a shunt based or a magnetic based system. Shunt based current sensing are best suited for audio applications due to its linearity, lower noise and higher dynamic range. However magnetic hall sensors on the other hand are lower cost to implement with drawbacks to lower dynamic range, higher noise and increased output sensitivity to external magnetic fields. [Table 1](#) describes a summary of pros and cons to using shunt based solution to a magnetic solution in audio.

**Table 1. CLASS-D current sensing summary**

| Current Sensing Application | Shunt based current sense solution  |  | Magnetic based current sense solution |  |
|-----------------------------|---|--|---------------------------------------|--|
|                             | Pros  | Cons   | Pros                                  | Cons   |
| Over Current Protection     | Accurate over current protection <1%  | Series shunt power loss, High series inductance of the shunt | No shunt power loss, No parasitics    | Output accuracy is unpredictable due to external magnetic and environmental fields |
| Analog feedback control     | High linearity feedback (<0.01%), High dynamic range, Lower noise   | Cost of solution   | Cost of solution                      | Lower linearity (>5%), Higher output noise, Lower output range control             |
| Smartamp control            | High linearity feedback (<0.01%), High dynamic range, Lower noise, Faster loop control, faster DSP processing | Cost of solution   | Cost of solution                      | Lower linearity (>5%), slower control loop response, longer DSP processing         |

## Discrete CLASS-D Protection and Diagnostics

For diagnostics, the shunt and the discrete current sense amplifier is preferred to be connected pre-filter as shown in Figure 2. The challenge with the pre-filter current measurement is the amplifier is subjected to fast switching transients. Amplifiers with high bandwidth and fast output settling is required to measure accurate currents. As the switching frequency increases beyond 150 kHz the need for unity gain bandwidth of current sense amplifier significantly increases to the order of 15 MHz. Such high bandwidth amplifiers has disadvantages of higher  $I_q$ , higher offset and limited output slew rate. However, pre-filter current measurements offers fast response to over current detection with ability to provide diagnostics of external LC filter to detect abnormalities in the passive.

To overcome the challenges of current sensing in pre-filter measurements, a possible solution to provide complete diagnostics with a cost effective solution would be to measure currents post LC filter. Post LC filter the common mode signal is a slow moving signal limited to <30 kHz. For post filter current sensing, the current sense amplifier can detect shorted speaker connections and provide information back to the control loop for shutdown.

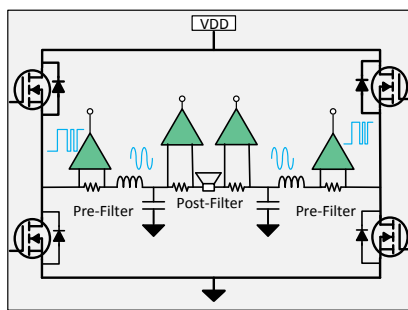


Figure 2. Current sensing in CLASS-D amplifier

## Speaker parameters extraction for smartamp implementation

As the advancements are being made in the digital signal processing technology, higher processing power, smaller DSP with lower power consumption are available today. Real time speaker parameters such as current, voltage, impedance and temperature are increasingly being measured to create a real time closed loop speaker system which can adapt to the changes in the environment the speaker system is subjected to. One of the key components to realize a closed loop smart amp system is a precision current sense amplifier with high dynamic range, lower noise and higher bandwidth (>200 kHz). Speaker parameters are measured in the DSP subsystem by measuring current in the feedback system as shown in Figure 3.

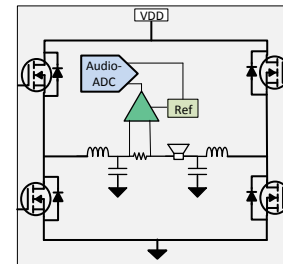


Figure 3. Closed loop CLASS-D system with current sensing

INA240 is a high voltage ( $V_{CM}$  -4 V to 80 V), high precision, bi-directional current sense amplifier with low input offset and gain drift across temperature range making it an ideal device for measuring currents in a CLASS-D subsystem. The INA240 is specifically designed to work in switched node environments where the common mode transients will have large  $dv/dt$  signals. The ability to reject high  $dv/dt$  signals enables accurate current measurements with high precision and linearity. With a large dynamic range of 80dB and the THD+N of <0.04% the INA240 ensures that the feedback system can correct for nonlinearities to as low as 0.04%. The signal throughput bandwidth of INA240 is 400kHz at the gain 20. The high bandwidth of the amplifier enables accurate current measurements with a flat response band up to 200 kHz and benefits in faster signal throughput for over current detection. The INA240 has low maximum input offset voltage of 25 $\mu$ V and a maximum gain error of 0.2% allowing for smaller shunt resistance values to be used without sacrificing measurement accuracy. The offset drift and gain error drift is as low as 0.25 $\mu$ V/ $^{\circ}$ C and 2.5ppm/ $^{\circ}$ C respectively enabling accurate and stable current measurements across temperature.

Table 2. Alternate Device Recommendations

| Device  | Optimized Parameter  | Performance Trade-Off                    |
|---------|--|--|
| INA168  | Bandwidth : 800kHz,<br>Package: SOT-23                                     | Adjustable gain,<br>external components  |
| LMP8601 | $V_{CM}$ -22 V to 60 V   | Offset voltage: 1mV,<br>bandwidth: 60kHz |
| INA253  | $V_{CM}$ -4 V to 80 V,<br>Integrated low-inductive 2m $\Omega$ , 3nH shunt | $\pm 15A$                                |

Table 3. Related TI TechNotes

|         |  |
|---------|--|
| SBOA174 | Current Sensing in an H-Bridge                                 |
| SBOA176 | Switching Power Supply Current Measurements                    |
| SBOA166 | High-Side Drive, High-Side Solenoid Monitor With PWM Rejection |

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated