

Low Temperature Drift Integrated Shunt vs Active Temperature Compensation of Shunt

Arjun Prakash, Current Sensing Products



Current sensing applications typically use a shunt as a sensing element. A shunt is a resistive material that is designed such that the maximum current flow is diverted across the shunt in the system. The current flowing through the shunt develops a differential voltage across its terminals which is then measured using a current sense amplifier. The selection of the shunt depends on the maximum current rating and the permissible power dissipation across the shunt in the system. To minimize power dissipation across the shunt often a low ohmic value shunt is preferred. For smaller currents, the differential voltage developed across the low ohmic shunt can be relatively small, a current sense amplifier with a high gain can amplify the signal across the shunt which can then be connected to ADC for further processing. As a lower shunt value is preferred in an application for lower power dissipation, at lower currents the signal generated across the shunt can be comparable to the noise in the system, a current sense amplifier with high gain, low offset and lower noise is required to measure the full dynamic range across the shunt. Often the offset error, bias currents and input referred noise of the current sense amplifier limits the least current that can be measured across a low ohmic shunt.

The [INA240](#) is a current sensing product from Texas Instruments that has the lowest offset voltage of 25 μV with a offset drift of 0.25 $\mu\text{V}/^\circ\text{C}$. Advancements in current sense amplifier specifications has lead to highest absolute accuracy with stable measurement across full temperature range with an max drift accuracy of 2.5 ppm/ $^\circ\text{C}$. However, to realize accurate stable measurements across the shunt the limitation is still in the maximum temperature error drift of the shunt. In a current sensing system the total error of a solution is the sum of squares of root (RSS) of error sources of shunt and the current sense amplifier. In a system with a discrete shunt and [INA240](#), the overall system error is limited by the precision and the type of the shunt. One methodology to minimize errors due to the shunt placement and layout is to implement a 4-wire kelvin connection to the amplifier. However, best layout and 4-wire kelvin connection can only address the accuracy at 25 $^\circ\text{C}$, the temperature drift of the shunt is unaccounted for. In order to address the temperature drift measurements a full temperature calibration is performed in the system and look up values are stored in the micro controller. An active

temperature compensation can be performed using a temperature sensor, the shunt variation due to temperature drift can now be accounted for. However, the extent of temperature calibration is limited due to placement of temperature, time to reach steady state, temperature gradient across the shunt etc, this is unpredictable often impracticable to be implemented in large scale production.

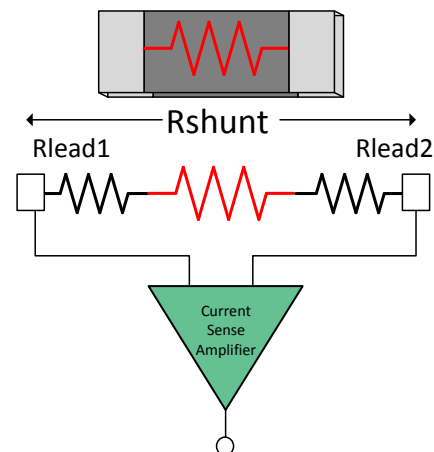


Figure 1. Shunt electrical resistance representation

[Figure 1](#) describes a common breakdown of the shunt resistance. For low ohmic shunts, the lead resistance can be unpredictable and often varies forcing the system to perform on board calibration. If the shunt leads are material based of copper then the accuracy of the shunt will worsen as copper has a temperature drift of 3900 ppm/ $^\circ\text{C}$. For applications that require precision measurement across temperature the solution to get higher accuracy is to use 4-wire kelvin connected shunts. Kelvin connected shunt ensures that even if the leads are constructed using copper the kelvin leads are connected across the shunt ensuring the current measurement is measured directly across the shunt and not influenced by changes in the lead resistance and immune to any application errors sources like placement and trace layout. [Figure 2](#) describes an electrical representation of a 4-wire kelvin shunt.

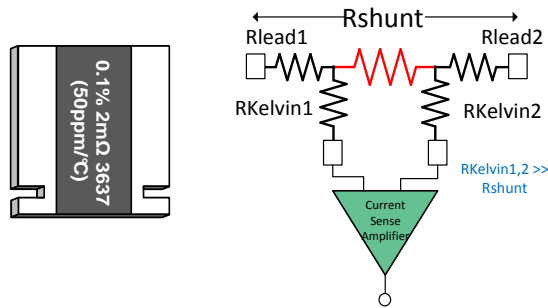


Figure 2. 4-wire Kelvin Shunt electrical resistance representation

One of the drawbacks of using low drift shunt material as a shunt is the cost associated with the manufacturing of the shunt and also its integration with the package leadframe. There has been other techniques in the industry to integrate copper leadframe as a shunt material due to its cost advantage. However, copper shunt metal has a temperature drift of 3900 ppm/°C that needs to be compensated. The compensation techniques has only been successful in achieving sub 100 ppm/°C of error correction. The solutions that can achieve <50 ppm/°C error correction tends to be performed in digital domain using an ADC. The absolute shunt error of copper at ambient temperature of 25°C can always be corrected using factory trim. The challenge lies in the temperature drift compensation. The error correction however is dependent on the accuracy of the temperature sensor and also its placement of the sensor inside the package. As the current flows through the copper shunt, the self heating of the shunt creates a temperature gradient within the shunt, this temperature gradient can be off by 5°C to 10°C. If the placement of the temperature sensor is offset by 10°C the drift error specification can see a change in 2% - 4%.

The challenge still lies ahead to use copper as a shunt material to achieve the drift specification accuracy levels of low drift metal shunt. The error correction technique requires temperature sensor, current sensor feedback loop to be operated in servo. This often adds complexity to the design if a current sense amplifier with analog output is desired. To address this feedback loop complexity the temperature sensor and current sense amplifier are error corrected in digital domain using ADCs and microcontroller. This techniques address the complexity but however adds latency and the application is restricted to current measurements with digital output domain. for fast feedback control applications like EPS systems, 3-Ph motor control systems and power supply loop control a digital output current sense amplifier can add too much latency for the system to perform any type compensation often compromising on the speed and control of the system.

Figure 3 illustrates a graphical representation of error of a shunt using calibrated copper metal and compared with using low drift metal alloy. The low drift metal alloy virtually has constant electrical resistance across temperature eliminating the need for drift correction for integrated shunts. Temperature compensation elimination saves valuable manufacturing costs and enables accurate precision solutions to be available in the market at a lower cost.

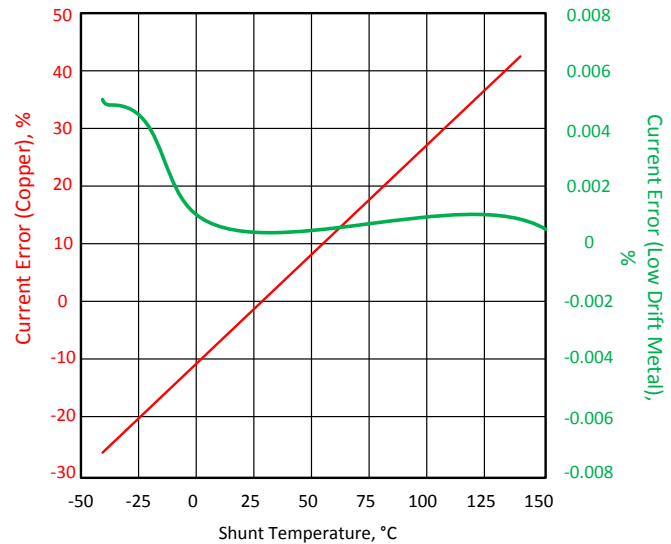


Figure 3. Current error output

The INA250 was designed to address the system accuracy challenge by integrating a 4-wire kelvin 2mΩ shunt inside a package. The INA250 provides a total system accuracy of <0.3% with a temperature drift of 45 ppm/°C. The INA260, a digital output solution with 2mΩ integrated shunt provides a gain error accuracy of 0.15% with a gain error drift of 35 ppm/°C. The 2mΩ integrated shunt is built using a low temperature drift shunt. The thermal coefficient of integrated shunt is ±15 ppm/°C.

Table 1. Alternate Device Recommendations

Device	Optimized Parameter	System Performance Trade-Off
INA240	25 μV offset, 0.2% gain error, 2.5 ppm/°C error drift	Discrete Shunt
INA282	DC CMRR: 140dB	Bandwidth: 10kHz, Discrete Shunt

Table 2. Related TI TechNotes

SBOA202	Benefits of Integated Low Inductive Shunt for PWM Applications
SBOA170	Integrating the Current Sensing Resistor

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated