

Current Sensing in Body Control Modules with Simulation

Peter Iliya

ABSTRACT

Current sense amplifiers (CSAs) are unique and simple-to-use devices, allowing designers to capture the current of a load with a small shunt resistor. They are a part of a growing need to cheaply, yet precisely, monitor, control, and protect loads on voltage rails that can greatly exceed the single-ended supply rail (V_S) of the CSA. Thus, CSAs can be beneficial to systems that need to monitor and control loads associated with electronic control units (ECU). The ECU of focus will be the body control module (BCM) of the automotive space. This report will show how to choose and evaluate CSAs for control and monitoring loads. Evaluation will be based off using the TINA-TI simulator.

Contents

1	Introduction	2
2	Overview of Current Sense, Difference, Instrumentation, and Operational Amplifiers	3
3	Current Sense Amplifiers and Integrated Current Sensing of High-Side Switches and Driver	3
4	Current Sensing for the H-bridge	3
5	Brushed-DC Motor Ripple Counting - Simple Simulation for Low-Side Current Sensing	4
6	High-Side Stepper Motor Stall Current Detection	15
7	High-Side Averaging PWM LED Current Sensing	18
8	Summary	22
9	References	22

List of Figures

1	Current Sensing in the H-bridge	4
2	Equation to Model BDC Current Ripple.....	5
3	Creating BDC Current Ripple in TINA-TI	5
4	Complete Schematic for Circuit A1	6
5	Simplified Schematic and Simulation for Circuit A1	6
6	Circuit A1 Transient Simulation at 20-A Motor Current	7
7	Circuit A1 Transient Simulation at 1-A Motor Current	7
8	Example Signal Conditioning for Counting Ripple Currents from TIDA-01421	8
9	Circuit A1 with Ripple Counting Signal Conditioning Circuitry	8
10	Simulation of Circuit A1 and Complete Ripple Counting Signal Conditioning Circuitry	8
11	Complete Schematic for Circuit A2.....	9
12	Circuit A2 Simulation Waveform at 10-A Motor Current.....	9
13	Circuit A2 Simulation Waveforms for Multiple Motor Current Levels	10
14	Simulation Schematic For Circuit A3	11
15	Circuit A3 Transient Simulation for 20-A Motor Phase Current	11
16	Circuit A3 Transient Simulation for 1-A Motor Phase Current.....	11
17	Circuit A3 with Modifications at 0-A Motor Current DC Simulation	12
18	Circuit A3 with Modifications (R1 = 10 k Ω) Transient Simulation at 20-A Motor Current.....	13
19	Circuit A3 with Modifications (R1 = 10 k Ω) DC Motor Current Range Sweep	13
20	Circuit A4 with Ripple Counting Signal Circuitry	14
21	Circuit A4 Transient Simulation at 20 A (Forward Direction)	14

22	Circuit A4 Transient Simulation at -20 A (Backward Direction)	15
23	Measuring High-Side Bipolar Stepper Motor Current	15
24	Circuit B1 Simulation Schematic	16
25	Circuit B1 of Transient Simulation for Normal Motor Operation with Two Shunt Values	17
26	Circuit B1 Transient Simulation with Stall Current and Two Shunt Values	17
27	Circuit B2 Simulation Schematic	18
28	Circuit B2 Transient Simulation of Switching in Stall Current	18
29	Creating the High Duty Cycle Current LED Load	19
30	Circuit C1 INA186-Q1 with Input Filter Averaging PWM Current	19
31	Circuit C1 Transient Simulation with 1% Duty Cycle Current	20
32	Circuit C1 Transient Simulation with 97% Duty Cycle Current	20
33	Internal INA169-Q1 Architecture	21
34	Circuit C2 INA169-Q1 with Input Filter Averaging PWM Current	21
35	Circuit C2 Transient Simulation for 1% Duty Cycle	22
36	Circuit C2 Transient Simulation for 97% Duty Cycle	22

List of Tables

1	Recommended Current Sense Amplifiers in the H-bridge	4
2	Circuit Solutions for BDC Ripple Counting	5
3	Summary of Circuit to Sense High-Side Stepper Motor Stall Current.....	16

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

The BCM is an electronic control unit (ECU) in charge of switching, controlling, and monitoring many loads and electrical systems in vehicles. Sometimes, the BCM can consist of multiple modules and host different names. The following are end systems that can be tied to the BCM:

- Seat motion
- Seat heating
- Mirrors
- Doors
- Cabin control
- Lighting
- Sunroof
- Wipers
- Lift-gate
- HVAC

These systems are controlled and protected with the following:

- Motors (brushed and compressor)
- Solenoids
- LEDs
- Smart diodes

The BCM will rely on multiple types of IC drivers to control, energize, and monitor loads throughout the vehicle. Many of these drivers can be quite complex and can monitor load current for several possible events: over-current protection (OCP), open-load detection, under-voltage lockouts, over-voltage protection, and so on. While this integration can save on board space and design, the performance and accuracy of integrated current sensing and event detection times can be far inferior to the capabilities of using current sense amplifier solutions. Additionally, it might prove beneficial to the system or host to accurately monitor load currents even when no fault event is present.

This report will detail how to use CSAs for monitoring various loads controlled by the BCM including H-bridge controller for brushed DC and stepper motors, as well as, monitoring LED current. As a complement this document will also show how to quickly develop proof-of-concept circuits using SPICE simulation techniques and models available from TI all within the free TINA-TI simulation environment.

2 Overview of Current Sense, Difference, Instrumentation, and Operational Amplifiers

One of the main differences between CSAs and instrumentation amplifiers and op amps is the input common-mode voltage (V_{CM}) rating. CSAs can measure current on a high-side voltage rail with a higher V_{CM} that is independent from the single-ended low voltage supply of the device (V_S). For the BCM, this is crucial because it controls the delivery of the 12-V battery power to loads throughout the car, thus high-side switching and monitoring are necessary. Placing current sense amplifiers on the high-side rails on the BCM boards allows for convenient layout for feeding current measurements back to the BCM processor. Many times, low-side sensing at the BCM board is not possible since the car chassis is the ground return path.

Current sense amplifiers also differ from closely related difference amplifiers. The internal resistor network of difference amplifiers is comprised of resistors trimmed to absolute values. Thus, input resistors allow for an extended V_{CM} range; however, this range is not completely independent of the supply voltage and cost usually increases for difference amplifiers. Current sense amplifiers contain an input bias stage before the input resistors. This input stage is what allows for the V_{CM} range of the current sense amplifiers to be completely independent of V_S .

3 Current Sense Amplifiers and Integrated Current Sensing of High-Side Switches and Driver

High-side switching ICs can deliver power to loads with a large input voltage range. Many high-side switches (HSS) have integrated current sensing circuitry; however, this can increase the HSS cost and the accuracy of these current measurements is inferior to the accuracy and high-dynamic range achievable with a CSA. This makes CSAs ideal for low-current monitoring, power monitoring, and detecting open loads.


Some motor drivers and antenna LDOs also possess internal amplifiers for low-side current sensing, but once again, accuracy is not as good as using a dedicated CSA. Additionally, amplifier gain and bandwidth can be limited, so a larger shunt resistor is needed, resulting in greater power losses.

4 Current Sensing for the H-bridge

The full-bridge circuit is fundamental to driving motors and understanding the features and limitations of CSAs helps you choose the right CSA for a specific location in the H-bridge. [Figure 1](#) is the standard H-bridge with shunt resistors in three general locations: high-side, in-line, and low-side. The high-side shunt resistor in [Figure 1](#) is on the shared trace of both motor phase currents, thus it is sensing the current of both phases all the time. The two low-side shunts are positioned for each half-bridge leg, so they only sense the phase current of the leg they are in-series with. Placing the shunts in the phase trace allows for the sensing of any recirculating currents.

The in-line shunt is sensing bidirectional current and thus needs a bidirectional current sense amplifier that can offset to mid-supply. As opposed to a constant V_{CM} seen by the high or low-side shunts, the in-line V_{CM} of the shunt quickly swings from supply to ground and vice versa once a new bridge is activated.

[Table 1](#) summarizes the best potential CSAs for each shunt locations.

 
Figure 1. Current Sensing in the H-bridge
Table 1. Recommended Current Sense Amplifiers in the H-bridge

	TI CSA DEVICE	FEATURES
High-Side	INA186-Q1 (INA190-Q1)	42-V survivable, high-input impedance (enables low-frequency measurements), low-power, ultra-precise, 1.8-V to 5.5-V supply rail
	INA290-Q1	110-V operational, 800-kHz BW, high CMRR, ultra-precise, 2.7-V to 20-V supply rail
	INA301-Q1	36-V operational, 550-kHz BW, 4 V/ μ s slew rate, integrated comparator, 0.1% gain error
In-line	INA240-Q1	80-V operational, 400-kHz BW, high CMRR, ultra-precise
	INA253-Q1	Similar to the INA240, but includes an integrated shunt resistor.
Low-side	INA180-Q1/INA181-Q1	Optimized for 0-V V_{CM} , 350-kHz BW, 2 V/ μ s slew rate, dual and quad package options
	INA302-Q1/INA303-Q1	Internal window comparator, bi-directional, 0.075% gain error, 550-kHz BW, 4 V/ μ s slew rate
	INA293-Q1	-4-V operational, -20-V survivable, 1-MHz BW, 3 V/ μ s, high CMRR, 2.7-V to 20-V supply rail
	INA186-Q1 (INA190-Q1)	Can extend negative V_{CM} range with kilo- Ω input resistors

5 Brushed-DC Motor Ripple Counting - Simple Simulation for Low-Side Current Sensing

Brushed DC (BDC) motors are prevalent for positioning many light loads in the vehicle. Motor current is usually provided from a half or full bridge connected to a battery. These examples will highlight using the INA180-Q1 and INA181-Q1 to measure low-side BDC current.

DC current is used to keep the motor running in a single direction, but current ripples occur as adjacent commutators are shorted during motion. This results in a small AC current ripple superimposed on the DC current driving the motor. Detecting these ripples will provide information on motor speed and position.

Let's consider how to measure low-side ripple-current on a full-bridge for a single BDC motor. DC current varies from 1 A to 20 A, and current is not pulse-width modulated (PWM). Ripple current can peak at 0.83 A and occurs at 333 Hz. A 5-V power rail is available. This example assumes the current ripple shape and amplitude were measured directly in the system.

First, create the current ripple waveform in a numerical programmer such as Microsoft Excel. Equation in Figure 2 dictates the shape of a single current ripple. It allows designer to model the current ripple as a piece-wise function with a linear charging half and then a logarithmic discharging component. T_s represents the sample time of the function, N is the number of points, I_{Peak} is the peak-to-peak AC-coupled amplitude in Amps, λ is the discharging time constant, and α is small current value to set the final discharging point before the ripple repeats.

$$I_{RIPPLE} = \begin{cases} \frac{I_{Peak} * T_S * N, 1 \leq N \leq 751}{t_{Rise}} \\ I_{Peak} * e^{(-\lambda * T_S * N)}, 752 \leq N \leq 1996 \\ \lambda = \frac{-\ln(\frac{\alpha}{I_{Peak}})}{t_{Fall}}, \alpha = 10^{-5} \end{cases}$$

Figure 2. Equation to Model BDC Current Ripple

Place a Current Generator TINA block into simulation, double-click it, and then click on the Signal text and ellipsis soft-key to open the Signal Editor window. Click the Arbitrary Waveform soft-key and copy and paste the time and current values directly into the waveform text window.

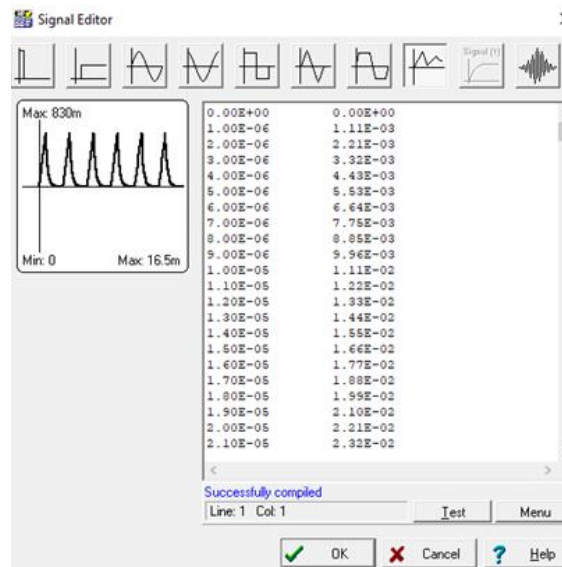


Figure 3. Creating BDC Current Ripple in TINA-TI

This circuit can require some iterative design to balance the CSA measuring from 1 A to 20 A while also amplifying the ripple without saturating the output of the device. As a start, minimize the shunt resistor to the smallest resistance that can be accurately sensed within manufacturer’s capability. This helps minimize power dissipation.

Table 2 is the summary of four possible solutions. Please keep in mind these solutions do not include extra signal chain/conditioning circuitry, however, an example signal chain is shown and can be applied to all of these solutions.

Table 2. Circuit Solutions for BDC Ripple Counting

CIRCUIT	HARDWARE	BENEFITS	TRADEOFFS
A1	INA2180-Q1	No reference needed. Utilizes entire full-scale range (FSR). Can measure low-side recirculating currents.	Two total ADC/GPIO inputs needed. 2x signal chain circuitry
A2	INA2181-Q1 + Reference voltage	Better suited for measuring fast PWM motor currents as output won't have to come out of saturation. Easier to perform one-time offset calibration.	Same as A1 except the Dynamic range reduced compared to solution A1. Need reference voltage circuitry
A3	INA2181-Q1 + Dual channel op-amp	Adjustable gain. One ADC input. No reference needed. Can measure recirculating currents. Can use lower gain, faster BW CSAs. Only one signal chain needed. Simple modification to offset output voltage to work with fast PWM currents.	Need extra op amp for each half-bridge

Table 2. Circuit Solutions for BDC Ripple Counting (continued)

CIRCUIT	HARDWARE	BENEFITS	TRADEOFFS
A4	One INA240-Q1	One CSA. INA240 can self-generate $V_s/2$ reference voltage. One ADC input. Can measure recirculating currents. Better suited for PWM motor current.	Need high AC CMRR CSA. Reduced FSR and ripple amplification. IC cost

5.1 Circuit A1 - One Low-side, Unidirectional INA2180-Q1 (or Two INA180-Q1)

This is the basic solution where one INA180-Q1 is used for each half-bridge leg. The INA180 is unidirectional so it does not have a reference pin to offset the output voltage and cannot measure bidirectional current alone. However, in this solution, one of the INA180-Q1s can measure low-side recirculating current while the other is saturated with a negative shunt voltage.

Figure 4 shows the complete circuit, but is simplified into a more practical simulation schematic in Figure 5. Executing transient simulations with open switches and floating amplifier inputs requires more setup time and simulation time. From now on, in this document, the simplified schematic is shown and used to generate waveforms since each bridge will have the same current. Figure 6 and Figure 7 show the transient simulation results of Circuit A1.

 


Figure 4. Complete Schematic for Circuit A1

 


Figure 5. Simplified Schematic and Simulation for Circuit A1

 


Figure 6. Circuit A1 Transient Simulation at 20-A Motor Current

 


Figure 7. Circuit A1 Transient Simulation at 1-A Motor Current

The transient simulations demonstrate that the INA180 can amplify an 830 mA ripple into a 166 mV output ripple ($V_{OUT, RIPPLE}$) over a 1 A to 20 A DC range using a 1-m Ω shunt resistor. Keep in mind that many BDC motors do not operate as high as 20 A. If the 20-A operating current requirement is lower for an application, then R_{SHUNT} and $V_{OUT, RIPPLE}$ can be increased.

Note that the remaining signal chain design is heavily dependent upon customer's system requirements. Although, given the accuracy of the models, an engineer can take these simulations and add filtering/amplification circuitry or SAR ADC front-end models to the V_{OUT} node. Many CSA models incorporate bandwidth and closed-loop output impedance (Z_{OUT}) behavior (among other things), which are needed to generate realistic signal chains.

An example signal chain for counting ripple currents from the [TI Design TIDA-01421](#) is shown in [Figure 8](#). The purpose of this signal chain is to convert each ripple into countable pulses for a digital I/O pin. [Figure 9](#) combines the schematics from [Figure 5](#) and [Figure 8](#), and the complete transient simulation is shown in [Figure 10](#).

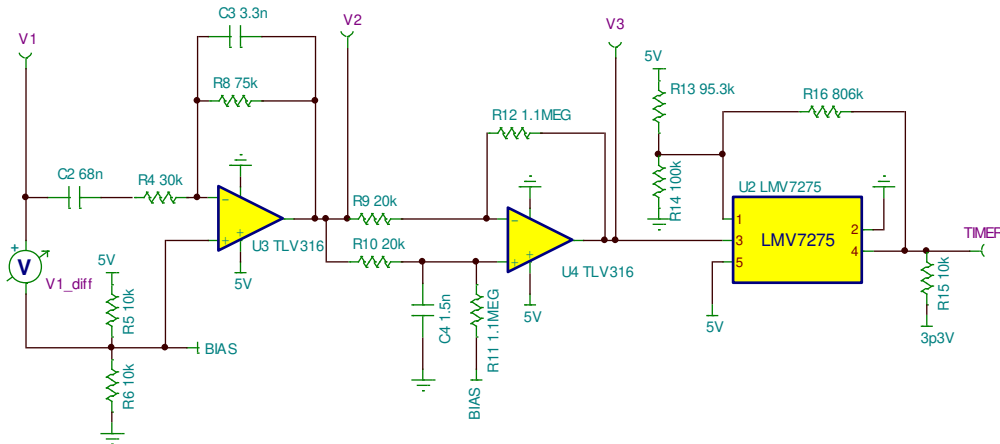


Figure 8. Example Signal Conditioning for Counting Ripple Currents from TIDA-01421

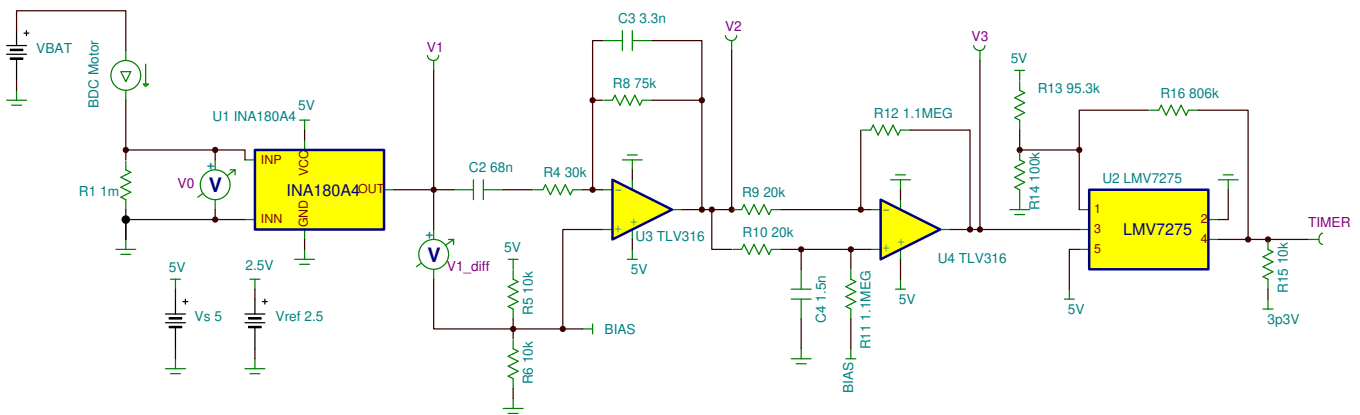


Figure 9. Circuit A1 with Ripple Counting Signal Conditioning Circuitry

 


Figure 10. Simulation of Circuit A1 and Complete Ripple Counting Signal Conditioning Circuitry

Note that this same signal chain can be used for all of the following circuit solutions and all simulation files are included with this design.

5.2 Circuit A2 – One Low-side, Bidirectional INA2181-Q1 (or Two INA181-Q1s)

The second solution shown in Figure 11 is almost the same as Circuit A1, except the INA2180-Q1 is replaced by the INA2181-Q1, the gain is reduced from 200 V/V to 100 V/V, and the output is offset by 2.5 V. The bidirectional versions of any CSA have the reference pin available to drive so that the V_{OUT} can be offset, allowing for both positive and negative currents to be measured.

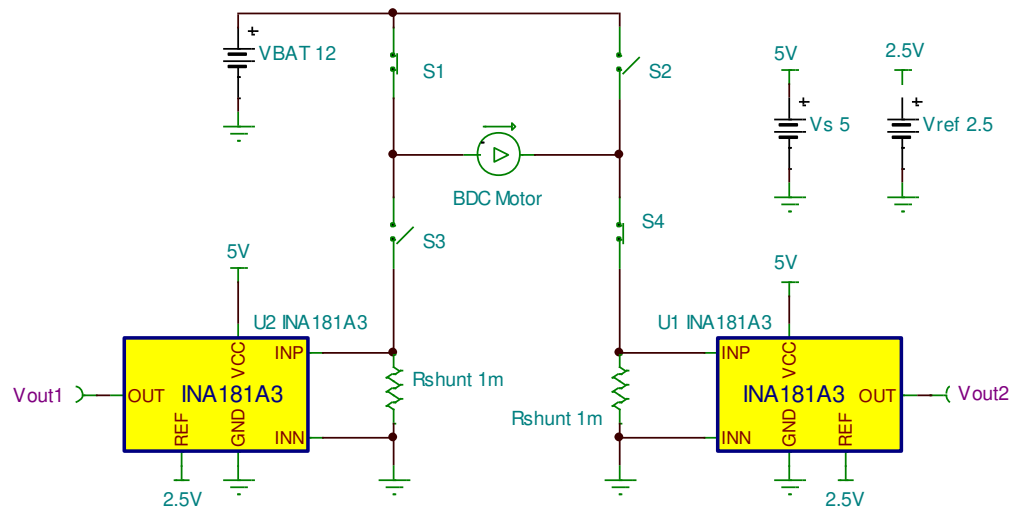


Figure 11. Complete Schematic for Circuit A2

The key benefit of offsetting the output voltage is avoiding output saturation when the motor current is ≤ 0 A. If the output is in saturation, then there is an extra delay (overload recovery time) during an input step response. This delay time becomes especially important when the motor current is pulse-width modulated (PWM) or duty cycles become very short. These scenarios give less time for the output to settle and ripples to be counted completely. Figure 12 and Figure 13 are the transient simulation results of Circuit A2.

 


Figure 12. Circuit A2 Simulation Waveform at 10-A Motor Current

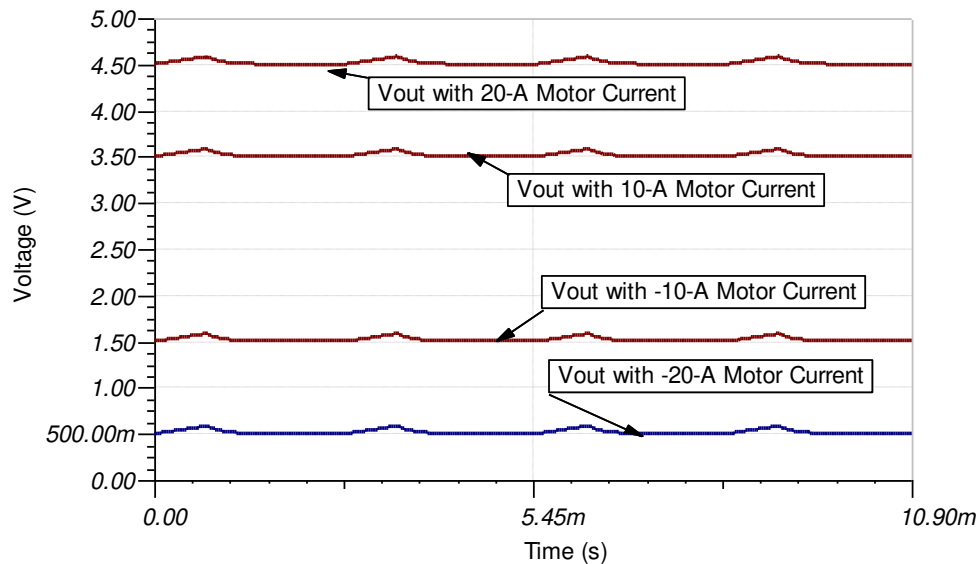


Figure 13. Circuit A2 Simulation Waveforms for Multiple Motor Current Levels

The tradeoffs of Circuit A2 are a compressed $V_{OUT, RIPPLe}$ voltage (83 mV) and extra circuitry to provide the V_{REF} voltage. Referencing the INA2181 to its mid-supply (2.5 V) is usually done because it is cheaper and the positive and negative load currents are symmetrical; however, the recirculating currents for BDC motors are not as high as the positive phase current. Thus, if one wants to maximize their dynamic range, then measuring and characterizing these recirculating currents is necessary to determine the correct value for V_{REF} . Note that in Figure 13, the full-scale range of DC motor current has now expanded to ± 20 A with the mid-supply reference.

5.3 Circuit A3 – One Low-side, Bidirectional INA2181-Q1 Converted into Current-output with Two Op Amps

The next circuit solution shown in Figure 14 transforms the CSAs from voltage-output to current-output circuits and then sums the current outputs together. This procedure is based off the Howland Current Pump and the design procedure for it can be found [here](#).

One benefit here is reducing the ADC input count needed to measure current for each half-bridge. This is possible because the circuit that is sensing 0 A does not add anything to the output current signal, thus the total current output only reflects the current of one half-bridge at a time.

Another benefit is that the load resistor that converts the output current to ground-referenced voltage can be relatively low-impedance and does not interact with downstream signal chain or SAR ADC operation. R_{OUT} also provides the ability to adjust overall circuit gain. The drawback of Circuit A3 is that measurement of each leg is indistinguishable of the other, and op amp buffers in the feedback are necessary for the circuit to maintain high common-mode rejection (CMR). Figure 12 and Figure 16 shows the simulation results for Circuit A3.

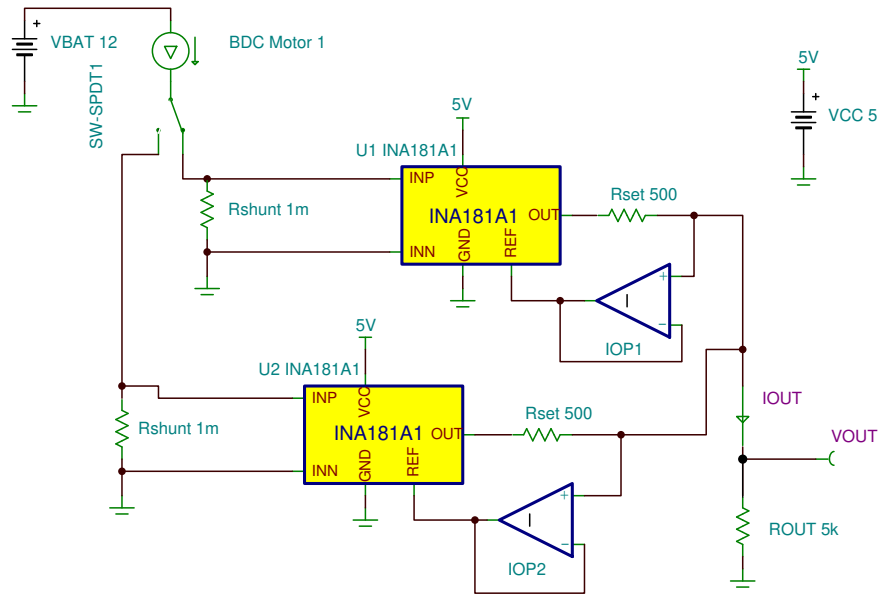


Figure 14. Simulation Schematic For Circuit A3

 


Figure 15. Circuit A3 Transient Simulation for 20-A Motor Phase Current

 


Figure 16. Circuit A3 Transient Simulation for 1-A Motor Phase Current

Note that the amplified ripple is the same magnitude as seen in Circuit A1 simulations.

One additional benefit with this circuit is the ability to decrease settling time by including the optional C_{SET} capacitors (see Figure 17). These work as feedforward caps that boost output response time at the expense of output overshoot. The C_{SET} value should be chosen carefully and can be experimented with using the TINA simulation environment given the CSA models have the correct Z_{OUT} and closed-loop gain (A_{CL}).

Another benefit of Circuit A3 is that the output voltage node can be offset by adding one resistor or current source. Offsetting the V_{OUT} node is effectively the same as providing a reference voltage for a bidirectional CSA. Doing this yields the same benefits as Circuit A2, where the output is always in the linear region and can react as quickly as possible to step inputs from PWM motor currents.

Figure 17 shows both optional modifications of Circuit A3.

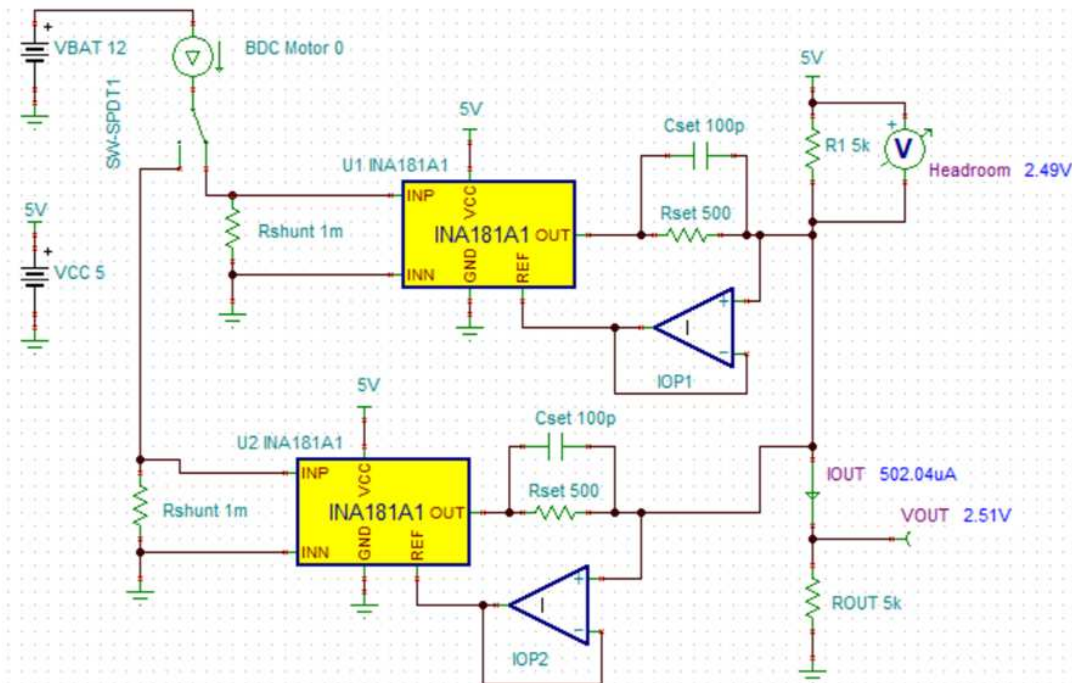


Figure 17. Circuit A3 with Modifications at 0-A Motor Current DC Simulation

One significant drawback to Circuit A3 with the offset output (Figure 17) is the loss of dynamic range due to the headroom voltage. The headroom voltage must remain high enough so that the INA181 is not swinging too close to its supply rail (V_S) and the V_{CM} of the op amp is not approaching the maximum operating value. The same is true for the swing-to-ground of the INA181 and the minimum operating V_{CM} of the op amp.

Offsetting the V_{OUT} to 2.5 V in Figure 17 results in a reduced dynamic range of ± 17 -A motor current; however, given that recirculating currents probably do not approach the motor rating, R1 can be increased to 10 k Ω to shift the dynamic range to -9 A to +20 A where V_{OUT} ranges from 480 mV to 4.35 V, respectively. The circuit behavior after changing R1 to 10 k Ω can be seen in Figure 18 and Figure 19. After making this change, the $V_{OUT, RIPPLE}$ voltage becomes 110 mV.

 


Figure 18. Circuit A3 with Modifications (R1 = 10 kΩ) Transient Simulation at 20-A Motor Current

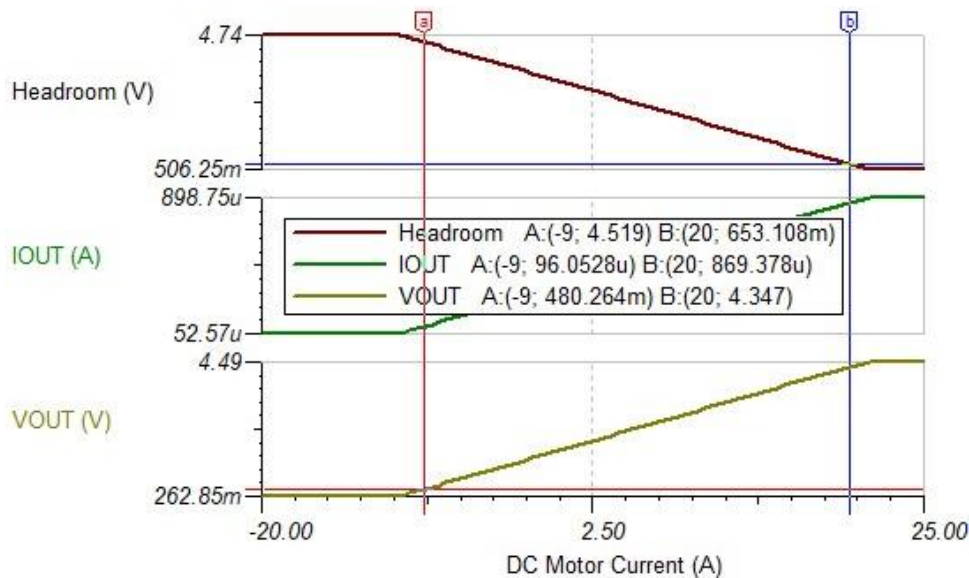


Figure 19. Circuit A3 with Modifications (R1 = 10 kΩ) DC Motor Current Range Sweep

5.4 Circuit A4 – One In-line, Bidirectional INA240-Q1

This circuit solution is used in the TI Design TIDA-01421 and moves the position of the CSA to in-line with the bridge. Specifically chosen for its unique PWM rejection circuitry and thus high AC CMR, the INA240 is the best choice for this application, since the output can settle quickly after phase current switches direction and V_{CM} changes rapidly.

The INA240 is a very accurate device (maximum 25 μ V offset) with good bandwidth (400 kHz). Furthermore, the INA240 is bidirectional, so only one device is needed to measure all phase and recirculating currents.

Using only one CSA for all currents has the drawback of a reduced dynamic range, compressed $V_{OUT, RIPPLE}$, and increased shunt power dissipation. The measured $V_{OUT, RIPPLE}$ for the reference design ranged from 100 mV to 250 mV depending on battery voltage and motor torque. While this is greater than the 166 mV ripple in the previous solutions A1 and A3, it was accomplished at the expense of higher shunt power dissipation and a reduced motor current range of ± 16 A.

For the sake of comparison, the shunt resistor can be reduced to 1 m Ω and the INA240A3 (gain of 100 V/V) can be substituted in to yield the simplified schematic in Figure 20. This is effectively the same schematic as Circuit A2, however, there is no way to increase $V_{OUT, RIPPLE}$. This is because the INA240 must remain referenced at mid-supply to measure both phase currents since this is an in-line application. Figure 21 and Figure 22 show the entire transient simulations with the 830-mA current ripple and motor current at 20 A in both motor directions.

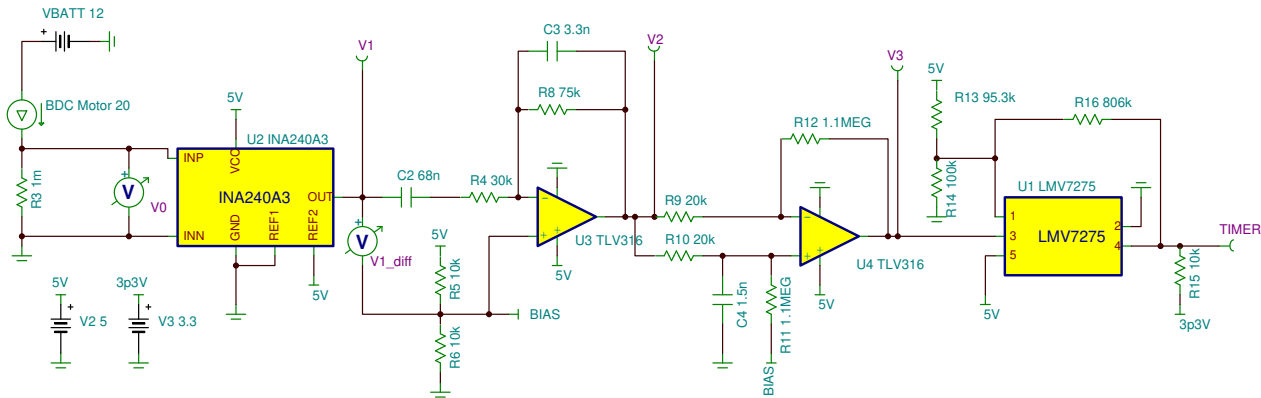


Figure 20. Circuit A4 with Ripple Counting Signal Circuitry

 


Figure 21. Circuit A4 Transient Simulation at 20 A (Forward Direction)

 


Figure 22. Circuit A4 Transient Simulation at -20 A (Backward Direction)

6 High-Side Stepper Motor Stall Current Detection

Detecting a motor stall is useful to determine if there is a mechanical fault condition, or if the motor has reached its final destination. If a motor is stalling, the motor current increases. This example uses a current sense amplifier to measure high-side current, which allows a control system to detect a stall by making a decision on the peak current. The engineer must characterize the stall current sufficiently to determine an appropriate stall current threshold.

Consider the example of measuring high-side current for two H-bridges driving current for a bipolar stepper motor as shown in Figure 23. A driver and algorithm control the switching, so assume continuous phase current lasts for 2.5 ms and the FET ON pulse is separated by 20 μ s of dead time. This is a non-overlap stepper motor control example.

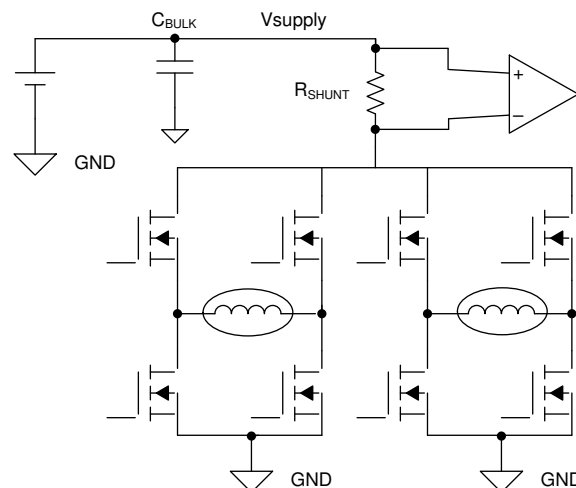


Figure 23. Measuring High-Side Bipolar Stepper Motor Current

Placing the shunt resistor (R_{SHUNT}) before or after the bulk capacitance (C_{BULK}) makes a difference in the current amplitude since the bulk capacitor is responsible for keeping the supply voltage stable during switching. There are pros and cons, but inserting the shunt in between C_{BULK} and the shared high-side supply trace allows you to sense the exact motor current. As always, it is best to measure these currents with hardware first so the real current waveform can be incorporated into simulation.

The simulation circuits for this section models the stepper motor as a resistor and inductor. To simplify the operation of the H-bridge, the simulation uses just one time-controlled switch ("FET"). This emulates the high-side current of both H-bridges. Another time-controlled switch ("Stall") suddenly increases motor current at 6.1 ms simulation run-time.

Table 3 is a summary of the potential circuit solutions.

Table 3. Summary of Circuit to Sense High-Side Stepper Motor Stall Current

CIRCUIT	HARDWARE	BENEFITS	TRADEOFFS
B1	INA180-Q1	No reference needed. Utilizes entire full-scale range. Can increase shunt resistance to remove overload recovery.	V_{OUT} enters non-linear regions when $I_{MOTOR} = 0$, which adds output delay time.
B2	INA181-Q1 + Reference voltage	Better suited for measuring fast PWM motor currents, as output does not have to come out of saturation. Easier to perform one-time offset calibration since measuring a differential output voltage. 50 mV reference voltage yields low impedance to REF pin, which minimizes error from loading REF pin.	Need reference voltage circuitry. Reduced dynamic range. May need a buffer to drive REF pin depending on the ADC being used.

6.1 Circuit B1 – One High-side, Unidirectional INA180A4-Q1

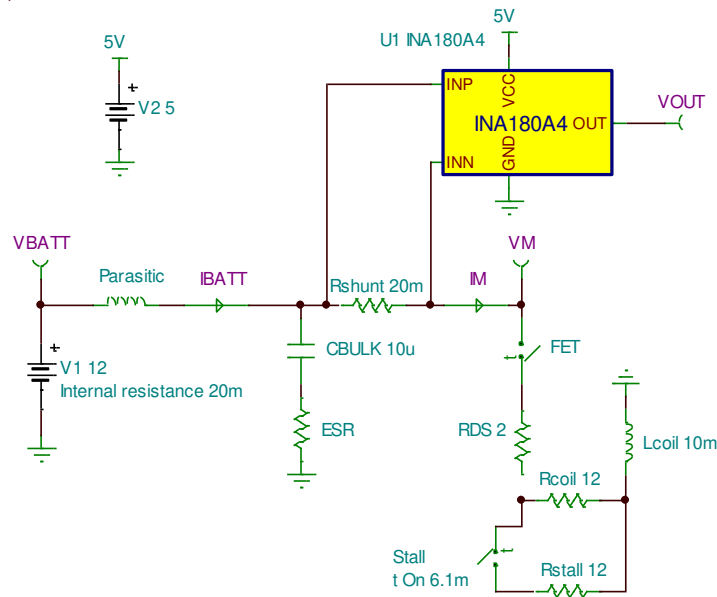


Figure 24. Circuit B1 Simulation Schematic

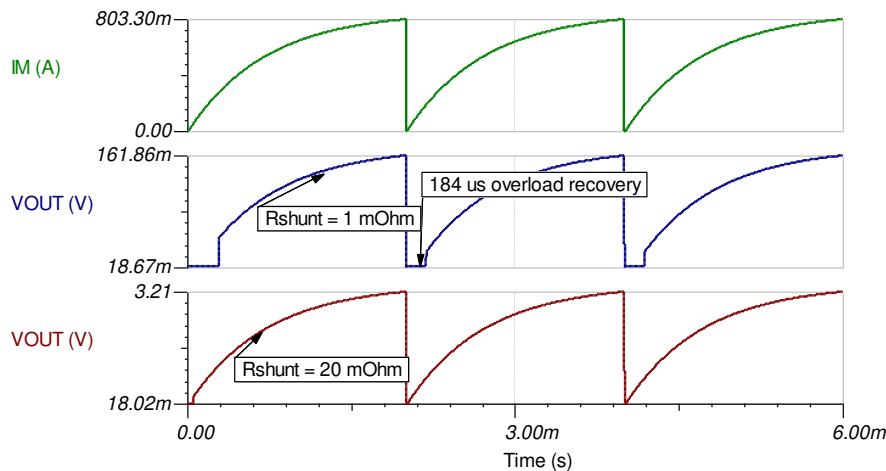


Figure 25. Circuit B1 of Transient Simulation for Normal Motor Operation with Two Shunt Values

 


Figure 26. Circuit B1 Transient Simulation with Stall Current and Two Shunt Values

Circuit B1 shown in Figure 24 is most likely the best option for measuring stepper motor stall current. Despite the occurrence of output saturation when motor current is 0 A during H-bridge dead time, there is still plenty of time for the INA180-Q1 to catch up for this relatively slow motor. Additionally, as shown in Figure 25, if the overload recovery time must be avoided, the engineer can increase the shunt resistance to 20 mΩ which accelerates the shunt voltage rise and forces the INA180 out of saturation quicker.

An additional benefit of using a larger shunt resistor is the difference between V_{OUT} for nominal and stall currents increases as shown in Figure 26. When R_{SHUNT} is 1 mΩ, the difference in V_{OUT} between the normal 800-mA and 1-A stall currents is 201.3 mV - 161.9 mV = 39.4 mV. This delta becomes 788 mV for a 20-mΩ shunt. Therefore, increasing R_{SHUNT} increases current measurement resolution and makes the system more immune to potential current transients or noise. The obvious tradeoff is the increase in power loss.

6.2 Circuit B2 – One High-side, Bidirectional INA181-Q1

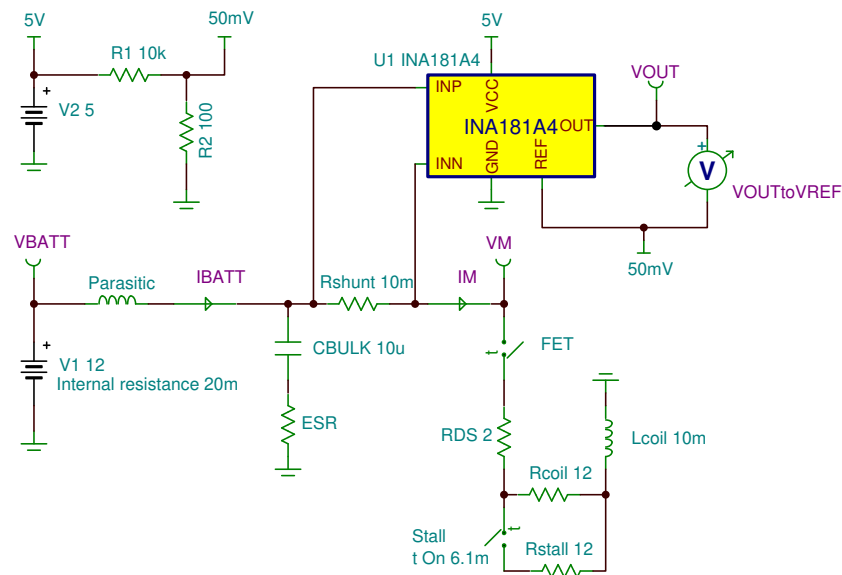


Figure 27. Circuit B2 Simulation Schematic

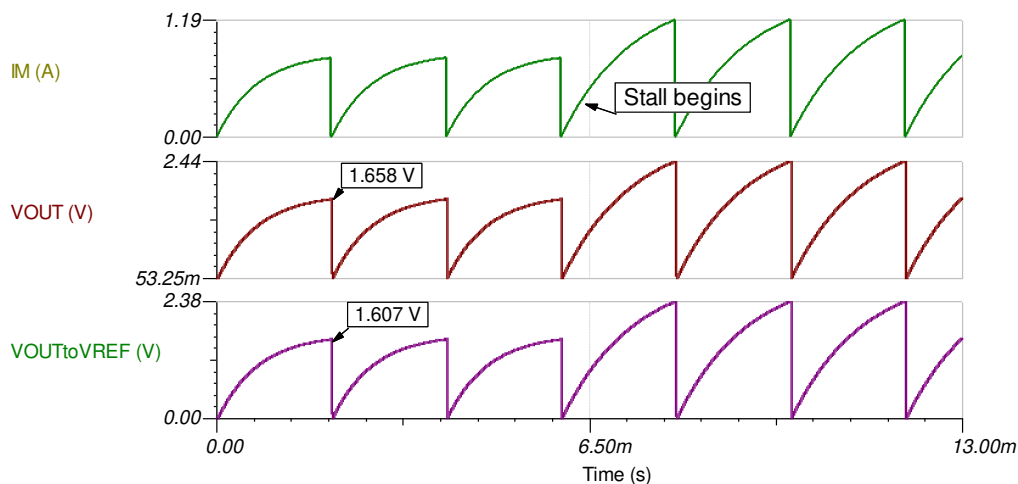


Figure 28. Circuit B2 Transient Simulation of Switching in Stall Current

Circuit B2 (shown in [Figure 27](#)) is the same as B1, except the bidirectional INA181-Q1 is used so a reference voltage can offset V_{OUT} . This scheme is only necessary if there is pulse-width modulation (PWM) to be sensed or if the stepping is done at very fast speeds (>20 kHz) where overload recovery time cannot be accepted. Another benefit with Circuit B2 is that a one-time offset calibration can be performed at every start-up, simply by reading V_{OUT} with no load current. If measuring small shunt voltages is important, then offset calibration reduces measurement error significantly. Note how in [Figure 28](#), the INA181 is responding immediately to the changing motor current since it is offset by 50 mV and is always in the linear region. The V_{OUT} waveform for Circuit B2 is actually the differential output measurement of the INA181.

7 High-Side Averaging PWM LED Current Sensing

The accuracy of a CSA provides the ability to sense undercurrent events, which is important for ensuring sufficient lighting levels for LEDs. When driving LEDs with a PWM current, measuring peak current can become unfeasible for very low duty cycles. Once the ON current time falls below a microsecond, most current sense amplifiers will fail to settle to an accurate voltage level before current falls back to 0 A.

One way around this is to average the shunt voltage signal before amplifying with a CSA. To average the shunt voltage, a differential RCR, PI filter is used at the input of the CSA. Many CSAs are low-input impedance (2 kΩ to 4 kΩ differential) and thus do not work infallibly with input resistors since this reduces effective gain and increases gain error. The increase in gain error is due to the fact that the CSA internal resistors are trimmed to a precise ratio, not an absolute value. Choosing a high input-impedance CSA, such as the INA190-Q1 or INA186-Q1, can mitigate this issue.

Consider how to measure high-side LED current from a PWM, current-controlled LED driver. The current frequency is 40 kHz (25 μs period), the highest duty cycle is 97% (24.36 μs ON time), and the lowest duty cycle is 1% (240 ns ON time). The LED load waveform shown in Figure 29 is created by double-clicking a current generator source, changing the signal to “General Waveform”, and setting the current amplitude, ON and OFF times.

 


Figure 29. Creating the High Duty Cycle Current LED Load

7.1 Circuit C1 – 42-V High-impedance CSA (INA186-Q1) with Input Filter

The solution shown in Figure 30 is used for the high-input impedance CSA INA186-Q1, or its more accurate version, the INA190-Q1. This device has an input differential impedance of 4.6 MΩ, so device performance is not significantly affected by large input impedance. Using the equation in the INA186-Q1 data sheet and setting differential input impedance to 4.6 MΩ, the system designer calculates only a 43.5 m% increase in gain error.

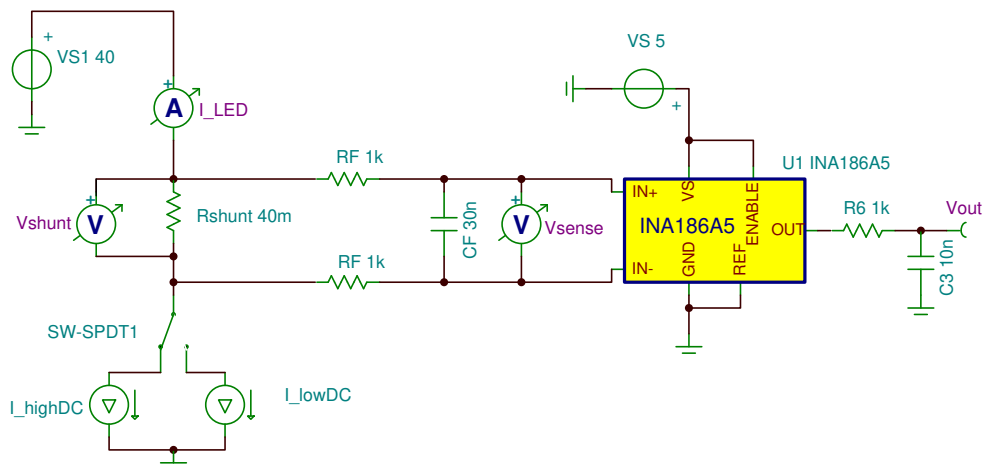


Figure 30. Circuit C1 INA186-Q1 with Input Filter Averaging PWM Current

 


Figure 31. Circuit C1 Transient Simulation with 1% Duty Cycle Current

 


Figure 32. Circuit C1 Transient Simulation with 97% Duty Cycle Current

The transient simulations of Circuit C1 (Figure 31 and Figure 32) show that the filtered input sense voltage (V_{SENSE}) varies from $\sim 100 \mu\text{V}$ to 9.37 mV, which is within the input dynamic range of the INA186A5-Q1. The input filter has a cutoff frequency of 2.654 kHz, or $1/(4 \cdot \pi \cdot R_F \cdot C_F)$. Try to reduce the tolerances of input filter components so averaged current values remain consistent.

7.2 Circuit C2 – 60-V Transconductance CSA (INA169-Q1) with Input Filter and Output Offset Modification (Requires Offset Calibration)

For LED boost drivers, the high-side voltage can be much higher than 42 V. Applications requiring high-side measurements up to 60-V need a high-voltage CSA. This example uses the INA169-Q1. While the INA16x/INA13x-Q1 families do not have a high input impedance like the INA186-Q1, the transconductance architecture (see Figure 33) allows the user to calculate the exact effective gain of the circuit once a known input resistance is used. Note that R_{G1} resistors are trimmed to the exact resistance reported in data sheet.

 


Figure 33. Internal INA169-Q1 Architecture

Figure 34 is the simulation schematic for the Circuit C2, showing the added input resistors (R_F) to the INA169. To calculate the new circuit gain when using an input filter with the INA169, simply add R_F to R_{G1} and take the reciprocal to get the new transconductance value. For Circuit C2, the new gain is $1 / (1 \text{ k}\Omega + 50 \text{ }\Omega) = 952.38 \text{ }\mu\text{A/V}$.

The INA169 has a substantial maximum input offset of $\pm 2 \text{ mV}$, thus modifications must be made to negate this offset. One way is to offset the output of the amplifier (see data sheet) by connecting a resistor from OUT to its 5-V supply rail. While this brings the output into the linear region for low LED currents, the extra step of offset calibration is needed to determine the zero-current voltage of the circuit. This is the only practical way to negate resistor tolerance and IC offset errors.

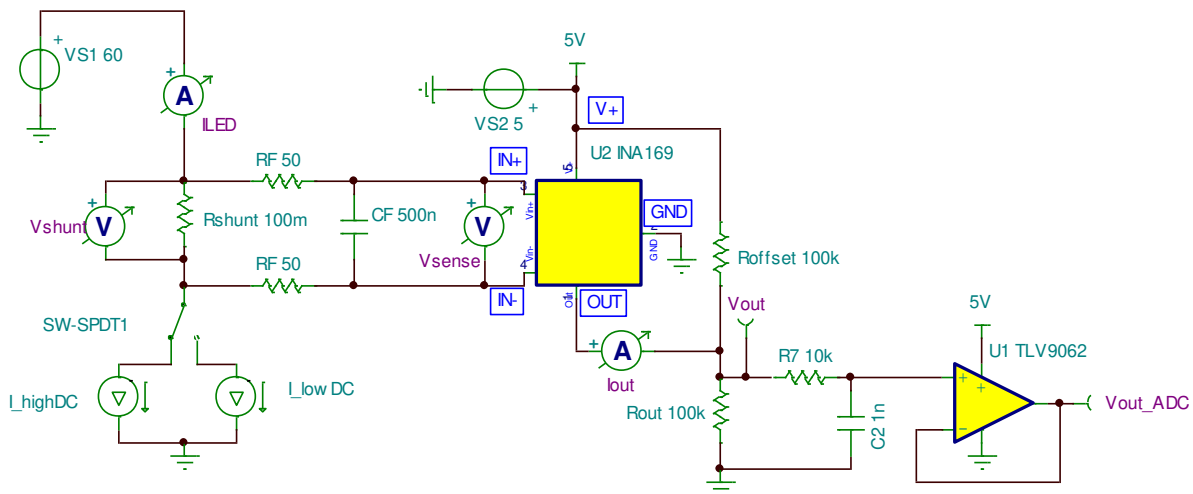
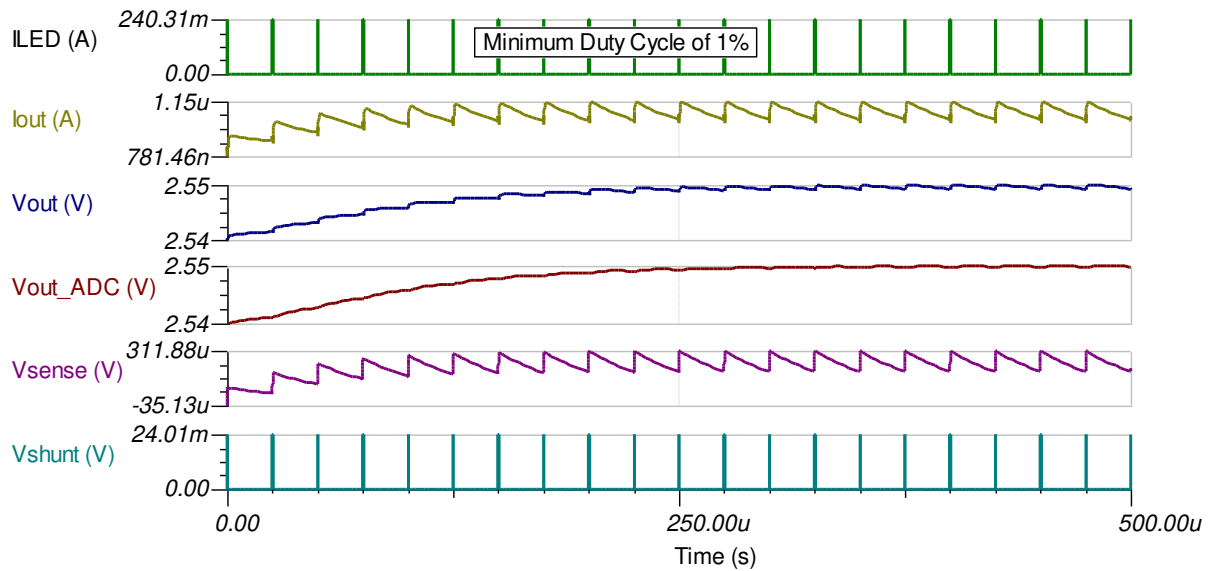
 


Figure 34. Circuit C2 INA169-Q1 with Input Filter Averaging PWM Current


Figure 35. Circuit C2 Transient Simulation for 1% Duty Cycle

Figure 36. Circuit C2 Transient Simulation for 97% Duty Cycle

Circuit C2 simulations (Figure 35 and Figure 36) show the zero-current voltage to be 2.54 V. During the 1% duty cycle, the V_{OUT} rises to 2.55 V, then reaches 3.65 V for the 97% duty cycle.

8 Summary

This document has covered how to choose a CSA that fits a range of requirements when monitoring loads associated with electronic control units, specifically in the automotive space. Several complete current sensing solutions were suggested and verified in TINA-TI simulation.

9 References

A special thanks to contributions of Dan Harmon and Steven Loveless.

- [TI Design TIDA-01421 Automotive Brushed-Motor Ripple Counter Reference Design for Sensorless Position Measurement](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated