

Load-sharing techniques: Paralleling power modules with overcurrent protection

By Lisa Dinwoodie (Email: lisa_dinwoodie@ti.com)

Power Applications Specialist

Paralleling low-current, low-voltage power modules for high-current, low-voltage applications has many benefits. Among them are: redundancy for enhanced reliability, hot-swap capability, distributed heat removal, and design flexibility. Paralleling power stages requires load sharing in order to equalize the stresses among the modules. One method of load sharing, based upon the automatic master/slave architecture, is to use a dedicated controller, such as the UCC39002, to provide for equal current distribution of the load current among the parallel-connected power supplies. The power modules must be equipped with true remote-sense capability or an output-adjustment terminal. The output current of each module is measured and compared to a common load-share bus. The positive sense voltage or the voltage of the output voltage adjust pin of each module is adjusted to provide equal current sharing.


Several modules are paralleled so that the entire assembly can support a full load much greater than an individual module would be capable of supplying. Due to manufacturing tolerances and component variations, startup delay times typically vary slightly from module to module. When the modules to be paralleled have an overcurrent protection circuit featuring constant current limit with automatic recovery, starting up fully enabled into the full system load does not pose a problem. Inevitably, one module will have

a faster turn-on than the others. The eager module will carry as much of the load as it can, sometimes up to 140% of its individual current capacity, before its output voltage falters. Meanwhile, the next module will come up and contribute to the load. After a brief transition time, all of the modules will be up, the master will be recognized, and accurate load sharing will take place.

When the modules to be paralleled have an overcurrent protection circuit featuring a hiccup mode, starting up fully enabled into full system load, regardless of the load sharing technique used, does pose a problem. The module with the fastest turn-on profile will come up into an overcurrent condition. Immediately, in an act of self-preservation, it will go into hiccup mode, alternately sinking and sourcing current. The next module to come up into the load will also fall into this hiccup mode, sinking current when the other module sources it. Because the load-share circuitry essentially adds a voltage loop to the output of each module, this hiccuping overcurrent protection mode will prevent loop closure. Simultaneously enabling the modules will prevent this hiccup mode from starting, and load sharing can be successfully achieved.

Figure 1 shows a simple comparator circuit that will simultaneously enable two modules and can be expanded to accommodate more if needed. It assumes that the only

Figure 1. Logic circuit to turn on two power modules simultaneously

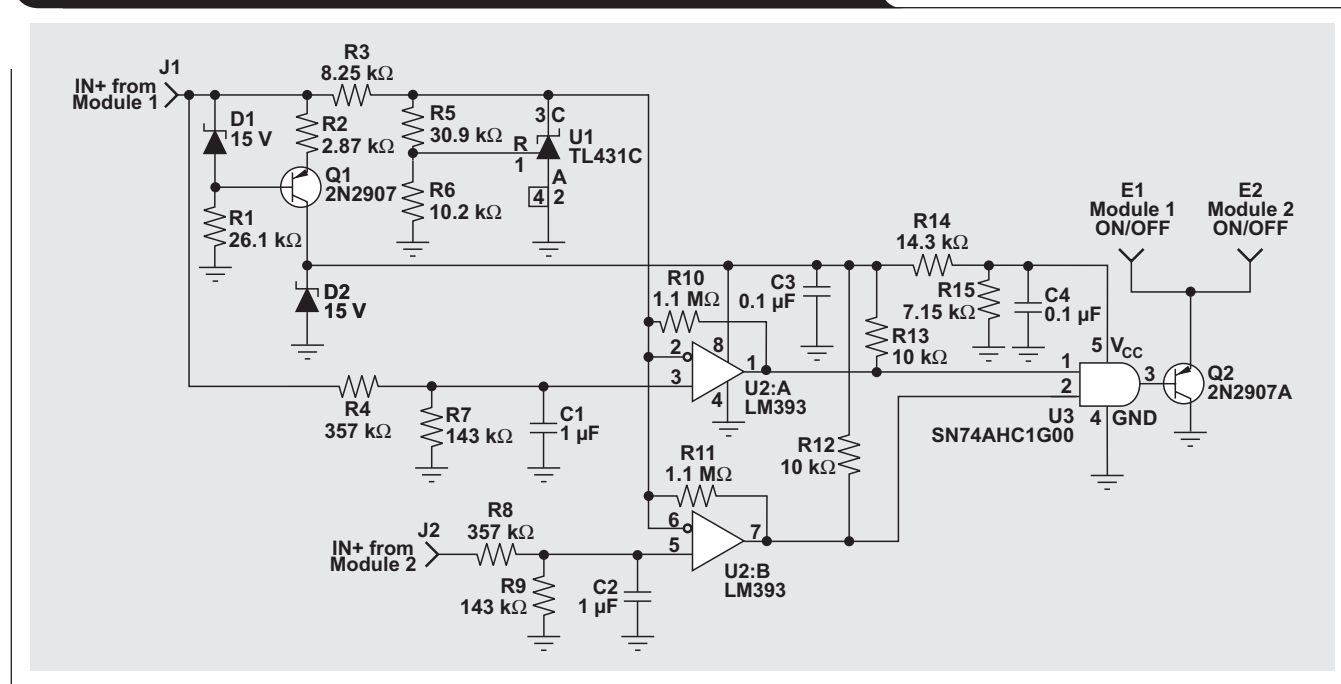

bias available for the logic gates is the 48-Vdc bus used as the input to the modules themselves. The circuit is designed to short the modules' on/off pins to ground simultaneously when their inputs reach 35 V, assuming that the modules' input range is between 36 V and 75 V and that they have a turn-on threshold of approximately 33 V.

The PNP transistor, Q1, its emitter and base resistors, and the two 15-V Zener diodes provide a 15-V, 5-mA bias to the comparators and the NAND gate from the input line, which could vary from 36 Vdc to 75 Vdc. The TL431 is set up to provide a regulated 10-V reference voltage for the inverted comparator inputs. The non-inverted comparator input signals are derived from resistively dividing the input voltages of the modules. Because the bias and

comparator signals are from the same source, capacitors are needed to delay the comparator input signals long enough so that the LM393, U2, is operational and "smart." This circuit is added to the load-share board and successfully turns on the modules simultaneously into a full system load without triggering the overcurrent hiccup mode of the modules.

Related Web sites

analog.ti.com

www.ti.com/sc/device/partnumber

Replace *partnumber* with LM393, SN74AHC1G00, TL431 or UCC39002

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated