

–48-V/+48-V hot-swap applications

By Heping Dai

Systems Design Engineering, Power Management Products, AAP

Introduction

The rapid growth of telecommunications and Internet access systems that run continuously has increased the need for hot-swap solutions that are more reliable and easier to upgrade and repair. Redundant systems or modules are required to prevent the systems from crashing. While redundant systems have been proven to be feasible, they may be costly. Furthermore, the use of a simple redundancy scheme as a backup may not be enough, as overall system integrity may be compromised even though the system is designed to handle such faults. In the end, we have to find a way to update the system regularly by removing redundant parts and/or inserting new modules while the system is still running. That is why hot-plug or hot-swap capability is required in today's high-availability electronic systems.

Realizing the needs of hot-swap applications, Texas Instruments has put a great deal of effort into providing solutions for a variety of end equipment requiring hot-swap capability. TI's hot-swap controllers provide inrush current control during hot insertion and fault protection during operation. They also prevent backplane power disruption during hot removal or insertion.

In particular, the TPS2300/01, TPS2310/11, TPS2320/21, and TPS2330/31 from TI (see References 1–4) cover a variety of hot-swap applications and were primarily designed for 3-V to 13-V applications. TI has already released and is planning several hot-swap devices targeting PCIx, CompactPCI®, and other mass-market applications. Devices like the UCC3913, UC3914, UCC3917, and UCC3921 operate across very wide voltage ranges, from large negative voltages to large positive voltages.

Most telecommunications applications use –48-V or +48-V power supplies, which are then distributed to the cards via the system's backplane. As there are many ways to implement hot-swap in a 48-V system, it is very important to understand the exact requirements of the system before selecting a power management solution. Certain features on some devices may no longer function at higher (or lower) voltage levels, although controlled ramp of power to the card during hot insertion/removal is still possible. By fully understanding the implementation requirements, you may find that there is a larger number of devices available, at a wide variety of price points, depending on the feature set required. The following discussion addresses different topologies in the TPS23xx series of TI's hot-swap controllers.

–48-V hot-swap application with low-side NMOSFET


Due to process limitations, the input voltage of the TPS23xx devices must be limited to 13 V (15 V maximum, dynamic). To manage higher voltages, some type of divider

or converter is required to reduce the input voltage (48 V) to somewhere below 13 V.

There are several implementations that will keep the TPS23xx input voltage below the maximum limit. Figure 1a demonstrates the simplest topology. Two resistors are used to divide the higher input voltage into a lower voltage. However, in this implementation, the voltage at the output of the divider will track all changes in the 48-V input supply. Because the fluctuations and tolerances of the 48-V supply may vary not only from system to system but also based on the operating mode of the system, use of this scheme may affect the functionality of the controller, or possibly damage the device if large variations, or spikes, occur.

A much better, very simple solution consists of a Zener diode in series with a resistor to get a very steady output voltage from the 48-V source (see Figure 1b). This implementation will allow the voltage to be controlled at the divider to match the input voltage requirements of almost any hot-swap power manager. To eliminate noise or control the ramp-up rate of the output voltage, a capacitor should be added as shown in the figure.

Figure 1. Simple voltage dividers

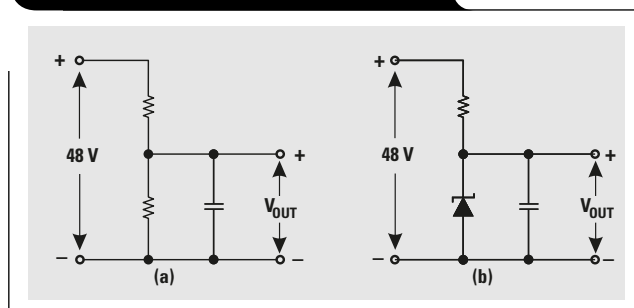


Of course, the performance of many other methods can equal or even surpass that of the Zener diode divider, but such methods tend to be more complicated and more expensive, and may be unnecessary for the –48-V applications. This is why the Zener diode divider is typically used in many 48-V hot-swap applications.

For –48-V hot-swap applications, the plug-in board can be configured as in Figure 2.

In this topology, the Zener diode is a 5.1-V 1N4733A, but higher-voltage (up to 10-V) Zener diodes can be used if desired. Since the TPS2330 consumes very little power for operation, the resistor (in series with the Zener diode) can be as large as 10 k Ω , depending on the threshold voltage desired. The load of the hot-swap control stage is a DC/DC converter—in this case, a Power Trends™ module

Figure 2. TPS2330 for -48-V hot-swap

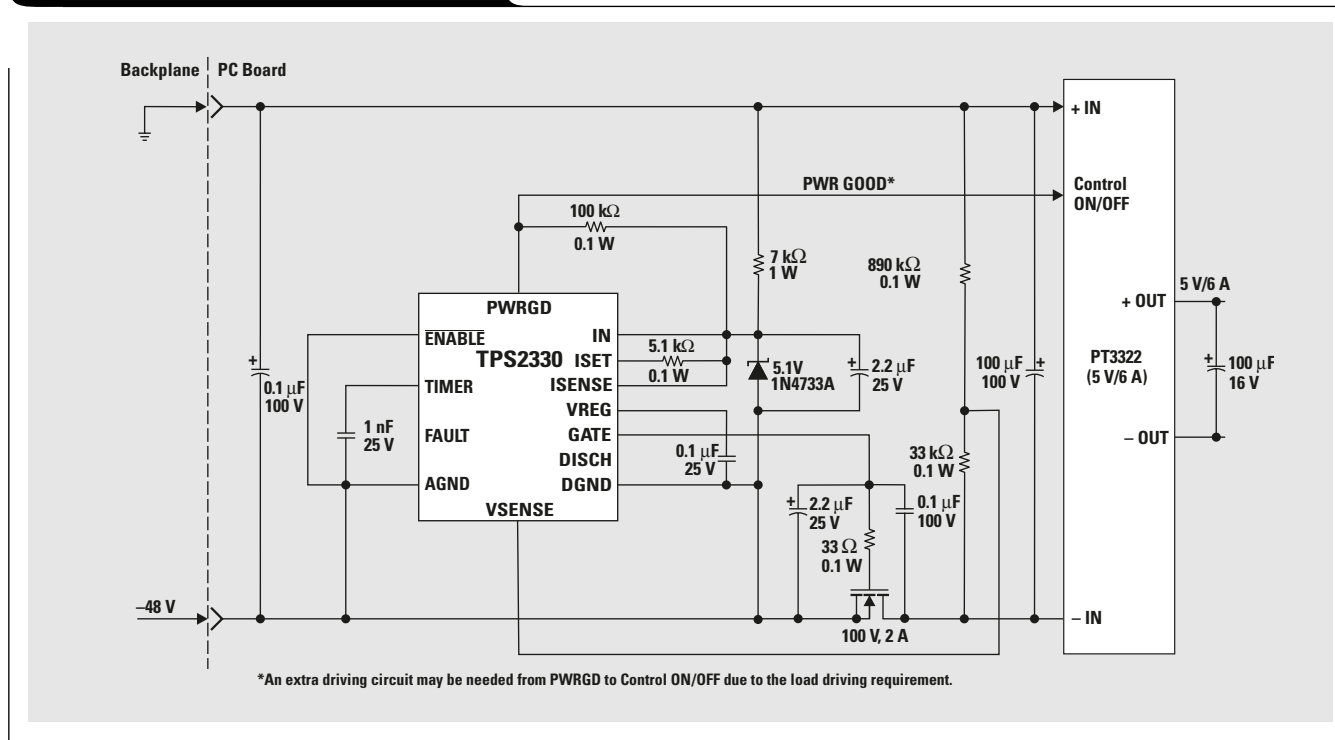

from TI. The main switch is a 100-V N-channel MOSFET, such as IRF530N.

With the component values shown in Figure 2, this circuit can work for -36-V to -72-V applications, which happens to cover the broad range of voltages in telecommunications applications. To make the voltage range wider, the 33-kΩ sensing feedback resistor can be increased.

The curves in Figure 3 show the performance of the TPS2330 during a hot-insertion event. Even though there is a 100-µF capacitor in the output circuit as a load, the inrush current during hot insertion is kept to less than 0.1 A. In a 48-V telecommunications system, a 0.1-A inrush current is negligible and will not cause any problems. If the output capacitance is much bigger than 100 µF, then the

value of the 4.7-µF capacitor between the TPS2330 GATE output and the -48-V rail should be increased accordingly. The output voltage curve seems to ramp up from low to high voltage because the output voltage was measured at ground opposed to -48 V to keep measurement simple and safe. Therefore, what we see on the curve is actually -V_{OUT}.


One shortcoming of this implementation is that the hot-swap controller loses the circuit breaker capability because the TPS23xx cannot sense current at voltages above 13 V. Since most implementations use some type of current-limited regulation scheme to bring the 48 V down to more useful voltages like 3.3 V and 5 V, the circuit breaker capability is merely redundant.

Other high-voltage hot-swap applications

If a hot-swap board has two inputs—for example, one at +3.3 V (potentially a V_{AUX} rail) and the other at -48 V—the TPS23xx family can still be used as shown in Figure 4. The trick here is to use a high-voltage PNP to drive the gate of the main power MOSFET. This minimizes the voltage levels applied to the TPS2300, thereby keeping them well within its operating range. In this example the TPS2300 can control the switching and the inrush current during hot insertion of both the low-voltage (+3.3-V) rail and the higher-voltage (-48-V) rail. The TPS2300 will not sustain any high voltage from the -48-V input, and the +3.3-V rail will still have circuit breaker capability.

However, the first input (+3.3 V) of this hot-swap board can operate only between 3.0 to 5.5 V because the IN2 maximum voltage rating is 5.5 V. To get the IN1's operation range up to 13 V, the connection between IN1 and IN2

Figure 3. Hot-insertion of -48-V system: output voltage (-V_{OUT}) and input inrush current (I_{IN})

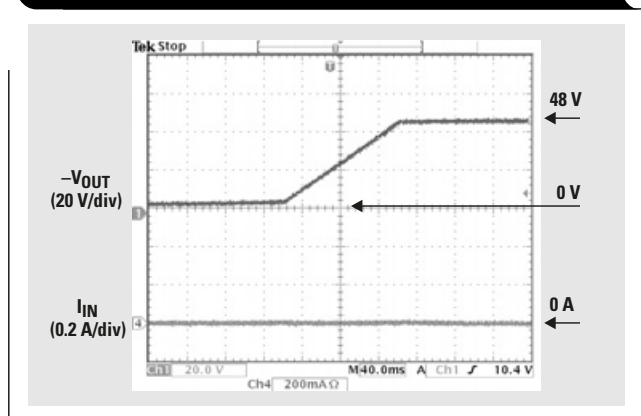

Continued on next page

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	support.ti.com/sc/pic/euro.htm		

Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		ti-china@ti.com

C011905

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: Power Trends is a trademark of Texas Instruments Incorporated. CompactPCI is a registered trademark of PICMG. All other trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated