

# Battery-charger front-end IC improves charging-system safety

By Mao Ye, Applications Engineer, Battery Management Applications

## Introduction


Battery-powered portable devices such as cellular phones have become an important part of people's daily lives in the past few years. Many types of adapters are available to charge the lithium-ion (Li-ion) battery and power the system, and their electrical specifications usually differ from one manufacturer to another. This challenges system designers to build portable devices that will meet safety and reliability requirements when used with different adapters. This article describes a new battery-charger front-end (CFE) IC, the Texas Instruments (TI) bq243xx, which is optimized to improve the safety of charging Li-ion-powered systems. Together with the battery-charger IC and the protection module in a battery pack, a charging system using the bq243xx CFE provides more robust system-level protection.

## Main safety concerns in charging systems

Damage to the charging system can occur due to input overvoltage, input overcurrent, battery overvoltage, or reverse input voltage.

Input overvoltage can be caused by hot-plugging an adapter or using the wrong adapter; or by a transient or steady-state overvoltage condition. The most common occurrences are from hot plugging a charged, unregulated, or incorrect adapter; or from load transients. The unregulated adapter under no load will charge the adapter's output capacitor to the peak rectified AC voltage, about 1.4 times the rated DC voltage. This is often an issue with "low-voltage-process" (7-V-process) ICs. Figure 1 shows the output voltage of a typical regulated adapter versus an unregulated adapter.

**Figure 1. Regulated- and unregulated-adapter load lines**

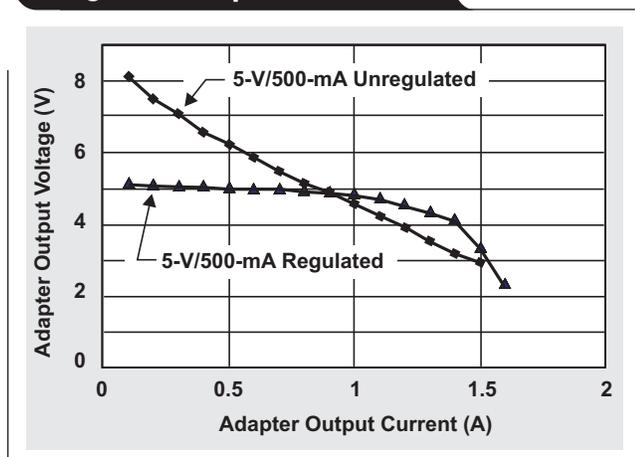



Input-overcurrent challenges are not an issue with stand-alone chargers, since their constant-current mode limits the amount of current delivered to the output or battery. However, with power-path-management parts, which have a direct connection from the input to the system bus voltage, there is often no protection from excessive current draw. Lately there has been some concern over the safety of operating adapters in their current-limit mode and a desire for a programmable input-current-limit circuit to ensure that the adapter does not get into this mode.

Li-ion and Li-polymer battery packs are known for the potentially dangerous "flaming" condition that can occur if they are overcharged under high temperature. The key indication of overcharging is excessive cell voltage. To improve battery safety, many manufacturers are adding second-level overvoltage protection to remove the input power source when battery overvoltage is detected.

With universal connectors, it is a concern that an adapter with reverse polarity will be connected to the input. Without input reverse-polarity protection, the parasitic diode between the substrate and the IC will become forward-biased, causing a malfunction or damage to the IC. The two basic solutions to achieving input reverse-polarity protection are shown in Figure 2. The first solution is to add a diode in series with the input to block any reverse current. However, this will increase the power dissipation. The second solution is to use a low- $r_{DS(on)}$  MOSFET in series with the input to minimize the power dissipation.

**Figure 2. Input-voltage reverse-polarity protection**

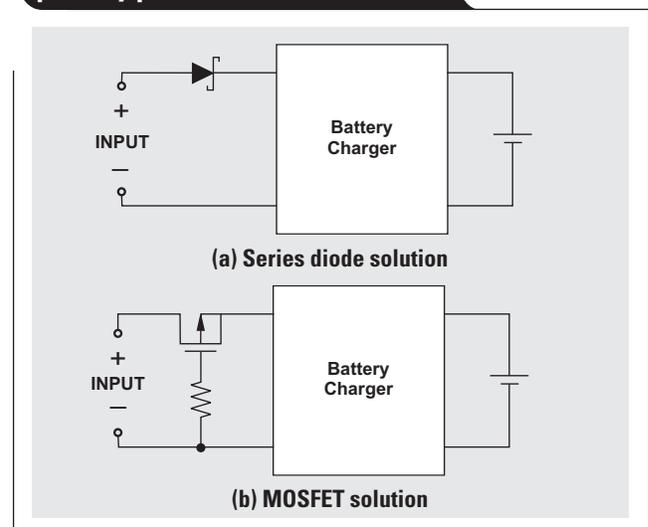


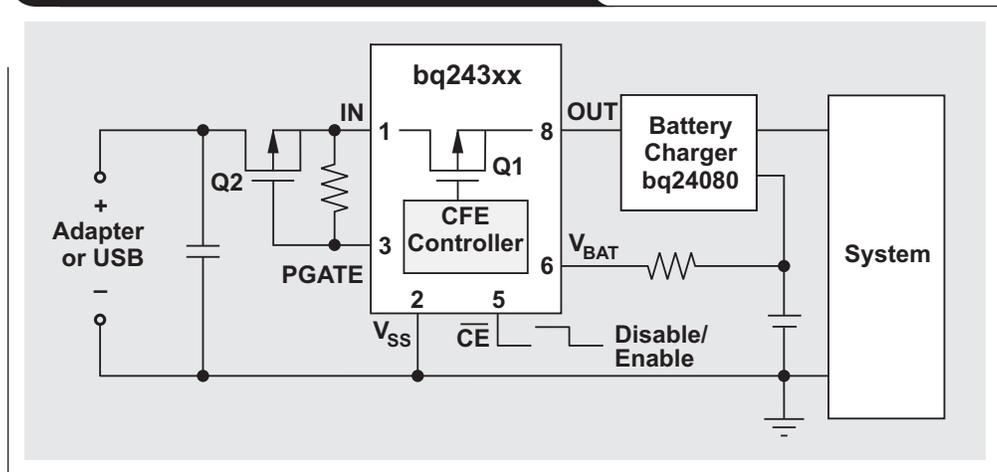
**Figure 3. Typical application circuit with CFE**

### CFE solution for improving battery-charger safety

Figure 3 shows a typical circuit for a battery-charging system with a bq243xx CFE. The CFE protects the system from input overvoltage by isolating high input voltage from the low-voltage charger and system. The bq243xx family offers a soft-start function to avoid inrush current and can provide input-current regulation and protection, output-voltage limiting/regulation, or battery overvoltage protection. Also available are optional features such as PGATE to drive an external FET for reverse-polarity protection; fault-status indication; a programmable input-current limit; and enable/disable input power.

Figure 4 shows the typical response of the bq24314 CFE to input overvoltage. The internal MOSFET switch immediately turns off with less than a 1- $\mu$ s delay once the input voltage reaches the predetermined input-overvoltage threshold.

When the system load exceeds the input-current limit, the CFE activates the input-current regulation loop and provides the maximum current limit set by the CFE. At a certain overcurrent blanking time, the CFE will turn off the MOSFET and may enter hiccup mode or latch mode after overcurrent protection is activated 15 times, depending on the IC version. The typical hiccup and latch response of the bq24314 CFE to input overcurrent is shown in Figure 5.

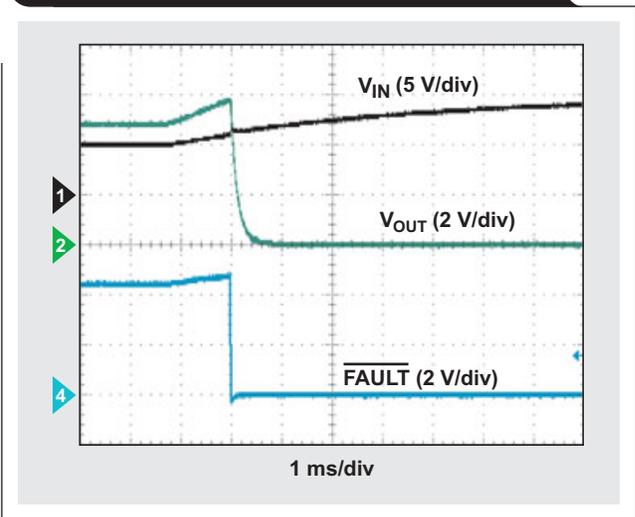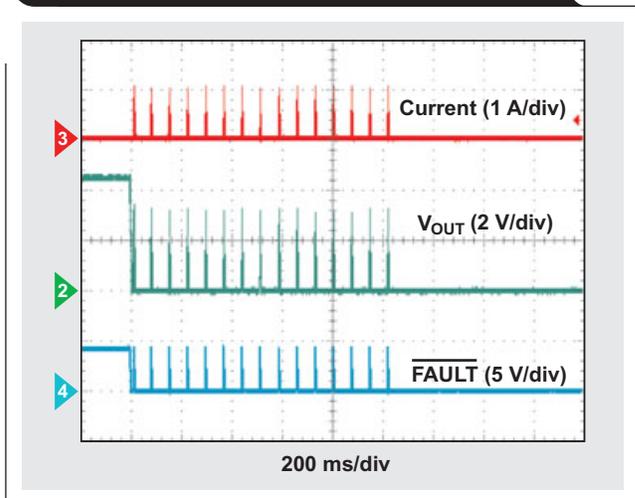**Figure 4. Protective response of bq24314 to input overvoltage****Figure 5. Protective response of bq24314 to input overcurrent**

Another important function of the CFE is to achieve battery second-level overvoltage protection for improved safety, although the battery pack itself achieves cell overvoltage protection by turning off the protection MOSFET in series with the cell. When the battery is overcharged due to any failure of the battery charger or protection MOSFET, the CFE will turn off its output with a 176- $\mu$ s delay time and will recover when the battery is no longer experiencing overvoltage. The typical response of the bq24314 CFE to battery overvoltage is shown in Figure 6.

### Summary

The CFE can significantly improve the safety of battery-operated systems by fully integrating protection from input overvoltage, input overcurrent, battery overvoltage, and reverse input polarity.


### Related Web sites

[power.ti.com](http://power.ti.com)

[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)

Replace partnumber with bq24080, bq24300, bq24304, or bq24314

**Figure 4. Protective response of bq24314 to battery overvoltage**

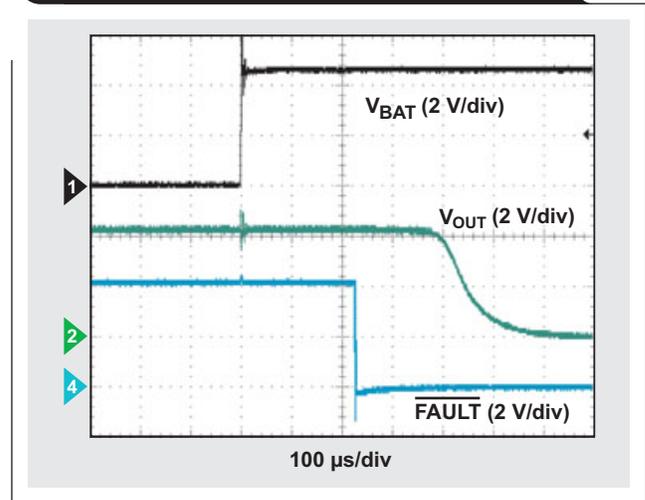

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Management	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

## TI Worldwide Technical Support

### Internet

**TI Semiconductor Product Information Center Home Page**  
[support.ti.com](http://support.ti.com)

**TI Semiconductor KnowledgeBase Home Page**  
[support.ti.com/sc/knowledgebase](http://support.ti.com/sc/knowledgebase)

### Product Information Centers

#### Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>		

#### Europe, Middle East, and Africa

##### Phone

European Free Call	00800-ASK-TEXAS (00800 275 83927)
--------------------	--------------------------------------

International	+49 (0) 8161 80 2121
---------------	----------------------

Russian Support	+7 (4) 95 98 10 701
-----------------	---------------------

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+(49) (0) 8161 80 2045
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>

#### Japan

##### Fax

International	+81-3-3344-5317	Domestic	0120-81-0036
---------------	-----------------	----------	--------------

Internet/Email	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>		
International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>		
Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>		

#### Asia

##### Phone

International	+886-2-23786800
---------------	-----------------

Domestic	Toll-Free Number
----------	------------------

Australia	1-800-999-084	Malaysia	1-800-80-3973
-----------	---------------	----------	---------------

China	800-820-8682	New Zealand	0800-446-934
-------	--------------	-------------	--------------

Hong Kong	800-96-5941	Philippines	1-800-765-7404
-----------	-------------	-------------	----------------

India	+91-80-41381665 (Toll)	Singapore	800-886-1028
-------	------------------------	-----------	--------------

Indonesia	001-803-8861-1006	Taiwan	0800-006800
-----------	-------------------	--------	-------------

Korea	080-551-2804	Thailand	001-800-886-0010
-------	--------------	----------	------------------

Fax	+886-2-2378-6808	Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>		<a href="mailto:ti-china@ti.com">ti-china@ti.com</a>

### C010208

**Safe Harbor Statement:** This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

**Trademarks:** All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

© 2008 Texas Instruments Incorporated