

A dual-polarity, bidirectional current-shunt monitor

By Thomas Kuehl


Senior Applications Engineer

Current-shunt-monitor ICs are an extension of the instrumentation amplifier family of products. They provide an easy method of monitoring circuit current and possess similarities to the sensitive analog voltmeter and external shunt resistor commonly used to measure current in the past. The analog voltmeter registered a small voltage drop that developed when current passed through a shunt resistor. With a current-shunt monitor, the voltmeter has been replaced by a specially adapted instrumentation amplifier that amplifies the voltage developed across the shunt resistor. An output measure is provided that is proportional to the current through the resistor. Analog voltmeters were commonly designed for a full-scale voltage of 50 or 100 mV, and the current-shunt monitor operates with comparable input-voltage levels. Instead of an analog meter-scale indication, the current-shunt monitor provides a voltage or current output level, or a digital output code, that directly corresponds to the measured current level.

A variety of current-shunt monitors are available that are designed for high-side or low-side circuit connection, with some offering different user functions. Often the voltage ranges of the current-shunt-monitor supply and the common-mode input are independent of each other. This allows the current-shunt monitor to be operated from a convenient supply-voltage level independent of the input voltage. Many applications need only monitor current flowing in one direction, and a current-shunt monitor such as the INA138/168 provides this capability. A monitor intended for single-direction, or unidirectional, current flow is referred to as a unidirectional current-shunt monitor. Other applications require a bidirectional current-shunt monitor where the circuit current can flow and be monitored in either direction.

An example of a bidirectional current-shunt monitor is the INA170. It is powered by a single supply voltage of +2.7 to +40 V, while the input common-mode voltage (CMV) may be any voltage between +2.7 and +60 V. The input CMV is the external voltage that is applied to the current-shunt-monitor input and provides current to the output load. When the current through the shunt resistor is zero, both inputs of the current-shunt monitor are ideally


Figure 1. The INA170 connected for bidirectional current monitoring

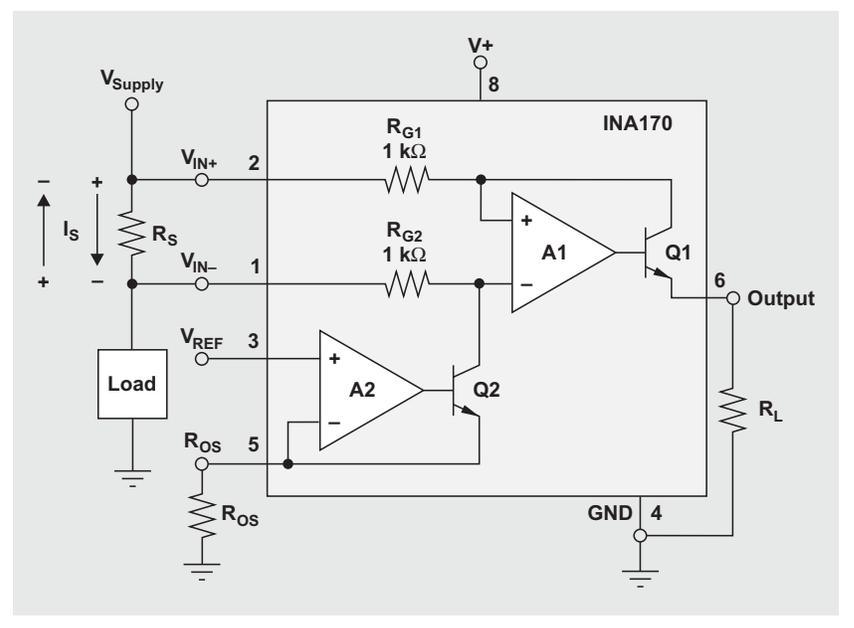

at the same CMV potential; but when a current flows through the shunt resistor, a differential voltage is developed and the inputs become separated by that amount. This voltage difference is amplified by the gain factor of the current-shunt monitor.

The bidirectional property allows the INA170 to monitor current between two voltage potentials that are more positive or negative relative to each other. A simple illustration of a bidirectional-current-flow system is a motor that draws current from a battery when operating at a constant speed or accelerating, but then acts as a generator, returning current to the battery during deceleration. Figure 1 shows the INA170 connected for bidirectional current monitoring.

Thus, two important current-shunt-monitor operating parameters are the unidirectional or bidirectional input voltage characteristic and the CMV range. The operational CMV range often extends from near 0 V to a specified maximum positive voltage, but some current-shunt monitors include a negative voltage range as well. For example, the INA193 through INA198 current-shunt-monitor family provides a CMV range of -16 to +80 V. These devices are unidirectional; so even if the input voltage is a negative voltage, the output has to be more negative for current to

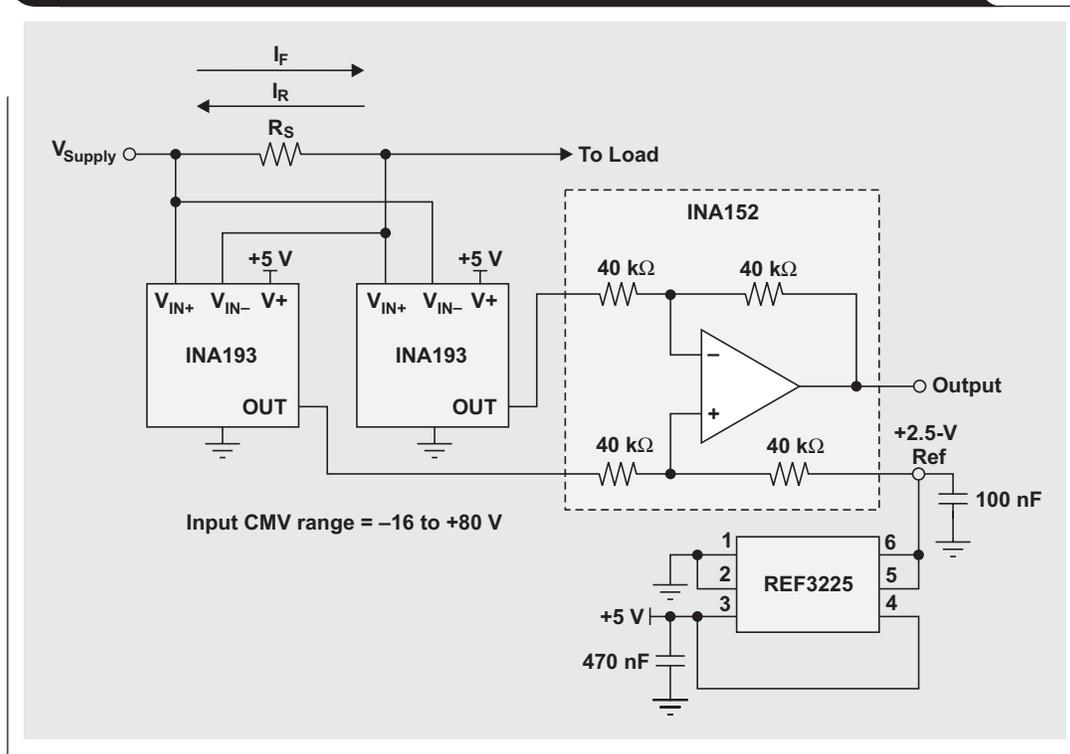Figure 2. Two INA193 ICs configured as a bidirectional current-shunt monitor


flow in the correct direction. Two of the unidirectional current-shunt-monitor ICs may be interconnected to form a bidirectional current-shunt monitor with a CMV range that extends from -16 to $+80$ V. The addition of the INA152 instrumentation amplifier and $+2.5$ -V reference completes the circuit. A circuit schematic for the INA193 bidirectional current-shunt monitor is shown in Figure 2.

Recently, a customer described an application where monitoring a DC motor's current was necessary. It was an automotive application, and the system supply was available to power a current-shunt monitor. The customer wanted to know the current levels when the motor was running normally in the forward direction and in reverse where a negative, back EMF developed. The circuit shown in Figure 2 is appropriate for this application; but the customer wanted to keep the number of components and the cost to a minimum, even if some precision had to be sacrificed. This called for a different approach.

Earlier it was mentioned that current-shunt monitors are an extension of instrumentation amplifiers. Also included in the family are difference amplifiers, which consist of an

instrumentation-grade operational amplifier and four or more precisely matched resistors. The difference amplifier amplifies the difference in voltages applied to the two inputs by a fixed gain. Gain and common-mode rejection of the difference amplifier are optimized by precise laser trimming of four thin-film resistors included on the integrated circuit die. Difference amplifiers with a fixed gain of 1:1, 10:1, and 100:1 V/V are commonly available; however, there is a unique product—the INA159—that has a fixed gain setting of 0.2 V/V. Its primary role is to serve as a level-translation amplifier between sensors having a bipolar output voltage with a range of ± 10 V, and a modern analog-to-digital converter having a unipolar input range of 0 to 5 V. The INA159 is a true difference amplifier that can sense a differential voltage of either polarity. Its input CMV range extends from -12.5 to $+17.5$ V when powered from a single $+5$ -V supply. These features allow the INA159 to be employed as a dual-polarity, bidirectional current monitor. An additional instrumentation or operational amplifier needs to be included after the INA159 to increase the overall gain of the monitor circuit.

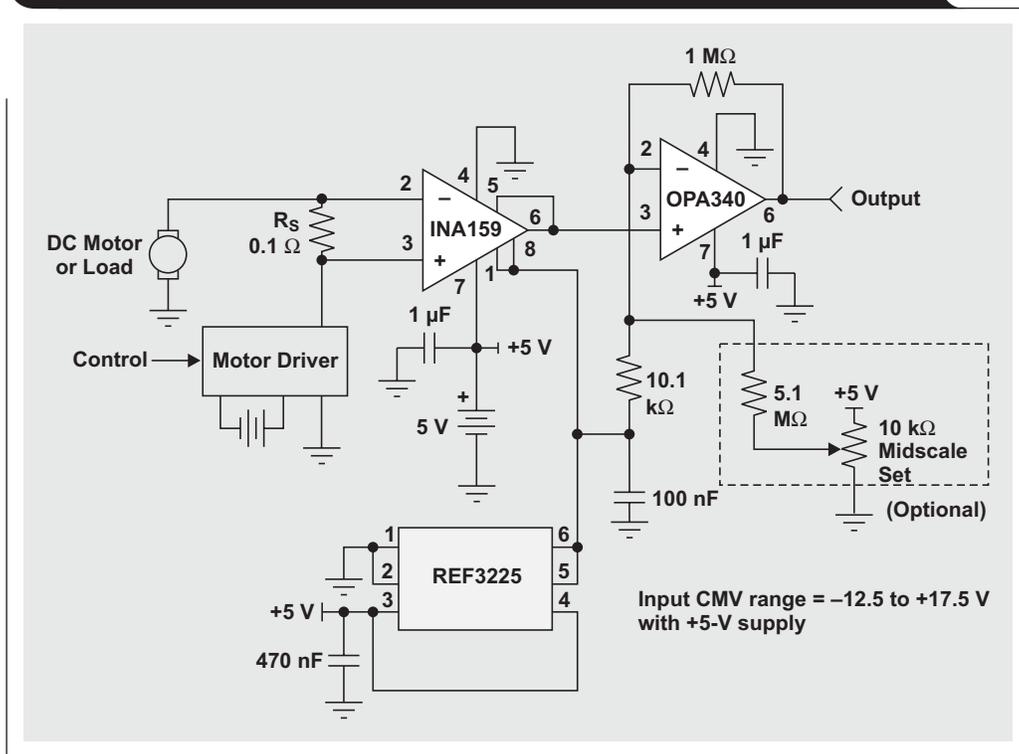
Figure 3. INA159 dual-polarity, bidirectional current-shunt-monitor circuit

Figure 3 shows the circuit of the INA159 current-shunt-monitor stage, followed by an OPA340 CMOS operational-amplifier gain stage. The OPA340 was selected because its near rail-to-rail input and output swing ranges allow the circuit's output voltage to approach 0 and 5 V at the extremes. The INA159 gain is +0.2 V/V, while the OPA340 gain is set to +100 V/V, for an overall circuit gain of +20 V/V. A higher OPA340 closed-loop gain could be used to increase sensitivity, but the DC errors and bandwidth would suffer. Also, the shunt resistor R_S , could be increased from 0.1 Ω to a larger value. This would increase the INA159 output, but the consequences of the larger voltage drop and higher resistor power dissipation should be evaluated before doing so.

The output voltage delivered from the INA159 current-shunt-monitor circuit is centered at a level of about +2.5 V. This is the approximate voltage level at the OPA340 output when no current is flowing through R_S . Figure 4 shows an oscilloscope image of the INA159 current-shunt monitor's output response when the input circuit is being driven by a 24-V_{PP}, 1-kHz sine wave. This input-voltage waveform is recorded as the upper trace image. The resistive load in the input circuit is 12 Ω , resulting in peak current levels of ± 1 A. The lower trace is that of the OPA340

output voltage swinging from 0.5 to 4.5 V, indicating a peak current of approximately ± 1 A. A center-scale, manual zeroing circuit is included in the OPA340 stage. It can be excluded if an exact 2.5-V center-scale voltage is not necessary. The INA159 and OPA340 combined exhibit a bandwidth of well over 100 kHz, making this circuit usable for a wide variety of AC-current-monitoring applications.

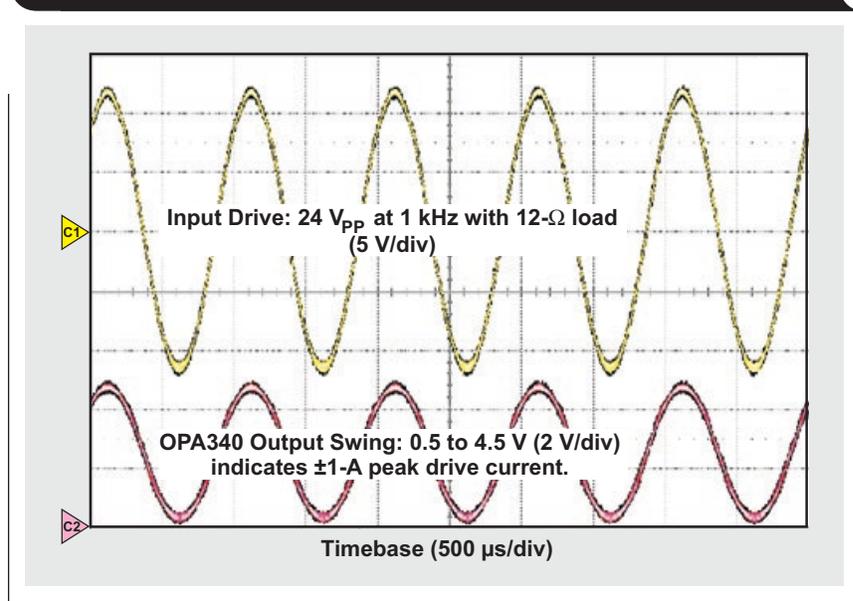
Figure 4. Input/output waveforms of current-shunt-monitor circuit

Figure 5 shows oscilloscope images of the INA159 current-shunt monitor monitoring the current of a DC pancake motor under load. The motor is being driven by a slow 9-V_{PP}, 0.1-Hz sine wave such that the armature direction follows the sine function, reversing direction every half cycle. This input drive voltage, shown as the upper trace, had to be adjusted to keep the motor from drawing more than 1 A of current. The lower trace shows the OPA340 output voltage where the peak motor current exceeds 1 A. Some evidence of clipping is seen at the OPA340 output as output-voltage-swing limits. With proper sizing of components, the circuit can be optimized for monitoring this particular motor's current levels. Nonetheless, this illustrates the utility of the INA159 in a motor-current-monitoring application.

Accuracy of the INA159 current-shunt monitor was measured at a little better than 4.5%. Standard 1% resistors were used, with no special selection being made. The circuit accuracy could be improved by replacing the OPA340 circuit with a precision, single-supply instrumentation amplifier such as the INA326. However, the AC bandwidth will decrease and the cost will be higher.


Related Web sites

amplifier.ti.com

www.ti.com/sc/device/partnumber

Replace *partnumber* with INA138, INA152, INA159, INA168, INA170, INA193, INA326, or OPA340

Figure 5. Input/output waveforms of current-shunt-monitor circuit of DC motor

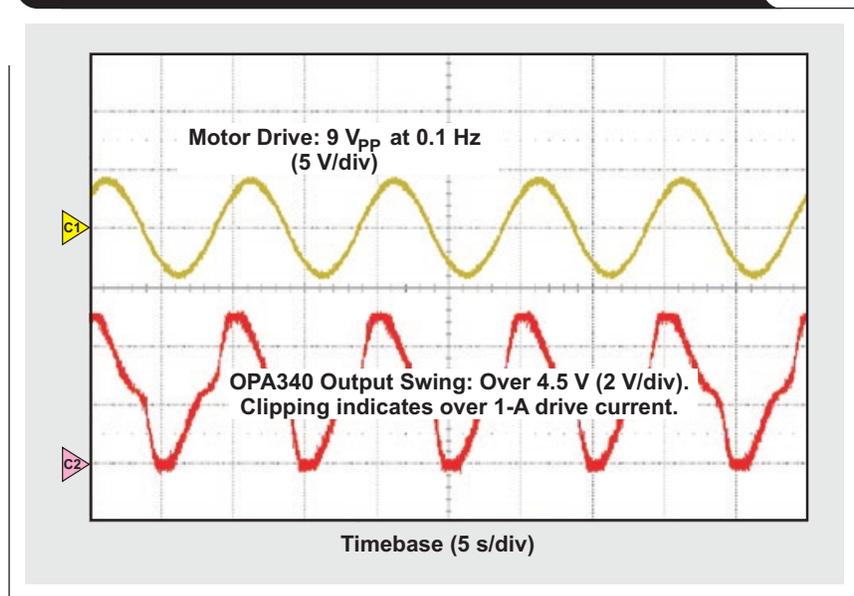

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
Clocks and Timers	www.ti.com/clocks	Broadband	www.ti.com/broadband
DSP	dsp.ti.com	Digital control	www.ti.com/digitalcontrol
Interface	interface.ti.com	Medical	www.ti.com/medical
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Telephony	www.ti.com/telephony
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI Semiconductor KnowledgeBase Home Page

support.ti.com/sc/knowledgebase

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm

Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+886-2-2378-6808
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

E093008

ZigBee is a registered trademark of the ZigBee Alliance. All other trademarks are the property of their respective owners.