

How the voltage reference affects ADC performance, Part 3

By **Bonnie Baker**, *Senior Applications Engineer*,
and **Miro Oljaca**, *Senior Applications Engineer*

This article is Part 3 of a three-part series that investigates the design and performance of a voltage-reference system for a successive-approximation-register (SAR) analog-to-digital converter (ADC). Part 1 (see Reference 1) examined the ADC characteristics and specifications, with a particular interest in the gain error and signal-to-noise ratio, while assessing how the voltage reference impacts the ADC transfer function and DC accuracy. Part 2 (see Reference 2) examined the voltage-reference characteristics, focusing on how the voltage-reference noise produces the most error at the converter's full-scale range. Part 2 concluded by presenting a design for a voltage-reference circuit that is appropriate for 8- to 14-bit converters. This article, Part 3, tackles the challenge of designing a voltage-reference circuit that is appropriate for converters with 16+ bits. Part 3 examines methods of improving noise filtering and of compensating for losses caused by the improved filters.

Basics of reducing voltage-reference noise

As discussed in Part 2, the two sources of noise in the reference voltage are the internal output amplifier and the

bandgap. The voltage-reference circuit from Part 2 that was configured with an 8- to 14-bit ADC can be used as a starting point to continue the discussion. The size of the least significant bit (LSB) of any converter in a 5-V system is equal to $5 V/2^N$, where N is the number of converter bits. The 8-bit LSB size in this environment is 19.5 mV, and the 14-bit LSB size is 305 μ V. The target value for voltage-reference noise should be less than these LSB values. The bandgap noise of the circuit from Part 2 was reduced by adding an external capacitor to the output to create a low-pass filter. This circuit's output noise can be further reduced by adding another capacitor as a passive low-pass filter. Figure 1 shows an example of such a design, which uses a voltage reference from the Texas Instruments (TI) REF50xx family. In this design, the 1- μ F capacitor (C_1) provides a minimal 21-dB noise reduction at the internal bandgap reference. C_2 , in combination with the open-loop output resistance (R_O) of the voltage reference's internal amplifier (see Reference 4), further reduces the output noise of the reference at the V_{REF_OUT} pin. In this case, the equivalent series resistance (ESR) of the 10- μ F ceramic capacitor (C_2) is equal to 200 m Ω .

Figure 1. Voltage-reference design appropriate for 8- to 14-bit converter

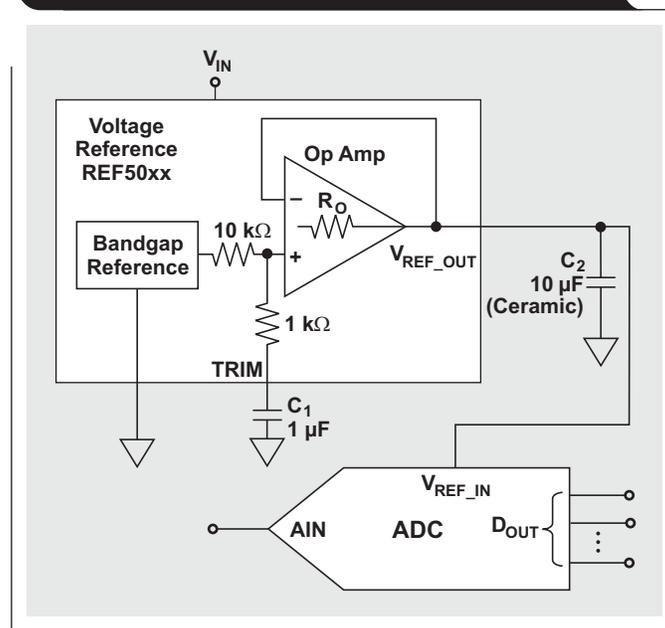


Figure 2 shows a fast-Fourier-transform (FFT) plot of the output signal of the circuit in Figure 1. Note that the output-noise level peaks at around 9 kHz because of the response of the circuit's internal amplifier to the capacitive load (C_2). This peaking is the main contributor to the overall measured noise. This output noise, measured with an analog meter over a frequency range of up to 80 kHz, is approximately $16.5 \mu V_{RMS}$. If the voltage-reference circuit was connected to the input of an ADC, the measured noise across a 65-kHz frequency range would be $138 \mu V_{PP}$. This noise level makes the solution in Figure 1 adequate for 8- to 14-bit converters.

Reducing voltage-reference noise for an ADC with 16+ bits

Since the voltage-reference circuit in Figure 1 would introduce too much noise into a converter with 16+ bits, another low-pass filter can be added to further reduce the reference's output noise. This filter consists of a 10-k Ω resistor (R_1) and an additional capacitor (C_3) as shown in Figure 3. The corner frequency of this added RC filter, 1.59 Hz, will reduce broadband noise as well as noise at extremely low frequencies.

Figure 2. FFT plot of V_{REF_OUT} signal of circuit in Figure 1

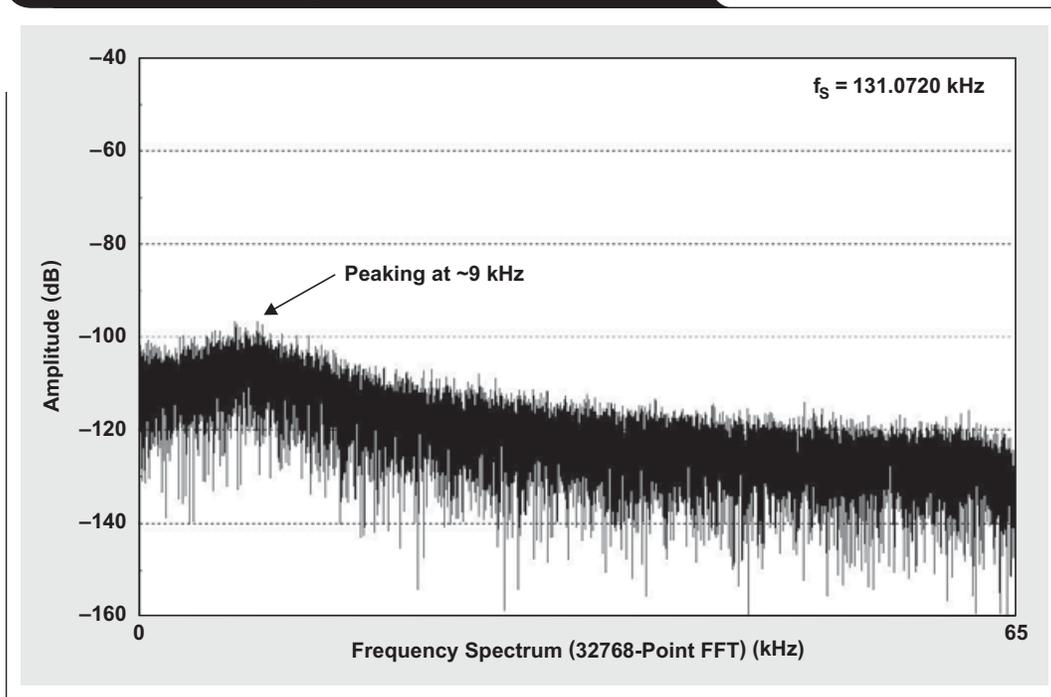


Figure 3. Voltage-reference circuit with R_1 and C_3 added as filters

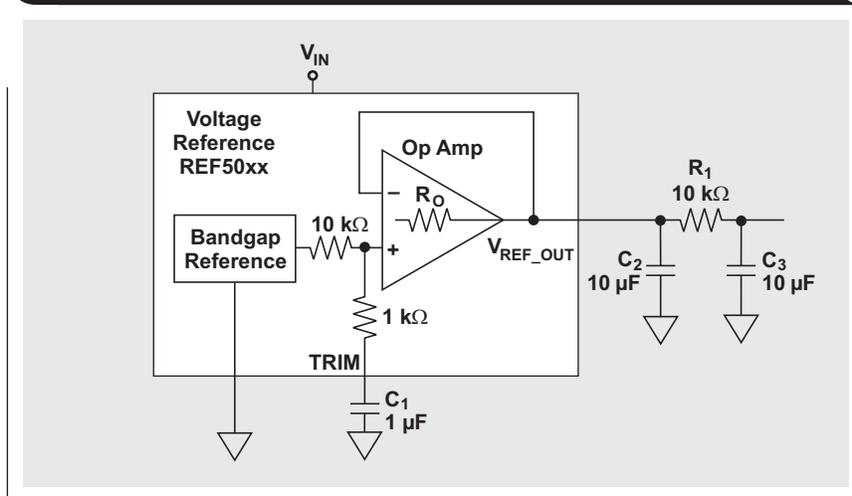


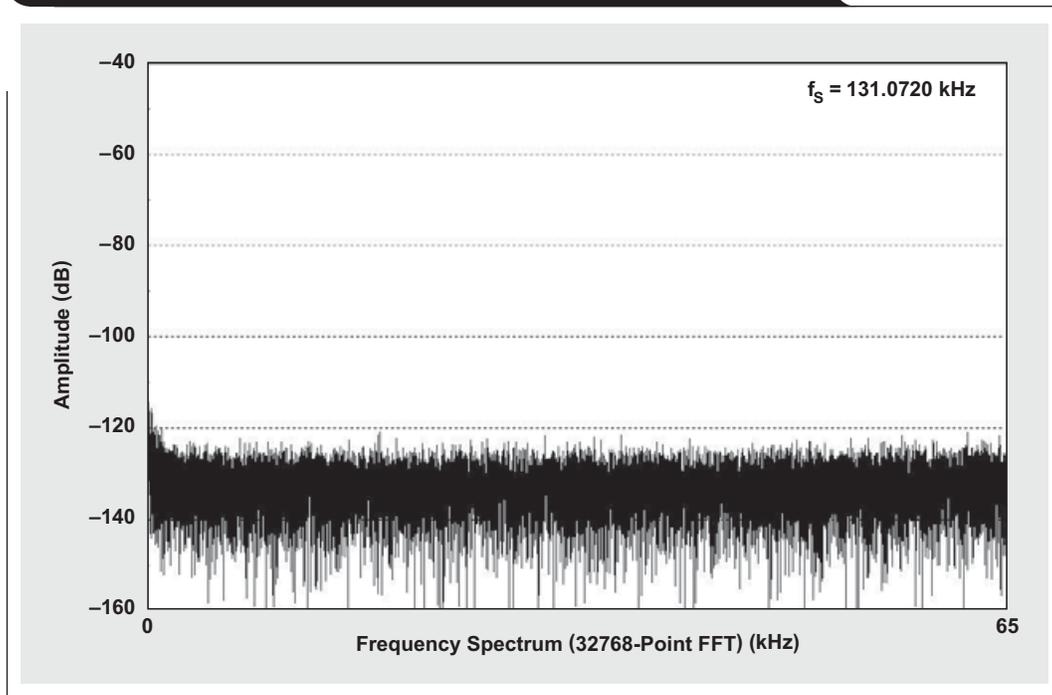
Figure 4. FFT plot of V_{REF_OUT} signal of circuit with RC filter added

Figure 4 shows that the addition of R_1 and C_3 has a significant effect on the output noise for this system. The 9-kHz noise peak is gone. With this signal response, the output noise of the reference circuit in Figure 3 becomes $2.2 \mu V_{RMS}$ or $15 \mu V_{PP}$, a reduction of nearly 90%. This improvement brings the noise level so well under control that the voltage-reference circuit is now appropriate for ADC resolutions of up to 20 bits.

This is encouraging; however, pulling current through R_1 from the ADC reference pin will corrupt the conversion by introducing a voltage drop equivalent to the average charge level from the reference pin of the ADC. Consequently, the output of this new circuit will not be able to adequately drive the ADC's voltage-reference input. To accomplish this, a buffer will need to be added to the low-pass filters.

Adding a buffer to the voltage-reference circuit

Figure 5 shows an example of the fluctuations in ADC reference drive current that can occur during a conversion. The signal was captured with a low-capacitance probe to show the voltage drop across the 10-k Ω resistor (R_1) between the input of the ADC voltage-reference pin and V_{REF_OUT} . The top trace in Figure 5 shows the trigger signal that the converter receives to initiate a new conversion. The ADC's voltage-reference

circuit demands different amounts of current (bottom trace) for the initiation of the conversion and for each code decision. Therefore, the voltage-reference analog circuitry connected to the ADC must be able to accommodate these high-frequency fluctuations efficiently while maintaining a strong voltage reference for the converter.

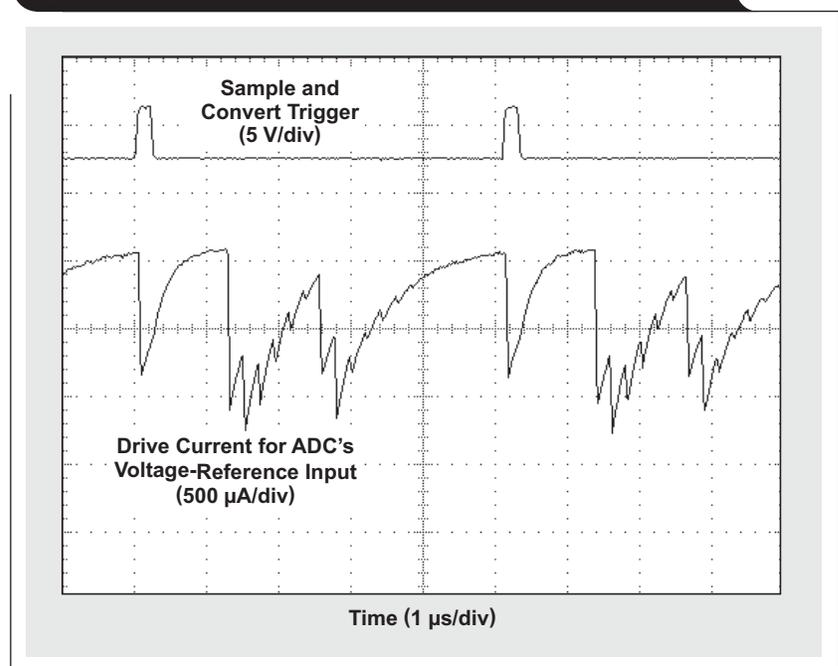
Figure 5. Drive current required by ADC's reference input


Figure 6. Voltage-reference circuit with added buffer and output filter

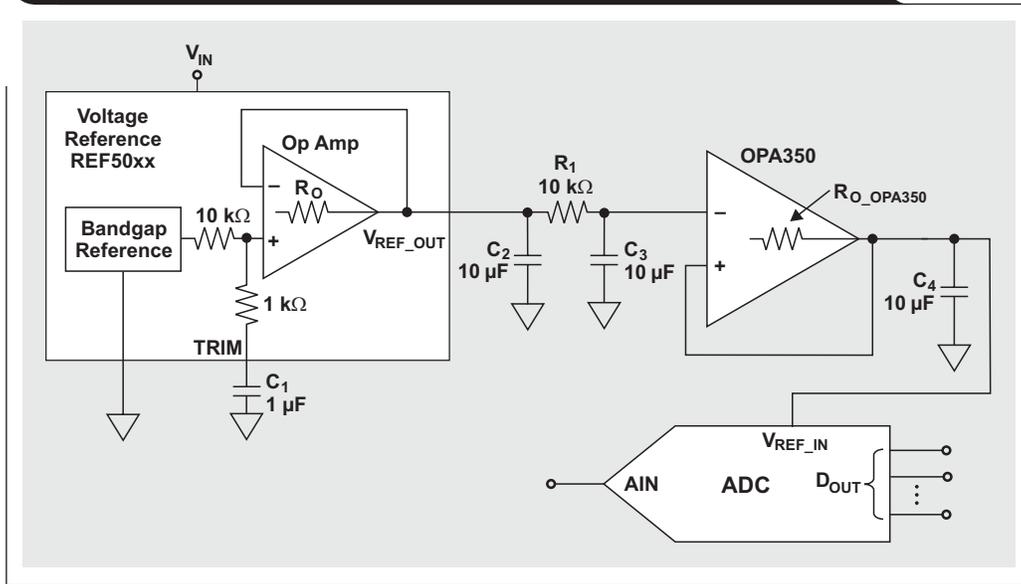
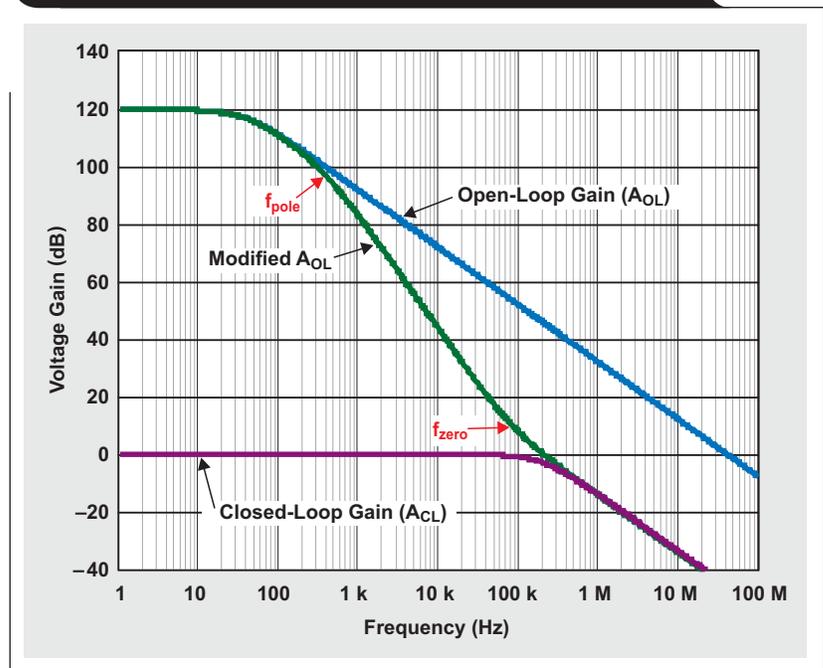
Figure 6 shows a voltage-reference circuit that will adequately drive a high-resolution ADC. In this circuit, the TI OPA350 is placed as a buffer after the low-pass filter that was constructed with R_1 and C_3 for the circuit in Figure 3. The OPA350 drives a 10- μF filter capacitor (C_4) and the voltage-reference input pin of the ADC. The noise measured at the output of the OPA350 in Figure 6 is 4.5 μV_{RMS} or 42 μV_{PP} . The input bias current of the OPA350 is 10 pA at 25°C. This current, in combination with the current through R_1 , generates a 100-nV, constant-DC drop. Note that this voltage drop does not change with the ADC's bit decisions. It is true that the input bias current of the OPA350 changes over temperature, but a maximum current that is no more than 10 nA at 125°C can be expected. This value generates a change of 100 μV over a temperature range of 100°C.

It is useful to put the voltage drop across R_1 into perspective. This voltage drop is added to the errors contributed by the REF50xx and the OPA350. The initial error of the REF50xx output is $\pm 0.05\%$, with an error over temperature of 3 ppm/°C. With a 4.096-V reference (REF5040), the initial reference error is equal to 2.05 mV at room temperature and an additional 1.23 mV at 125°C. Therefore, the reference output error is significantly larger than the errors produced by R_1 and variations in the OPA350's offset and input bias current.

Amplifier stability

There is a final word of caution about the circuit in Figure 6. The stability of the OPA350 can be compromised if C_4 and the

OPA350's open-loop output resistance (R_{O_OPA350}) modify the open-loop voltage-gain (A_{OL}) curve to create a marginally stable state. To illustrate this phenomenon, Figure 7 shows how the output capacitor (C_4), with a 0.2- Ω ESR and the OPA350's open-loop output resistance (43 Ω), modifies the OPA350's A_{OL} curve. These curves can be used to quickly determine the stability of the circuit. A circuit with good stability would basically be one where the rate of closure of the operational amplifier's modified A_{OL} curve and closed-loop voltage-gain (A_{CL}) curve is

Figure 7. Frequency response of buffer with an RC load


20 dB/decade. This rule of thumb is presented in Reference 4. The open-loop output resistance of the OPA350 is 43 Ω , and the ESR of C_4 (R_{ESR_C4}) is 200 m Ω . The frequency locations of the pole and zero that are created by these values are

$$f_{\text{pole}} = \frac{1}{2 \times \pi \times (R_{O_OPA350} + R_{ESR_C4}) \times C_4} = 368 \text{ Hz and}$$

$$f_{\text{zero}} = \frac{1}{2 \times \pi \times R_{ESR_C4} \times C_4} = 79.6 \text{ kHz.}$$

Per Figure 7, the circuit in Figure 6 is stable.

Thinking ahead

Unfortunately, the voltage-reference designs in this article can degrade ADC performance by adding unwanted temperature drift and initial gain error. Higher-performance systems with 21+ bits may require a voltage-reference design that addresses these issues. Future articles will explore a new approach with auto-zero amplifiers that will compensate for these errors.

References

For more information related to this article, you can download an Acrobat® Reader® file at www-s.ti.com/sc/techlit/litnumber and replace “litnumber” with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Bonnie Baker and Miro Oljaca, “How the Voltage Reference Affects ADC Performance, Part 1,” <i>Analog Applications Journal</i> (2Q 2009)	slyt331
2. Miro Oljaca and Bonnie Baker, “How the Voltage Reference Affects ADC Performance, Part 2,” <i>Analog Applications Journal</i> (3Q 2009)	slyt339

Document Title	TI Lit. #
3. Bonnie Baker, “A Glossary of Analog-to-Digital Specifications and Performance Characteristics,” Application Report	sbaa147
4. Tim Green. Operational amplifier stability, Parts 3, 6, and 7. <i>EN-Genius Network: analogZONE: acquisitionZONE</i> [Online]. Available: http://www.en-genius.net/includes/files/acqt_000000.pdf (Replace “000000” with “030705” for Part 3, “070405” for Part 6, or “052906” for Part 7.)	—
5. Bonnie C. Baker and Miro Oljaca. (2007, June 7). External components improve SAR-ADC accuracy. <i>EDN</i> [Online]. Available: http://www.edn.com/contents/images/6447231.pdf	—
6. Wm. P. (Bill) Klein, Miro Oljaca, and Pete Goad. (2007). Improved voltage reference circuits maximize converter performance. Analog eLab™ Webinar [Online]. Available: http://dataconverter.ti.com (Scroll down to “Videos” under “Analog eLab™ Design Support” and select webinar title.)	—
7. Art Kay. Analysis and measurement of intrinsic noise in op amp circuits, Part I. <i>EN-Genius Network: analogZONE: audiovideoZONE</i> [Online]. Available: http://www.en-genius.net/includes/files/avt_090406.pdf	—

Related Web sites

dataconverter.ti.com
www.ti.com/sc/device/OPA350
www.ti.com/sc/device/REF5040

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Broadband	www.ti.com/broadband
DSP	dsp.ti.com	Digital Control	www.ti.com/digitalcontrol
Clocks and Timers	www.ti.com/clocks	Medical	www.ti.com/medical
Interface	interface.ti.com	Military	www.ti.com/military
Logic	logic.ti.com	Optical Networking	www.ti.com/opticalnetwork
Power Mgmt	power.ti.com	Security	www.ti.com/security
Microcontrollers	microcontroller.ti.com	Telephony	www.ti.com/telephony
RFID	www.ti-rfid.com	Video & Imaging	www.ti.com/video
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI Semiconductor KnowledgeBase Home Page

support.ti.com/sc/knowledgebase

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm

Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+886-2-2378-6808
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

E093008

Analog eLab is a trademark of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated