

Discrete design of a low-cost isolated 3.3- to 5-V DC/DC converter

By Thomas Kugelstadt
Senior Applications Engineer

Isolated 3.3- to 5-V converters are often required in long-distance data-transmission networks, where the bus-node controller operates from a 3.3-V supply to conserve power while the bus voltage is 5 V to maintain signal integrity and to provide high drive capability over long distances. Although isolated DC/DC converter modules for 3.3- to 3.3-V and 5- to 5-V conversion are readily available on the market, 3.3- to 5-V converters in integrated form are still hard to find. Even if a search for the latter proves successful, these specific converters—in particular, those with regulated outputs—often possess long lead times, are relatively expensive, and are usually limited to certain isolation voltages.

A discrete design can be a low-cost alternative to integrated modules if an application requires isolation voltages higher than 2 kV, converter efficiency higher than 60%, or reliable availability of standard components. The drawback of designing a discrete DC/DC converter is that it requires a great deal of work—choosing a stable oscillator structure and break-before-make circuit, selecting good MOSFETs that can be driven efficiently by standard logic gates, and performing temperature and long-term-reliability tests. This entire effort costs time and money. Therefore, before rushing into such a project, the designer should consider the following: Integrated modules have usually passed temperature tests and have met other industrial qualifications. These modules not only represent the most reliable solution but also provide a fast time to market.

Converters with unregulated output are priced at around \$4.50 to \$5.00 each in quantities of 1000 units, while converters with regulated output often cost twice as much, approximately \$10.00 or more. Thus, it makes sense to purchase a converter with unregulated output and either buffer the output with bulk capacitance or feed it into a low-cost, low-dropout regulator (LDO) such as the Texas Instruments (TI) TPS76650 at around \$0.50.


The discrete DC/DC converter design in Figure 1 uses only readily available, standard components (such as logic ICs and MOSFETs) for the transformer driver and an LDO for a regulated output voltage. While this circuit has been prototyped with through-hole components, thus making its form factor larger than that of integrated modules, the board space can be drastically reduced by using TI's Little Logic™ devices.

The main benefits of this design are its low bill of material (BOM) and the freedom to choose an isolation transformer for isolation voltages ranging from 1 to 6 kV. The goal is to offer a low-cost alternative to fully integrated DC/DC converters with regulated outputs, and to stand-alone transformer drivers (usually priced at around \$1.80), by making the transformer-driver stage as inexpensive as possible.

Operation principle

Low-cost, isolated DC/DC converters are commonly of the push-pull driver type. The operation principle is fairly simple. A square-wave oscillator with a push-pull output stage drives a center-tapped transformer, whose output is rectified and made available in regulated or unregulated DC form. An important, functional requirement is that the square wave must have a 50% duty cycle to ensure

Figure 1. Isolated 3.3- to 5-V push-pull converter

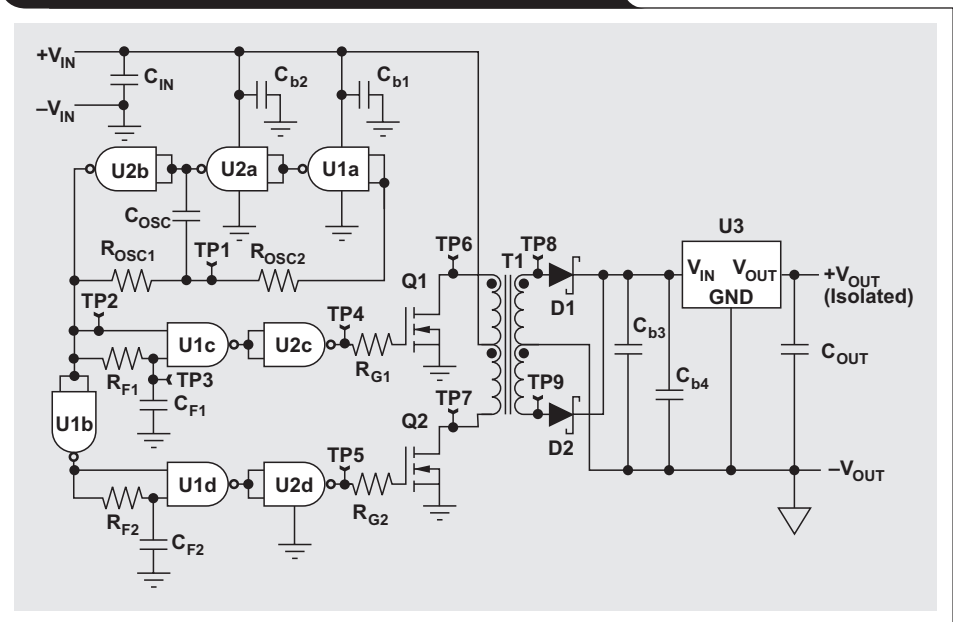

symmetrical magnetization of the transformer core. Another requirement is that the product of magnetizing voltage (E) and magnetizing time (T), known as the ET product and measured in $V\mu s$, must not exceed the transformer's characteristic ET product specified by its manufacturer. A break-before-make circuit following the oscillator must also be implemented to prevent the two legs of the push-pull output stage from conducting simultaneously and causing a circuit failure.

The discrete design

The well-known three-inverter-gate oscillator, consisting of U1a, U2a, and U2b, has been chosen because it is stable with supply variations. Its nominal frequency is set to 330 kHz through a 100-pF ceramic capacitor (C_{OSC}) and two 10-k Ω resistors (R_{OSC1} and R_{OSC2}). The oscillator possesses a duty cycle of close to 50% and a maximum frequency variation of less than $\pm 1.5\%$ across a 3.0- to 3.6-V variation in supply voltage. Figure 2 shows the waveforms at the summing point of R_{OSC1} and R_{OSC2} (TP1) and at the oscillator output (TP2). All voltages are measured with respect to circuit ground.

Two Schmitt-trigger NAND gates (U1c, U1d) perform a break-before-make function to avoid overlapping of the MOSFET's conducting phases. Two other NAND gates (U2c, U2d) are configured as inverting buffers, generating the correct signal polarity necessary to drive the n-channel MOSFETs (Q1, Q2). The complete break-before-make action is shown in Figure 3. To accommodate the limited drive capability of standard logic gates, the MOSFETs have been selected for their low total charge and their fast response times.

The isolation transformer (T1) has a secondary-to-primary winding ratio of 2:1, a primary inductance of 0.9 mH, and a guaranteed isolation voltage of 3 kV. The input and output waveforms of the transformer are shown in Figure 4.

Figure 2. Oscillator waveforms at TP1 and TP2

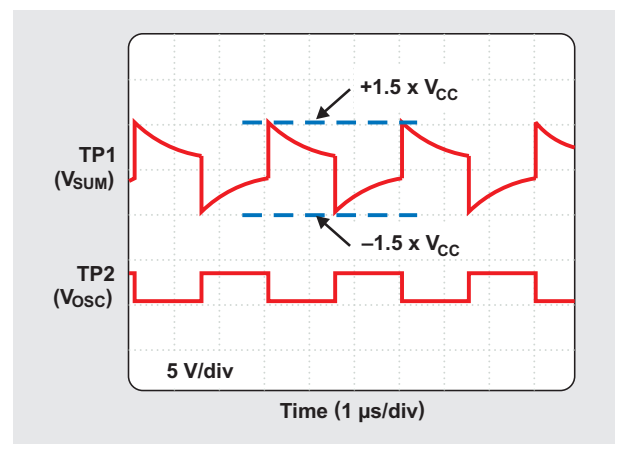


Figure 3. Break-before-make waveforms


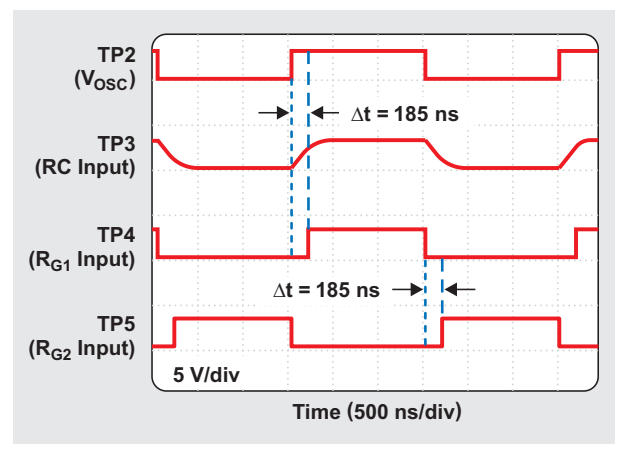


Figure 4. Transformer waveforms

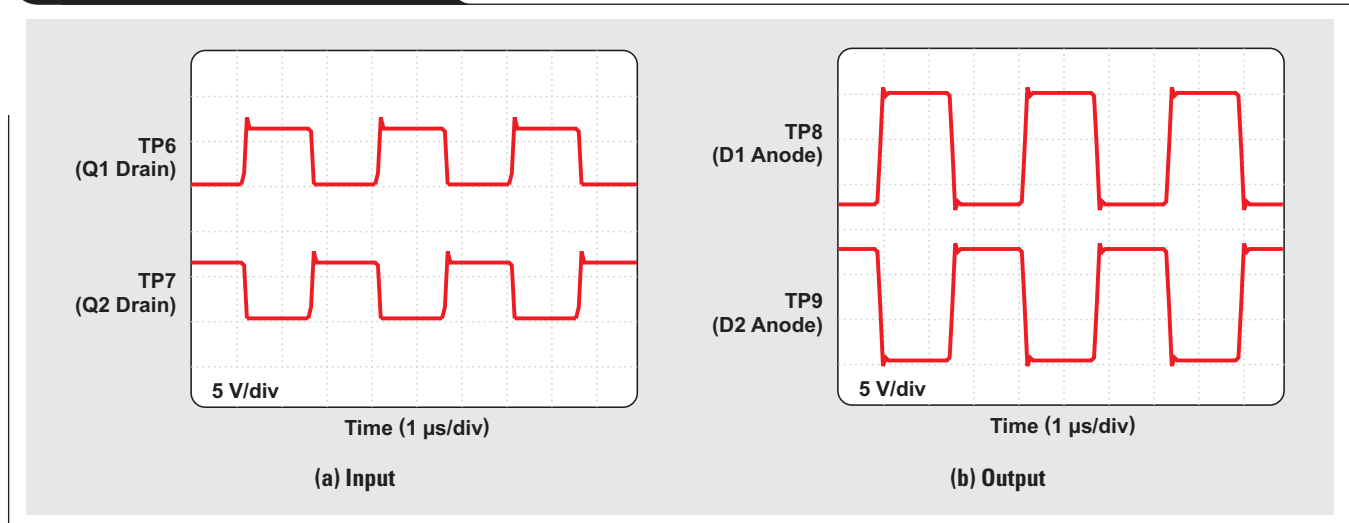

The two diodes (D1, D2) are fast Schottky rectifiers performing a full-wave rectification while providing low forward voltage at full load current ($V_{FW} < 0.4 \text{ V}$ at 200 mA). It is possible to take the output voltage directly from a bulk capacitor (Cb3) following the diodes. In this case, the output is unregulated but provides the maximum efficiency of the DC/DC converter. However, the designer must ensure that the maximum supply of the affected circuitry is not exceeded, which can easily occur under low-load or open-circuit conditions. If the unregulated output voltage under minimum load proves to be too high, it is necessary to use a linear regulator after the full-wave rectifier to provide a stable output supply.

The main benefit of a linear regulator is the low ripple output. Other benefits include short-circuit protection and overtemperature shutdown. The main drawback, however, is a significantly reduced efficiency.

Figure 5 shows the ripple of the circuit in Figure 1 at an output voltage of 4.93 V, and Figure 6 compares the circuit's efficiency with that of an integrated DC/DC module with regulated output.

Table 1 on the next page provides an approximate BOM for the discrete converter. Note that the values of the bypass capacitors are larger than the 10 nF commonly implemented in low-speed applications. This is because high-speed CMOS technologies such as AHC, AC, and LVC possess high dynamic loading, so the values for bypass capacitors must be 0.1 μF or higher to assure proper operation. This is of particular importance for the inverter buffers driving the MOSFETs, where the bypass capacitor is 0.68 μF .

Conclusion

Where board-space constraints are not an issue, the discrete design of an isolated 3.3- to 5-V DC/DC converter with regulated output can present a viable low-cost alternative to an integrated DC/DC module with regulated output. A major benefit of the discrete design is the freedom to choose an isolation transformer for varying isolation-voltage requirements.

Related Web sites

power.ti.com

www.ti.com/sc/device/partnumber

Replace *partnumber* with SN74AC00, SN74AHC132, or TPS76650

Figure 5. Output ripple at $V_{OUT} = 4.93 \text{ V}$

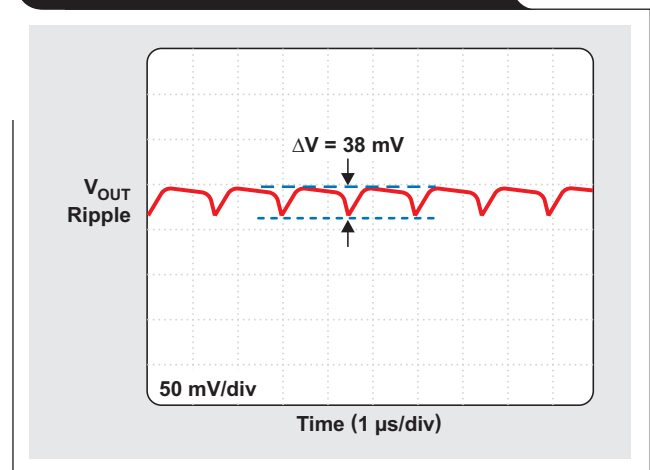


Figure 6. Efficiency comparison

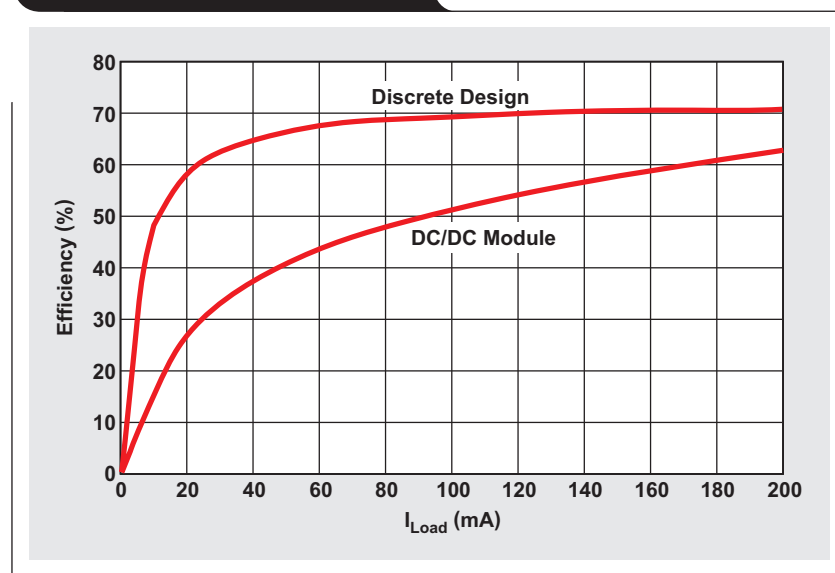


Table 1. BOM for discrete DC/DC converter

| DEVICE LABEL | PART NUMBER OR VALUE | DESCRIPTION | COMPONENT PRICE* (EACH) | QUANTITY | TOTAL PRICE* | TRANSFORMER DRIVER PRICE* |
|--|----------------------|---------------------------|-------------------------|--------------|--------------|---------------------------|
| U1 | SN74AHC132 | Quad Schmitt-trigger NAND | 0.17 | 1 | 0.17 | 0.17 |
| U2 | SN74AC00 | Quad NAND | 0.17 | 1 | 0.17 | 0.17 |
| U3 | TPS76650 | 250-mA LDO | 0.53 | 1 | 0.53 | — |
| Q1, Q2 | FDN335 | n-channel power MOSFET | 0.105 | 2 | 0.21 | 0.21 |
| R _{OSC1} , R _{OSC2} | 10 k Ω | OSC resistor | 0.04 | 2 | 0.08 | 0.07 |
| R _{F1} , R _{F2} | 1.54 k Ω | Delay resistor | 0.035 | 2 | 0.07 | 0.07 |
| R _{G1} , R _{G2} | 150 Ω | Gate-drive resistor | 0.035 | 2 | 0.07 | 0.07 |
| C _{OSC} | 100 pF | Oscillator capacitor | 0.04 | 1 | 0.04 | 0.04 |
| C _{F1} , C _{F2} | 47 pF | Delay capacitor | 0.04 | 2 | 0.08 | 0.08 |
| C _{b1} | 0.1 μ F | Bypass capacitor | 0.02 | 3 | 0.06 | 0.02 |
| C _{b2} | 0.68 μ F | Bypass capacitor | 0.03 | 1 | 0.03 | 0.03 |
| C _{b3} | 0.1 μ F | LDO input capacitor | 0.02 | 1 | 0.02 | — |
| C _{IN} , C _{b4} , C _{OUT} | 4.7 μ F | Bulk capacitor | 0.12 | 3 | 0.36 | 0.12 |
| D1, D2 | MBR0520L | Schottky diode | 0.045 | 2 | 0.09 | — |
| T1 | TGRTI-360NARL | 1:2 transformer, 3 kV | 2.31 | 1 | 2.31 | — |
| | | | | TOTAL | 4.28 | 1.09 |

*Typical price in U.S. dollars in quantities of 1000 units.

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

| | | |
|-----------------|----------------|--|
| Americas | Phone | +1(972) 644-5580 |
| Brazil | Phone | 0800-891-2616 |
| Mexico | Phone | 0800-670-7544 |
| | Fax | +1(972) 927-6377 |
| | Internet/Email | support.ti.com/sc/pic/americas.htm |

Europe, Middle East, and Africa

| | |
|--------------------|--------------------------------------|
| Phone | |
| European Free Call | 00800-ASK-TEXAS (00800 275 83927) |
| International | +49 (0) 8161 80 2121 |
| Russian Support | +7 (4) 95 98 10 701 |

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

| | |
|----------|--|
| Fax | + (49) (0) 8161 80 2045 |
| Internet | support.ti.com/sc/pic/euro.htm |

Japan

| | | |
|----------------|---------------|--|
| Phone | Domestic | 0120-92-3326 |
| Fax | International | +81-3-3344-5317 |
| | Domestic | 0120-81-0036 |
| Internet/Email | International | support.ti.com/sc/pic/japan.htm |
| | Domestic | www.tij.co.jp/pic |

Asia

| | |
|---------------|--|
| Phone | |
| International | +91-80-41381665 |
| Domestic | <u>Toll-Free Number</u> |
| Australia | 1-800-999-084 |
| China | 800-820-8682 |
| Hong Kong | 800-96-5941 |
| India | 1-800-425-7888 |
| Indonesia | 001-803-8861-1006 |
| Korea | 080-551-2804 |
| Malaysia | 1-800-80-3973 |
| New Zealand | 0800-446-934 |
| Philippines | 1-800-765-7404 |
| Singapore | 800-886-1028 |
| Taiwan | 0800-006800 |
| Thailand | 001-800-886-0010 |
| Fax | +886-2-2378-6808 |
| Email | tiasia@ti.com or ti-china@ti.com |
| Internet | support.ti.com/sc/pic/asia.htm |

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A042210

E2E and Little Logic are trademarks of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | | Applications | |
|-----------------------------|--|----------------------------|--|
| Amplifiers | amplifier.ti.com | Audio | www.ti.com/audio |
| Data Converters | dataconverter.ti.com | Automotive | www.ti.com/automotive |
| DLP® Products | www.dlp.com | Communications and Telecom | www.ti.com/communications |
| DSP | dsp.ti.com | Computers and Peripherals | www.ti.com/computers |
| Clocks and Timers | www.ti.com/clocks | Consumer Electronics | www.ti.com/consumer-apps |
| Interface | interface.ti.com | Energy | www.ti.com/energy |
| Logic | logic.ti.com | Industrial | www.ti.com/industrial |
| Power Mgmt | power.ti.com | Medical | www.ti.com/medical |
| Microcontrollers | microcontroller.ti.com | Security | www.ti.com/security |
| RFID | www.ti-rfid.com | Space, Avionics & Defense | www.ti.com/space-avionics-defense |
| RF/IF and ZigBee® Solutions | www.ti.com/lprf | Video and Imaging | www.ti.com/video |
| | | Wireless | www.ti.com/wireless-apps |

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated